


Diode Equivalent Circuit

An equivalent circuit is a combination of elements (e.g. R, L, C , etc.) properly chosen to best represent the actual characteristics of device in a particular operating region.

Why we need equivalent circuit? we cannot use traditional circuit analysis techniques (like, KVL, KCL, network theorems, etc.) with actual device.

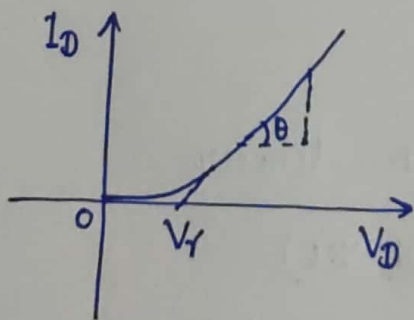1. Piecewise linear model:



Assumption: I-V characteristics is linear in forward wise (with small linearity)



Forward resistance,

$$r_{fD} = \frac{1}{\text{Slope}} = \frac{1}{\tan \theta}$$

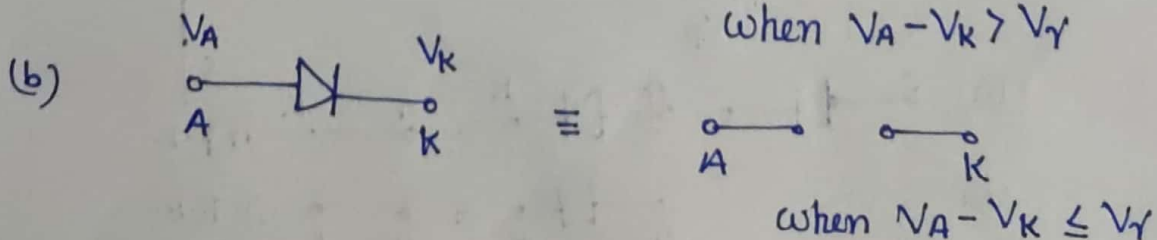
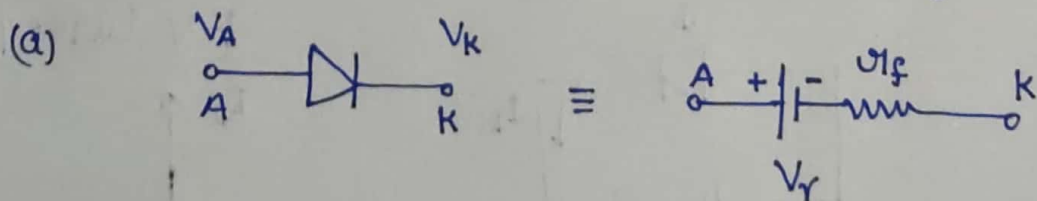
$$\tan \theta = \frac{\Delta I_D}{\Delta V_D}$$



2. Constant Voltage Drop / Simplified Equivalent CKT.

- Assumptions: (i) I-V curve is piece-wise linear
(ii) r_f is very small ($r_f \approx 0$)

I-V characteristics

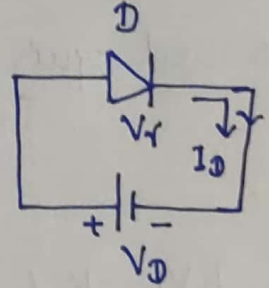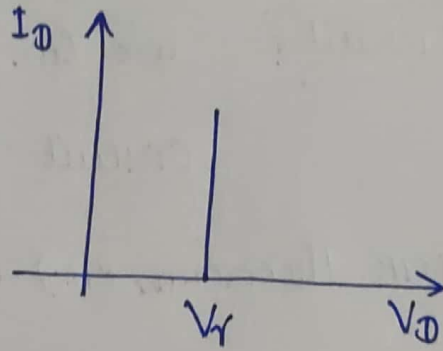


(a) $\begin{matrix} V_A \\ \circ \\ A \end{matrix} \begin{matrix} \rightarrow \\ \text{Diode} \end{matrix} \begin{matrix} V_K \\ \circ \\ K \end{matrix} \equiv \begin{matrix} A \\ \circ \end{matrix} \begin{matrix} \text{Voltage Source } V_f \\ | \end{matrix} \begin{matrix} K \\ \circ \end{matrix} \text{ when } V_A - V_K > V_f$


(b) $\begin{matrix} V_A \\ \circ \\ A \end{matrix} \begin{matrix} \rightarrow \\ \text{Diode} \end{matrix} \begin{matrix} V_K \\ \circ \\ K \end{matrix} \equiv \begin{matrix} A \\ \circ \end{matrix} \begin{matrix} \text{Open Circuit} \end{matrix} \begin{matrix} K \\ \circ \end{matrix} \text{ when } V_A - V_K \leq V_f$

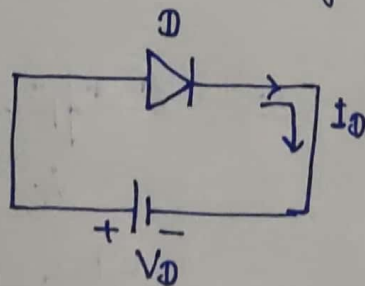3. Ideal model

- Assumptions: (i) I-V curve is piece-wise linear
(ii) r_f is very small ($r_f \approx 0$)
(iii) Cut-in Voltage is very small ($V_f \approx 0$)




I-V curve / characteristics

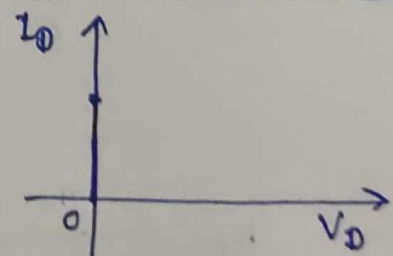


(a) $\begin{matrix} \text{Forward Bias} \\ \text{Diode} \end{matrix} \equiv \begin{matrix} A \\ \circ \end{matrix} \begin{matrix} \text{Short Circuit} \end{matrix} \begin{matrix} K \\ \circ \end{matrix} \text{ if F.B.}$

(b) $\begin{matrix} \text{Reverse Bias} \\ \text{Diode} \end{matrix} \equiv \begin{matrix} A \\ \circ \end{matrix} \begin{matrix} \text{Open Circuit} \end{matrix} \begin{matrix} K \\ \circ \end{matrix} \text{ if R.B.}$

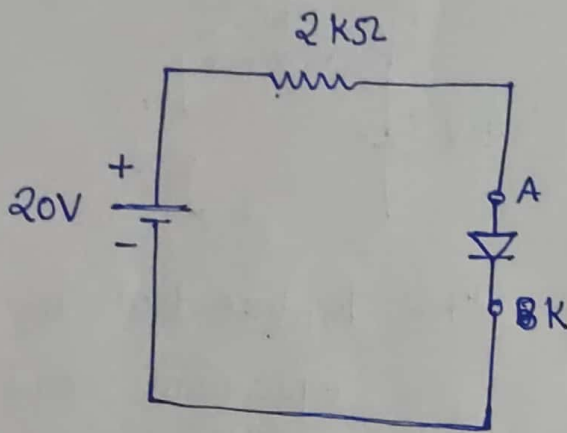Q.1: Find the current I in the given circuit? Given that $V_f = 0.7$ and $r_f = 200 \Omega$.



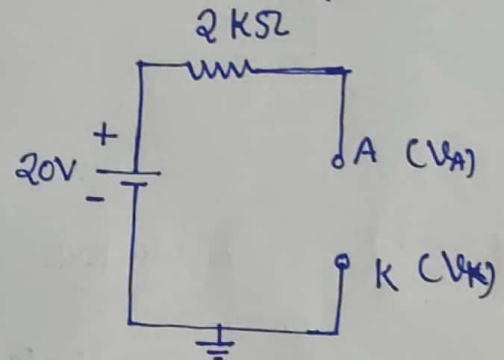
Sol: Step 1: Determine the state of Diode



$$V_A - V_K > V_f \Rightarrow V_{AK} = 20V$$

$$V_{AK} > V_f$$

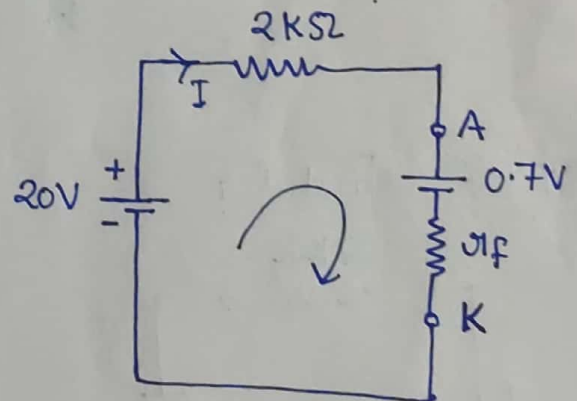Step 2: Replace diode by equivalent ckt model



Apply KVL


$$2I + 0.7I$$

$$2000I + 0.7I + r_f I = 20$$

$$I = \frac{20 - 0.7}{2000 + 200}$$

$$= \frac{19.3}{2200} = 8.73 \text{ mA}$$

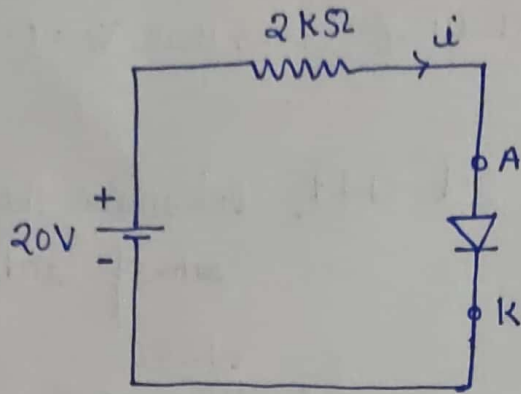
Example 2:- Find current i if $V_f = 0.7V$.




Apply KVL

$$\begin{aligned} i &= \frac{20 - 0.7}{20000} \\ &= \frac{19.3}{20000} \\ &= 9.65 \text{ mA} \end{aligned}$$


Step 1: Determine the state of diode

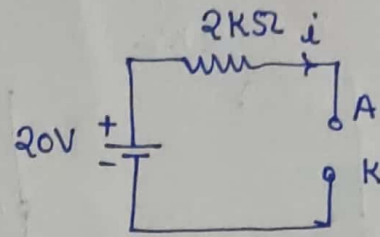

Step 2: Replace diode by the equivalent model

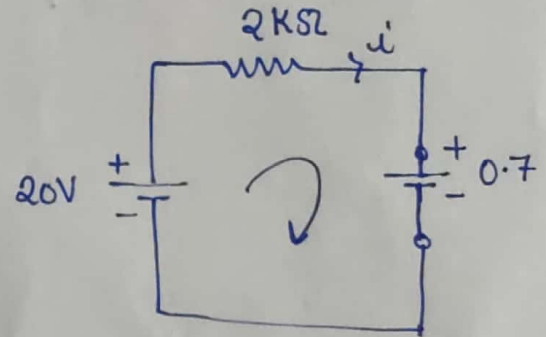


Example 3:- Find i ?

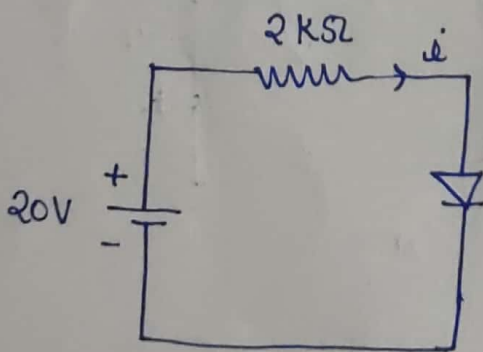

Step 1: Determine the state of diode


Diode is in F.B.

Step 2:

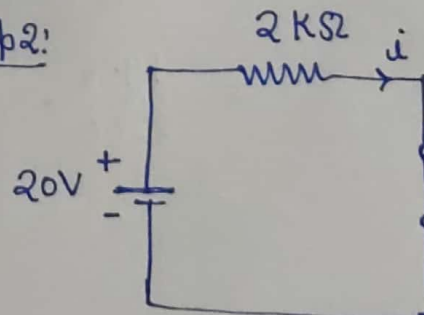

$$\begin{aligned} i &= \frac{20}{20000} \\ &= 1 \text{ mA} \\ &= 10 \text{ mA} \end{aligned}$$

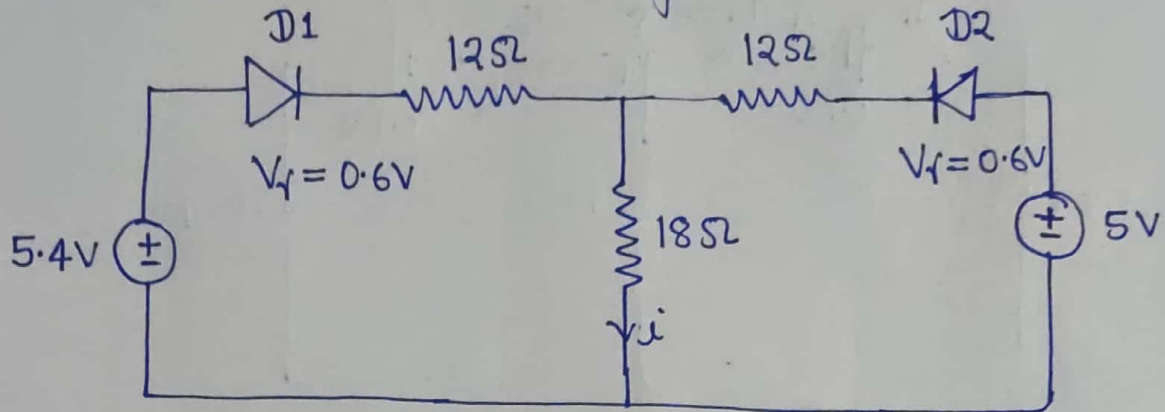
Ex:- Determine the current i in the given circuit?



Sol:-

Step 1: Determine the state of diodes

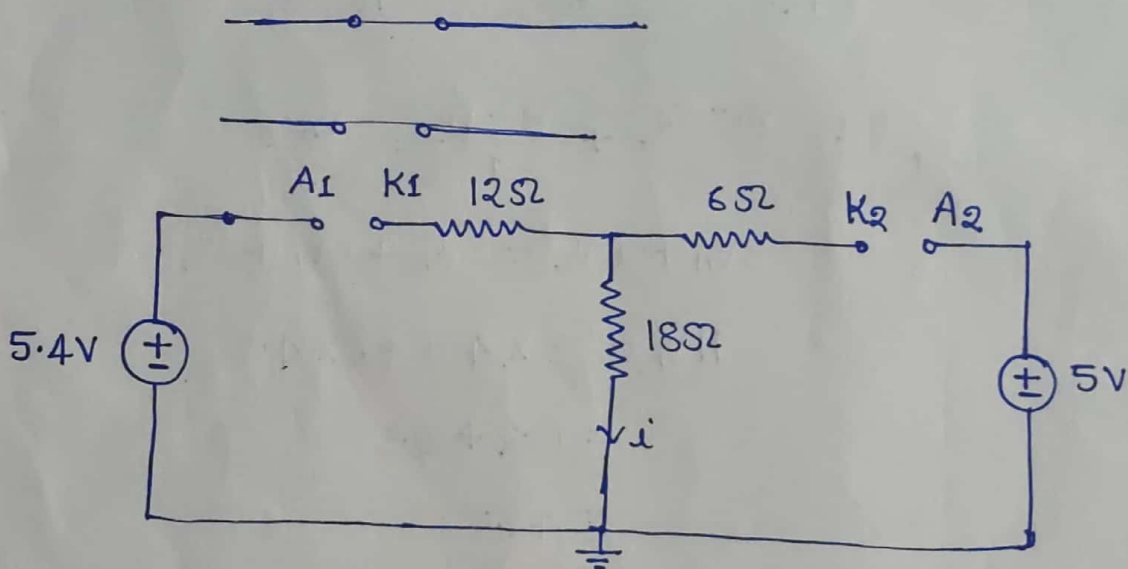(i) Assume that all diodes are in reverse bias



$$V_{A1} = 5.4V ; V_{A2} = 5V$$

$$V_{K1} = 0V ; V_{K2} = 0V$$

$$V_{A1} =$$

$$V_{A1} - V_{K1} = 5.4 - 0 ; V_{A2} - V_{K2} = 5 - 0$$

$$= 5.4V$$


$$V_{A2K2} = 5.0 > V_f$$

$$> V_f$$

D1 is F.B.

D2 is F.B.

Step 2:

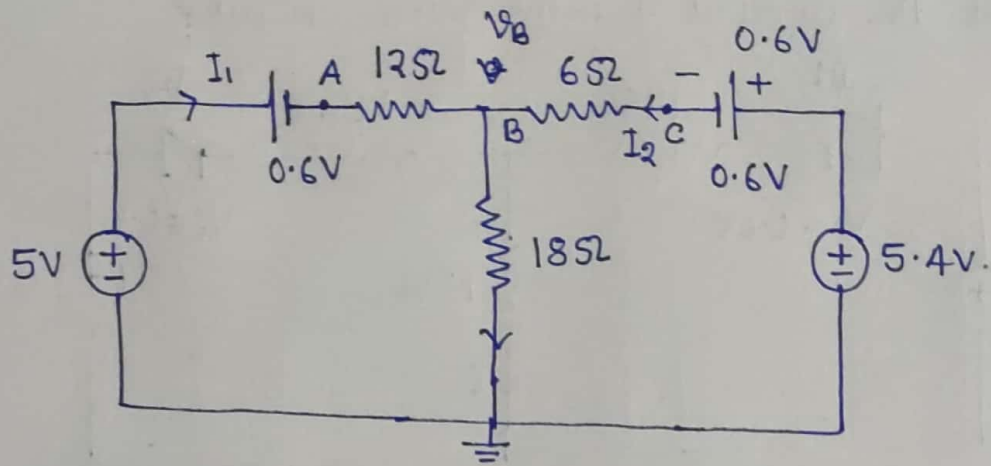

$$V_A = 5 - 0.6 \quad ; \quad V_C = 5.4 - 0.6 \\ = 4.4V \quad ; \quad = 4.8V$$

$$\frac{V_A - V_B}{12} + \frac{V_C - V_B}{6} = \frac{V_B - 0}{18}$$

$$\text{Or } \frac{V_A - V_B}{2} + \frac{V_C - V_B}{1} = \frac{V_B}{3}$$

$$3V_A + 6V_C = 2V_B + 6V_B + 3V_B$$

$$11V_B = 3 \times 4.4 + 6 \times 4.8$$


$$= 13.2 + 28.8$$

$$= 42.0$$

$$V_B = \frac{42}{11}$$


$$I = \frac{\frac{42}{11} - 0}{18} = \frac{42 \times 7}{18 \times 11} \\ = \underline{7/33 A}$$

Ex Determine the current I ?

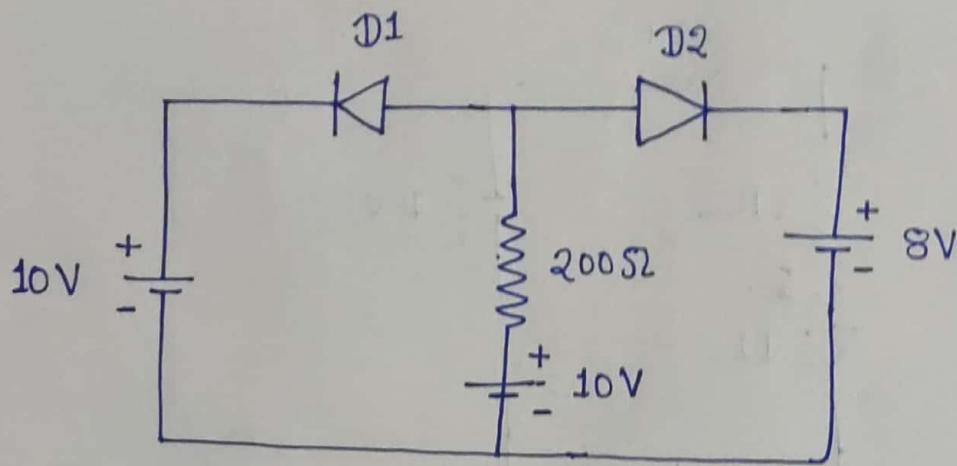

Sol:

Step 1:

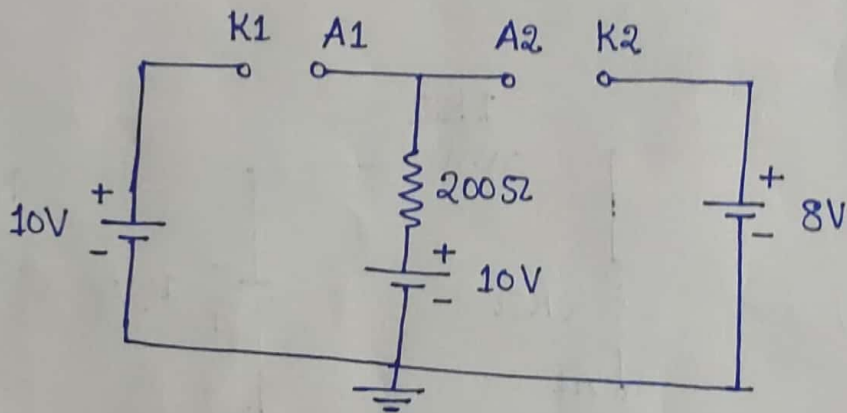

For D1

$$V_{K1} = 10V$$

$$V_{A1} = 10V$$

$$V_{A1} - V_{K1} = 0V$$

D1 R.B.

For D2

$$V_{K2} = 8V$$


$$V_{A2} = 10V$$

$$V_{A2K2} = V_{A2} - V_{K2}$$

$$= 10 - 8$$

$$= 2V$$

D2 F.B.

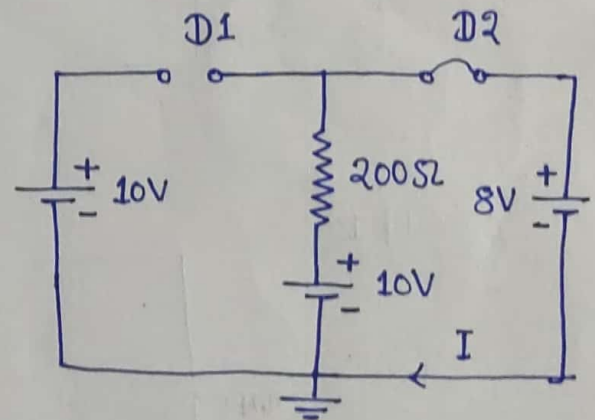


$$8 - 10 + 200I = 0$$

$$\text{or } I = \frac{2}{200}$$


$$= 10mA$$

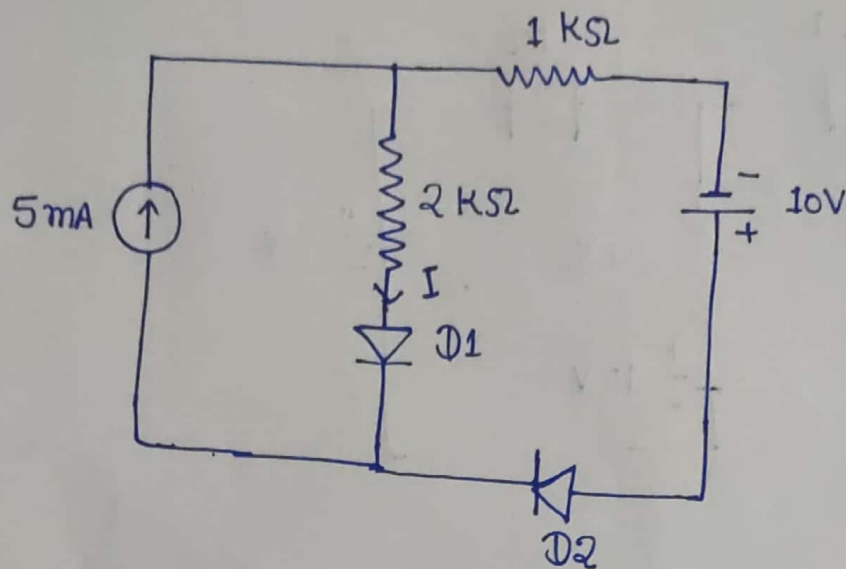Ex:- Determine the current I ? (Both diodes are ideal.)




Sol:

Step 1:

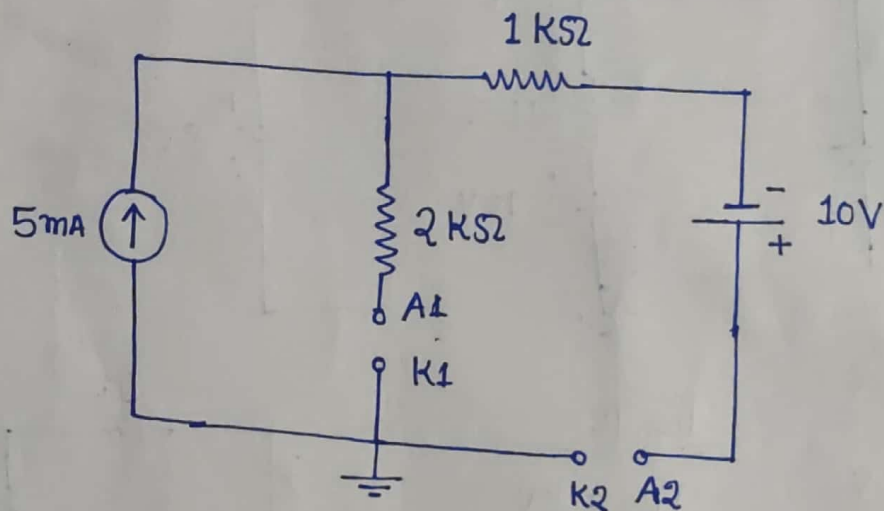

KCL is
Violated

Step 1:

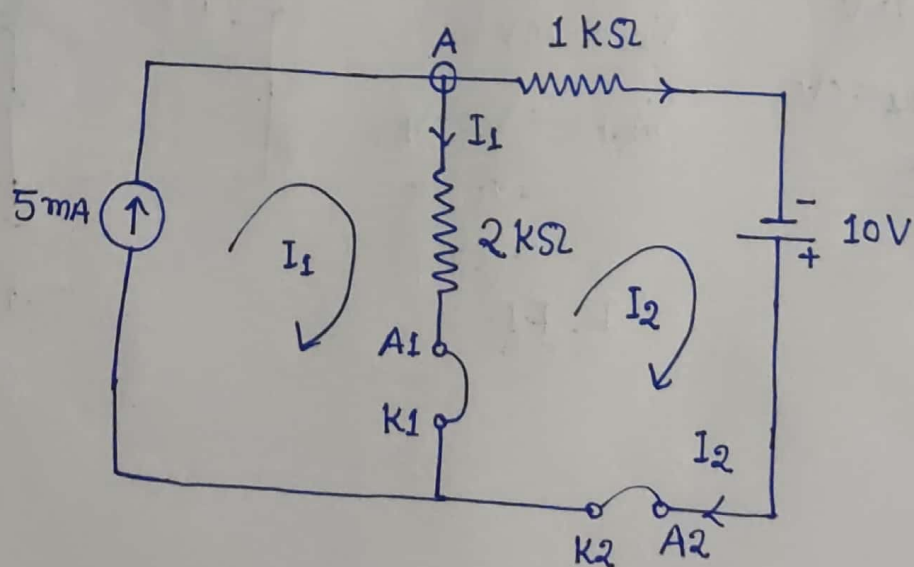

For I_2

$$\begin{aligned} -10 - 2000I_1 \\ + 1000I_2 \\ = 0 \end{aligned}$$

Apply KCL at A

So

$$I = I_1 + I_2$$

$$5 \text{ mA} = I_1 + I_2$$

$$\text{or } I_1 = 5 - I_2$$

$$\begin{aligned} I_1 &= 5 - I_2 \\ &= 5 - \frac{20}{3} = -\frac{5}{3} \text{ A} \end{aligned}$$

D1: R.B.


$$-10 - 2I_1 + I_2 = 0$$

$$I_2 - 2I_1 = 10$$


$$\begin{aligned} I_2 - 2(5 - I_2) &= 10 \Rightarrow I_2 - 10 + 2I_2 = 10 \\ \Rightarrow I_2 &= \frac{20}{3} \text{ A} \end{aligned}$$

D2: F.B.

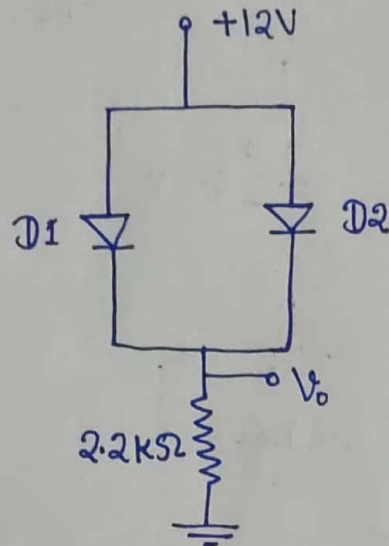Ex:- Find V_o ? Given that $(V_f)_{D1} = 0.7V$ and $(V_f)_{D2} = 0.3V$.



Sol.: Step 1: Determine state of diodes

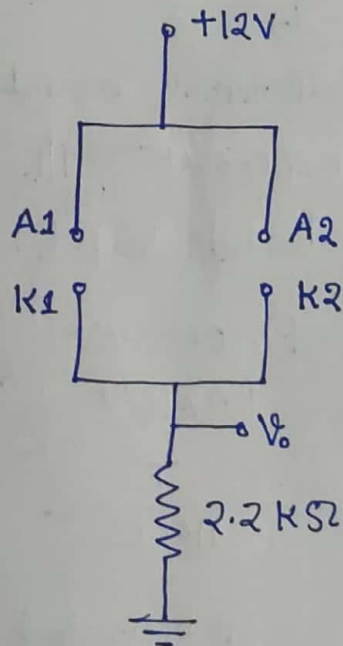

For D1

$$V_{A1} = 12V$$

$$V_{K1} = 0V$$

$$V_{A1} - V_{K1} = 12 - 0 = 12V$$

D1 → F.B.

For D2


$$V_{A2} = 12V$$

$$V_{K2} = 0V$$

$$V_{A2} - V_{K2} = 12 - 0 = 12V$$


D2 → F.B.

Step 2:

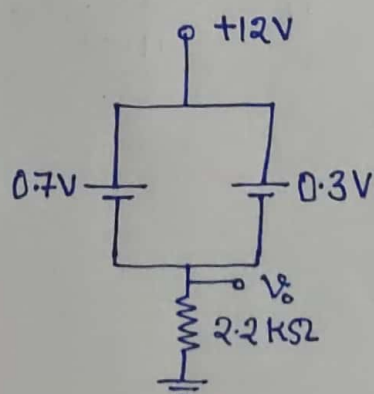

Not Possible

Sol:

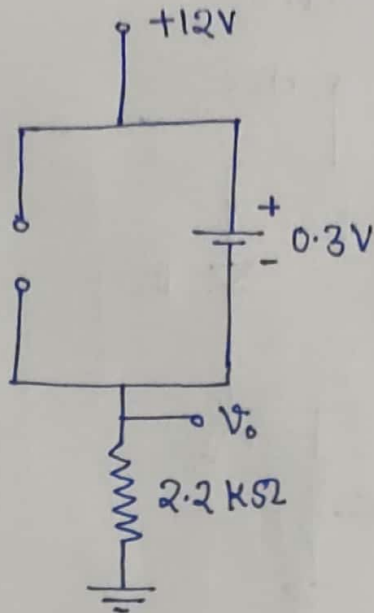

$$-12 + 0.3V + 2.2i = 0$$

$$2.2i = 12 - 0.3$$

$$i = \frac{11.7}{2.2} \text{ mA}$$

□

Thermal Voltage

$$V_T = \frac{kT}{q} =$$

$$k = \text{Boltzmann's constant} ; e = 1.6 \times 10^{-19} \text{ C} \\ = 1.38066 \times 10^{-23} \text{ J/K} :$$

$$T = \text{absolute temp. } [T = 273 + T'(^{\circ}\text{C})]$$

$$V_T = \frac{1.38066 \times 10^{-23}}{1.6 \times 10^{-19}} \times T \\ = \frac{T}{11600}$$





At Room temp.

$$T = 27^{\circ}\text{C} = 27 + 273 = 300 \text{ K}$$



$$V_T = \frac{300}{11600} = \frac{3}{116} = 0.029 \text{ V}$$

Clipping Circuits (Limiting Circuits)

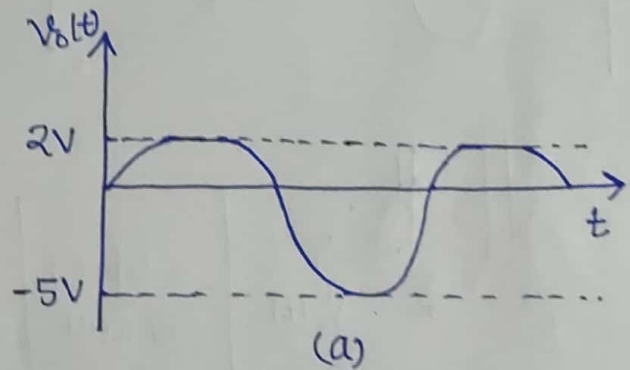
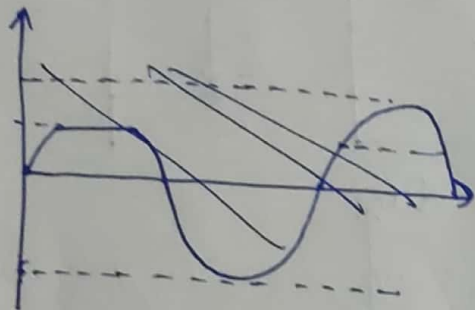
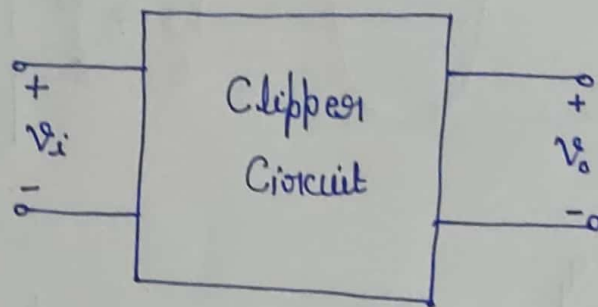
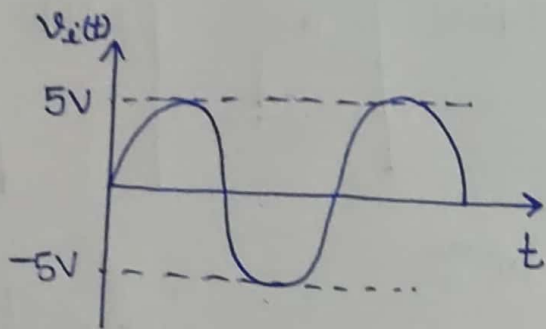
Function: To limit the minimum and/or maximum value of the input voltage.





Possible outputs of
a Clipping circuit

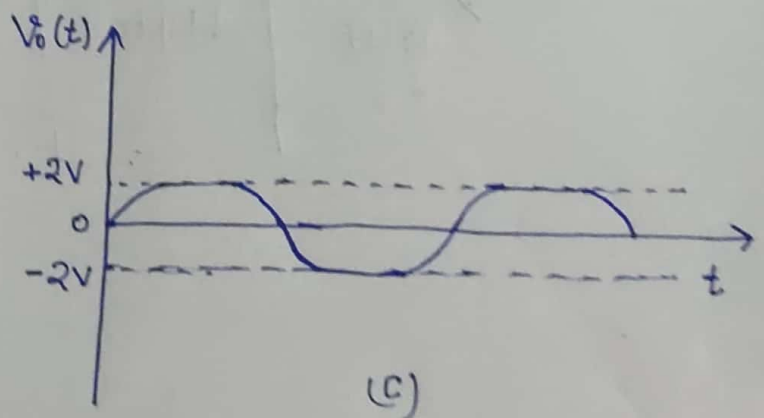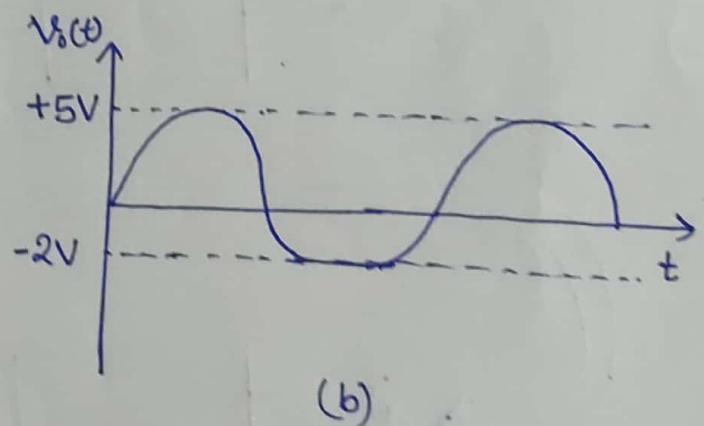

Application of Clipper Circuit

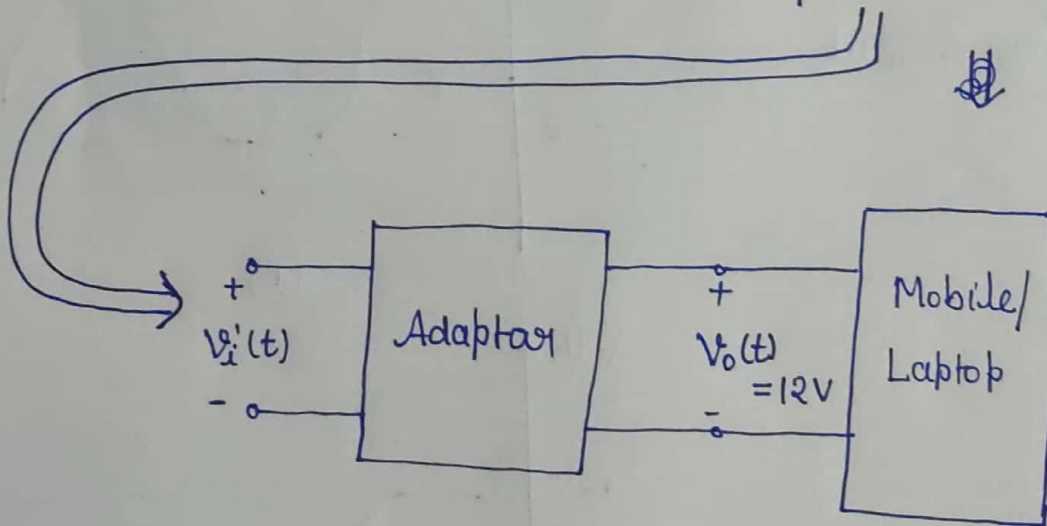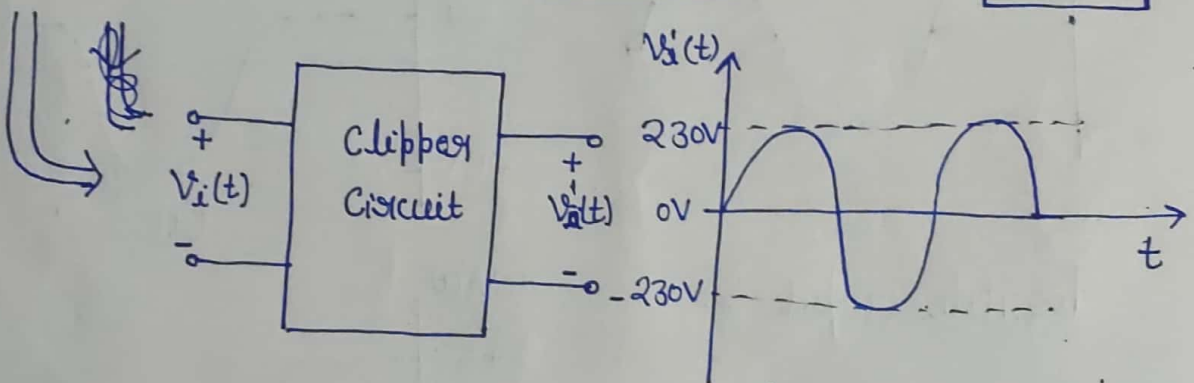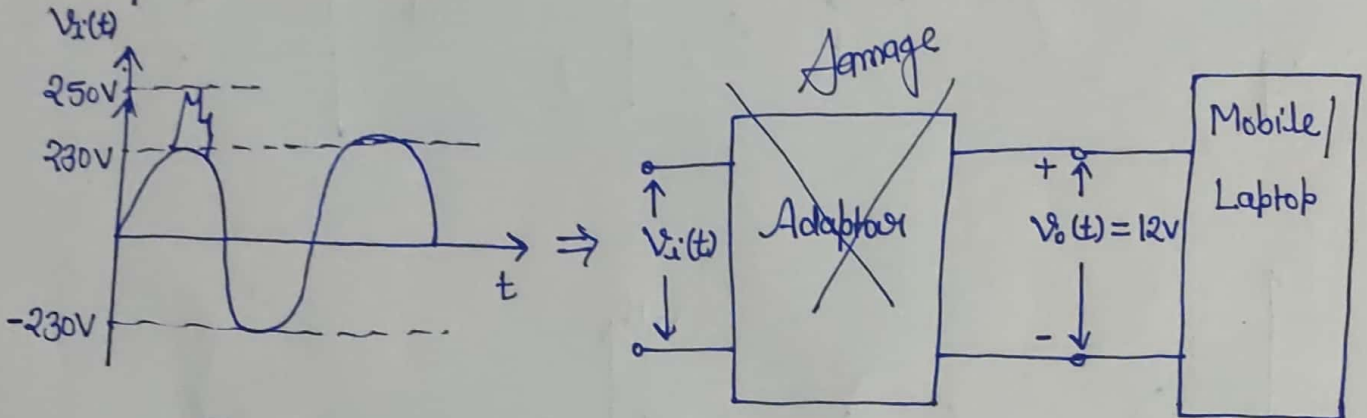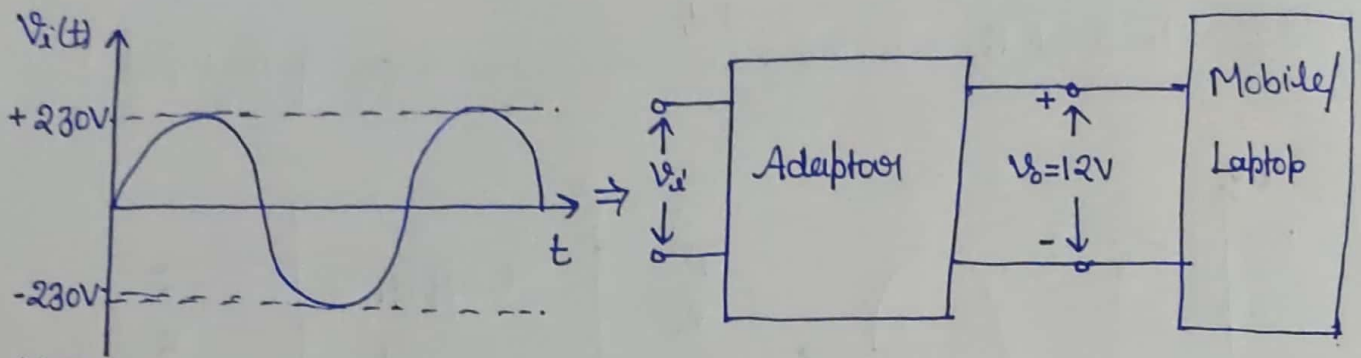

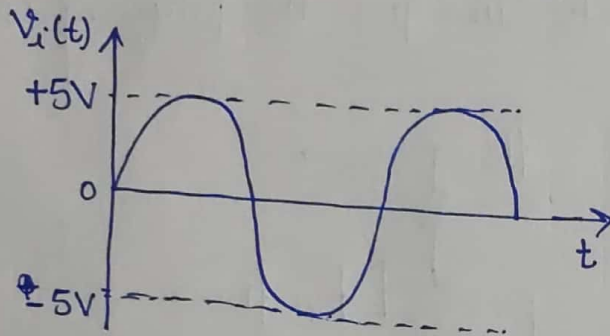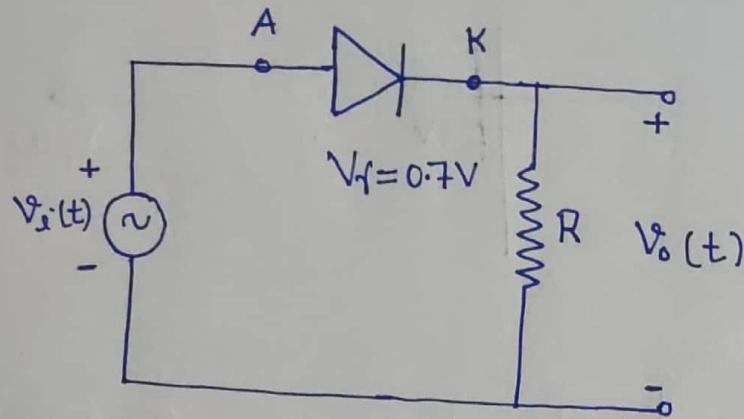
Example-1: Determine V_o and transfer characteristics for the given circuit?



$$V_i(t) = 5 \sin \omega t$$


Sol:-

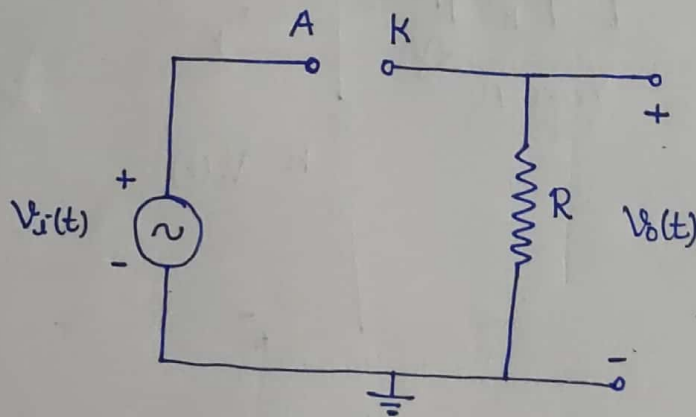Step 1: Determine the condition for F.B. and R.B.




D is F.B. if
 $V_A - V_K > 0.7V$



D is R.B. if
 $V_A - V_K \leq 0.7V$

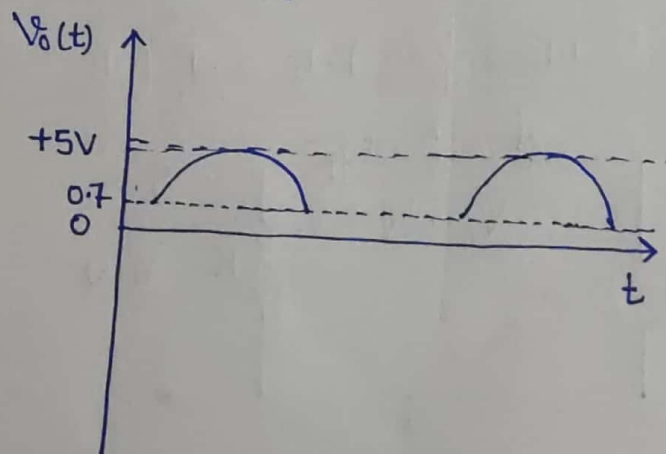


Transfer characteristics

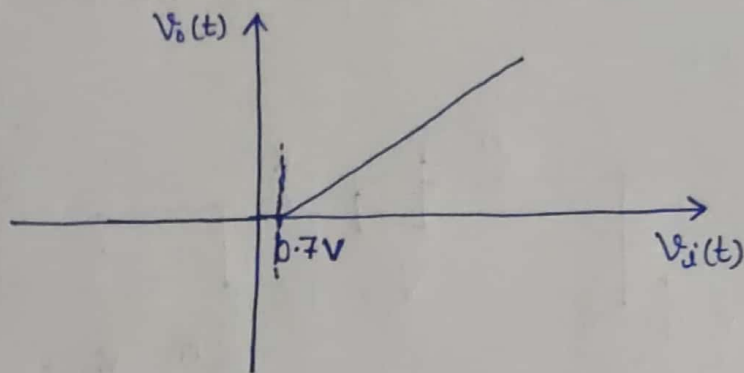

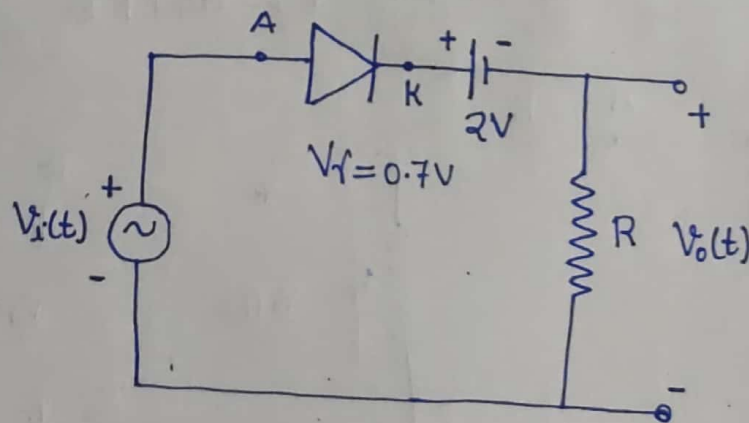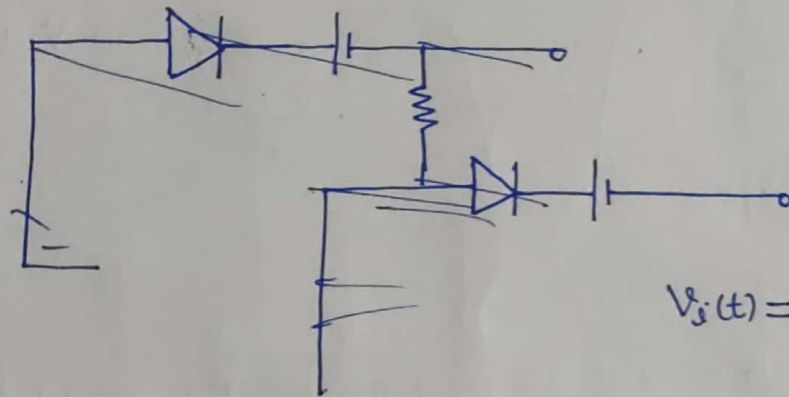Ex:- Find V_o and transfer characteristics for the following circuit?



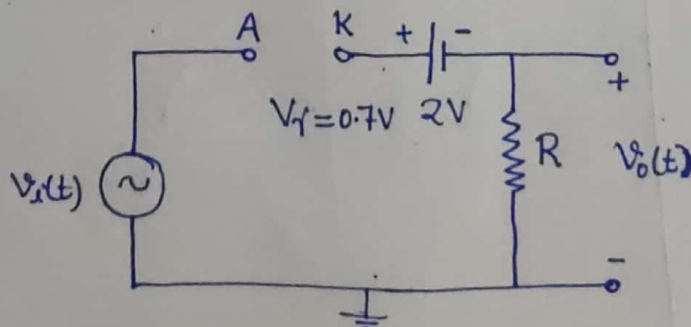
Sol: Determine the condition for F.B. and R.B.



For F.B.


$$\begin{aligned} V_A - V_K &> 0.7 \\ V_i(t) - 2 &> 0.7 \\ V_i(t) &> 2.7V \end{aligned}$$

Step 2: Determine $V_o(t)$

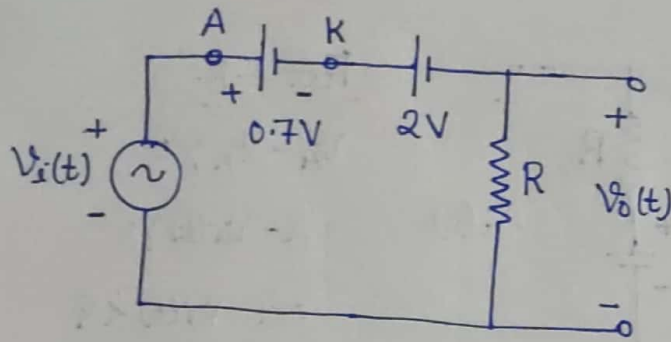


$$V_o(t) = \begin{cases} V_i(t) & \text{if } V_i(t) > 2.7 \\ -2.7 & \text{if } V_i(t) \leq 2.7 \end{cases}$$

Step 3: Transfer characteristics

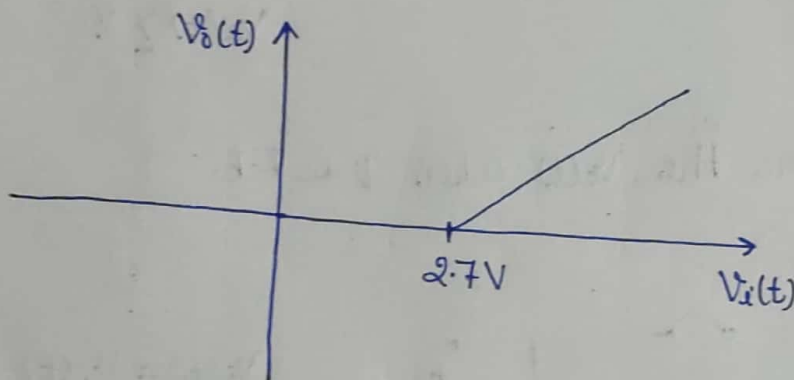


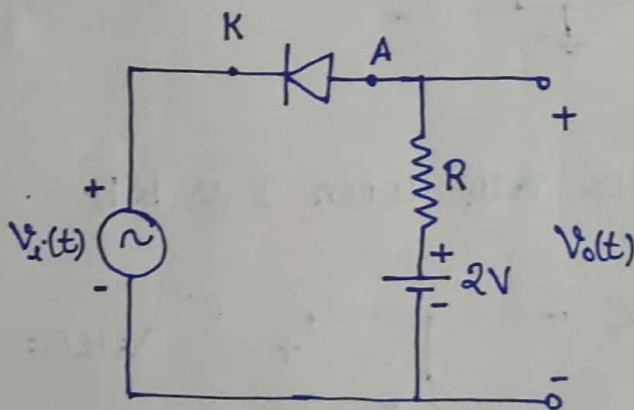Example 4: Find V_o and transfer characteristics for the given circuit?



Given that
 $V_i(t) = 10 \sin \omega t$

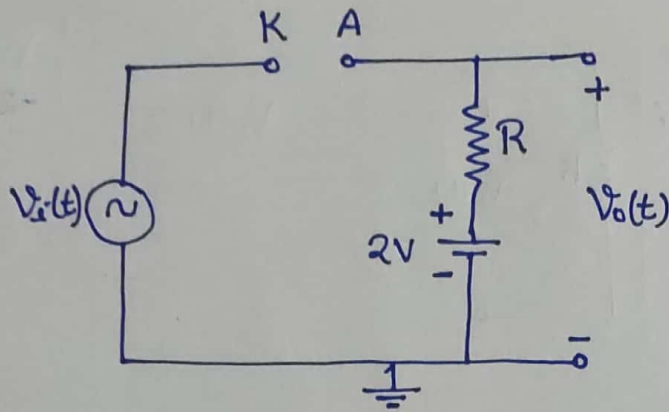Sol: Step 1: Determine the condition for F.B. and R.B.



For F.B.

$$V_A - V_K > 0$$

$$2 - v_i(t) > 0$$


$$\text{or } v_i(t) < 2$$

For R.B.

$$V_A - V_K \leq 0$$


$$v_i(t) \geq 2$$

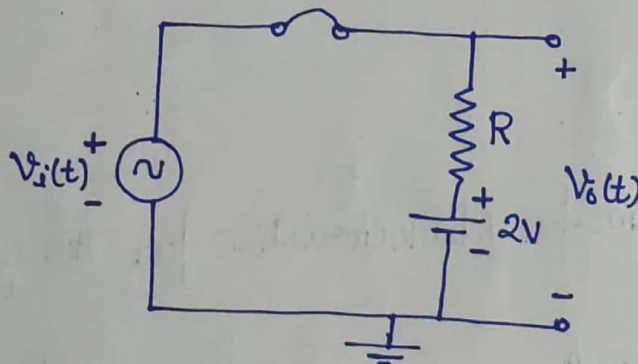Step 2: Determine the $v_o(t)$ when \mathcal{D} is F.B.



$$v_o(t) = v_i(t)$$

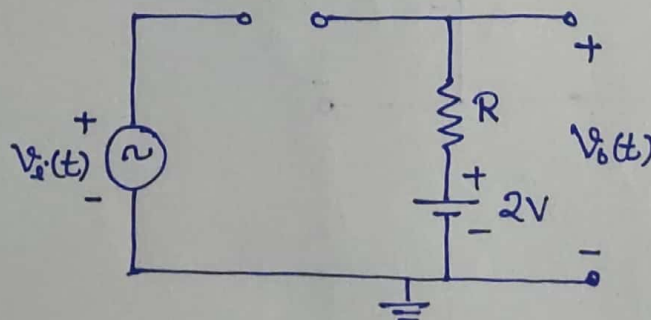
Step 3: Determine the $v_o(t)$ when \mathcal{D} is R.B.




$$v_o(t) = 2V$$

Step 4: Plot $V_o(t)$


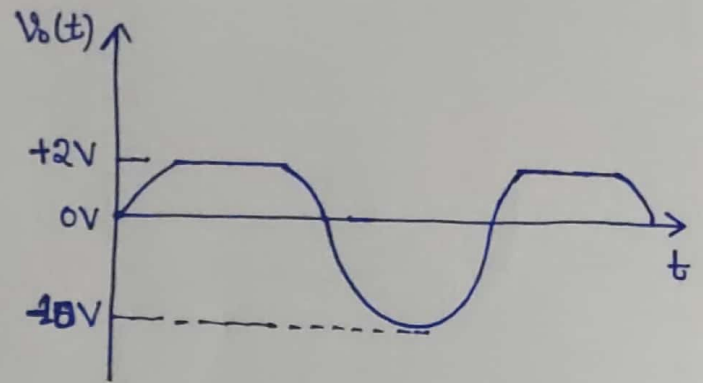
$$V_o(t) = \begin{cases} V_i(t) ; & \text{if } V_i(t) < 2V \\ 2V ; & \text{if } V_i(t) \geq 2V \end{cases}$$




Step 5: Transfer Characteristics

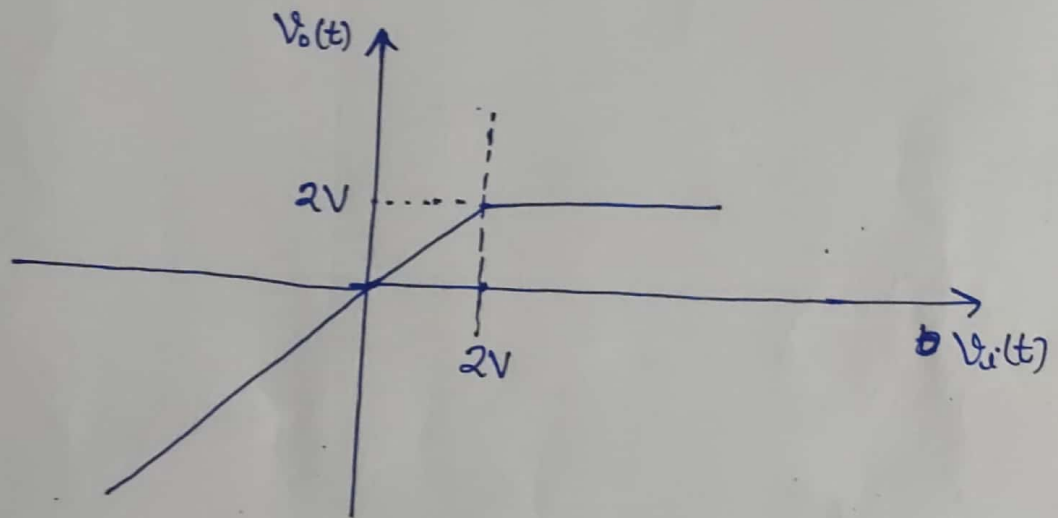

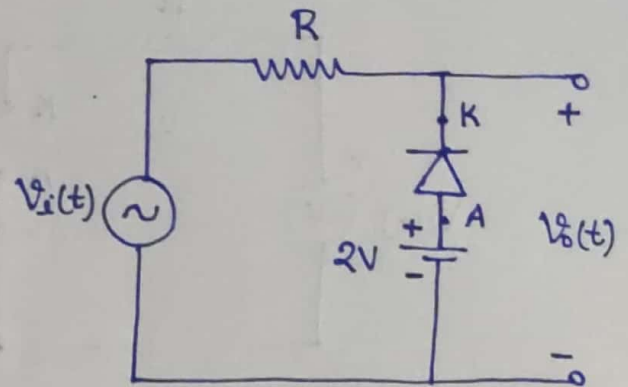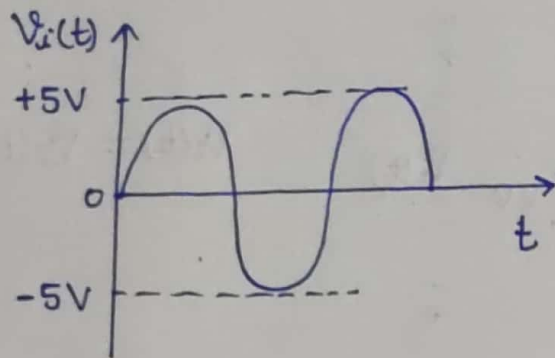Example: Determine $V_o(t)$ and transfer characteristics for the given circuit?



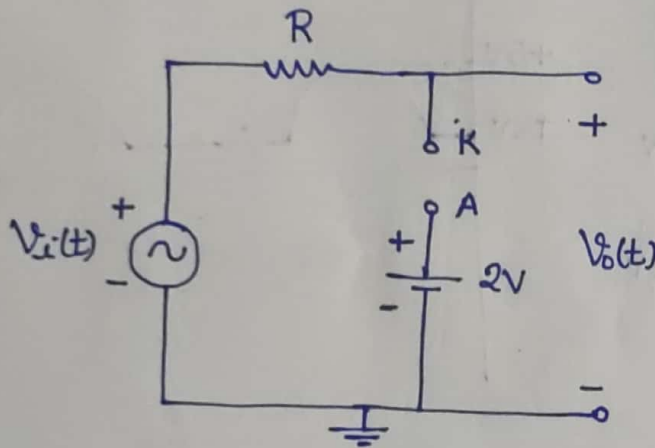Sol: Step 1: Determine condition for F.B. and R.B.



For F.B.

$$V_A - V_K > 0$$

$$2 - V_i(t) > 0$$

$$V_i(t) < 2V$$


For R.B.

$$V_A - V_K \leq 0$$

$$2 - V_i(t) \leq 0$$


$$V_i(t) \geq 2V$$

Step 2: Determine V_o when D is in F.B.

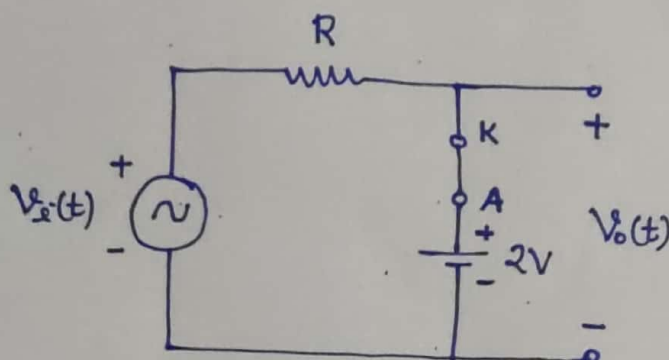


$$V_o(t) = 2V ; \text{ if } V_i(t) < 2V$$

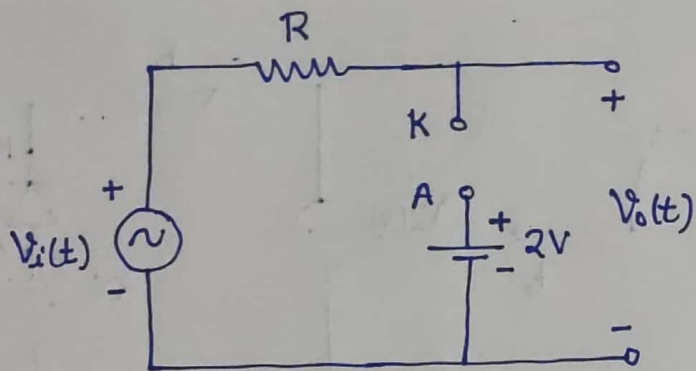Step 3: Determine $V_o(t)$ when \mathcal{D} is R.B.



$$V_o(t) = V_i(t); V_i(t) \geq 2V$$

Step 4: Plot $V_o(t)$

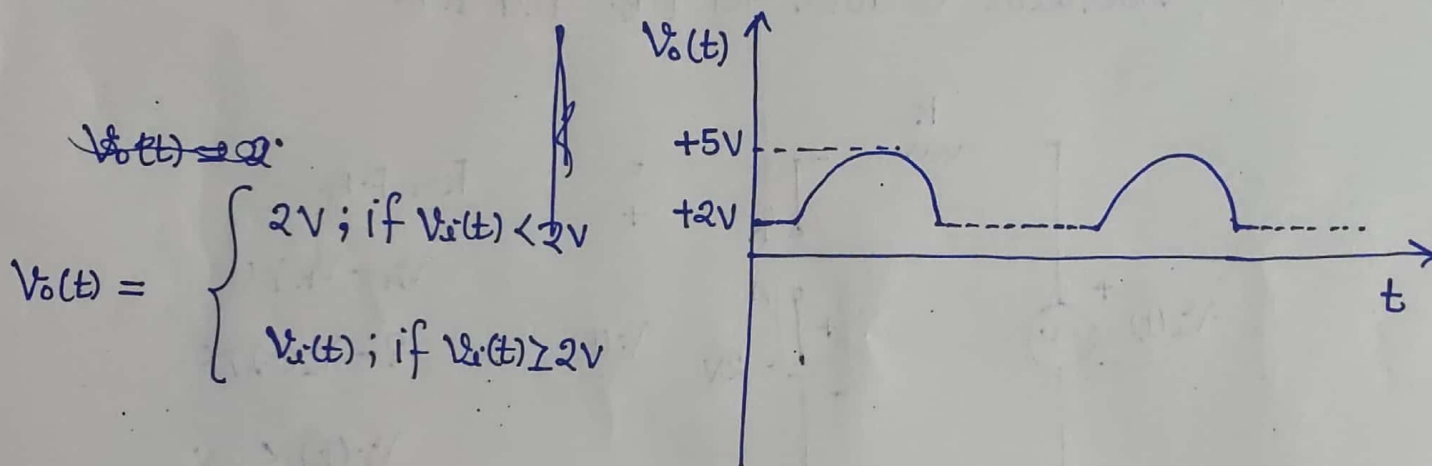

Step 5: Plot Transfer characteristics

