
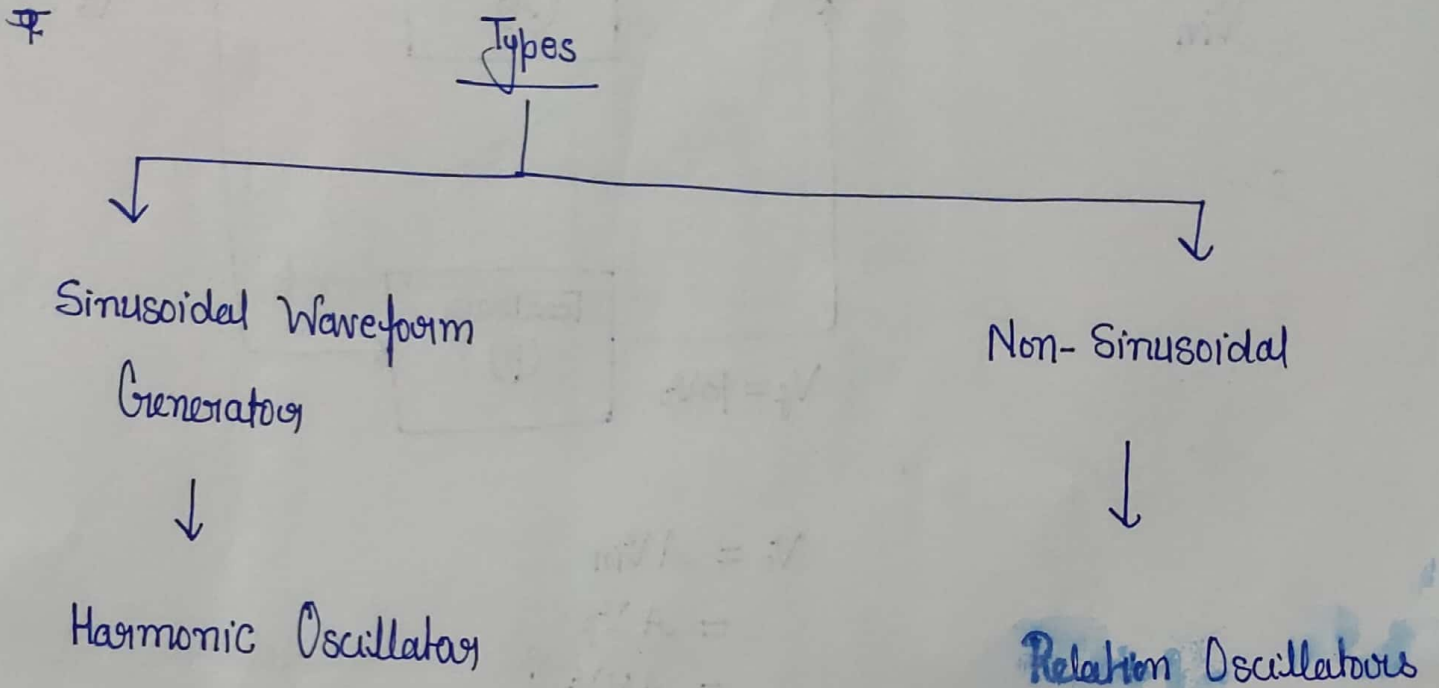


Oscillators


Function: Waveform generator/Generation

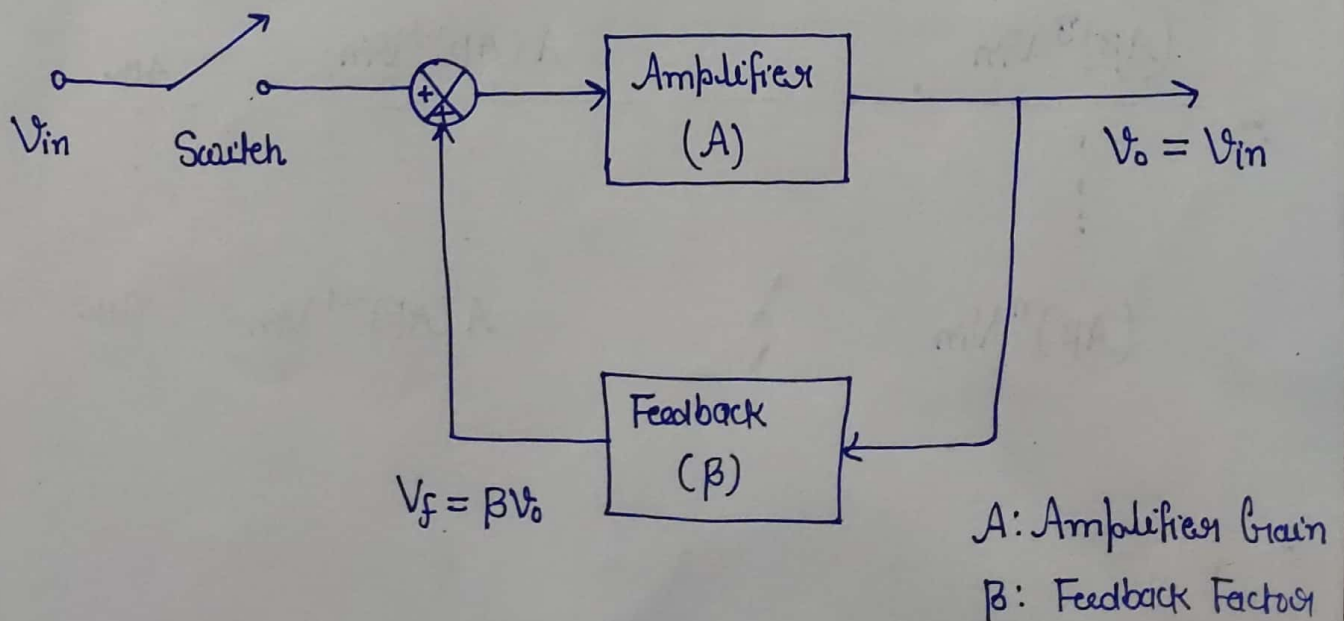

Principle of operation



Case-3: Sustained Oscillations

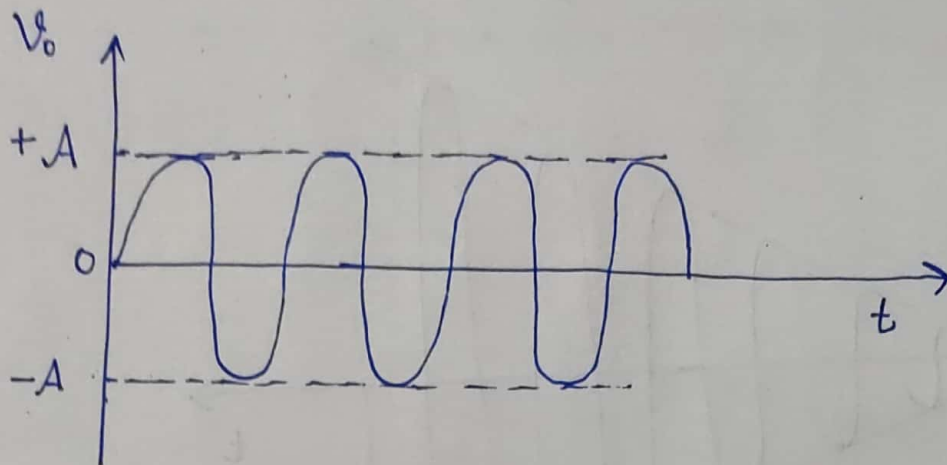

$$|AB| = 1$$

$$\angle AB = 2n\pi$$

Barkhausen Criteria

Classification of Oscillators

↓
Audio Frequency Oscillators

$$(20 \text{ Hz} < f < 20 \text{ KHz})$$


- ✓ 1. RC Phase Shift
- ✓ 2. Wein Bridge

↓
Radio Frequency Oscillators

$$(f > 20 \text{ KHz})$$

- ✓ 1. LC Oscillators
2. Crystal Oscillators

RC Phase-Shift Oscillators

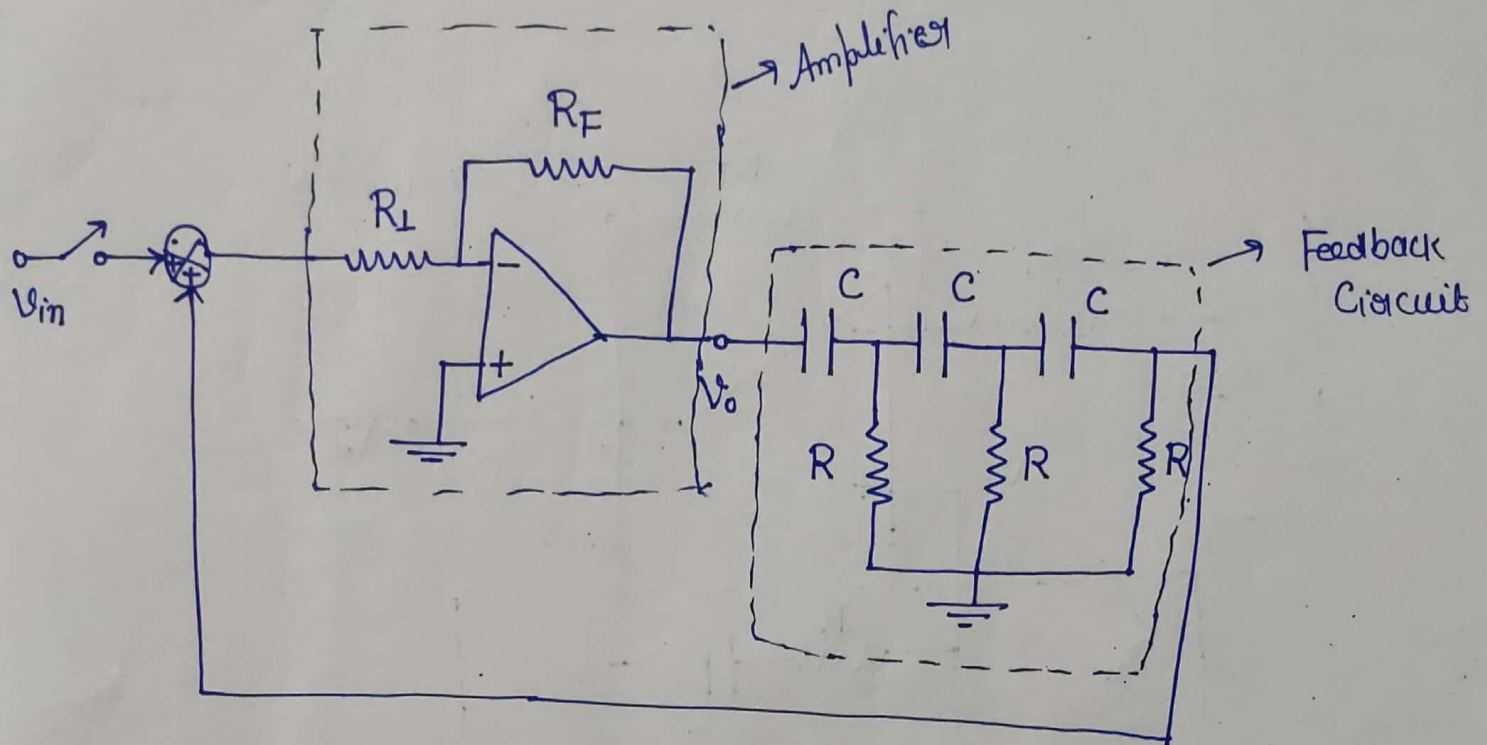

$$A = - \frac{R_F}{R_1} = \frac{V_o}{V_f}$$

$$|A\beta| = 1$$
$$\angle A\beta = 2n\pi; \quad n=1,2,\dots$$

$$\omega = \frac{1}{RC\sqrt{6}}$$


$$\beta = - \frac{1}{29}$$

$$A\beta = 1$$

$$\left(-\frac{R_F}{R_1}\right)\left(-\frac{1}{29}\right) = 1$$

$$R_F = 29R_1$$

Wien Bridge Oscillator

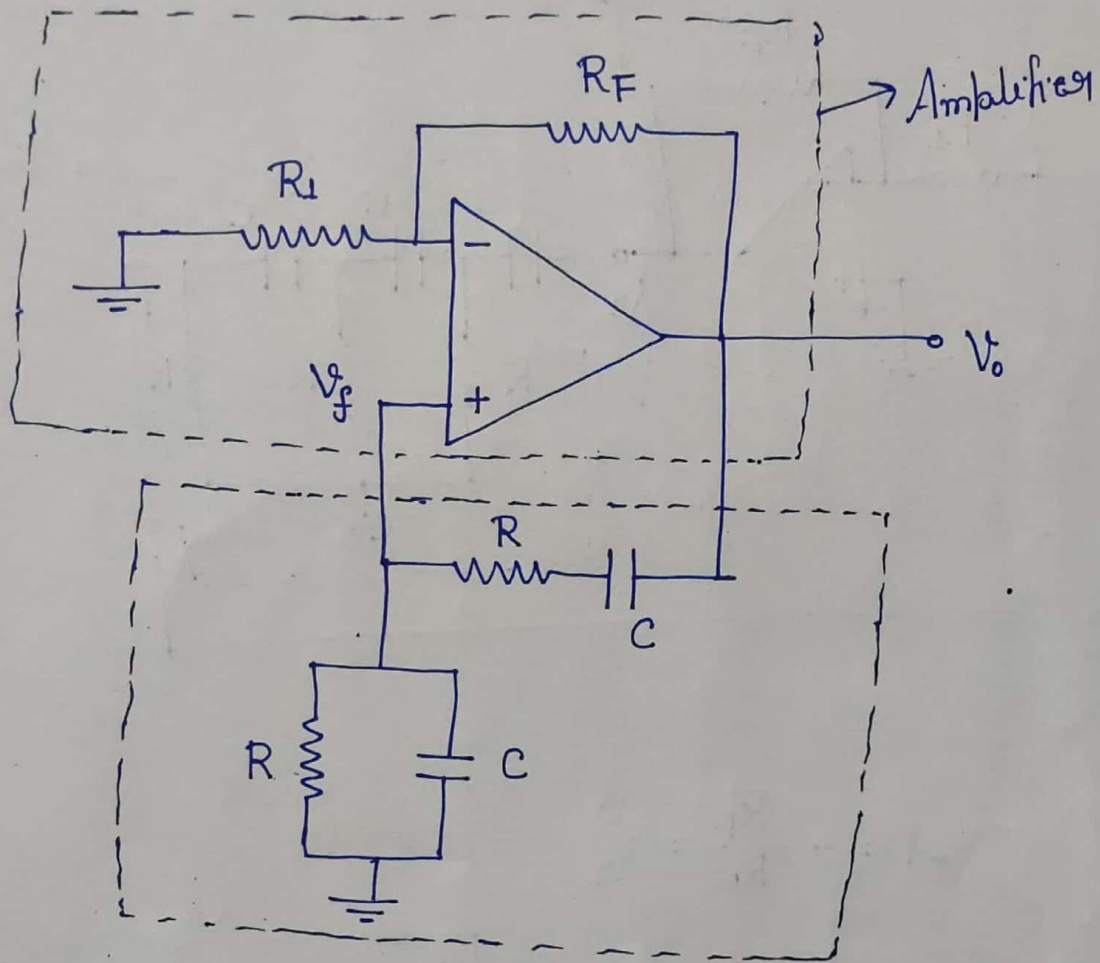

$$A = - \frac{R_F}{R_1}$$

$$\beta = ?$$

$$\omega = ?$$


$$\omega = \frac{1}{RC}$$

$$\beta = \frac{1}{3}$$

$$|AB| = 1$$

$$\left| -\frac{R_F}{R_1} \cdot \frac{1}{3} \right| = 1 \Rightarrow R_F = 3R_1$$

LC Oscillator

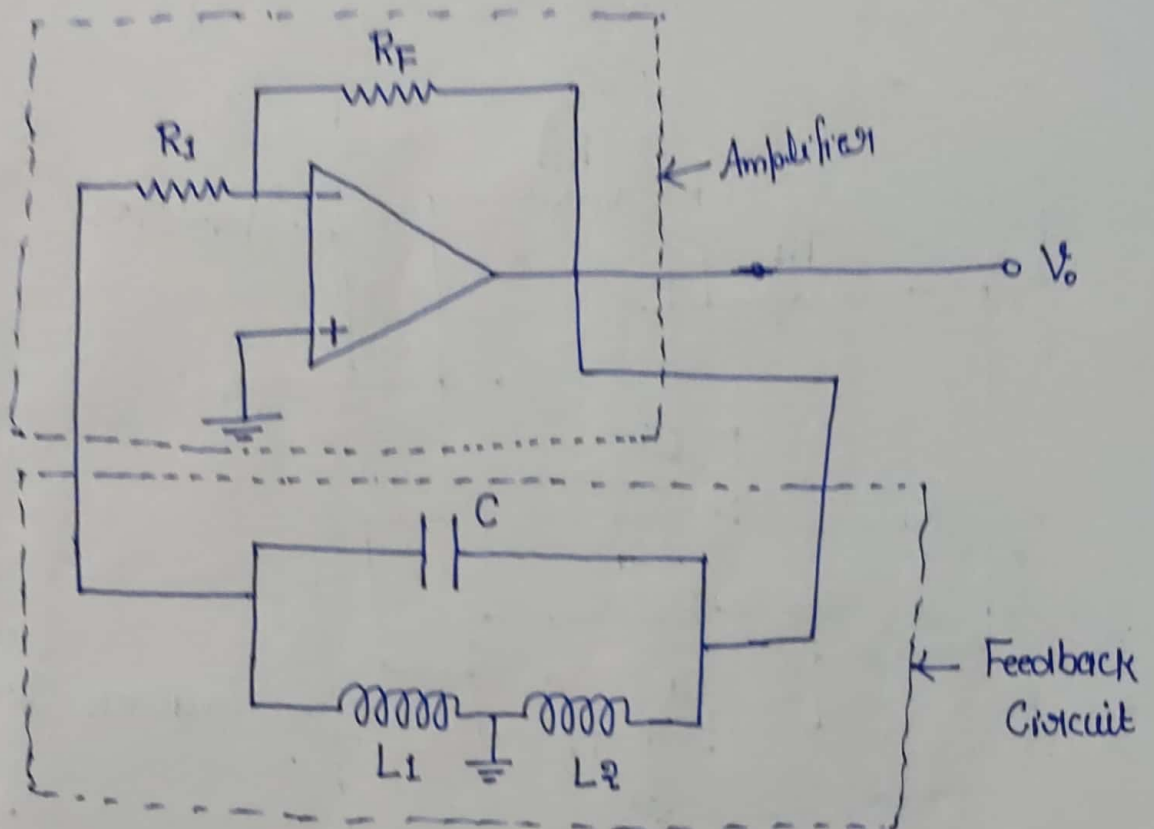

$$A = - \frac{R_F}{R_1}$$

$$\beta = ?$$

$$\omega = ?$$


$$\omega = \frac{1}{\sqrt{(L_1 + L_2)C}} = \frac{1}{\sqrt{L_{eq}C}}$$

If inductors are mutually coupled, then

$$L_{eq} = L_1 + L_2 + 2M$$

$$f = \frac{1}{2\pi \sqrt{L_{eq}C}}$$

Colpitts Oscillator

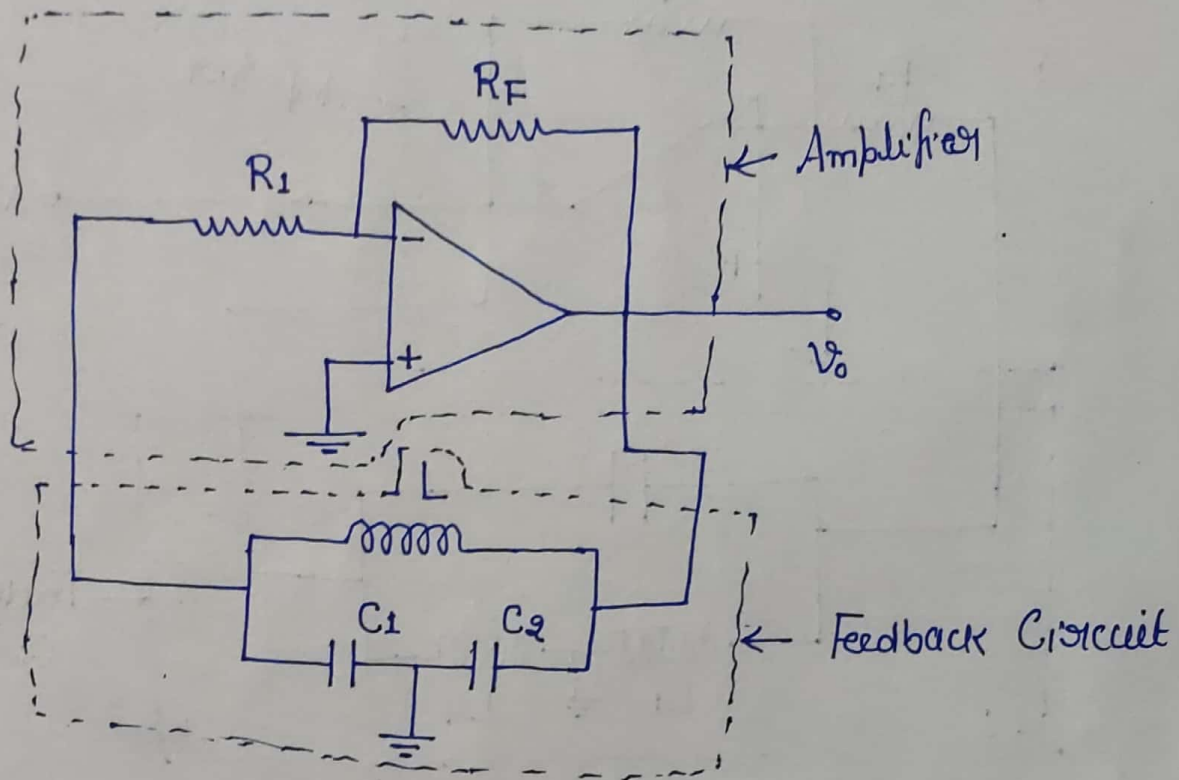

$$A = - \frac{R_F}{R_1}$$


$$\beta = ?$$

$$\omega = ?$$

$$\omega = \frac{1}{\sqrt{L C_{eq}}} \quad \text{and} \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$f = \frac{1}{2\pi \sqrt{L \cdot C_{eq}}}$$

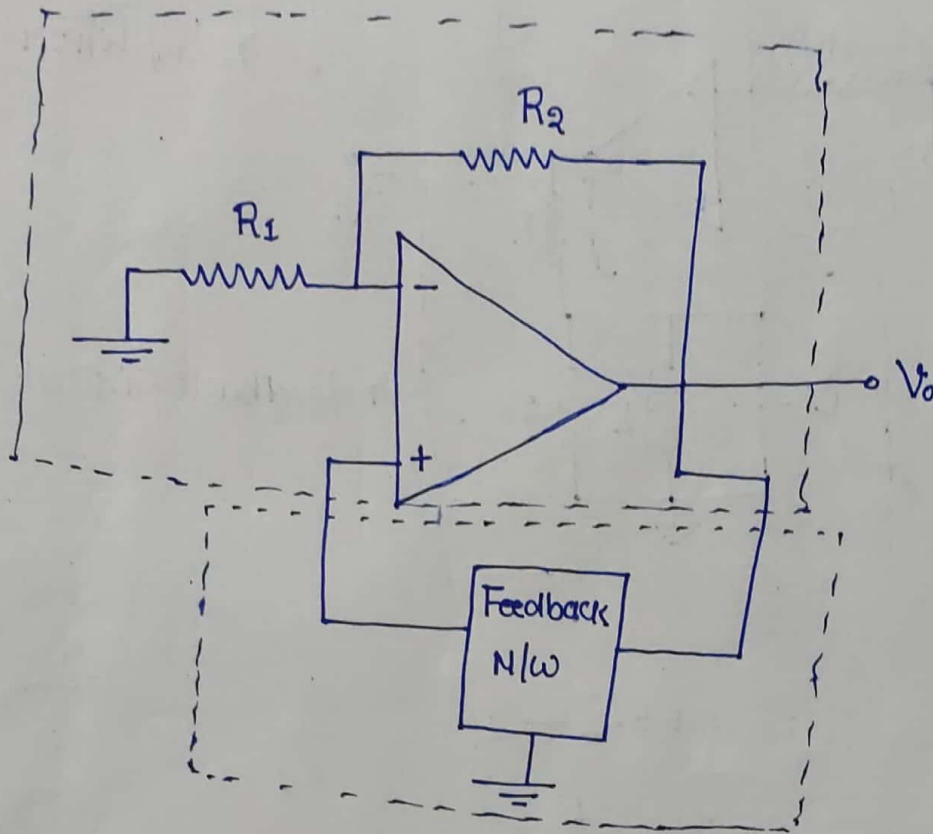Example:- Determine $\frac{R_1}{R_2}$? Given that $\beta = \frac{1}{6}$. Assume that the oscillator is providing sustained oscillations.




$$\text{Gain} = 1 + \frac{R_2}{R_1} = A$$

$$|A\beta| = 1$$

$$\left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1}{6} = 1 \Rightarrow \boxed{\frac{R_1}{R_2} = \frac{1}{5}}$$

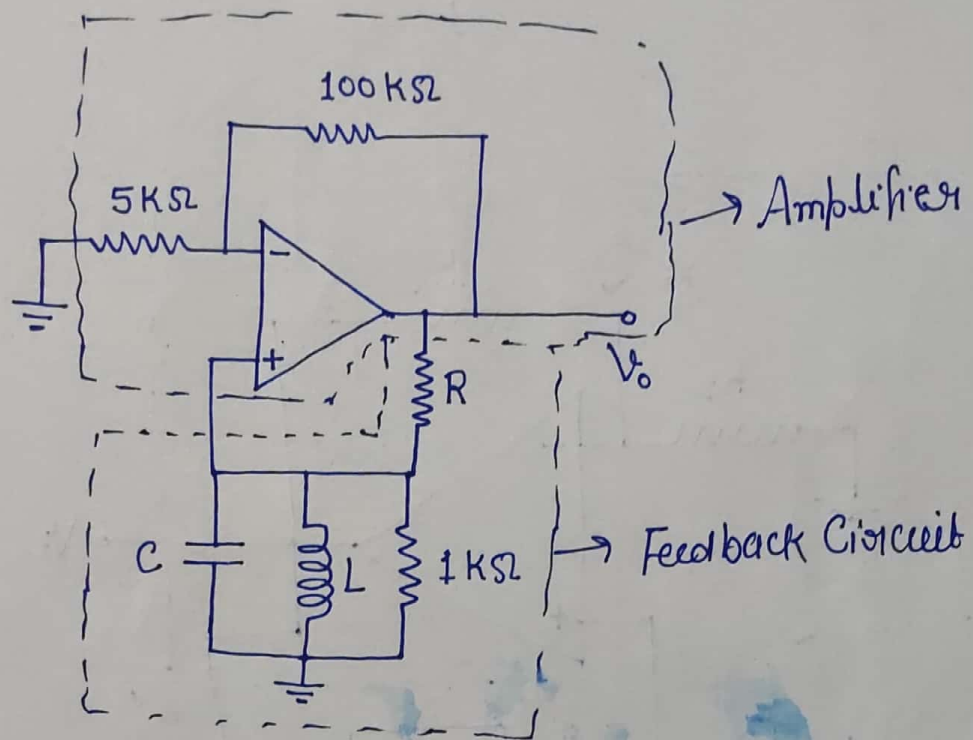Ex:- Find the Value of R ? Given that $L = 10 \text{ mH}$ and $C = 0.01 \mu\text{F}$.



$$A = 1 + \frac{100}{5} = 21$$

$$\beta = \frac{1}{1+R}$$

$$|A\beta| = 1 \Rightarrow 21 \times \frac{1}{1+R} = 1$$

$$R = 20 \Omega$$