
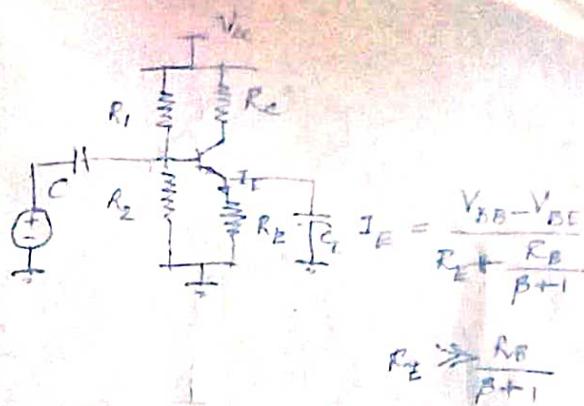


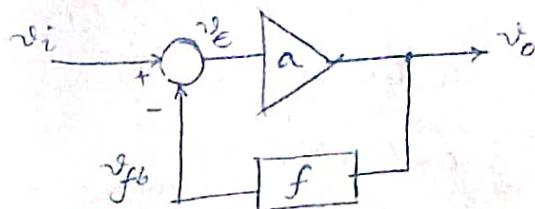

Ideal feedback configuration:



$$\begin{aligned} v_e &= v_i - v_{fb}, \quad v_{fb} = f \cdot v_o \\ &= v_i - f \cdot v_o \end{aligned}$$

$$V_{EB} = \frac{R_2}{R_1 + R_2} V_{cc}$$

$$v_o = a v_e$$

$$= a(v_i - f v_o)$$

$$= a v_i - a f v_o$$

$$v_o (1 + af) = a v_i$$


$$I = \frac{1}{2} \mu A e^{\frac{V_T}{V_{af}}} \quad (V_{af} - V_T)$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{a}{1 + af} = A \rightarrow \text{closed loop gain.}$$

$$af = T \rightarrow \text{loop gain}$$


100 K
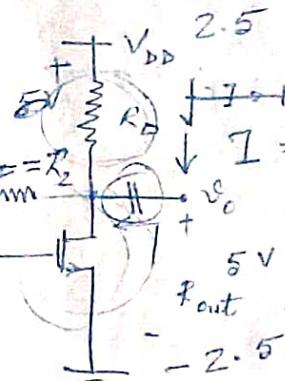
$$R_D = 10 \text{ k}\Omega \quad V_{RD} = 25 \text{ V}$$



shunt-shunt  
feedback amplifier

$$R_D, R_1, R_2 \gg 1$$

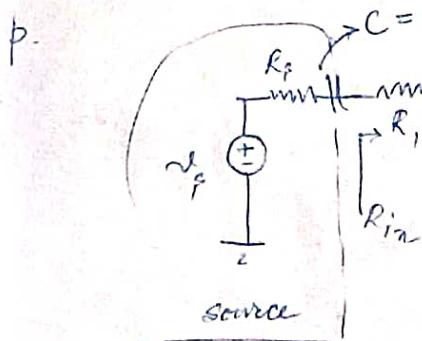

Pin no.:

G →

D →

S →

$$V_{DD} = 10 \text{ V}$$

$$\begin{aligned} R_1 &= 10 \text{ k}\Omega \\ R_2 &= 10 \text{ k}\Omega \end{aligned}$$

$$R_D = 1 \text{ M}\Omega, \quad 0.8 \text{ V}$$

$$\text{with } R_D = 10 \text{ k}\Omega$$

	<u>Input</u>	<u>f</u>	<u>Out</u>
(w/fb)	+0.001V	1 kHz	700 mV
(wo/fb)	1.08V	1 kHz	900 mV
with $R_D = 100 \text{ k}\Omega$			

$$(w/fb)$$

$$0.82 \text{ mV}$$

$$800 \text{ mV}$$

$$\frac{f}{1 \text{ Hz}} \quad \text{out}$$


$$1 \text{ kHz} \quad 1 \text{ kHz}$$

$$(wo/fb)$$

$$800 \text{ mV}$$

$$1 \text{ kHz}$$
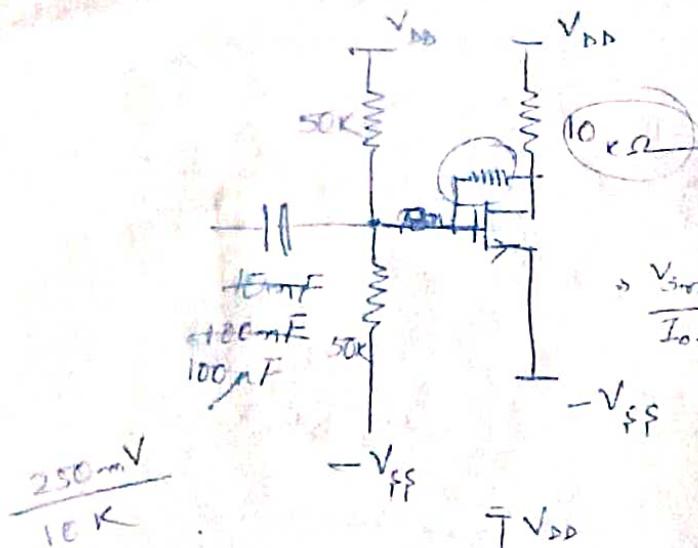
$$\frac{I_D}{2.5} = \frac{76 \mu A}{2.5}$$



$$V_F = 1.08 \text{ V p-p}$$

$$V_{IF\text{ rms}} = 360 \text{ mV}$$

$$V_R =$$


$$\frac{V_{IF\text{ rms}}}{I_{IF\text{ rms}}} = \frac{360 \text{ mV}}{250 \text{ mV}}$$

$$V_{DD} = 2.5$$

$$X 10 \text{ k} \quad R_D$$

$$= 14.4 \text{ k} \quad - \frac{V_{RD}}{R_D} = \frac{0.955}{10 \text{ k}}$$

$$= 95.5 \mu \text{A}$$

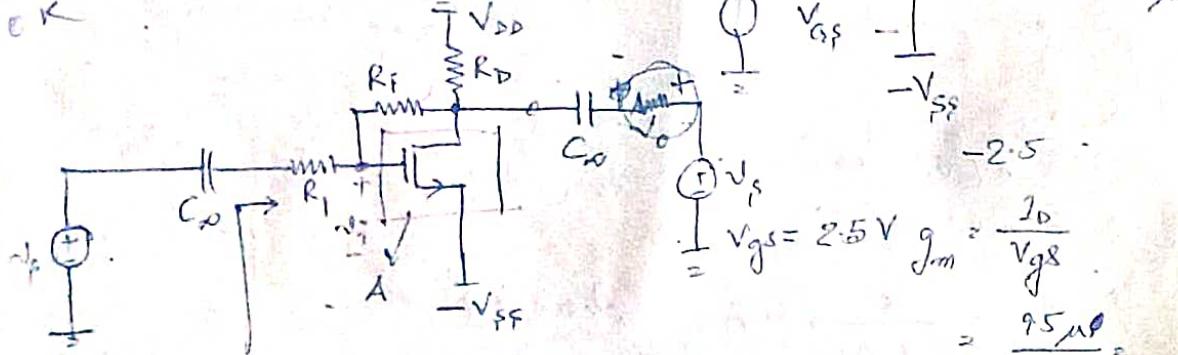

$$V_{GS} = 2.5 \text{ V}$$



$$g_m = \frac{I_D}{V_{GS}}$$

$$= \frac{95 \mu \text{A}}{2.5}$$

$$= 38.2 \text{ A/V}$$

$$= 38.4$$

A akt.

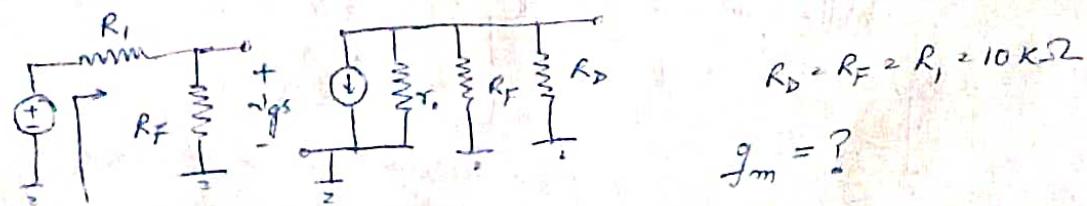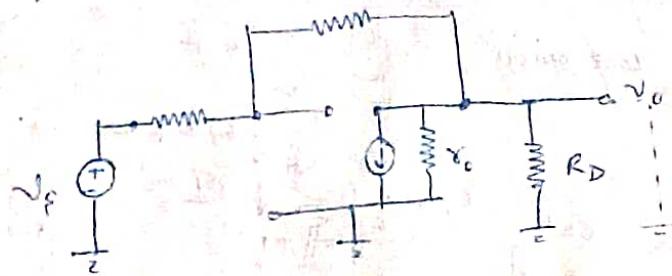

$$g_m = ?$$


$$R_i \quad r_o \rightarrow \infty$$

$$V_{GS} = V_{IF} \times \frac{R_F}{R_i + R_F}$$

$$R_i = \frac{(R_i + R_F)}{(1 + A_F)}$$

$$V_o = -g_m \times r_o \parallel R_F \parallel R_D \times V_{GS}$$
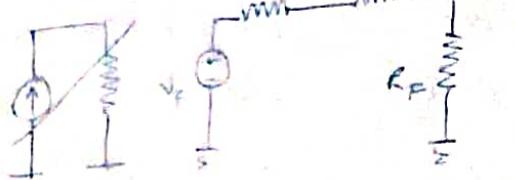
$$\approx -g_m \cdot R_F \parallel R_D \times V_{IF} \times \frac{R_F}{R_i + R_F}$$



$$= -g_m \times$$

$$V_o = -g_m \times (R_F \parallel R_D) \times V_{GS}$$

$$I_{IF}' = I_{IF} \times R_F \parallel (R_F + R_i)$$

$$= -g_m \cdot (R_F \parallel R_D) \times$$


$$\Rightarrow v_o = -g_m (R_F \parallel R_D) \times (R_F \parallel R_X) \times I_F$$

$$R_X > R_S + R_1$$

$$\Rightarrow \frac{v_o}{I_F} = \alpha A = -g_m (R_F \parallel R_D) \times (R_F \parallel R_X)$$

$$= -38.2 \text{ pA } 50K \times (50K) = -\frac{955}{2} = -95,500 \text{ for}$$

P indirekt:

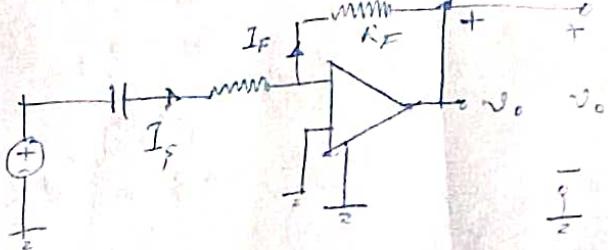

$$I_F = R_F \parallel R_D = 50K$$

$$\frac{I_F \cdot R_2}{V_o} = -\frac{I_F}{V_o} \cdot \frac{R_2}{R_2} = -\frac{1}{R_2}$$


$$\beta = \frac{I_F}{V_o}$$

$$\beta = -\frac{1}{R_2}$$

$$A\beta = + g_m (R_F \parallel R_D) \times (R_F \parallel R_X) \times \frac{1}{R_2} = + \frac{955}{10K} = \underline{\underline{-0.955}}$$

$$\frac{V_o}{I_F} = \frac{A}{1+A\beta} \approx \frac{1}{\beta} = \underline{\underline{-R_2}}$$


$$A\beta \approx +441.5$$

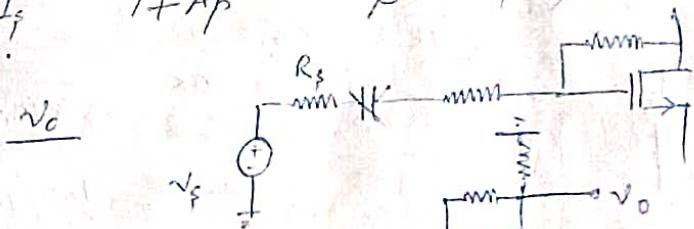

$$R_1 = R_2 = R_D = 50K$$

$$A_F = \frac{95500}{2.91}$$

$$= 32,817$$

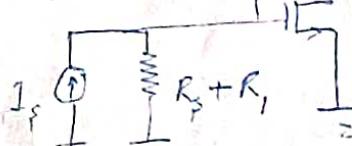

$$\frac{V_o}{I_F} = A_F$$

$$A_F = \frac{76,000}{2.52}$$

$$= 30,158$$

$$\frac{V_o}{I_F \times (R_F + R_1)} = -\frac{R_2}{R_F + R_1}$$

$$\approx -\frac{R_2}{R_1}$$

~~Handwritten note~~

$$\frac{V_o}{I_F} = -\frac{955}{1+0.0955} = -871$$

$$\frac{32,817}{50K}$$

$$\Rightarrow \frac{V_o}{R_F \times (R_F + R_1)} = -\frac{871}{10K}$$

$$\approx 0.65$$


$$R_F \parallel R_D = 50K \parallel 50K$$

$$= 25K$$




$$= \frac{25K}{2.52} = 10K$$

$$\frac{30,158}{50K} = 0.6$$

# Shunt-series feedback

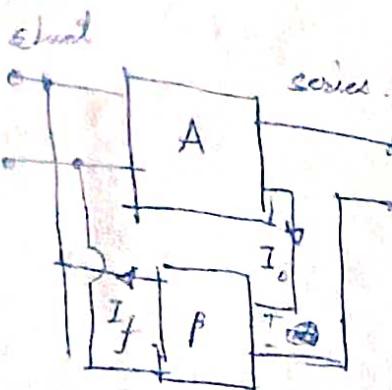

$$\rho = \frac{I_f}{I_o}$$

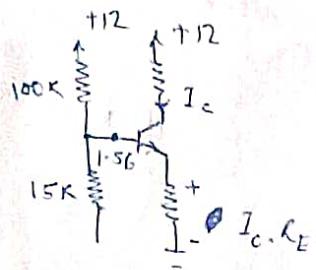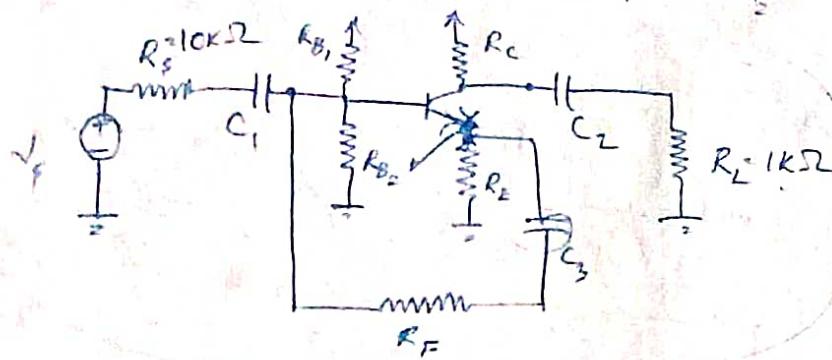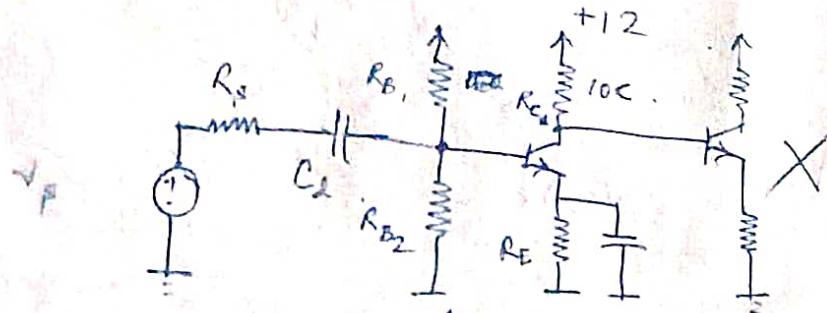

$$1.56 = 0.7 + I_c$$

$$\Rightarrow I_c = 865 \text{ mA}$$

$$\Rightarrow 0.865 \text{ mA}$$

$$R_{B1} = 100K$$

$$R_{B2} = 15K$$


$$R_{C_0} = 10K$$

$$R_E = 1K \quad R_F = 10K$$


$$C_1 = C_2 = C_3 = 1\mu F / 10\mu F$$

$$V_{BE} = 0.7$$

A ckt:

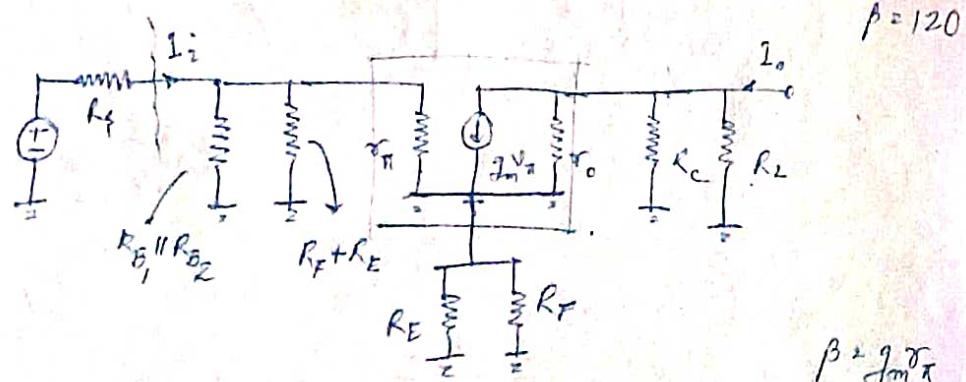

$$\beta = g_m r_\pi$$

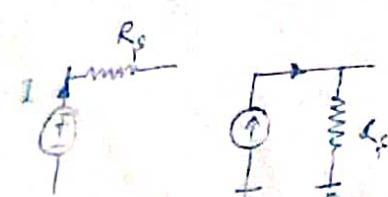

$$\text{with } R_{B1} = R_{B2} \quad g_m = \frac{I_c}{V_T} = \frac{33.27}{203.8} \text{ m}$$

$$\therefore I_c = \frac{6 - 0.7}{1K}$$


$$= 5.3 \text{ mA}$$

$$\Rightarrow r_\pi = \frac{120}{33.27} \text{ m}$$

$$= 3.6 \text{ K}$$

$$\therefore g_m^2 \Rightarrow r_\pi = \frac{120}{203.8} \text{ m} = 588$$

find  $1/P$  & o/p resistance

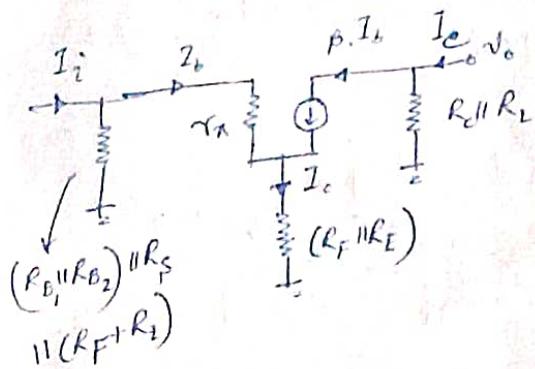

$$\frac{I_t}{I_i} \approx 1000$$

$$\frac{I_o \times (R_C || R_L)}{I_i \times 10K} = \frac{3 \times 1K}{10K}$$

$$(I_i - I_b) \left\{ (R_E || R_{B2}) || R_S || (R_F + R_E) \right\} = I_b \cdot r_a + \beta \cdot I_b (R_F + R_L)$$

$$I_o = (I_c - \beta I_b) R_C || R_L = I_c \approx I_o$$

$$I_o = \beta I_i + I_L = (\beta + 1) I_b$$

$$I_i \left\{ (R_E || R_{B2}) || R_S || (R_F + R_E) \right\} = I_b \left\{ r_a + \beta (R_F + R_E) + (R_E || R_{B2}) \right. \\ \left. || R_S || (R_F + R_E) \right\}$$

$$I_b = \frac{I_2 \times \{(13.0K) || 10K || 11K\}}{r_a + 120 \times (1K || 10K) + 3.73K} = \frac{I_2 \times 3.73K}{r_a + 109K + 3.73K} \\ \text{with } R_B = R_{B2} = 50K, \\ \Rightarrow 25K || 5.24K = 4.33K$$

$$1.3 \mu A$$

$$0.02 \mu A = \frac{I_2 \cdot 3.73K}{r_a + 109K + 3.73K} \Rightarrow I_o = (\beta + 1) \times I_2 \times \frac{(3.73K)}{(116.33K)}$$

$$= \frac{I_2 (3.73K)}{(116.33K)} = \frac{I_2 \times 4.33K}{109K + 109K + 4.33K} \quad \frac{I_o}{I_2} = 2.87 = \frac{121 \times 4.33}{113.9} \\ \Rightarrow \beta = 0.09 \quad = 4.6$$

$$\beta = \frac{R_E}{R_E + R_f} = \frac{1K}{11K} = I_2 \times \frac{4.33K}{113.9K} \cdot 1 + A\beta = 1 + 0.35 = 1.35$$

$$\Rightarrow A =$$

$$A = \frac{7.64K}{0.58K + 109K + 7.64K} \Rightarrow A_f = \frac{3.87}{1.35} = 2.86, \quad = 1.42 (R_B^2 R_f) \\ \therefore \frac{7.64}{117.22} \Rightarrow A_f = \frac{4.6}{1.42} = 3$$

$$f = 3.97$$

$$\frac{A}{1+AB} = 3.97$$

$$A = 3.97(1 + A \cdot 0.09)$$

$$A = 3.97$$

$$A = 0.36$$

$$A = 6.2$$

$$1 + AB$$

$$= 1 + 6.2 \times 0.09$$

$$1.58$$


$$V_{RF} = 287 \text{ mV}$$

$$I_f = \frac{287 \text{ mV}}{10K} = 28.7 \mu\text{A}$$

$$A = 3.97$$

$$V_{RE} = 119 \text{ mV}$$
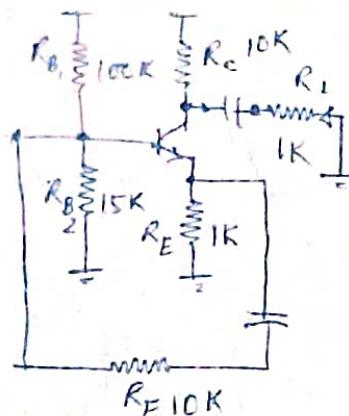
$$I_L = \frac{119 \text{ mV}}{1K} = 119 \mu\text{A}$$




$$A = 3.97$$

$$1 + AB = 1 + 3.97 \times$$

$$V_{RE} = 119 \text{ mV}$$
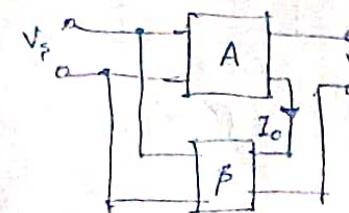
$$I_L = \frac{119 \text{ mV}}{1K} = 119 \mu\text{A}$$



$$R_F = 10K = R_C$$

$$R_L = R_E = 1K$$


$$V_{cc} = 12$$

$$V_c = 9.82V$$

$$I_c = 218 \mu\text{A}$$

$$g_m = \frac{218 \mu}{26m}$$

$$= 8.38 \text{ m}$$

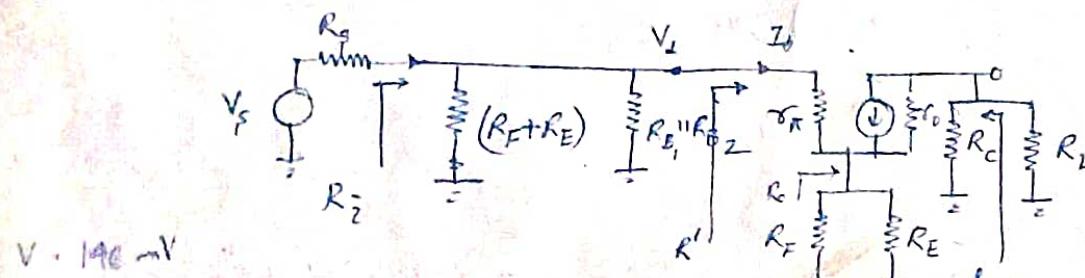

$$i_o R_L = i'_o R_C$$

$$R_i = (R_F + R_E) \parallel (R_B \parallel R_S) \parallel R' \quad \leftarrow \rightarrow \infty \quad \Rightarrow i'_o = \frac{i_o R_L}{R_C} \\ = i_o \cdot \frac{R_L}{R_C} = i_o \cdot \frac{1}{10}$$

$$R' = \frac{V_I}{I_b} \quad V_I = I_b \cdot r_\pi + (\beta + 1) I_b \cdot (R_F \parallel R_E)$$

$$= I_b \left\{ r_\pi + (\beta + 1) (R_F \parallel R_E) \right\}$$

$$\Rightarrow R_i = (R_F + R_E) \parallel (R_B \parallel R_S) \parallel \left\{ r_\pi + (\beta + 1) \left( \underline{\underline{R_F \parallel R_E}} \right) \right\}$$

$$= 11K \parallel 13K \parallel \{ 3.6K + 121 \times 0.9K \}$$

$$= 11K \parallel 13K \parallel 112.5K$$

$$= 11K \parallel 11.65K = 5.65K$$

$$\Rightarrow R_{if} = \frac{5.65K}{1.35} = 4.19K$$

$$R_i = 5.087 K\Omega$$

Exp

$$-I_f R_f = (I_f + I_o)$$

$$I_f R_f + (I_f + I_o) R_E = 0$$

$$\Rightarrow I_f (R_f + R_E) = -I_o R_E$$

$$\Rightarrow \frac{I_f}{I_o} = \beta = -\frac{R_E}{R_f + R_E}$$

Output Res.:

$$R_o = R_c$$

$$R_{of} = R_o(1 + A\beta) \quad r_o \approx 86 \text{ M}\Omega$$

$$R_c = (R_E \parallel R_F) + \frac{r_o}{\beta+1} + \frac{R_C \parallel r_o}{\beta+1}$$

$$= 0.9K + \frac{8.6K + 8.9K}{121}$$

$$= 0.9K + 10\Omega = 1K$$

$$R_{of} = 1K \times (1 + A\beta) = 1.35K$$


$$R_{out} = r_o [1 + 33.27m \times (r_o \parallel R_{of})]$$

$$= 86K [1 + 33.27m \times 0.98K]$$


$$= 2.8M\Omega$$



$$\Rightarrow R_{out, net} = 2.8M \parallel 10K$$

shunt-shunt

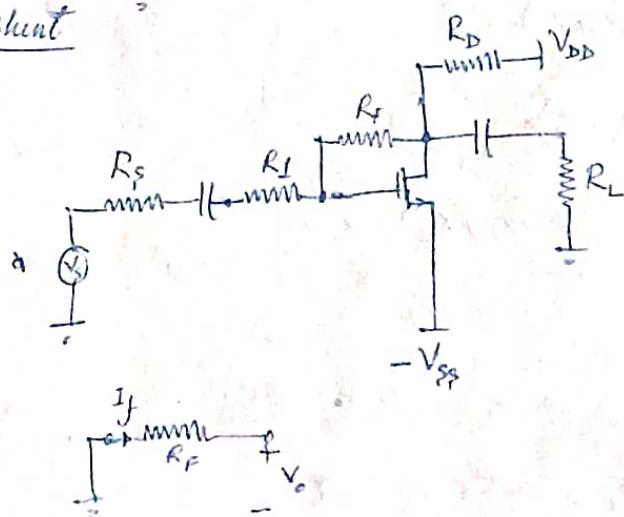

Acht:

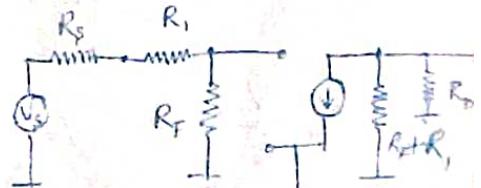

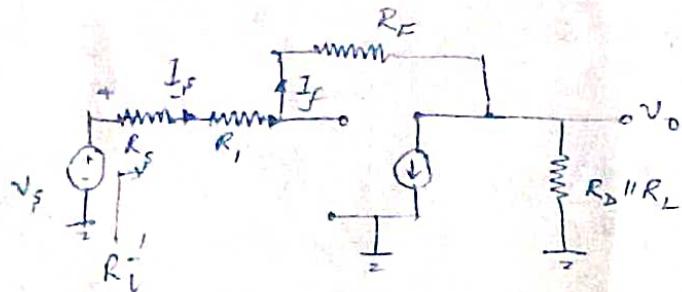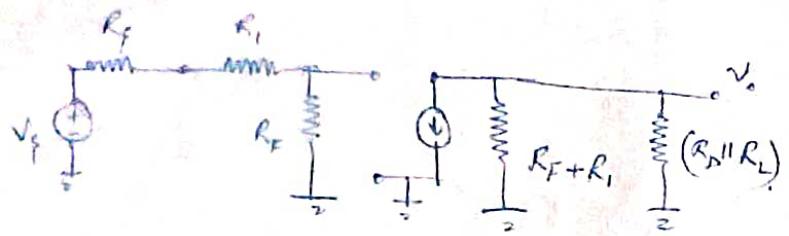


$$\text{ist, } R_D = R_L = 10K$$

$$R_f = 10K$$

$$R_i = R_f = 50K$$

Acht:

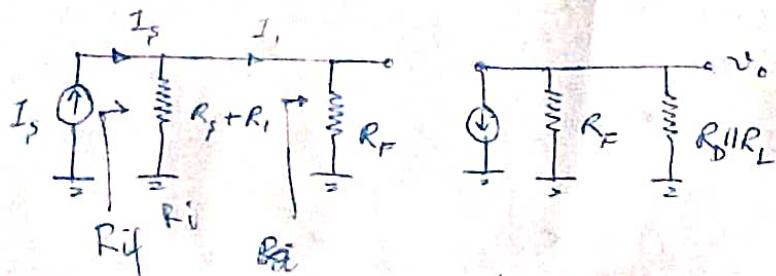

$$R_f' = R_f + R_i$$

$$\Rightarrow V_{GS} = (I_s - I_o) R_f' = I_o R_f$$

$$\Rightarrow I_o (-) \rightarrow (I_s - I_o) R_f' = I_o R_f$$

$$\Rightarrow I_o (R_f' + R_f) = I_s R_f'$$

$$\Rightarrow I_o = \frac{I_s R_f'}{R_f' + R_f}$$

$$V_o = -g_m \times (R_f' || R_D || R_L) V_{GS} \quad g_m = 38.2 \mu A/V$$


$$\frac{V_o}{I_s} = -g_m \times (R_f' || R_D || R_L) \times \frac{R_f' R_f}{R_f' + R_f}$$

$$\frac{V_o}{I_s} = -g_m \times \frac{(R_f' || R_D || R_L) \times R_f' R_f}{R_f' + R_f} = A$$

$$= -38.2 \times 4.5K \times (60K || 50K)$$

$$= -38.2 \mu \times 4.5K \times 27.27K$$

$$= -4675.7 \text{ V/A}$$

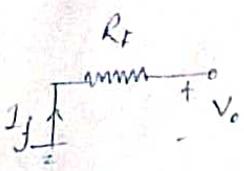

$$V_o = -I_f R_F \quad \rho = \frac{I_f}{V_o}$$

~~$\therefore A_f = \frac{I_f}{V_i} = \frac{1}{R_F}$~~

$$\begin{aligned} \therefore A\beta &= -4675.7 \times -\frac{1}{R_F} \\ &= -4675.7 \times -\frac{1}{50K} \\ &= 0.0935 \end{aligned}$$

$$\therefore 1 + A\beta = 1.0935$$

$$\Rightarrow A_f = \frac{A}{1 + A\beta} = -4276$$

$$R_i = \frac{R_F}{1 + A\beta} = \frac{50K}{1.09} = 45.87K$$

$$\therefore R'_i = R_s + R_i + R_i = 60K + 45.87K = 105.87K$$

$$R_{if} = \frac{R_i}{1 + A\beta} \quad R_i = (60K \parallel 50K) \\ = 27.27K$$

$$\Rightarrow R_{if} = \frac{27.27K}{1.09} \approx 25.02K$$


If  $R_D = R_L = R_s = R_i = R_F = 10K$ ,

$$\frac{V_o}{I_S} = -38.2 \times 0.33K \times 6.67K \\ \approx -848.46$$


$$\rho = -\frac{1}{R_F} = A\beta = 0.085 \quad R_{if} = \frac{6.67K}{1.08} = 6.15K$$

~~$\therefore 1 + A\beta = 1.085$~~


series series

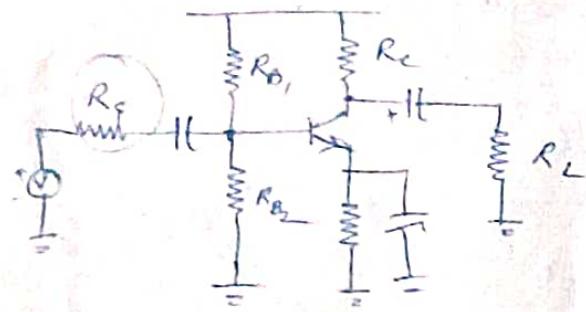
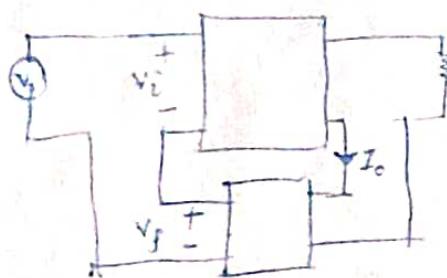
$$\begin{aligned}
 R_B1 &= 100\text{K} \\
 R_B2 &= 15\text{K} \\
 R_E &= 1\text{K} \\
 R_C &= 10\text{K} \\
 R_L &= 1\text{K} \\
 R_S &= 10\text{K}
 \end{aligned}$$




$$\beta = \frac{V_f}{I_o}$$

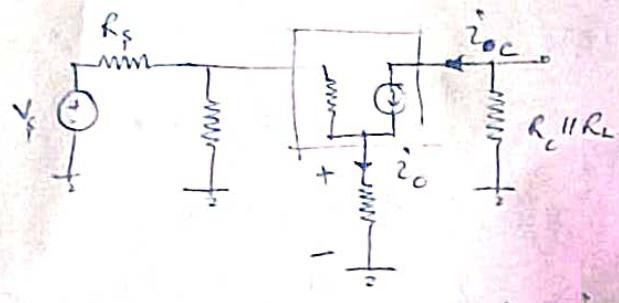

$$Z_o \approx Z_0$$

A akt:

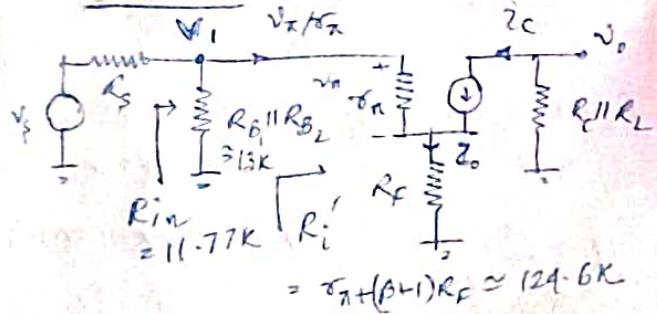

$$A = \frac{Z_o}{V_s}$$

$$= r_\pi + (\beta + 1) R_F \approx 124.6\text{K}$$

$$i_o = I_m \cdot r_\pi$$

$$\begin{aligned}
 i_o &= \frac{v_\pi}{r_\pi} + \beta \frac{v_\pi}{r_\pi} \\
 &= (\beta + 1) \frac{v_\pi}{r_\pi}
 \end{aligned}$$

(\*)

$$\frac{V_o - V_i}{R_s} = \frac{V_i}{R_B1 R_B2} + \frac{v_\pi}{r_\pi}$$

g (\*)

$$V_i = v_\pi + i_o R_F$$

$$V_s = V_i \left( \frac{1}{R_s} + \frac{1}{R_B1 R_B2} \right) + \frac{v_\pi}{r_\pi}$$

$$= (v_\pi + i_o R_F) \left( \frac{1}{R_s} + \frac{1}{R_B1 R_B2} \right) + \frac{v_\pi}{r_\pi}$$

$$\Rightarrow \frac{V_s}{R_s} = \left( \frac{i_o \cdot r_a}{(\beta+1)} + i_o R_F \right) \left( \frac{1}{R_s} + \frac{1}{R_E'' R_{E_2}} \right) + \frac{i_o \cdot r_a}{\beta+1}$$

$$= i_o \left\{ \left( \frac{r_a}{\beta+1} + R_F \right) \left( \frac{1}{R_s} + \frac{1}{R_E'' R_{E_2}} \right) + \frac{1}{\beta+1} \right\}$$

$$\Rightarrow \frac{V_s}{i_o} = A = R_s \times \left\{ i_o \left\{ (29.75 + 1K) \left( \frac{1}{10K} + \frac{1}{10K} \right) + \frac{1}{121} \right\} \right\}$$

$$\Rightarrow \frac{i_o}{V_s} = \frac{1}{R_s \times} = i_o \times \left\{ (29.75 + 1K) \left( \frac{1}{10K} + \frac{1}{10K} \right) + \frac{1}{121} \right\}$$

$$r_a = 3.6K$$

$$= i_o \times 0.19$$

$$\Rightarrow \frac{i_o}{V_s} = \frac{1}{R_s \times 0.19} = \frac{1}{10K \times 0.19} = 526.3 \mu$$

$$\Rightarrow A = 526.3 \mu$$

$$\hat{\rho} = \frac{V_f}{I_o} = R_F = 1K$$

$$\Rightarrow A\hat{\rho} = 0.526 \Rightarrow 1 + A\hat{\rho} = 1.526$$

$$\Rightarrow A_f = \frac{A}{1 + A\hat{\rho}} = \frac{526.3 \mu}{1.526} = 345 \mu = \frac{i_o}{V_s}$$

$$\hat{i}_o \approx i_o, \text{ & } v_o = - i_o \times (R_C || R_L)$$

$$\equiv - i_o \times 0$$



$$\begin{aligned} \hat{i}_o &\approx A_f \times \\ A_f &= \frac{i_o}{V_s} \Rightarrow \hat{i}_o \approx i_o \\ &= A_f \cdot V_s \end{aligned}$$

$$A' G_o = \frac{v_o}{V_s}$$

$$\begin{aligned} \frac{v_o}{V_s} &= - A_f \cdot (R_C || R_L) \\ &= - 345 \mu \times 0.9K \end{aligned}$$

$$= - \frac{R_C || R_L}{R_F} \times \frac{R_{in}}{R_{in} + R_F} = - 0.3105$$

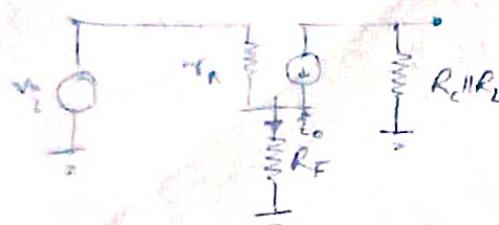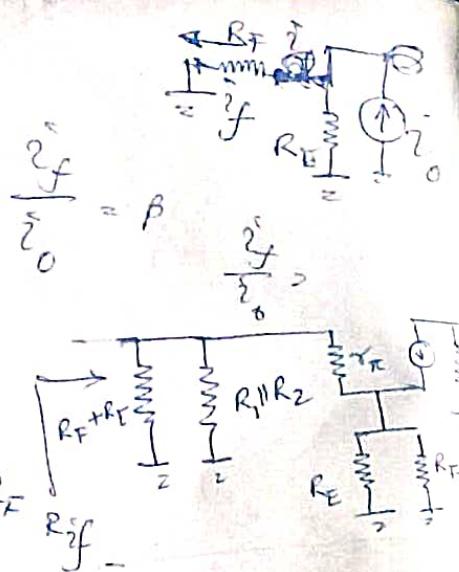
$$= - \frac{0.9K}{1K} \times \frac{11.77K}{11.77K + 10K} = - 0.48$$



$$V_f = \frac{V_{\pi}}{\gamma_{\pi}}$$

$$V_i$$
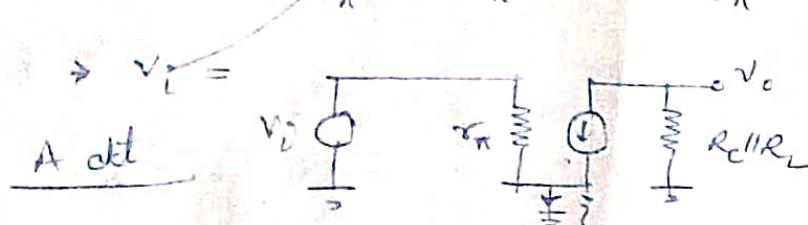
$$V_i = V_{\pi} + i_o R_F \quad \Rightarrow \quad i_o = \frac{V_{\pi}}{\gamma_{\pi}} + \beta \cdot \frac{V_{\pi}}{\gamma_{\pi}} = (\beta+1) \frac{V_{\pi}}{\gamma_{\pi}}$$



$$\Rightarrow i_o = \frac{V_{\pi}}{\gamma_{\pi}} + \beta \cdot \frac{V_{\pi}}{\gamma_{\pi}}$$

$$= (\beta+1) \frac{V_{\pi}}{\gamma_{\pi}} = (\beta+1) \frac{V_i}{\gamma_{\pi}}$$

$$\Rightarrow \frac{i_o}{V_i} = \frac{1}{\gamma_{\pi}(\beta+1)} = 33.6 \text{ m}$$

$$i_o R_F = V_f \Rightarrow \frac{V_f}{i_o} = \beta = R_F$$

$$\Rightarrow A_f \beta = \frac{1}{\gamma_{\pi}(\beta+1)} \times R_F = \frac{1}{3.6 \times 121} \times 1K =$$

$$\Rightarrow 1+A\beta = 1+33.61 = 34.61 = \frac{1000}{29.75} = 33.61$$




$$\Rightarrow A_f = \frac{i_o}{V_i} = \frac{A}{1+A\beta} = \frac{33.6 \text{ m}}{34.61} = 97/\mu$$

$$\Rightarrow i_o \approx i_c, \quad \frac{V_o}{V_i} \approx - \frac{R_C \parallel R_L}{R_F} = \frac{0.9K}{1K} = 0.9$$

$$\Rightarrow V_o = -i_o \times (R_C \parallel R_L) = -A_f \cdot V_i \cdot (R_C \parallel R_L)$$

$$\Rightarrow \frac{V_o}{V_i} = -A_f (R_C \parallel R_L) = -97/\mu \times 0.9K = -0.874$$

series-shunt

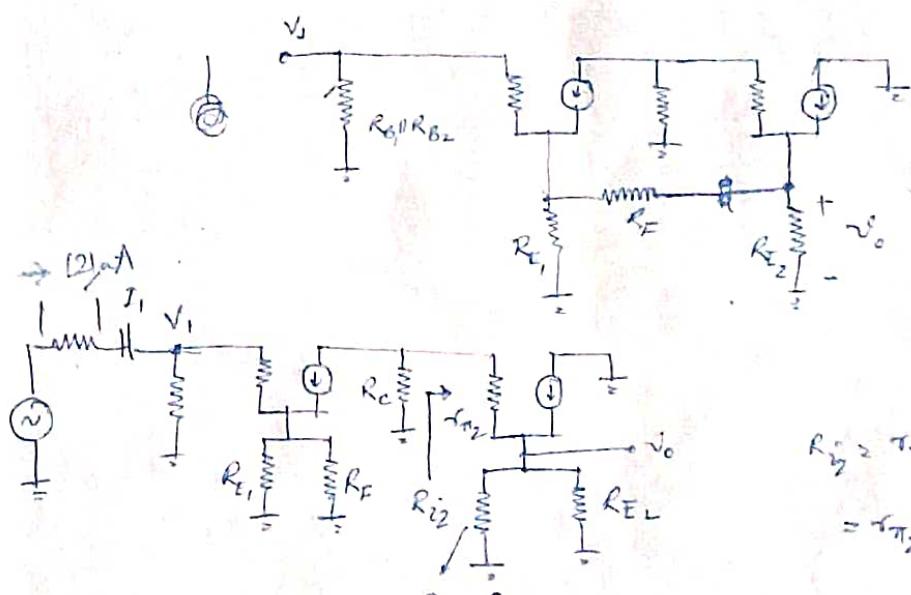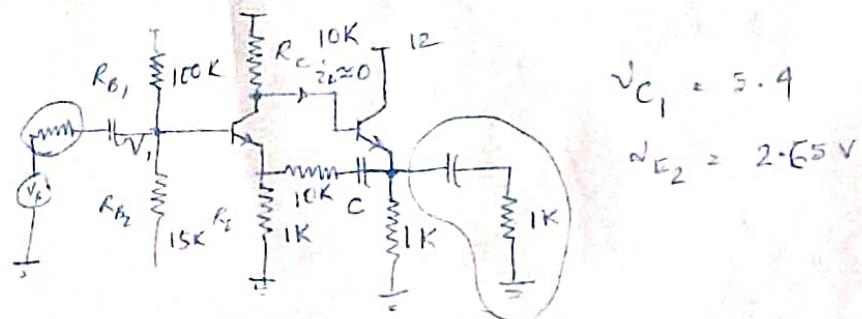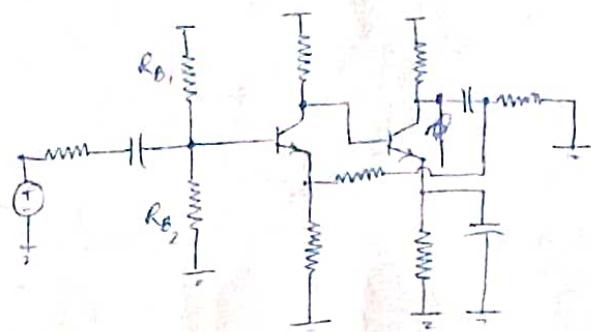

$$R_{\text{sh}} = r_{\pi_2} + (\beta + 1) \left[ (R_E + R_F) \parallel R_E \right]$$


$$\approx r_{\pi_2} +$$

$$\frac{V_0}{V_1} = \frac{2.68}{20.5m}$$

$$= 130$$

$$\therefore V_1 = 658 \text{ mV}$$
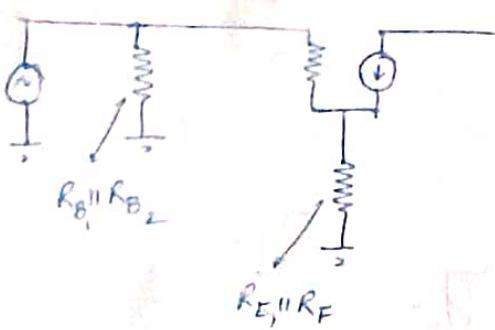
$$\frac{V_1}{I_1} = \frac{658 \text{ m}}{12 \mu} = 5.43 \text{ k}\Omega$$






class note

-ve

a typical feedback ckt

car speed example

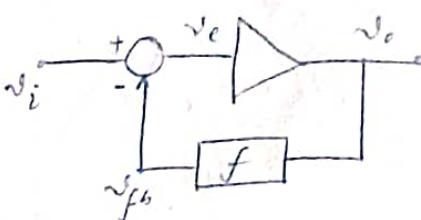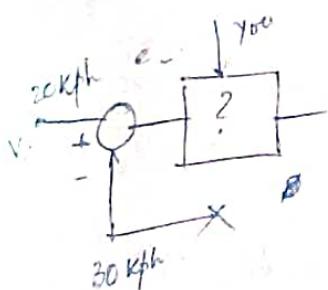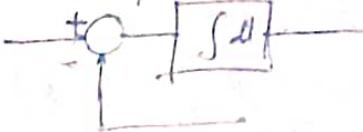

$$V_e = V_i - V_{fb}$$

$$= V_i - f V_o$$

$$\left\{ \begin{array}{l} V_o = a V_e \\ = V_i - f.a V_o \\ \Rightarrow V_o(1+af) = V_i \end{array} \right.$$


$$\left\{ \begin{array}{l} T = af = \text{loop gain} \\ V_e = \frac{V_i}{1+af} \\ \Rightarrow V_e = \frac{V_i}{af} \end{array} \right.$$

most often, it is found that  $af \gg 1$ ,

in such cases, closed loop gain:  $\frac{V_o}{V_i} \approx \frac{1}{af} = \frac{1}{f}$


as objective is  $V_{fb} \approx V_i$

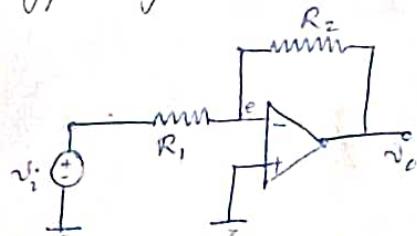a typical feedback ckt: inverting amplifier



$$\frac{V_i - e}{R_1} = \frac{e - V_o}{R_2}$$
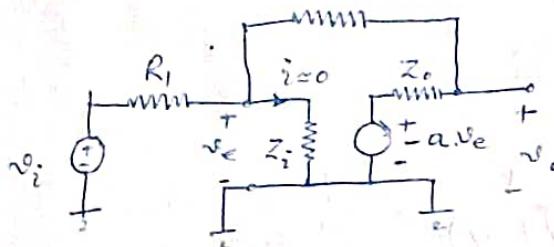
$$\Rightarrow V_i \text{ as } e \approx 0 \quad \frac{V_o}{R_2} = - \frac{V_o}{R_1} \Rightarrow \frac{V_o}{V_i} = - \frac{R_1}{R_2}$$



$$Z_i \rightarrow \infty$$

$$\frac{dV_o}{dt} = V_o \frac{dV_i}{dt} - V_o \frac{dV_o}{dt}$$


$$V_o(t) = K V_i \left( 1 - e^{-\frac{t}{R_1 C}} \right) + V_o(0) e^{-\frac{t}{R_1 C}}$$

$$\Rightarrow \frac{V_i - V_o}{R_1} = \frac{V_o - V_o}{R_2} \quad \text{if } V_o = -a \cdot e \Rightarrow V_o = -\frac{V_o}{a}$$

$$\Rightarrow \frac{V_i + e}{R_1} = - \frac{V_o}{a} - \frac{V_o}{R_2} \Rightarrow \frac{V_i}{R_1} + \frac{e}{R_1} = - \frac{V_o}{a} - \frac{V_o}{R_2}$$

$$\Rightarrow \frac{V_i}{R_1} = - \frac{V_o}{a R_1} - \frac{V_o}{a R_2} - \frac{V_o}{R_2}$$
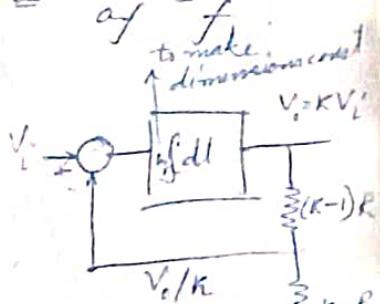
$$\Rightarrow \frac{V_i}{R_1} = - V_o \left[ \frac{1}{R_2} + \frac{1}{a} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \right]$$



$$\frac{V_o}{R_1} = -V_o \left\{ \frac{1}{R_2} + \frac{1}{a} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \right\}$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{V_o}{R_2} \left\{ 1 + \frac{1}{a} \left( 1 + \frac{R_2}{R_1} \right) \right\}$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{R_2}{R_1} \times \frac{1}{\left\{ 1 + \frac{1}{a} \left( 1 + \frac{R_2}{R_1} \right) \right\}} = A$$

now, closed loop gain of an amplif a feedback dkt:

$$A = \frac{a}{1+af}$$

determination of gain sensitivity

$$\begin{aligned} \frac{dA}{da} &= \frac{1}{1+af} - \frac{af}{(1+af)^2} \\ &= \frac{1+af - af}{(1+af)^2} = \frac{1}{(1+af)^2} \end{aligned}$$

$$\Delta A = \frac{\Delta a}{(1+af)^2}$$

in terms of % change,

$$\frac{\Delta A}{A} = \frac{\Delta a}{(1+af)^2} \times \frac{1}{\frac{a}{(1+af)}}$$

$$= \frac{\Delta a}{a} \times \frac{1}{(1+af)}.$$



now,  $\frac{v_o}{v_i}$  of the inverting ckt:

$$\frac{v_o}{v_i} = - \frac{R_2}{R_1} \times \frac{a}{\left\{ a + \left(1 + \frac{R_2}{R_1}\right)^2 \right\}}$$

$$= - \frac{a}{\left\{ \frac{a}{\left(1 + \frac{R_2}{R_1}\right)} + 1 \right\}} \times \frac{R_2}{R_1}$$

$$= \underline{\underline{A_{in}}}$$

consider,

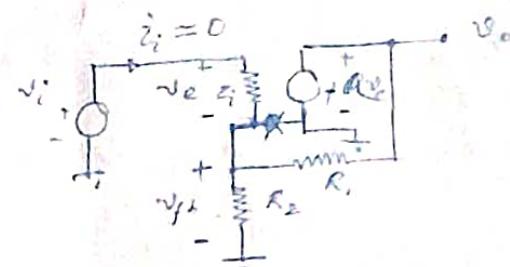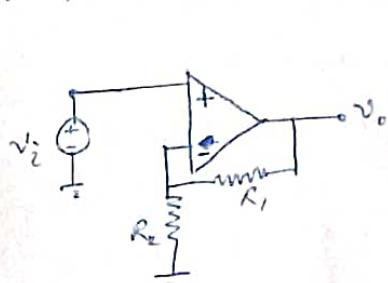

$442.57 \mu$

$$\therefore v_i - v_e - v_{fb} = 0 \quad v_{fb} = \frac{R_2}{R_1 + R_2} \times v_o \quad v_o = A_{in} v_e \\ \Rightarrow v_i = v_e + v_o \cdot \frac{R_2}{R_1 + R_2} = v_o \left\{ \frac{1}{a} + \frac{R_2}{R_1 + R_2} \right\}$$

$$\therefore v_i = \frac{v_o}{A_{in}} + v_o \cdot \frac{R_2}{R_1 + R_2}$$

$$\therefore v_i = \frac{v_o}{A_{in}} + v_o \cdot \frac{R_2}{R_1 + R_2} = v_o \left\{ \frac{1}{a} + \frac{R_2}{R_1 + R_2} \right\} = \frac{900}{450 + 1} v_o = \frac{900}{451} v_o$$

$$\therefore \frac{v_o}{v_i} = \frac{1}{\left\{ \frac{1}{a} + \frac{R_2}{R_1 + R_2} \right\}} = \frac{a}{\left\{ a \times \frac{R_2}{R_1 + R_2} + 1 \right\}} = A_{in} \frac{1000}{1000 + 1} = \frac{1000}{1001}$$

$$\text{as } a \rightarrow \infty, \quad \frac{v_o}{v_i} = A_{in} = \frac{R_1 + R_2}{R_2} = \left(1 + \frac{R_1}{R_2}\right)$$

$$\text{Let, } a \times \frac{R_2}{R_1 + R_2} = 100, \quad \text{find } \frac{\Delta A}{A} \text{ if } \frac{\Delta a}{a} \text{ is}$$

$$\text{det}, \alpha = 200 \Rightarrow \frac{R_2}{R_1+R_2} = 0.5$$

change of 10%  $\Rightarrow \alpha_1 = 200 + 20 = 220$ .

$$A_{CL1} = \frac{200}{200 \times 0.5 + 1} = \frac{200}{101} = 1.98$$


$$A_{CL2} = \frac{220}{220 \times 0.5 + 1} = \frac{220}{111} = 1.982$$

$$\left| \frac{A_{CL1} - A_{CL2}}{A_{CL1}} \right| \times 100 = \frac{1.982 - 1.98}{1.98} \times 100 = 0.1\%$$

$\rightarrow$  advantage of having feedback.

Leads to another advantage: less distortion.

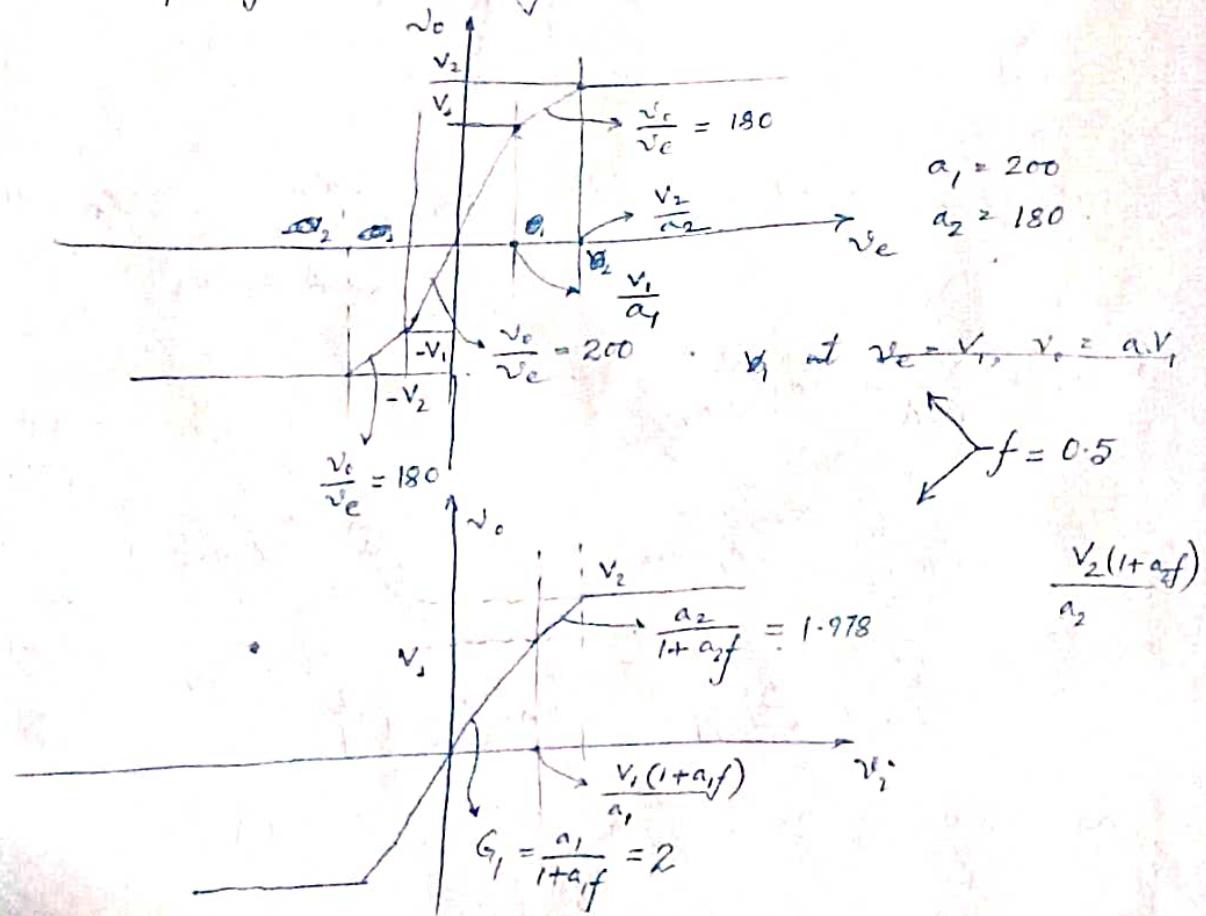Let, the op-amp has following I/P - O/P char:




distortion can not be removed beyond  $V_2$

~ gain open loop gain  $a=0 \Rightarrow A_{OL}=0$

Different feedback configurations:

Inverting amplifier:

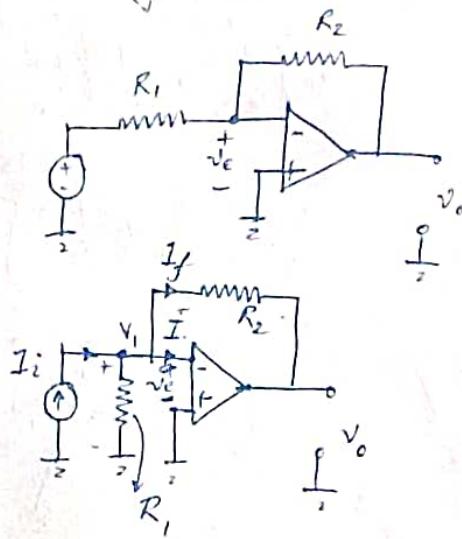

$$V_o = -\alpha V_i$$

$$\approx -\alpha (I_i - I_f) R_1$$

$$\rightarrow -\frac{V_o}{R_f}$$

$$V_i = -\frac{V_o}{\alpha} = (I_i - I_f) R_1$$

$$\rightarrow I_i R_1 - I_f R_1 = -\frac{V_o}{\alpha}$$

$$\rightarrow I_f R_1 = I_i R_1 + \frac{V_o}{\alpha}$$

$$\rightarrow I_f = \frac{1}{R_1} \left( I_i R_1 + \frac{V_o}{\alpha} \right)$$

$$\Rightarrow V_o \left\{ \frac{R_1 + R_2}{R_1} \times \frac{1}{\alpha} + 1 \right\} = -I_i R_2$$

$$\Rightarrow \frac{V_o}{I_i} = - \frac{R_2}{\left\{ 1 + \frac{1}{\alpha} \times \frac{R_1 + R_2}{R_1} \right\}} = - \frac{\alpha}{\left\{ \alpha + \frac{R_1 + R_2}{R_1} \right\} R_2}$$

$$V_i = -\frac{V_o}{\alpha}$$

$$\rightarrow I_i = \frac{V_i}{R_1} + \frac{V_i - V_o}{R_2}$$

$$(I_i - I_f) R_1 =$$

$$= I_f R_2 + V_o$$

$$\rightarrow I_i R_1 = I_f (R_1 + R_2) + V_o$$

$$\rightarrow I_i R_1 = \cancel{I_f}$$

$$= \frac{1}{R_1} (I_i R_1 + \frac{V_o}{\alpha}) \times (R_1 + R_2)$$

$$+ V_o$$

$$\rightarrow I_i R_1 - \frac{1}{R_1} \cdot I_i R_1 (R_1 + R_2)$$

$$= \frac{1}{R_1} \cdot \frac{V_o}{\alpha} \cdot (R_1 + R_2) + V_o$$


$$\rightarrow I_f R_1 - I_i R_1 - I_i R_2$$

$$= \frac{1}{R_1} \cdot \frac{V_o}{\alpha} (R_1 + R_2) + V_o$$

$$I_i = \frac{V_i}{R_1} + \frac{V_i - V_o}{R_2}, \quad V_i = -\frac{V_o}{a}$$

$$\begin{aligned} \Rightarrow I_i &= -\frac{V_o}{R_1} + \frac{-\frac{V_o}{a} - V_o}{R_2} = -\frac{V_o}{aR_1} + \frac{-\frac{V_o}{a} - V_o}{R_2} \\ &= -V_o \left\{ \frac{1}{R_1} + \frac{1}{R_2} \left( \frac{1}{a} + 1 \right) \right\} \\ &= -V_o \left\{ \frac{1}{R_1} + \frac{1}{R_2} \left( \frac{1+a}{a} \right) \right\} \\ &= -V_o \left\{ \frac{1}{R_1} + \frac{1}{R_2} \right\} \\ &= -V_o \left\{ \frac{1}{R_1} + \frac{1}{R_2} \left( \frac{1+a}{a} \right) \right\} \\ &= -V_o \cdot \left\{ \frac{1}{R_1} + \frac{1+a}{R_2} \right\} \\ &= -V_o \left\{ \frac{aR_2 + R_1(1+a)}{R_1 R_2 a} \right\} \\ &= -V_o \end{aligned}$$
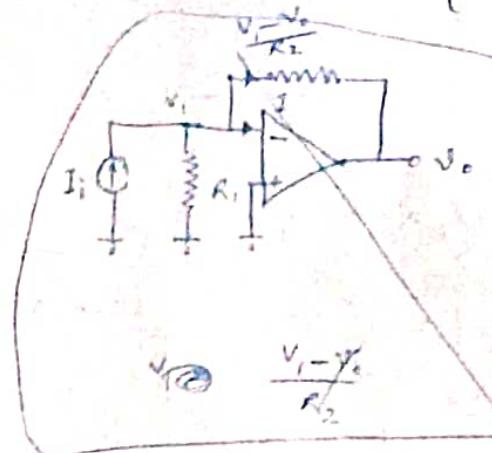
$$\frac{V_o}{I_i} = -\frac{a R_1 R_2}{R_1 + a(R_1 + R_2)}$$



$$I = -\frac{V_o}{a}$$

$$I_i = \frac{V_i}{R_1} + \frac{V_i - V_o}{R_2} + I$$

$$I = -\frac{V_o}{a}$$

$$\Rightarrow \frac{V_o}{I_i} = -\frac{a}{\left\{ \frac{1}{R_1} + \frac{1+a}{R_2} \right\}}$$

$$= -\frac{a}{\left\{ \frac{R_2 + R_1(1+a)}{R_1 R_2} \right\}} = -\frac{a}{\left\{ \frac{R_2 + R_1 + aR_1}{R_1 R_2} \right\}}$$

$$\Rightarrow \frac{V_o}{Z_i} = \frac{a}{\left( \frac{R_2 + R_1}{R_1 R_2} \right) (1 + a)}$$

$$\Rightarrow \frac{V_o}{I_i} = - \frac{a}{\left\{ \frac{R_2 + R_1}{R_1 R_2} + \frac{a}{R_2} \right\}}$$

$$= - \frac{a}{\left\{ \frac{1}{R_1 R_2} + \frac{a}{R_2} \right\}}$$

$$\frac{R_1 R_2}{R_2}$$


$$= - \frac{a \times (R_1 R_2)}{\left\{ 1 + \frac{a \times (R_1 R_2)}{R_2} \right\}}$$

$$\frac{A_f}{R_1 + R_2}$$

as  $\frac{V_o}{V_c} = -a$ , actual gain should come in terms of resistance ( $V/I$ ), not voltage ratio

Feedback det. practical considerations


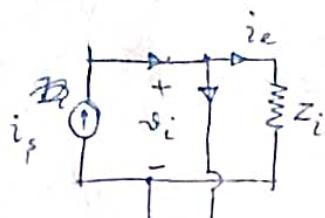
i.e., where feedback det load the amplifier ckt



$$z_f = \frac{v_i}{i_s}, \quad i_s = i_e + \gamma_{if} v_o$$


$$\frac{v_o}{i_s} = \frac{a}{1+a} \cdot \frac{a}{1+a}$$
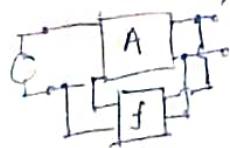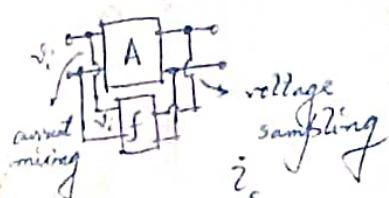
$$\therefore \frac{v_o}{i_e} = a \cdot a = -\frac{\gamma_{21o}}{\gamma_i \gamma_o}$$



$$\begin{aligned} \frac{v_o}{i_s} &= \frac{v_o}{(-\frac{\gamma_{21o}}{\gamma_i \gamma_o})} + \gamma_{if} v_o \\ &= v_o \left\{ \frac{1}{a} + \gamma_{if} \right\} \\ &= v_o \left\{ \frac{1}{a} + f \right\} \end{aligned}$$

shunt shunt

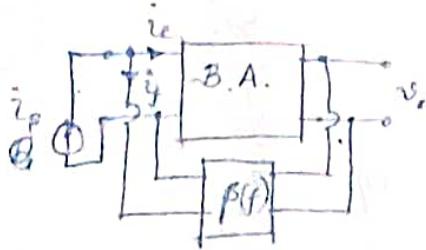

$$\gamma P \rightarrow I_1 = Z_1 V_1 + Z_{12} V_2$$

$$I_2 = Z_{21} V_1 + Z_{22} V_2$$

$$ZP \rightarrow V_1 = I_1 + I_2$$

$$V_2 = I_1 + I_2$$

$$hP \rightarrow V_1 = I_1 + V_2$$

$$I_2 = I_1 + V_2$$

$$gP \rightarrow \frac{I_1}{V_2} = V_1 + \frac{I_2}{V_2}$$



$$\frac{V_1}{I_2} = V_1 + \frac{I_2}{V_2}$$

mixing  $\rightarrow$  current mixing  
sampling  $\rightarrow$  voltage sampling

i/P  $\rightarrow$  current

v/P  $\rightarrow$  voltage

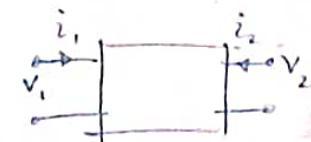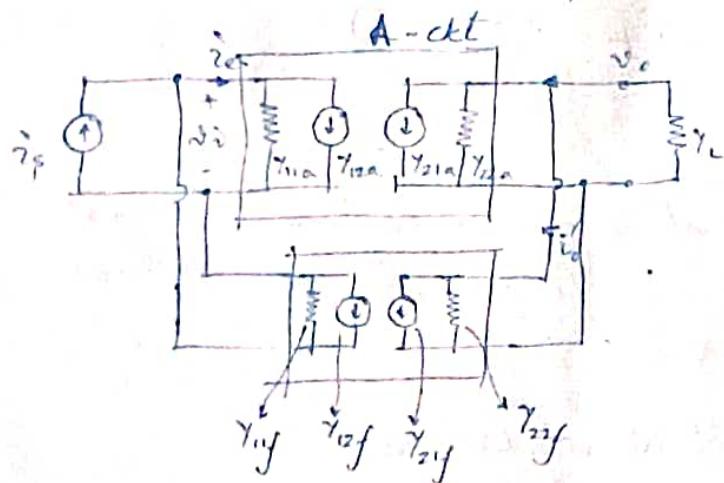Both B.A. & f.b. op-amps are replaced with  $\gamma$  parameters.



$$i_1 = \gamma_{11} V_1 + \gamma_{12} V_2$$

$$i_2 = \gamma_{21} V_1 + \gamma_{22} V_2$$

$$\gamma_{11} = \left. \frac{i_1}{V_1} \right|_{V_2=0}$$

$$\gamma_{12} = \left. \frac{i_1}{V_2} \right|_{V_1=0}$$

= return signal

$$\gamma_{21} = \left. \frac{i_2}{V_1} \right|_{V_2=0}$$


forward signal

clearly, for A-ckt,

$$\gamma_{21a} \gg \gamma_{12a}$$

so,  $\gamma_{12a}$  neglected,

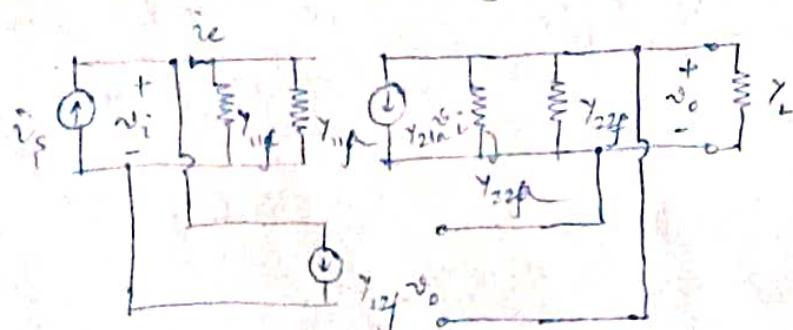thus, for f. ckt.,  $\gamma_{21f} \ll \gamma_{12f}$ .



$$\gamma_{1f} = \left. \frac{i_f}{V_1} \right|_{V_2=0}$$

$$\gamma_{2f} =$$

$$\hat{i}_f = v_i(\gamma_{1a} + \gamma_{1f}) + \gamma_{12f} v_o$$

$$\& \gamma_{21a} \hat{v}_i + v_o (\gamma_{22a} + \gamma_{22f}) + v_o = 0$$

Let,  $\gamma_{1a} + \gamma_{1f} = \gamma_i$

$$\gamma_{22a} + \gamma_{22f} + v_o = \gamma_o$$

$$\Rightarrow \hat{i}_f = v_i \cdot \gamma_i + \gamma_{12f} v_o$$

$$0 = \gamma_{21a} \hat{v}_i + \gamma_o v_o$$

$$v_i = -\frac{\gamma_o v_o}{\gamma_{21a}}$$

$$\Rightarrow \hat{i}_f = -\frac{\gamma_o \gamma_i v_o}{\gamma_{21a}} + \gamma_{12f} v_o$$

$$= v_o \left( \gamma_{12f} - \frac{\gamma_o \gamma_i}{\gamma_{21a}} \right)$$

$$= v_o \left( \frac{\gamma_{12f} \gamma_{21a} - \gamma_o \gamma_i}{\gamma_{21a}} \right)$$

$$\frac{v_o}{i_f} = \frac{\gamma_{21a}}{\gamma_{12f} \gamma_{21a} - \gamma_o \gamma_i} =$$

$$= \frac{\left( -\frac{\gamma_{21a}}{\gamma_o \gamma_i} \right)}{1 + \left( -\frac{\gamma_{21a}}{\gamma_o \gamma_i} \right) \cdot \gamma_{12f}}$$

$$= \frac{A}{1 + Af}$$

$$\hat{i}_f = \gamma_i \hat{v}_i + \gamma_{12f} v_o$$

$$\gamma_{21a} \hat{v}_i + v_o \gamma_o = 0$$

$$\Rightarrow v_i = -v_o \frac{\gamma_o}{\gamma_{21a}}$$


$$\Rightarrow \hat{i}_f = \frac{v_i \gamma_i + \gamma_{12f} v_o}{\gamma_{21a}}$$

$$i_f = -\frac{v_o \gamma_o \gamma_i}{\gamma_{21a}} + \gamma_{12f} v_o$$

for the amplifier circuit,

without feedback,

$$\text{gain: } \frac{v_o}{i_f}$$

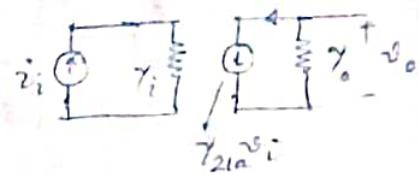


$$v_o = -\frac{\gamma_{21a} v_i}{\gamma_o} = -\frac{\gamma_{21a} \hat{v}_i}{\gamma_o \gamma_i}$$

$$v_i = \frac{\hat{v}_i}{\gamma_i} \Rightarrow \frac{v_o}{\hat{v}_i} = -\frac{\gamma_{21a}}{\gamma_o \gamma_i}$$

$$\frac{\gamma_{21a}}{\gamma_o \gamma_i} = \frac{\gamma_{12f} \gamma_{21a}}{\gamma_o \gamma_i} - 1$$

$$= -\frac{A}{1 + Af}$$

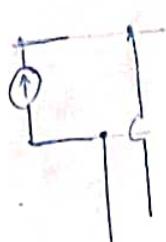


i/P impedance with feedback:

$$\hat{i}_s = \hat{i}_q + \gamma_{12f} v_o$$

$$\hat{i}_q = v_i \gamma_i$$
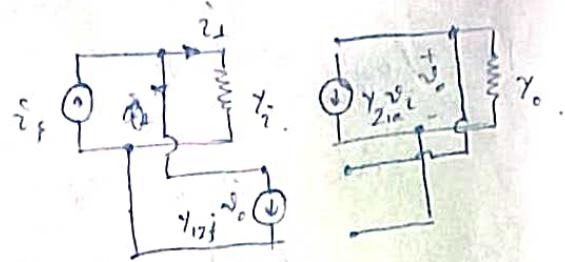
$$\Rightarrow \hat{i}_s = v_i \gamma_i + \gamma_{12f} v_o$$



$$v_o = A \frac{1}{1+Af} \times \hat{i}_s$$

$$\Rightarrow \hat{i}_s = v_i \gamma_i + \frac{\gamma_{12f} \times \gamma_{21a}}{\gamma_{12f} \times \gamma_{21a} - \gamma_i \gamma_o} \hat{i}_s$$

$$\Rightarrow \hat{i}_s \left\{ 1 - \frac{\gamma_{12f} \times \gamma_{21a}}{\gamma_{12f} \times \gamma_{21a} - \gamma_i \gamma_o} \right\} = v_i \gamma_i$$

$$\Rightarrow \frac{\hat{i}_s}{\hat{i}_s} \left\{ 1 - \frac{\gamma_{12f}}{\gamma_{12f} \times \gamma_{21a} - \gamma_i \gamma_o} \right\} \rightarrow \hat{i}_s \left\{ \frac{\gamma_{12f} \gamma_{21a} - \gamma_i \gamma_o - \gamma_{12f} \gamma_{21a}}{\gamma_{12f} \gamma_{21a} - \gamma_i \gamma_o} \right\} = v_i \gamma_i$$


$$\Rightarrow \hat{i}_s \left\{ \frac{\frac{\gamma_i \gamma_o}{\gamma_{12f} \gamma_{21a}} - 1}{\frac{\gamma_{12f} \gamma_{21a}}{\gamma_i \gamma_o} + 1} \right\} = v_i \gamma_i$$

$$\Rightarrow \frac{v_i}{\hat{i}_s} \cdot z_{if} = \frac{1}{\gamma_i} \times \frac{1}{1 + \left( -\frac{\gamma_{21a}}{\gamma_i \gamma_o} \right) \times \gamma_{12f}}$$

$$= \frac{1}{\gamma_i} \times \frac{1}{1 + Af}$$

O/P impedance with feedback:

$$z_{of} = ? \quad z_f = ?$$

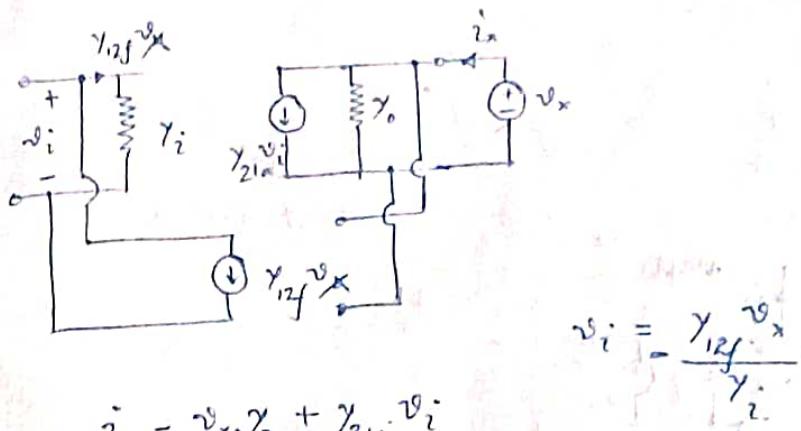

$$v_i = -\frac{\gamma_{12f} v_x}{\gamma_i}$$

$$i_x = v_x \cdot \gamma_o + \gamma_{21a} v_i$$


$$= v_x \gamma_o + \gamma_{21a} \times \frac{\gamma_{12f}}{\gamma_i} \cdot v_x$$

$$= v_x \gamma_o \left\{ 1 + \left( \frac{-\gamma_{21a} \gamma_{12f}}{\gamma_o \gamma_i} \right) \right\}$$


$$\frac{v_x}{i_x} = \frac{1}{Z_o} \times \frac{1}{1 + \left( \frac{-\gamma_{21a}}{\gamma_o \gamma_i} \right) \times \gamma_{12f}}$$

p-

consider the ckt

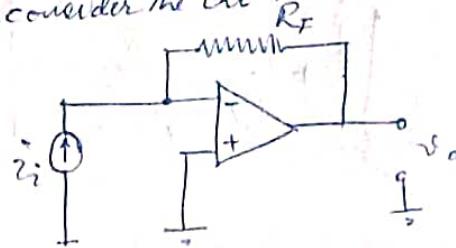

model the op-amp as

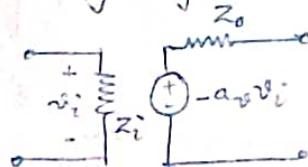

$$Z_i = 2 M\Omega$$


$$Z_o = 75 \Omega$$

$$a_v = 200,000$$

$$R_L = 10 k\Omega$$

$$R_F = 1 M\Omega$$

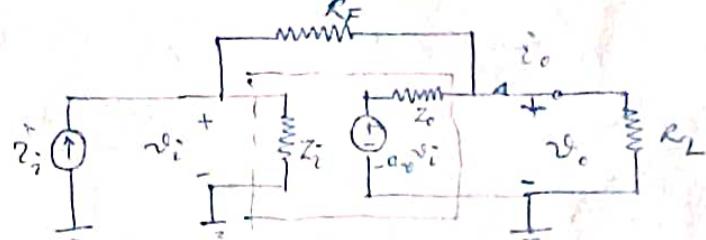find the closed loop gain  $\frac{v_o}{v_i}$



$$i_o = -\frac{v_o}{R_L}$$

$$i_i = \frac{v_i}{Z_i} + \frac{v_i - v_o}{R_F}$$



$$-a_v v_i + \left\{ i_o - \left( \frac{v_o - v_i}{R_F} \right) \right\}$$

$$\gamma_{1f} = \frac{i_f}{v_i} \Big|_{v_o=0}$$

$\Rightarrow$  O/P shorted


$$\gamma_{R2f} = \frac{v'_o}{v_i} \Big|_{v_i=0}$$

$\Rightarrow$  I/P shorted

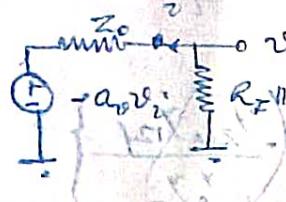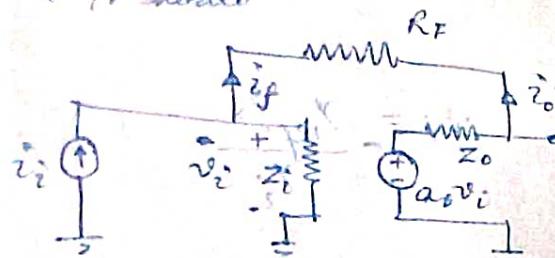


formation of  
amplifier with  
feedback loading.

& feedback ckt.

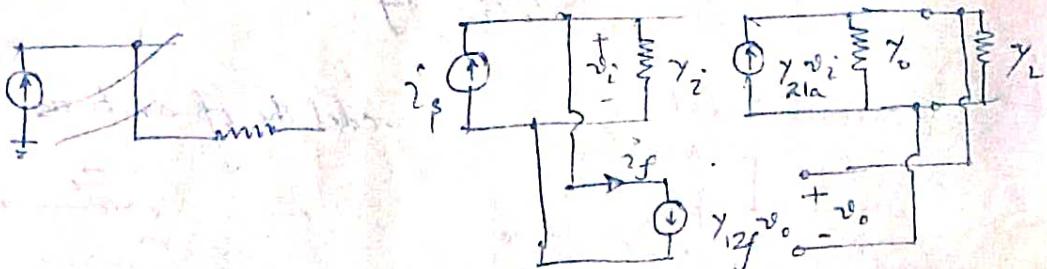



$$\gamma_{1f} = \frac{i_f}{v_o} \Big|_{v_i=0} \Rightarrow \text{I/P shorted}$$

i.e.,

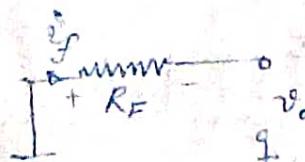

$$i_f R_F + v_o = 0$$

$$\Rightarrow \frac{i_f}{v_o} \Big|_{v_i=0} = \gamma_{1f} = -\frac{1}{R_F}$$

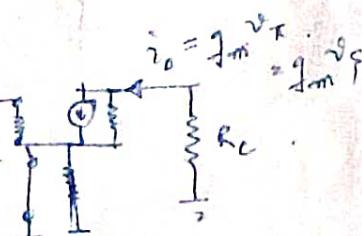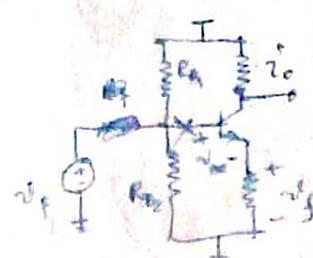

$$\frac{v_o}{v_i} = g_m$$

$$\frac{g_m R_C}{1 + g_m}$$

$$i = \frac{v_o + a_v v_i}{Z_0}$$

$$\Rightarrow v_o = -i R_F' = -\frac{v_o + a_v v_i}{Z_0} \times R_F'$$

$$v_i = i_i \times (R_F \parallel Z_i) \quad R_F' = R_F \parallel R_L$$

$$\Rightarrow v_o = -v_o \times \frac{R_F}{Z_0} - a_v v_i \times \frac{R_F}{Z_0}$$

$$\Rightarrow v_o \left(1 + \frac{R_F}{Z_0}\right) = -a_v \times i_i (R_F \parallel Z_i) \times \frac{R_F'}{Z_0}$$

$$\Rightarrow \frac{v_o}{i_i} = -\frac{a_v \times (R_F \parallel Z_i) \times \frac{R_F}{Z_0}}{\left(1 + \frac{R_F'}{Z_0}\right)}$$

$$\Rightarrow \frac{v_o}{i_i} = -\frac{a_v \times (R_F \parallel Z_i) \times \frac{R_L \parallel R_F}{Z_0}}{\left(1 + \frac{R_L \parallel R_F}{Z_0}\right)}$$

$$= -\frac{200,000 \times (2M \parallel 1M) \times \frac{(10K \parallel 1M)}{75}}{\left(1 + \frac{10K \parallel 1M}{75}\right)}$$

$$= -\frac{200,000 \times 667K \times 8.132}{133}$$

$$= -1.324 \times 10^{-11} \Omega$$


$$f = -\frac{1}{R_F}$$

$$\Rightarrow A_{CL} = \frac{A}{1 + A.f} = \frac{-1.324 \times 10^{-11}}{1 + \frac{1.324 \times 10^{-11}}{1M}}$$

$$= 999.97 K \Omega$$


series-series feedback

representation with  $Z$  parameters

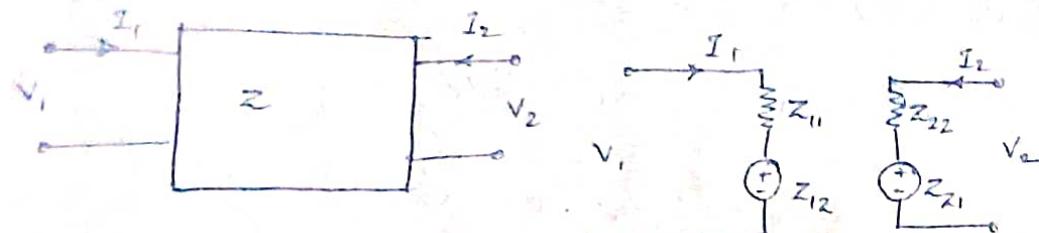

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

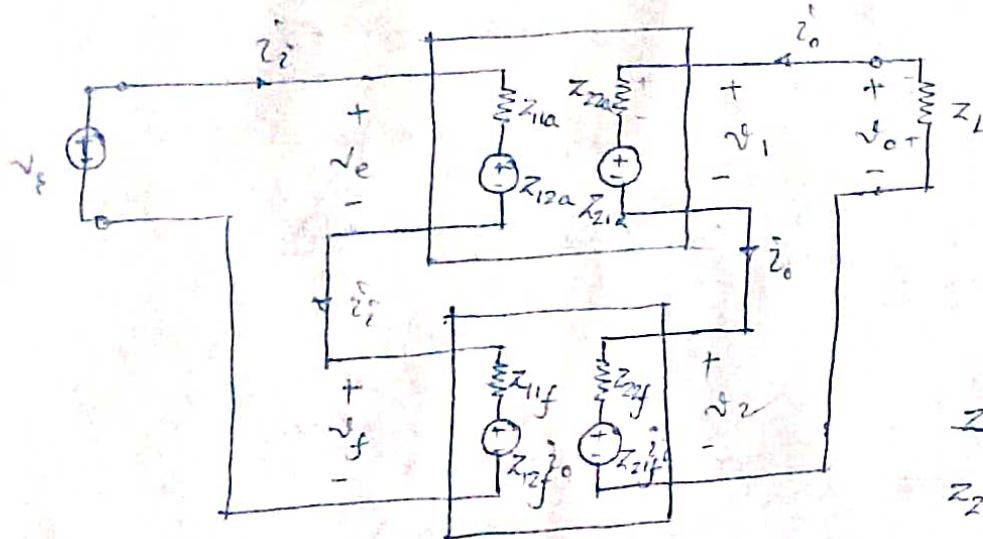

$$\bar{Z}_{12f} = Z$$

$$\bar{Z}_{21f} = Z_{12a} \approx 0$$
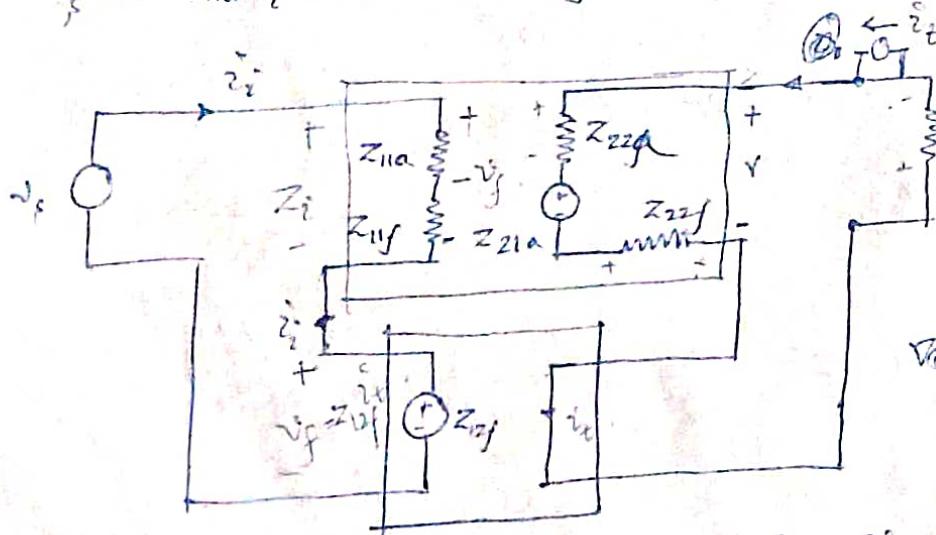
$$v_f = Z_{11a}i_1 + Z_{12a}v_0 + Z_{12f}i_2 + Z$$



$$v = Z_0 i_2 + Z_{21a} i_1$$

$$= Z_0 i_2 + Z_{21a} \frac{v_0}{Z_0}$$

$$\bar{Z}_0 i_2 = Z_0 i_2 (1 + A_f)$$

$$v = Z_{21a} i_2 + Z_{22f} i_0 + Z_{21a} i_1$$

$$i_2 = \frac{v_f - Z_{12f} i_2}{Z_0} = \frac{Z_{12f} i_2}{Z_0}$$

$$v_f = i_i (z_{11a} + z_{11f}) + z_{12f} \cdot i_o$$

$$i_o (z_L + z_{22a} + z_{22f}) + z_{21a} \cdot i_i = 0$$

$$\Rightarrow i_o (z_L + z_{22a} + z_{22f}) + z_{21a} \cdot i_i (\cancel{z_{11a} + z_{11f}}) = 0$$

Let,  $z_{11a} + z_{11f} = z_i$ ,  $z_L + z_{22a} + z_{22f} = z_o$

$$\Rightarrow v_f = i_i z_i + z_{12f} i_o$$

$$0 = i_o z_o + z_{21a} \cdot \cancel{i_i} \Rightarrow$$

$$\Rightarrow \cancel{i_i} = -\frac{\cancel{i_o} z_o}{z_{21a} \cdot z_i} \Rightarrow i_i = -\frac{i_o z_o}{z_{21a}}$$

$$\Rightarrow v_f = -\frac{i_o z_o}{z_{21a}} \cdot z_i + z_{12f} \cdot i_o$$


$$= -\frac{i_o z_o z_i}{z_{21a}} + z_{12f} \cdot i_o$$

$$\Rightarrow i_o \left( -\frac{z_o z_i}{z_{21a}} + z_{12f} \right)$$

$$\Rightarrow \frac{i_o}{v_f} = A_{CL} = \frac{z_{21a}}{z_{21a} z_{12f} - z_o z_i} = \frac{\left( -\frac{z_{21a}}{z_o z_i} \right)}{1 + \left( -\frac{z_{21a}}{z_o z_i} \right) z_{12f}}$$

$$z_o = z_{22a} + z_{22f}$$


How to form a ckt:

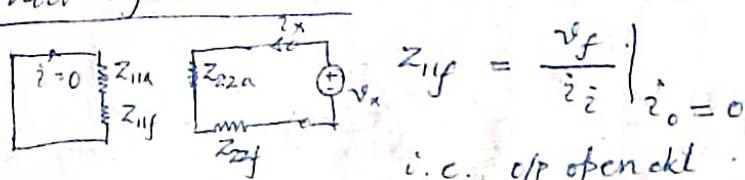

i.e., o/p open ckt.

$$z_{22f} = \frac{v_o}{i_o} \Big|_{i_i=0}$$

i.e. i/p open ckt.

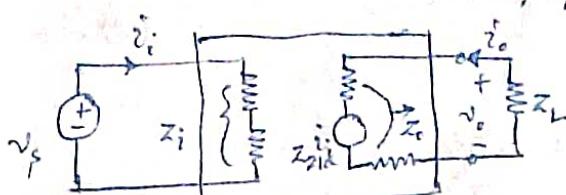

$$i_o = i_o \cdot z_o + z_{21a} i_i = 0$$

$$\Rightarrow i_o = -\frac{z_{21a} i_i}{z_o} = -\frac{z_{21a} i_i}{z_o z_L}$$

$$\therefore i_i = \frac{v_f}{z_i}$$

$$\therefore \frac{i_o}{v_f} = -\frac{z_{21a}}{z_i z_L}$$

TF S O/P impedance


$$\frac{v_f}{i_i} = ?$$

$$v_f = i_i z_i + z_{12f} i_o \Rightarrow \frac{v_f}{i_i} = \left( \frac{z_o}{z_i z_o - z_{12f} z_{21o}} \right)^{-1} = z_i z_o \left( 1 - \frac{z_{12f} z_{21o}}{z_i z_o} \right)$$

how to form fb ckt:

$$i_o = -\frac{z_{21o} i_i}{z_o}$$

$$Z_{12f} = \frac{v_f}{i_i} \Big|_{i_i=0} \Rightarrow v_f = i_i z_i + z_{12f} \frac{z_{21o}}{z_o} i_i = z_i (1 + (-\frac{z_{21o}}{z_i z_o}) z_{12f}) i_i = z_i (1 + A\beta) i_i$$

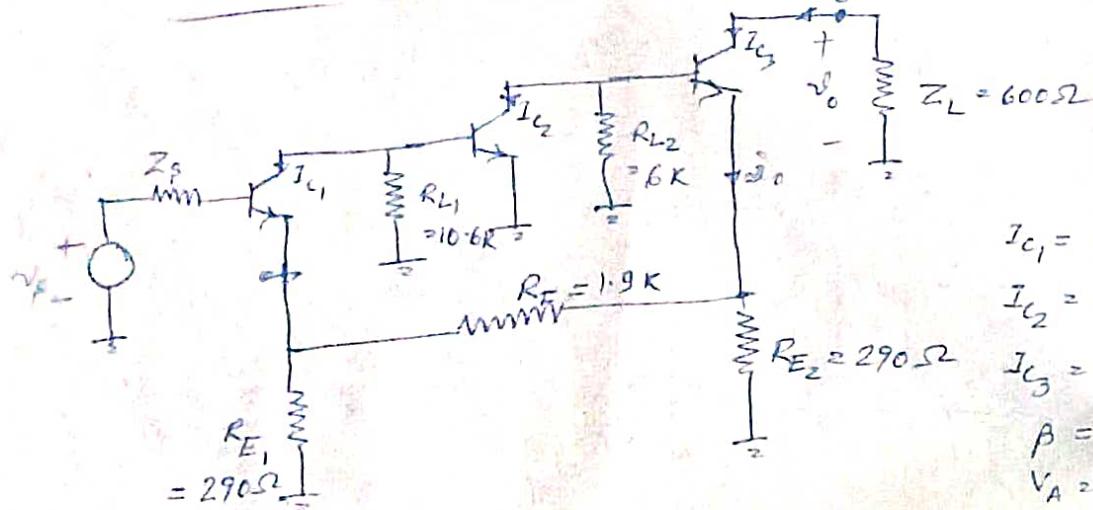


$$I_{c_1} = 0.5 \text{ mA}$$

$$I_{c_2} = 0.77 \text{ mA}$$

$$I_{c_3} = 0.73 \text{ mA}$$

$$\beta = 120, V_A = 40$$

A ckt

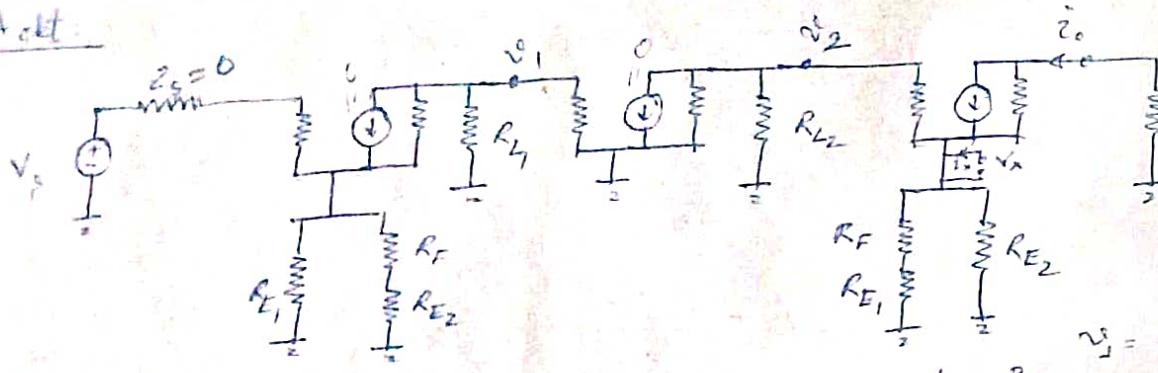


$$v_o = R_E2 \parallel (R_F + r_b) \times i_o$$

$$\frac{v_f}{i_o} = R_E \times i_o$$

$$v_f = \frac{R_E1 \times R_E2 \parallel (R_F + r_b) \times i_o}{R_E1 + R_E2 \times i_o}$$

$$= \frac{R_E1 \times R_E2 \parallel (R_F + r_b)}{(R_E1 + R_E2) \times (R_F + r_b)}$$

$$\text{gain} = \frac{i_o}{v_p}$$

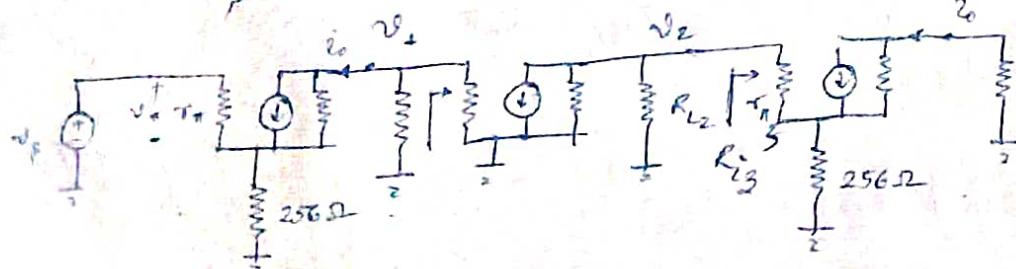


$$\tau_{\pi_1} = \frac{R}{2m_1} = \frac{120}{(0.5m)} = 6.24K$$

$$\tau_{\pi_2} = \frac{R}{2m_2} = \frac{120}{(0.77m)} = 4.05K$$

$$\tau_{\pi_3} = \frac{120}{2.6m} = 4.27K\Omega$$
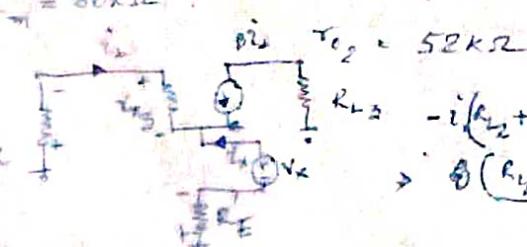
$$\tau_{\pi_1} = \frac{40}{0.5m} = 80K\Omega$$



$$\tau_{\pi_3} = 54K\Omega$$

$$-i(r_{\pi_2} + \tau_{\pi_3}) \cdot v_x + i_x R_E' = 0 \Rightarrow \frac{\partial (r_{\pi_2} + \tau_{\pi_3}) i_x}{\beta + 1} + i_x R_E' = v_x$$

open loop

$$i_o + i_{\pi_1} + i_{\pi_2} = 0$$

$$i_o = (r_{\pi_1} + r_{\pi_2}) i_x$$

out factors:

$$\frac{v_o}{v_s} = \frac{i_o}{v_{\pi}}$$

$$R_E'$$

$$v_1 = -i_o \times (R_L \parallel r_{\pi_2})$$

$$v_p = v_{\pi} + \left( i_o + \frac{v_{\pi}}{r_{\pi}} \right) \times R_E'$$

$$i_o = g_m v_{\pi} + \frac{v_1 - \left( i_o + \frac{v_{\pi}}{r_{\pi}} \right) \times R_E'}{r_{\pi}}$$

$$v_{\pi} = v_{\pi} + \frac{v_{\pi} R_E'}{r_{\pi}}$$

$$= g_m v_{\pi} +$$

$$+ i_o R_E'$$

$$= v_{\pi} \left( 1 + \frac{R_E'}{r_{\pi}} \right) + i_o R_E'$$

$$\frac{v_1}{v_p} \approx \frac{(R_L \parallel r_{\pi_2})}{R_E'} = \frac{10.6K \parallel 4.05K}{256}$$

$$= \frac{2.93K}{256} \approx -11.44 \text{ V/V}$$

$$\alpha = 4.5 \text{ A/V}$$

$$\frac{i_o}{v_p} / C_2 = 29 \text{ mA/V}$$

$$R_{i_3} = r_{\pi_3} + (\beta + 1) R_E''$$

$$= 4.27K + 121 \times 256$$

$$= 35.25K$$

$$R_i = 5.73 \text{ M}\Omega$$

$$R_o = 355.5 \text{ M}\Omega$$

$$\frac{2o}{v_s} = 6.03$$

$$\Rightarrow \frac{v_2}{v_1} = -g_{m_2} \times (r_{\pi_2} \parallel R_{i_3} \parallel R_L)$$

$$f =$$

$$= -g_{m_2} \times (52K \parallel 30K \parallel 6K)$$

$$r_{\pi_1} = 6.24K \quad g_{m_1} =$$

$$= -g_{m_2} \times (19K \parallel 6K)$$

$$r_{\pi_2} = 4.05K \quad g_{m_2} =$$

$$= -g_{m_2} \times 4.56K$$

$$r_{\pi_3} = 4.27K \quad g_{m_3} =$$


$$= -135 \text{ V/V}$$

$$\Phi \quad \frac{v_o}{v_s} = -i_o R_L \quad \frac{v_o}{v_2} \approx -\frac{R_L}{R_E''} = -\frac{600}{256} = -2.34 \text{ V/V}$$

$$\Phi \quad \frac{v_o}{v_2} = -2.34 = -\frac{i_o R_L}{v_2} \Rightarrow \frac{i_o}{v_2} = \frac{2.34}{R_L}$$

$$\Rightarrow \frac{i_o}{v_s} = \frac{2.34 \times 11.44 \times 135}{600} \approx 6.03$$
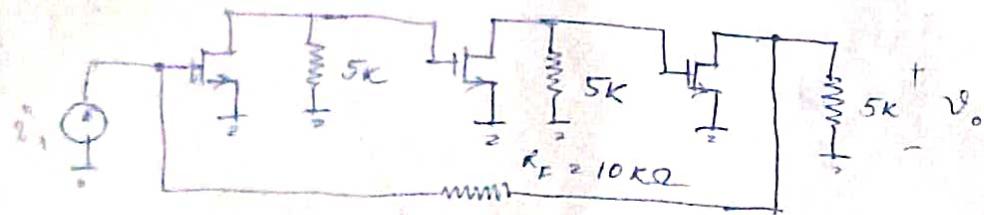
$$\frac{i_o}{v_s \times 11.44 \times 135} = \frac{2.34}{600}$$




$$I_D = 1\text{mA}, W/L = 100, K' = 60 \mu\text{A}/\text{V}^2, \lambda = \frac{1}{50} \text{V}^{-1}$$

$$\begin{aligned} R_{in} &\times 2 \\ R_{out} &\times 2 \\ \frac{V_2}{V_1} &\times 2 \\ \frac{V_o}{V_2} &\times 2 \end{aligned}$$



$$a_{cl} \approx -10k\Omega$$

$$Z_{if} = 16.4 \Omega$$

$$Z_{of} = 1.13 \Omega$$

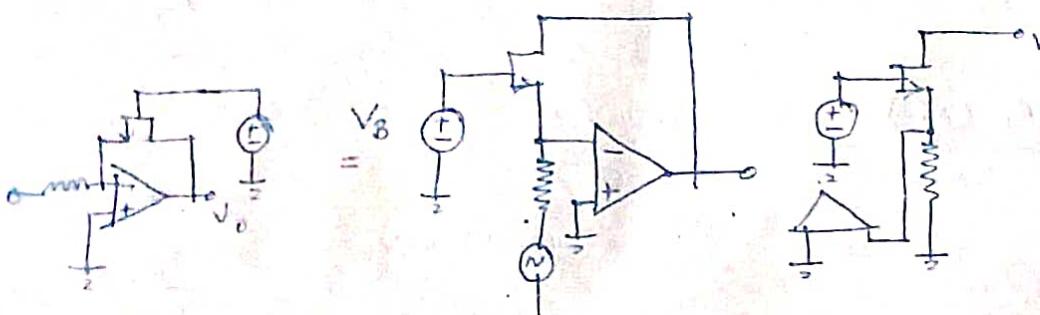

series-shunt feedback:

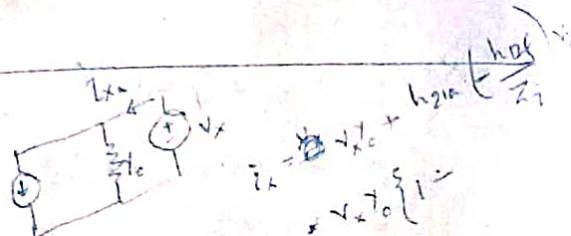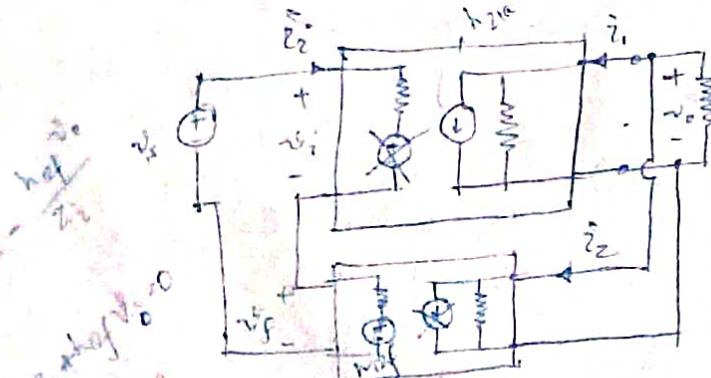

h parameters:

for BA clt:

$$v_{i1} = h_{11a}i_1 + h_{12a}v_o$$


$$i_1 = h_{21a}i_1 + h_{22a}v_o$$

for feedback clt

$$v_f = h_{11f}i_2 + h_{12f}v_o$$

$$i_2 = h_{21f}i_2 + h_{22f}v_o$$

modified clt.

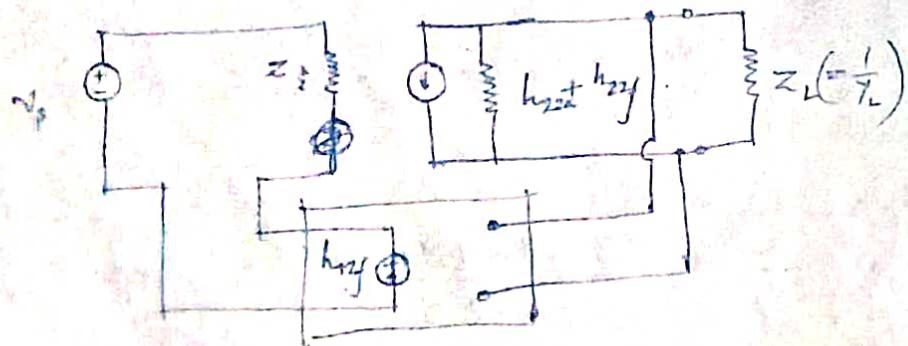

$$v_f = i_i z_i + h_{12f} v_o$$

$$\therefore v_o = -h_{21a} i_i \times \frac{1}{h_{22a} + h_{22f} \gamma_o} \Rightarrow i_i = -\frac{h_{21a} i_i}{\gamma_o}$$

But,  $h_{22a} + h_{22f} \gamma_o = \gamma_o$   $\Rightarrow i_i = -\frac{v_o \gamma_o}{h_{21a}}$

$$\Rightarrow v_f = i_i z_i + h_{12f} \times \cancel{v_o}$$

$$= -\frac{v_o \gamma_o}{h_{21a}} \times z_i + h_{12f} v_o$$

$$= v_o \left( -\frac{z_i + h_{12f} h_{21a}}{h_{21a}} \right)$$

$$\therefore \frac{v_o}{v_f} = \frac{h_{21a}}{-\gamma_o z_i + h_{12f} h_{21a}}$$


$$= \frac{\left( -\frac{h_{21a}}{\gamma_o z_i} \right)}{1 + \left( -\frac{h_{21a}}{\gamma_o z_i} \right) h_{12f}}$$

$$h_{12f} = \frac{v_f}{v_o} \Big|_{i_i=0}$$

$$h_{11f} = \frac{v_f}{i_i} \Big|_{v_o=0}$$

$$h_{22f} = \frac{i_i}{v_o} \Big|_{i_i=0}$$

BA circuit with feedback load:

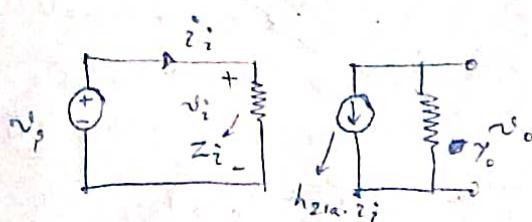


$$v_f = i_i z_i \quad \text{&} \quad v_o = -\frac{h_{21a} i_i}{\gamma_o}$$

$$\therefore v_f = -\frac{v_o \gamma_o z_i}{h_{21a}} \Rightarrow i_i = -\frac{v_o \gamma_o}{h_{21a}}$$

$$\therefore \frac{v_f}{v_o} = -\frac{h_{21a}}{\gamma_o z_i} = a \quad A_{CL} = \frac{v_o}{v_f} = \frac{a}{1+af}$$

$$f = h_{12f} = \frac{v_f}{v_o} \Big|_{i_i=0}$$

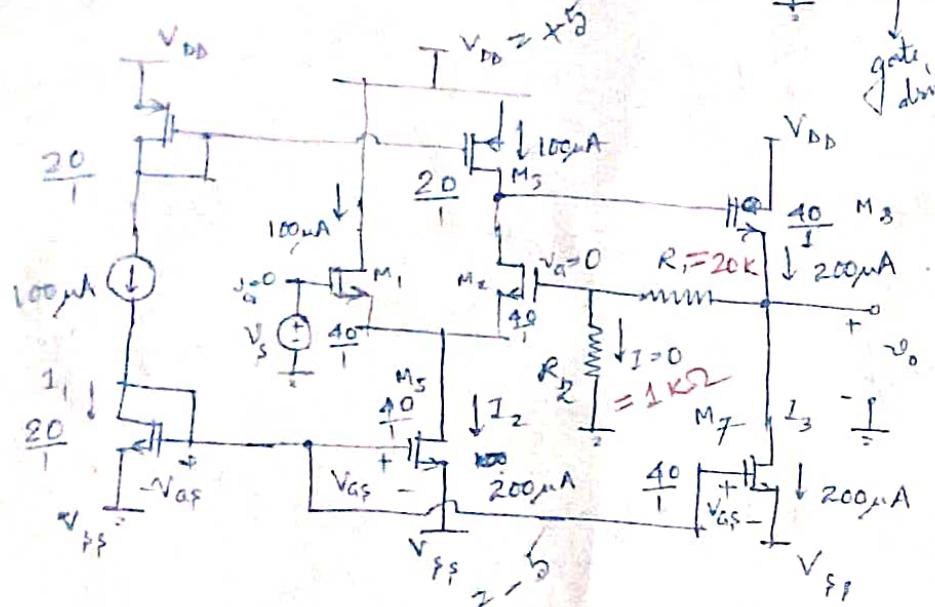

$$\mu_{nCox} = 60 \mu A/V^2$$

$$I_{pCox} = 30 \mu A/V^2$$

$$V_{ex} = |V_{tp}| = 0.8V$$

$$\lambda_n = |\lambda_p| = 0.03 \text{ v}^{-1}, \text{ i.e., assume } \tau_c \rightarrow \infty$$

assume all the transistors are in saturation region.

neglect  $\tau_{\alpha_1}, \tau_{\alpha_2}$  of  $M_1 \oplus M_2$ .

$$I_{D_1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_{tn})^2$$

$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \cdot (V_{OF} - V_{tn})^2 \cdot (1 + \lambda_n V_{DS}) \Rightarrow V_{OF} - V_{tn} = \sqrt{\frac{2 \times 100}{60 \times 49 \times}}$$

for  $I_1$ ,  $V_{A_F} = V_{D_F}$

$$\Rightarrow V_{AS_1} = \text{E} 1.11$$

$$\frac{I_1 \times 2}{\mu_n C_{ox}(\frac{W}{L})} = (V_{DS} - 0.8)^2 (1 + 2\gamma V_{DS})$$

$$\Rightarrow V_{S_1} = -1.1V$$

$$\Rightarrow V_{GF} = \sqrt{\frac{2 \cdot I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + 0.8 = 1.21V$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS2} - V_t)$$

$$\frac{d}{dt} \nabla_{\tilde{g}} = \text{[Redacted]}$$

$$V_{CC} = V_T - V_S$$

13 20

$$Z_{\text{Cox}} = \frac{1}{2} \mu_m C_{\text{ox}} \left( \frac{w}{L} \right) \times (V_{\text{OF}} - V_{\text{FB}})^2 (1 + \alpha_m V_{\text{OF}})$$



$$= \frac{1}{2} \times 6G_F \times 40 \times (1.21 - 0.8)^2 (1 + 0.03 \cdot V_{D_S})$$

$$\frac{R00 \times 2}{60 \times 40 \times 0.168} = (1 + 0.03 V_{np})$$

$$V_{p2} = 0.1 + 0.03 V_{p1} = 0.992$$


$$\Rightarrow Q_{0.03} V_{DF} = \Rightarrow V_{DF} = -0.267$$

basic amplifier circuit:

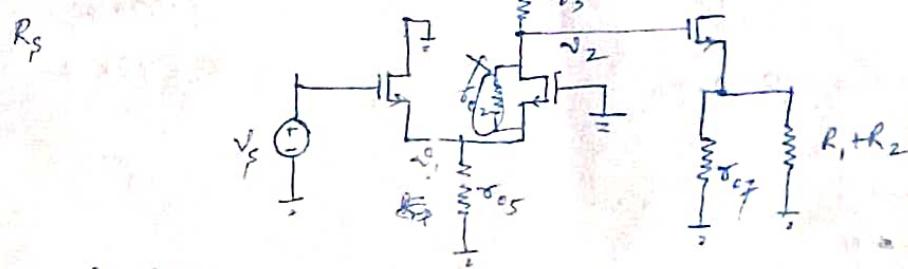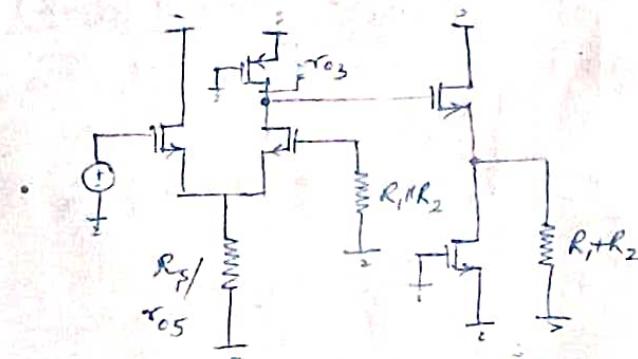

Consider \$r\_{o1}, r\_{o2} \rightarrow \infty\$ for \$M\_1 \& M\_2\$.

Now

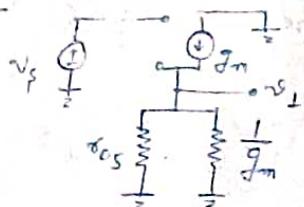

$$v_o = g_m v_{gs} \times \left( r_{o3} \parallel \frac{1}{g_m} \right)$$

$$\frac{v_{gs}}{v_s} = \frac{v_{gs} + v_i}{v_s}$$

$$\Rightarrow v_i = \cancel{g_m} \left( v_s - v_o \right) \left( r_{o3} \parallel \frac{1}{g_m} \right)$$

$$\Rightarrow v_i = v_s - v_o$$

$$\Rightarrow v_o = g_m v_s \left( r_{o3} \parallel \frac{1}{g_m} \right) \approx v_o g_m \left( r_{o3} \parallel \frac{1}{g_m} \right)$$

$$\therefore v_o (1 + g_m \cdot \cancel{r}) = \cancel{g_m} \cdot g_m \cdot \cancel{r}$$


$$\Rightarrow \frac{v_o}{v_s} = \frac{g_m \cancel{r}}{1 + g_m \cdot \cancel{r}} \approx 1$$

$$\Rightarrow v_o \left( 1 + \frac{r_{o3}}{r_{o2}} \right) \approx v_o \left( g_m + \frac{1}{r_{o2}} \right) r_{o3}$$

$$\Rightarrow v_o \left( \frac{r_{o2} + r_{o3}}{r_{o2}} \right) = v_o \left( \frac{g_m r_{o2} + 1}{r_{o2}} \right) r_{o3}$$

$$\Rightarrow \frac{v_o}{v_s} = \frac{\left( 1 + g_m r_{o2} \right) r_{o3}}{r_{o2} + r_{o3}}$$

$$\approx g_m \left($$

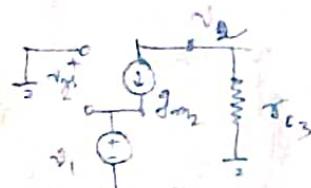

$$v_i = -g_m v_{gs} \times r_{o3}$$

$$= -g_m (-v_i) \times r_{o3}$$

$$v_o = +v_i + g_m r_{o3} \times v_i$$

$$v_o = v_i + g_m r_{o3} v_i$$



$$v_{gs} + v_i = 0 \Rightarrow v_i = -\cancel{r_{o3}} r_{o3}$$

$$\cancel{r_{o3}} = g_m v_{gs} + \frac{v_{ds2} - v_i}{r_{o2}}$$

$$\Rightarrow \cancel{r_{o3}} = -g_m v_i + \frac{v_{ds2} - v_i}{r_{o2}}$$

$$= -g_m v_i - \frac{v_i}{r_{o2}} + \frac{v_{ds2}}{r_{o2}}$$

$$\Rightarrow v_{ds2} + \left\{ v_i \left( g_m + \frac{1}{r_{o2}} \right) \right\} = \frac{v_{ds2}}{r_{o2}}$$

$$\Rightarrow \cancel{r_{o3}} = -g_m v_i - \frac{v_i}{r_{o2}} + \frac{v_{ds2}}{r_{o2}}$$

$$= -v_i \left( g_m + \frac{1}{r_{o2}} \right) + \frac{v_{ds2}}{r_{o2}}$$

$$\Rightarrow v_{ds2} = -\left\{ -v_i \left( g_m + \frac{1}{r_{o2}} \right) + \frac{v_{ds2}}{r_{o2}} \right\}$$

$$+ v_i \left( g_m + \frac{1}{r_{o2}} \right) r_{o3} - \cancel{v_i r_{o3}}$$

$$+ v_i \left( g_m + \frac{1}{r_{o2}} \right) r_{o3} - \cancel{v_i r_{o3}}$$

$$\approx v_i \left( g_m + \frac{1}{r_{o2}} \right) r_{o3}$$

$$v_1 \approx v_s$$

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{gs} - v_T)^2$$

$$v_2 = g_m \cdot r_{o3}$$

$$\frac{\partial i_D}{\partial v_{gs}} = \mu_n C_{ox} \frac{W}{L} (v_{gs} - v_T)$$

$$v_0 \approx v_2 \Rightarrow v_0 = g_m r_{o3} v_s$$

$$= \mu_n C_{ox} \frac{W}{L} \times \frac{\sqrt{2} i_D}{\sqrt{\mu_n C_{ox} \frac{W}{L} \cdot i_D}}$$


$$a = g_m \cdot r_{o3}$$

$$r_{o3} = \frac{1}{2 I_D}$$

$$= 693 \mu \times 333 K$$

$$= \frac{1}{0.03 \times 100 \mu} \\ = 333 K \Omega$$

$$= 230 \Omega$$

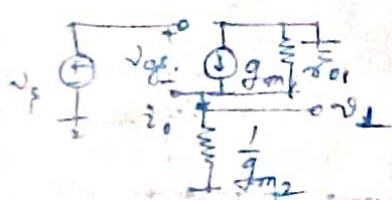

$$v_f = v_{gs} + v,$$

$$\Rightarrow v_{gs} = v_f - v,$$

$$\frac{1}{g_m} = \frac{1}{693 \mu}$$

$$= \frac{1}{0.03 \times 200 \mu} \\ = 166.7 K \Omega$$

$$v_1 = g_{m1} \times v_{gs} \times \frac{1}{g_{m2}}$$

$$\Rightarrow \frac{1}{g_m} \ll r_{o5}$$

$$= g_{m1} (v_s - v_1) \times \frac{1}{g_{m2}}$$

$$v_1 = \frac{g_{m1}}{g_{m2}} (v_s - v_f) - v_f \times \frac{g_{m1}}{g_{m2}}$$

$$\Rightarrow v_1 \left(1 + \frac{g_{m1}}{g_{m2}}\right) = \frac{g_{m1}}{g_{m2}} \cdot v_f \Rightarrow v_1 = \frac{v_f}{2}$$

$$\frac{v_2}{v_1} \approx (g_{m2} + \frac{1}{r_{o2}}) \times (r_{o2} || r_{o3})$$

$$v_f = v_{gs} + v,$$

$$\Rightarrow v_{gs} = v_f - v,$$

$$i_o = g_m v_{gs} + \frac{0 - v_1}{r_{o1}} \Rightarrow v_1 = i_o \times \frac{1}{g_{m2}}$$

$$= \left\{ g_m, v_f - v_1 \left( g_{m1} + \frac{1}{r_{o1}} \right) \right\} \frac{1}{g_{m2}}$$


$$= g_{m1} (v_f - v_1) - \frac{v_1}{r_{o1}}$$

$$= v_f - v_1 \left( g_{m1} + \frac{1}{r_{o1}} \right) \frac{1}{g_{m2}}$$

$$= g_{m1} v_s - v_1 \left( g_{m1} + \frac{1}{r_{o1}} \right)$$

$$= v_f - v_1 \left( 1 + \frac{1}{g_{m2} r_{o1}} \right)$$
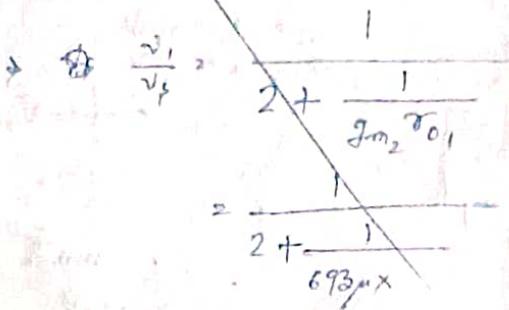
$$\Rightarrow v_1 \left( 1 + \frac{1}{g_m \tau_{c1}} \right) = v_s$$





$$\frac{v_2}{v_s} = \frac{(g_m \tau_{c2} + 1) \tau_{c3}}{(\tau_{c2} + \tau_{c3})}$$

$$= \frac{g_m \tau_{c2} \tau_{c3}}{\tau_{c2} + \tau_{c3}}$$

$$\Rightarrow a = \frac{1}{2} g_m \tau_{c3} = 109.25$$
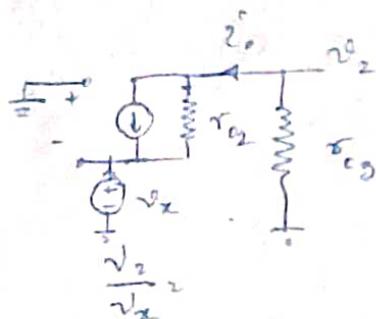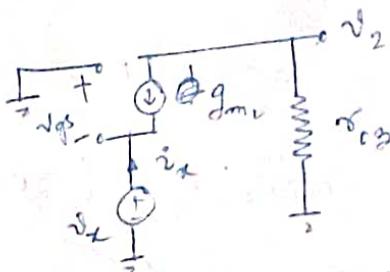
$$f = \frac{1}{21} \quad \Rightarrow \quad A_{CL} = \frac{a}{1+af} = \frac{109.25}{1+109.25 \times \frac{1}{21}} = \frac{109.25}{6.2} \\ = 17.62$$



$$v_{gs} + v_x = 0$$

$$\Rightarrow v_{gs} = -v_x$$

$$i_x = -g_m v_{gs} \tau_{c3}$$

$$\Rightarrow v_x = +g_m \tau_{c3} v_x$$

$$\Rightarrow i_x = -g_m v_{gs} = +g_m v_x \quad \Rightarrow \frac{v_x}{v_s} = g_m \tau_{c3}$$

$$\Rightarrow \frac{v_x}{v_s} = \frac{1}{g_m}$$

$$\Rightarrow a = \frac{1}{2} g_m \tau_{c3}$$

$$v_x + v_{gs} = 0$$

$$> \frac{1}{2} 693 \mu x 0.53 K$$

$$\Rightarrow v_2 = \left\{ 4 \left( g_m + \frac{1}{\tau_{c2}} \right) v_x + \frac{v_x}{\tau_{c2}} \right\} \tau_{c3}$$

$$\Rightarrow v_2 \left( 1 + \frac{\tau_{c3}}{\tau_{c2}} \right) = v_x \cdot \left( g_m + \frac{1}{\tau_{c2}} \right) \tau_{c3}$$

$$\begin{aligned} v_2 &> g_m v_{gs} + \frac{v_x - v_x}{\tau_{c2}} \\ &= g_m (-v_x) + \frac{v_x}{\tau_{c2}} - \frac{v_x}{\tau_{c2}} \end{aligned}$$

short - short open - open feedback technique



$$i_1 = \frac{v_1}{R_1} + \frac{v_2}{R_2}$$

assuming &

$$\therefore i_2 = v_2 \left( \frac{1}{R_2} + \frac{1}{R_p} \right) = \frac{v_2}{R_2} + \left( -\frac{v_2}{R_p} \right) = 0$$

$$\therefore v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_1}{R_1} + \frac{v_2}{R_2} = \frac{v_1}{R_1} + \frac{v_2 - V_2}{R_p}$$

$$\therefore v_1 + v_2 \left( \frac{1}{R_2} + \frac{1}{R_p} \right) = \frac{v_1 + v_2}{R_1} + v_2 \left( \frac{1}{R_2} + \frac{1}{R_p} \right) = \frac{v_1}{R_1}$$

$$\therefore v_1 + v_2 \left( \frac{1}{R_2} + \frac{1}{R_p} \right) = \left\{ v_1 + v_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_1}{R_1} \right\} + v_2 = v_2 = 0$$

$$\therefore v_1 + v_2 \left( \frac{1}{R_2} + \frac{1}{R_p} \right) = v_1 + v_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\therefore v_1 + v_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = v_1 + v_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_p} \right) = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2}{R_p}$$

$$\therefore \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_p} \right) v_1 + \left( \frac{1}{R_1} R_p + \frac{1}{R_2} R_p \right) v_2 = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2}{R_p}$$

$$\therefore \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_p} \right) v_1 + \left( \frac{1}{R_1} (R_2 + R_p) + \frac{1}{R_2} R_p \right) v_2 = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2}{R_p}$$

$$\therefore \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_p} \right) v_1 + \left( \frac{1}{R_1} (R_2 + R_p) + \frac{1}{R_2} R_p \right) v_2 = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2}{R_p}$$

$$\therefore \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_p} \right) v_1 + \left( \frac{1}{R_1} (R_2 + R_p) + \frac{1}{R_2} R_p \right) v_2 = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2}{R_p}$$

$$w_1 = \frac{1}{\tau_p} (t_1 + z_1) + \frac{z_1 - z_0}{(t_1 + t_0)}$$

$$\left( -a_0 + \frac{z_0}{\tau_p} \right) \left\{ i_1(t_0 + z_1) + \frac{z_1 - z_0}{\tau_1 + t_0} \right\} = w_1 \left\{ 1 + \frac{z_1}{\tau_1 + t_0} \right\}$$

$$-a_0 i_1(t_0 + z_1) = \frac{a_0 z_0 z_1}{\tau_1 + t_0}$$

$$+ \frac{z_0}{\tau_p} (t_0 + z_1) i_1 + \frac{z_0 z_1}{\tau_0 \tau_1 + t_0} i_1$$

$$= w_1 \left\{ 1 + \frac{z_1}{\tau_1 + t_0} \right\}$$

~~$$w_2 = \left\{ i_2(t_0 + z_2) \right\}$$~~

$$i_2 \left\{ -a_0 (t_0 + z_1) + \frac{z_1}{\tau_0} (t_0 + z_1) \right\}$$

$$= w_2 \left\{ 1 + \frac{z_0}{\tau_0 + t_0} + \frac{z_0 z_1}{\tau_0 (t_0 + z_1)} + \frac{z_0 z_1}{(\tau_0 + t_0) (\tau_1 + t_0)} \right\}$$

$$\tau_0 + t_0 \approx \tau_1 + t_0 \approx 2.2$$

$$w_2 w_1 \approx 0.67 M$$

$$i_2 = 2 m \cos \alpha \approx 0.770 \approx \frac{2 \pi}{0.77} \approx 2.63 \text{ rad}$$

$$= w_2 \left\{ 1 + \frac{z_0}{\tau_0} + \frac{z_0 z_1}{\tau_0 + t_0} + \frac{z_0 z_1}{\tau_0 (\tau_0 + t_0)} \right\}$$


$$i_2 \left\{ -2 m \cos \alpha + 0.77 \cdot 0.77 \right\} = w_2 \left\{ 1 + \frac{z_0 z_1}{\tau_0 (\tau_0 + t_0)} \right\}$$

$$+ 0.77 \cdot 0.77 \approx 1.23 \text{ rad}$$

$$\frac{z_0 z_1}{\tau_0 (\tau_0 + t_0)} \approx 0.09$$

## Variable gain Amplifier

1

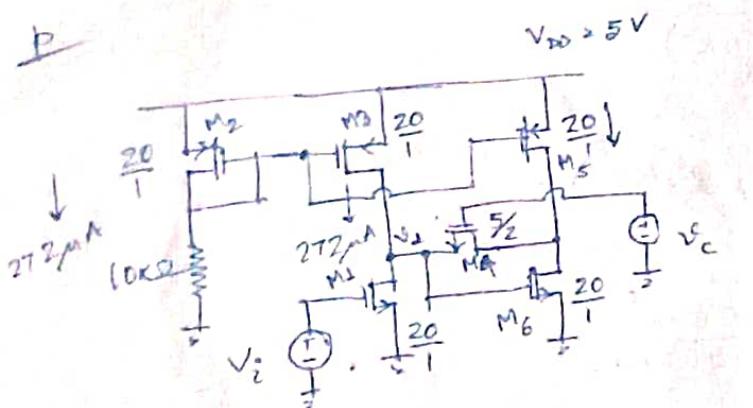

$$\mu_{\text{mCox}} = 60 \mu\text{A/N}^2$$

$$\mu_F C_{ox} = 30 \mu A/V^2$$

$$V_{th} = |V_{th}| = 0.8 \text{ V}$$

$$\lambda_n = \lambda_p = 0$$

$$V_{thq} = 1.14V \quad \lambda$$

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{SG} - V_{TH})^2$$

$$I_D = \frac{V_{DD} - V_{SG}}{10k\Omega}$$

$$\Rightarrow I_D = \frac{5 - V_{SG}}{10k\Omega}$$

$$\frac{5 - V_{SG}}{10K} = \frac{1}{2} \cdot 30 \mu \times \frac{20}{1} (V_{SG} - 0.8)^2$$

$$\Rightarrow 5 - V_{SG} = 3(V_{SG} - 0.8)^2$$


$$= 3(V_{SG}^2 - 1.6V_{SG} + 0.64)$$

$$\Rightarrow 3V_{SG}^2 - 4.8V_{SG} + 1.92 = 5 - V_{SG}$$

$$\Rightarrow 2V_{SG}^2 - 3.8V_{SG} - 6.92 = 0$$

$$\rightarrow V_{SG} = \frac{3.8 \pm \sqrt{3.8^2 + 4.3.6}}{2.3} = \frac{3.8 + 7.16}{6} \\ \cancel{\rightarrow \frac{3.8 \pm 9.87}{6} = 2.28V} = 1.83V$$
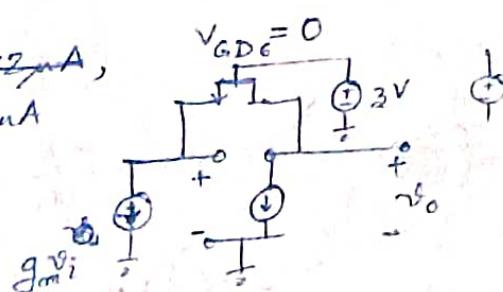
$$\Rightarrow I_D = \frac{5 - 2.08}{10k} = 272 \mu A$$



$$\text{now, } \frac{q_1 I_{\mu}}{2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS6} - V_{th})^2$$

$$\Rightarrow \frac{1}{2} GM_1 \cdot 20 (V_{ASD} - 0.8)^2$$

$$\Rightarrow V_{GSE} = 1.53 \text{ V}$$

~~總計~~ =

$$I_D = \frac{1}{2} \mu n C_s \frac{W}{L} (V_{GF} - V_{TH})^2$$

In linear region,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{N}{L} \left\{ 2(V_{C_{ox}} - V_T) V_{D_{N1}} - V_{D_{N0}}^2 \right\}$$


$$\Rightarrow \frac{2I_D}{2V_{DS}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left\{ 2(V_{GS} - V_{TH}) - 2V_D \right.$$

$$\left. + \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) - \mu_n C_{ox} \frac{W}{L} V_D \right\}$$

$$\Rightarrow g_{dsg} = \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{TH})$$


$$= 60\mu \times \frac{5}{2} \cdot (V_c - 1.53 - \cancel{0.05})^{1.14}$$
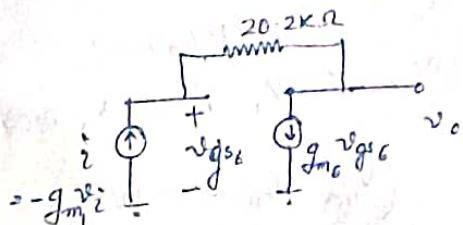
$$\Rightarrow 60\mu \times \frac{5}{2} (3 - 1.53 - \cancel{0.05})^{1.14} \Rightarrow (20.2 \text{ k}\Omega)^{-1}$$



$$g_{m1} = g_{m6} = g_m$$

BA →

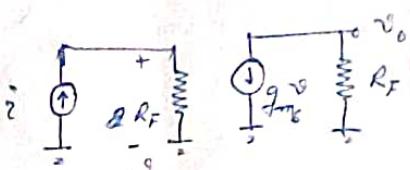


$$= \sqrt{2\mu_n C_{ox} \frac{W}{L} I} \\ = \sqrt{2 \cdot 60\mu \cdot 20 \cdot 217\mu}$$

$$v_o = -g_{m6} \cdot v_i \cdot R_F \\ = -g_{m6} \cdot (i \cdot R_F \cdot R_F) \Rightarrow \frac{v_o}{i} = -g_m \cdot R_F^2$$

$$\begin{aligned} &= -g_{m6} \cdot (-g_m v_i) R_F \\ &= +g_{m6}^2 R_F^2 = -8T_2 \mu \times (20.2k)^2 \\ &= -355.81 \times 10^3 \end{aligned}$$

$$f = -\frac{1}{20.2k} =$$
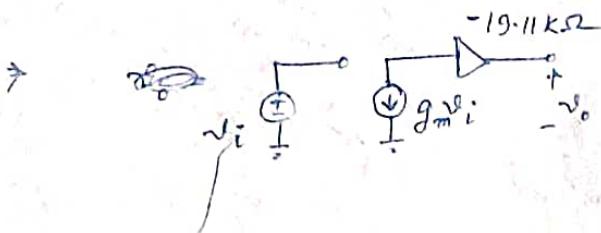
$$\Rightarrow \left( \frac{v_o}{i} \right)_{CL} = \frac{-355.81 \times 10^3}{1 + \frac{355.81 \times 10^3}{20.2 \times 10^3}} = -19.11 \text{ k}\Omega$$



$$v_o = -g_m v_i \times (-19.11 \text{ k}\Omega)$$


$$\Rightarrow \left( \frac{v_o}{v_i} \right)_{CL} = 8T_2 \mu \times 19.11k$$

$$= 16.66 \text{ V/V}$$

$$\therefore R_{of} = \frac{R_F}{(1+af)} = \frac{R_F}{18.61} = \frac{20.2 \text{ k}\Omega}{18.61} \\ \approx 1.085 \text{ k}\Omega$$

|| ROUGH ||

active cascode  $\varphi$

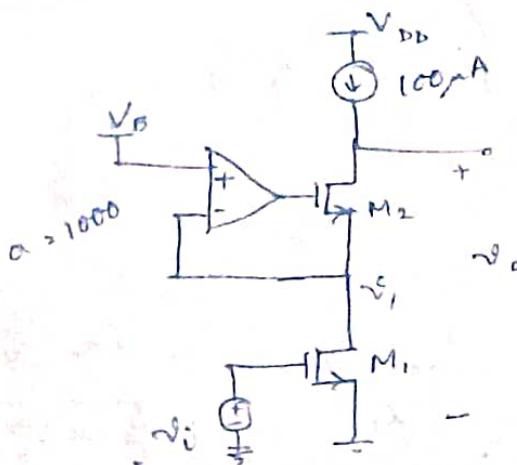



$$K_n' = \mu_n C_{ox} = 140 \mu A/V^2$$

$$V_{ov} = 0.3V, V = 0, \lambda_n = 0.03V^{-1}$$

$$(V_{GS_1} - V_{TH}) = 0.3V$$

$$-av, -v_{gs_2} - v_i = 0$$
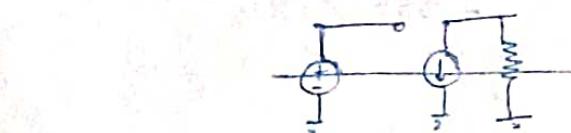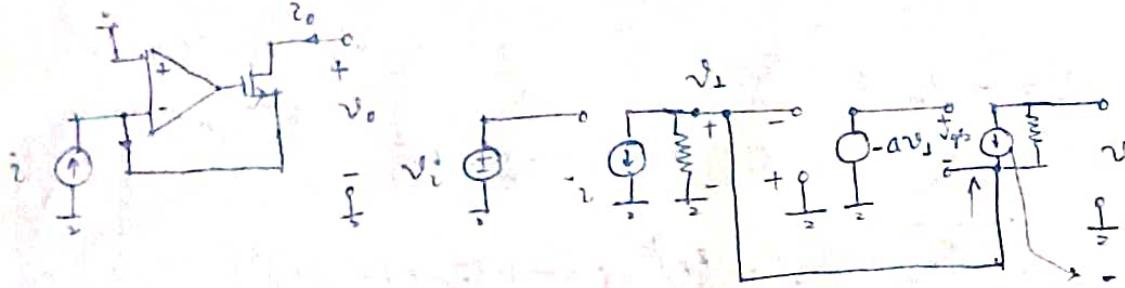
$$\Rightarrow v_{gs_2} = -(a+1)v, \approx -av,$$




$$v_1 = i_x \frac{r_{o1}}{1 + g_m r_{o2}}$$

$$\Rightarrow v_1 = i_x \frac{r_{o1} \parallel r_{o2}}{1 + g_m (r_{o1} \parallel r_{o2})}$$

$$v_2 = -av_1 = -\frac{a \times i_x (r_{o1} \parallel r_{o2})}{1 + g_m (r_{o1} \parallel r_{o2})}$$

$$v_o = -g_m r_{o2} v_2$$
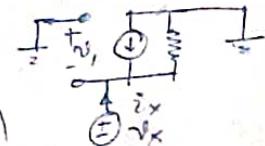
$$= + \frac{a \times g_m (r_{o1} \parallel r_{o2}) \times r_{o2}}{1 + g_m (r_{o1} \parallel r_{o2})} \times i_x = \frac{r_{o1} \parallel r_{o2}}{1 + g_m (r_{o1} \parallel r_{o2})}$$



$$i_x = g_m v_1 + \frac{c}{r_c} \quad v_1 + v_x = 0 \quad \Rightarrow i_x - g_m v_x - \frac{v_x}{r_c} = 0$$

$$\Rightarrow v_x (g_m + \frac{1}{r_c}) = i_x \quad \Rightarrow \frac{v_x}{i_x} = \frac{r_c}{1 + g_m r_c}$$

$$\frac{v_x}{i_x} = \frac{r_{o1} r_{o2}}{1 + g_m r_{o2}} \quad \frac{r_{o1} r_{o2}}{r_{o1} + \frac{r_{o2}}{1 + g_m r_{o2}}} = \frac{r_{o1} r_{o2}}{r_{o1} + g_m r_{o1} r_{o2} + r_{o2}}$$

$$\frac{r_{o1} r_{o2}}{1 + g_m r_{o2}}$$

$$= \frac{r_{o1} r_{o2}}{r_{o1} + g_m r_{o1} r_{o2} + r_{o2}}$$

$$= \frac{r_{o1} \parallel r_{o2}}{1 + g_m (r_{o1} \parallel r_{o2})}$$

$$\hat{i}_o = -\frac{v_o}{r_{o2}}$$

$$\hat{i}_i = -g_m v_i$$


$$\frac{v_o}{i} = -\frac{\alpha r_{o2} \times g_{m2} (r_o || r_{o2})}{1 + g_{m1} (r_o || r_{o2})}$$

$$\left( \frac{v_o}{i} \right)_{CL} = \frac{-g_{m2} \alpha r_{o1}}{1 + g_{m2} \alpha r_{o1}}$$

$$\therefore \left( \frac{v_o}{i} \right)_{CL} \approx -\alpha r_{o2} g_{m1}$$

feedback ckt:

$r_{o2}$

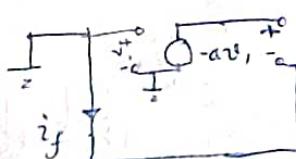

$$\hat{i}_o = g_{m2} v_{GS2} \quad \hat{i}_o = g_m v_{GS2} + \frac{v_o}{r_{o2}}$$

$$= g_{m2} (-av_1) \quad = g_{m2} (-av_1) + \frac{v_o}{r_{o2}}$$

$$\hat{i}_i = g_{m2} (-av_1)$$

$$= -g_{m2} \alpha v_i$$


$$= -g_{m2} \alpha \hat{i}_i r_{o1}$$

$$= -g_{m2} \alpha \hat{i}_i r_{o1} + \frac{v_o}{r_{o2}}$$

$$\frac{v_o}{\hat{i}_i} = -g_{m2} \alpha r_{o1} R_f = \frac{R_f}{1 + \alpha}$$

$$\Rightarrow \hat{i}_o (1 + \frac{R_f}{r_{o2}}) = g_{m2} (-\alpha) \hat{i}_i r_{o1}$$

$$\left( \frac{v_o}{i} \right)$$

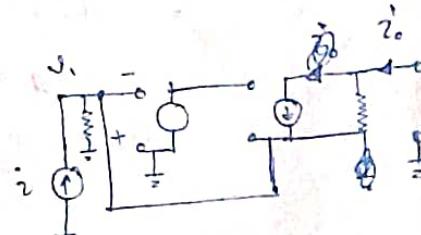

$$\Rightarrow \frac{v_o}{\hat{i}_i} = A_{o2} = \frac{-\alpha g_{m2} r_{o1}}{(1 + \frac{R_f}{r_{o2}})}$$

$$\hat{i}_o = g_{m2} (-av_1) \quad \hat{i}_o = \frac{v_o}{r_{o2}} + g_{m2} v_{GS2}$$

$$= -\alpha g_{m2} \hat{i}_i r_{o1} \quad = -\alpha g_{m2} \hat{i}_i r_{o2} (1 + \alpha f)$$

$$= -\alpha g_{m2} v_{GS2} \quad f = 1 \quad \hat{i}_o = \frac{v_o}{r_{o2}} (1 + \alpha g_{m2} r_{o1})$$

$$= -g_{m2} \alpha v_i \quad = -g_{m2} \times \alpha \times r_{o1} \times i$$

$$\Rightarrow \frac{v_o}{\hat{i}_i} = -g_{m2} \alpha r_{o1}$$

$$\frac{\hat{i}_o}{\hat{i}_i} = \frac{(-\alpha g_{m2} r_{o1} r_{o2}) / R_L}{1 + \frac{\alpha g_{m2} r_{o1} r_{o2} i_f}{R_L}} \quad \hat{i}_o = -\frac{\alpha g_{m2} r_{o1} r_{o2}}{R_L} \hat{i}_i$$

$$\hat{i}_o = -\frac{\alpha g_{m2} r_{o1} r_{o2}}{R_L} \quad i_f = 0$$

$$\hat{i}_o = -\frac{\alpha g_{m2} r_{o1} r_{o2}}{R_L} \quad \hat{i}_i = -\frac{\alpha g_{m2} r_{o1} r_{o2}}{R_L} \hat{i}_i$$

$$\left( \frac{v_o}{i} \right)_{CL} = -\frac{g_{m2} \alpha r_{o1}}{1 + \frac{g_{m2} \alpha r_{o1}}{R_L}} = -\frac{g_{m2} \alpha r_{o1}}{R_L}$$

$$\hat{i}_o = -\frac{v_o}{R_L} \quad \hat{i}_i = -g_{m1} v_i$$


$$\Rightarrow \frac{v_o}{R_L g_{m1}} \Rightarrow \frac{v_o}{\hat{i}_i} = -\alpha g_{m1} g_{m2} r_{o1} r_{o2} \frac{\hat{i}_o}{-g_{m1} v_i} = -g_{m2} \alpha r_{o1}$$

$$\Rightarrow \frac{\hat{i}_o}{\hat{i}_i} = +g_{m1} g_{m2} \alpha r_{o1}$$


$$\hat{i}_o = -\hat{i}_i r_{o2} \quad \frac{v_o}{v_i} = -g_{m1} g_{m2} r_{o1} r_{o2}$$

Shunt - Series

$g$  parameter representation:

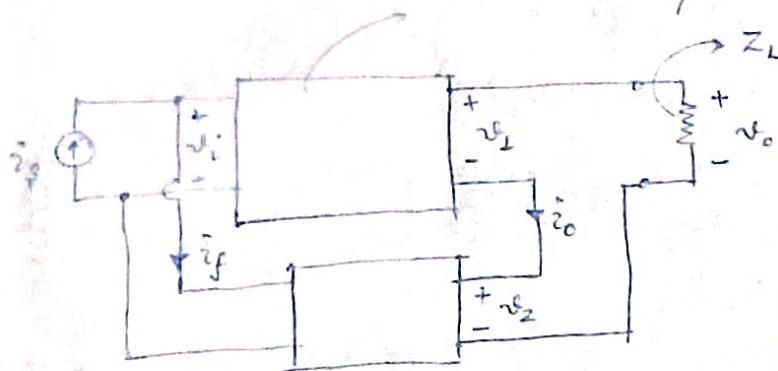



$g$  parameter:

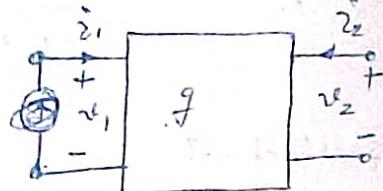

now, for the feedback amplifier.

$$g_{12f} \ll g_{21a}$$


$$\therefore g_{12f} \gg g_{21f}$$

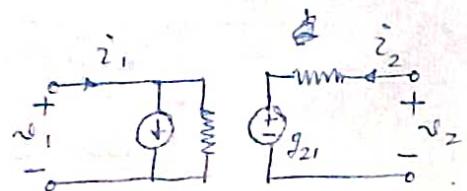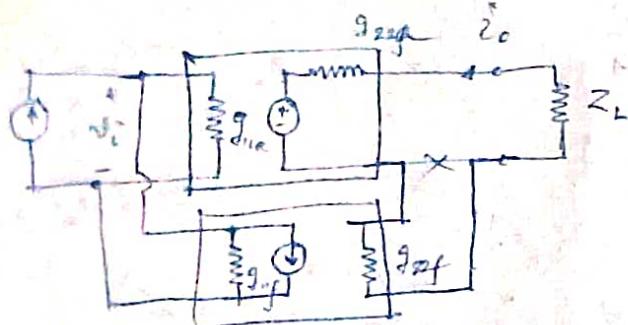

$$i_1 = g_{11}v_i + g_{12}i_2$$

$$v_2 = g_{21}v_i + g_{22}i_2$$

Basic Amplifier akt:

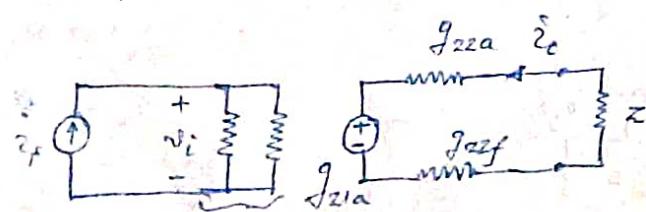

$$g_{11a} + g_{12f} = g_i$$

$$v_i = \frac{i_s}{g_i} \quad \therefore i_o = -\frac{g_{21a}v_i}{g_o}$$

$$\therefore i_o = -\frac{g_{21a} \cdot i_s}{g_o g_i}$$


$$\therefore \frac{i_o}{i_s} = a = -\frac{g_{21a}}{g_o g_i}$$

$$20 \log \frac{a_o}{1+a_o\beta} = -20 \log \beta \quad 20 \log 10^5 = 100$$


feedback ckt:  $g_{12f}$  .  $10 \log 10^{10} = 10^5$ ,  $\beta = 0.707$

$$g_{12f} = \left. \frac{i_f}{i_o} \right|_{v_i=0}$$
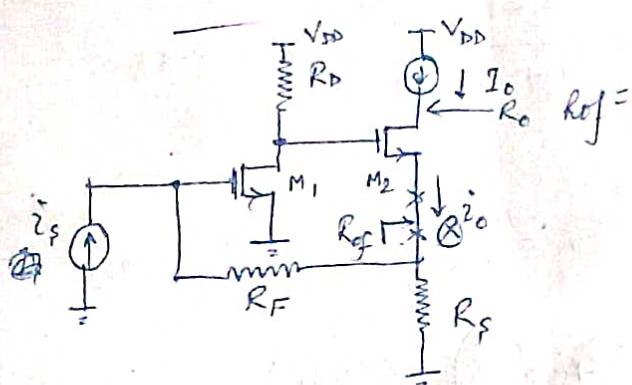
$$\left( \frac{i_o}{i_s} \right)_{CL} = \frac{\left( -\frac{g_{21a}}{g_o g_i} \right)}{1 + \left( -\frac{g_{21a}}{g_o g_i} \right) \cdot g_{12f}}$$



Basic amplifier

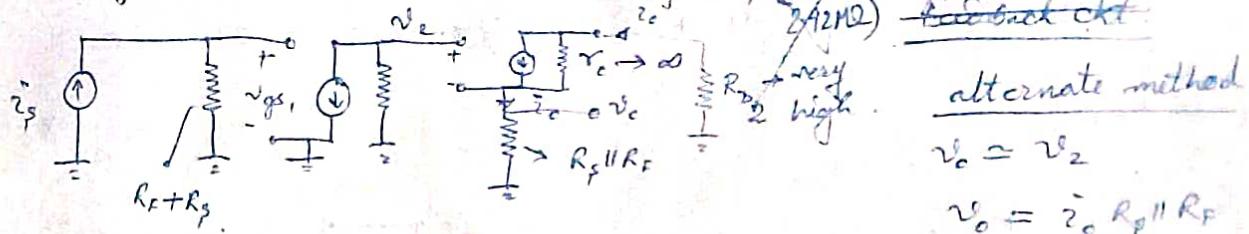

$$i_{gs1} = i_s (R_F + R_S)$$

$$v_2 = -g_m v_{gs1} \times R_D \quad i_o = g_m v_{gs2} + \frac{(-i_s R_D - v_o)}{r_o}$$

$$i_o = g_m v_{gs2} \quad \Rightarrow i_o (1 + \frac{R_D}{r_o}) = g_m^2 v_{gs2} - \frac{v_o}{r_o}$$

$$i_o (1 + g_m \times R_F \parallel R_S)$$

$$\frac{v_{gs2}}{i_s} =$$

$$v_2 = v_{gs2} + i_o (R_F \parallel R_S)$$

$$\Rightarrow i_o (1 + \frac{R_D}{r_o} + \frac{R_S \parallel R_F}{r_o})$$

$$= -g_m g_m R_D \times i_s (R_F + R_S)$$

$$\Rightarrow v_{gs2} = v_2 - i_o (R_F \parallel R_S)$$

$$= g_m \frac{(i_s - i_o)}{i_s}$$

$$\frac{i_o}{i_s} = \frac{-g_m g_m R_D (R_F + R_S)}{1 + g_m \times (R_S \parallel R_F)}$$

$$\Rightarrow i_o = g_m (v_2 - i_o R_F \parallel R_S)$$


$$\approx - \frac{g_m R_D (R_F + R_S)}{R_F \parallel R_S}$$

$$\Rightarrow i_o (1 + g_m R_F \parallel R_S) = g_m v_2$$

$$= g_m \times (-g_m) v_{gs1} \times R_D$$

$$= - \frac{5m \times 10K \times 100K}{9K} = -555.5 \text{ A/A}$$

O/P resistance at X

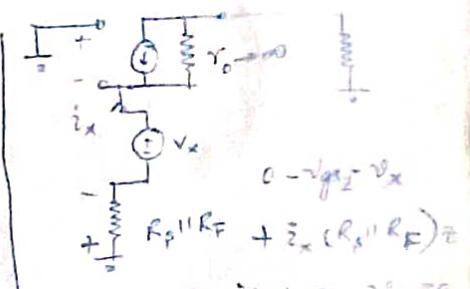

$$g_{m1} = g_{m2} = 5 \text{ mA/V}$$

$$R_D = 10K\Omega, R_S = 10K\Omega$$

$$R_F = 90K\Omega$$


$$r_o \rightarrow \infty \Rightarrow \frac{i_x}{i_o} = \frac{1 + g_m (R_o \parallel R_F)}{g_{m2}} \approx R_o \parallel R_F$$

alternate method

$$v_o = v_2$$

$$v_o = i_o R_o \parallel R_F$$

feedback akt:

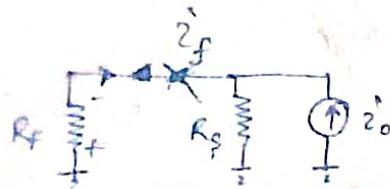

$$\Rightarrow -i_f \cdot R_F = -(i_f + i_o) R_S = 0$$

$$\Rightarrow -i_f (R_F + R_S) = i_o R_S$$

$$\Rightarrow \frac{i_f}{i_o} = f = -\frac{R_S}{R_F + R_S} = \frac{10K}{100K} = 0$$

$$\Rightarrow \left( \frac{i_o}{i_f} \right)_{CL} = \frac{-555 \cdot 5}{1 + 55 \cdot 5} = -9.83$$

$$\Rightarrow R_{if} = \frac{R_F + R_S}{(1 + af)} = \frac{100K}{56.5} = 178K \Omega$$

$$R_{if} = ((R_F \parallel R_S) + \tau_{c2}) \times (1 + af)$$

$$i_{ifT} = (9K + 20K) \times 56.5 = 519.8K \Omega$$

$$v_{gs2} - v_x + i_x (R_S \parallel R_F) = 0$$

$$v_{gs2} - v_x - i_x (R_S \parallel R_F) = 0$$

$$i_x = g_m v_{gs2} - \frac{i_x (R_S \parallel R_F)}{\tau_{c2}} = 0 \Rightarrow v_{gs2} = -i_x (R_S \parallel R_F)$$

$$i_x = g_m v_{gs2} - \frac{i_x (R_S \parallel R_F)}{\tau_{c2}} + i_x R_T - v_x + i_x (R_S \parallel R_F)$$



$$i_x \left( 1 + g_m \left( R_S \parallel R_F \right) + \frac{R_T \parallel R_F}{\tau_{c2}} \right) = \frac{v_x}{\tau_{c2}} + \frac{v_x}{\tau_{c2}} - i_x \frac{(R_S \parallel R_F)}{\tau_{c2}}$$

$$\Rightarrow i_x \left( \tau_{c2} + g_m \tau_{c2} (R_S \parallel R_F) + \underline{R_S \parallel R_F} \right) = v_x$$

$$\Rightarrow v_x = 20K + 9K + 5m \times 20K \times 9K$$

$$\Rightarrow \frac{v_x}{i_x} \times (1 + af) = 52M \Omega$$


$R_{out}$ :

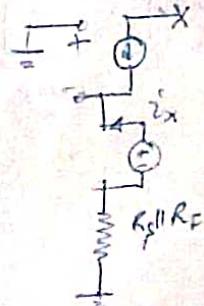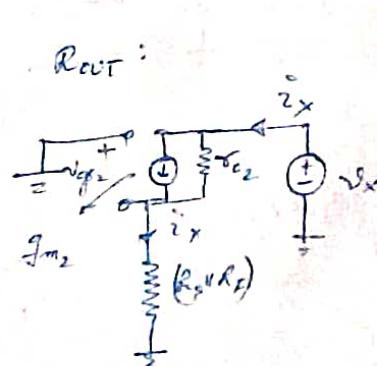


$$\Rightarrow i_x = g_m v_{gs2} + \frac{v_x - i_x (R_S \parallel R_F)}{\tau_{c2}}$$

$$\Rightarrow i_x (1 + g_m) = -g_m i_x (R_S \parallel R_F)$$
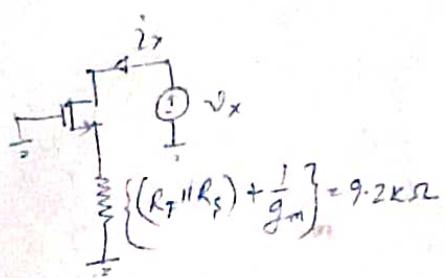
$$\Rightarrow i_x = \frac{g_m v_{gs2}}{1 + g_m} + \frac{v_x - i_x (R_S \parallel R_F)}{\tau_{c2}}$$



$$i_x \tau_{o2} = g_m \tau_{o2} v_x$$

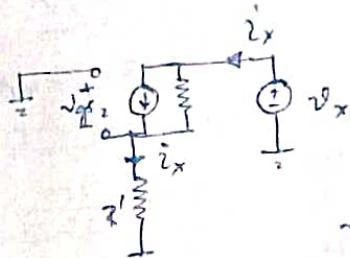

$$i_x = g_m v_{g2} + \frac{v_x - i_x R'}{\tau_{o2}}$$

$$\cancel{i_x} \Rightarrow i_x = -g_m R' i_x - i_x \frac{R'}{\tau_{o2}} + \cancel{\frac{v_x}{\tau_{o2}}} + \cancel{\frac{v_x}{\tau_{o2}}}$$



$$v_{g2} + i_x R' = 0 \Rightarrow i_x (1 + g_m R' + \frac{R'}{\tau_{o2}}) = \frac{v_x}{\tau_{o2}}$$

$$\Rightarrow \frac{v_x}{i_x} = \tau_{o2} + g_m \tau_{o2} R' + \underline{R'}$$

$$= 20k + 9.2k + 5m \times 20k \times 9.2k$$

=

|| ROUGH ||

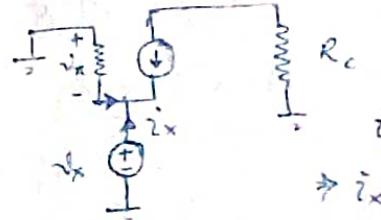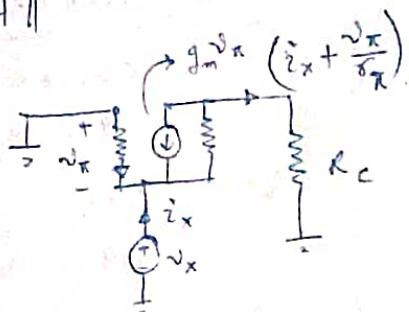

$$i_x + \frac{v_x}{r_n} + g_m v_x = 0 \Rightarrow i_x = -v_x \left( \frac{g_m}{r_n} + \frac{1}{r_n} \right)$$

$$v_R + v_x = 20 \Rightarrow i_x + g_m v_x + \frac{v_x}{r_n} - \frac{v_x - (i_x + \frac{v_x}{r_n}) R_c}{\tau_o \tau_o} = 0$$


$$\Rightarrow i_x + \frac{i_x R_c}{\tau_o \tau_o} = \left( g_m + \frac{1}{r_n} + \frac{1}{r_n} + \frac{R_c}{\tau_o \tau_o} \right) v_x$$

$$\Rightarrow i_x \frac{(\tau_o + R_c)}{\tau_o} = \left( \frac{g_m \tau_o \tau_o + \tau_o + R_n + R_c}{\tau_o \tau_o} \right) v_x$$

$$\Rightarrow \frac{v_x}{i_x} = \frac{\tau_o (\tau_o + R_c)}{g_m \tau_o \tau_o + \tau_o + R_n + R_c} = \frac{i_x (\tau_o + R_c)}{(\beta + 1) \tau_o + (\tau_o + R_c)}$$

$$= \frac{\tau_o}{1 + \frac{(\tau_o + R_n)(1 + g_m \tau_o)}{\tau_o + R_c}} = \frac{\left( \frac{\tau_o}{\beta + 1} \right) (\tau_o + R_c)}{\tau_o + \frac{\tau_o + R_n}{\beta + 1}}$$

Q37  
Q37

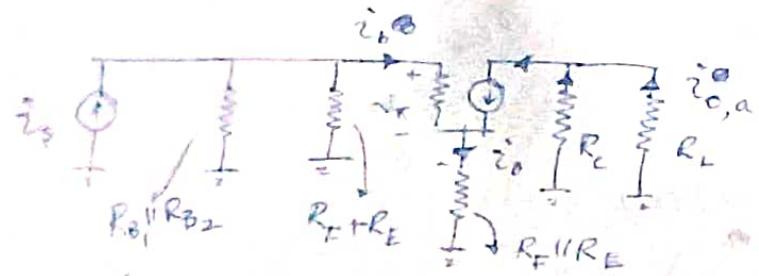

$$g_m = \frac{\partial I_c}{\partial V_T} = \frac{865 \mu A}{26 m} = 33.27 \text{ mA/V}$$

$$\beta = 120 = g_m r_\pi$$

$$\Rightarrow r_\pi = \frac{120}{33.27} = 3.6 \text{ k}\Omega$$

$$(i_s - i_b) \{ (R_B \parallel R_E) \parallel (R_F + R_E) \}$$

$$= i_b (\tau_\pi + (\beta + 1)(R_F \parallel R_E))$$

$$i_o = g_m v_\pi + \frac{\partial v_\pi}{\partial \tau_\pi} i_b \tau_\pi \quad v_\pi = i_b \tau_\pi$$

$$= \left( g_m + \frac{1}{\tau_\pi} \right) i_b \tau_\pi$$

$$\Rightarrow i_b = \frac{i_s \times \{ (R_B \parallel R_E) \parallel (R_F + R_E) \}}{\{ (R_B \parallel R_E) \parallel (R_F + R_E) \} + r_\pi + (\beta + 1)(R_F \parallel R_E)}$$

$$= \frac{\beta + 1}{r_\pi} i_s \tau_\pi = (\beta + 1) i_s$$

$$i_b = (\beta + 1) \times i_s \times \frac{6}{119 \cdot 6}$$

$$= \frac{121 \times i_s \times 6}{119 \cdot 6}$$

$$= i_s \times \frac{13 \text{ k} \parallel 11 \text{ k}}{\{ 6 \text{ k} + 3.6 \text{ k} + 121 \times 909 \}}$$

$$= i_s \times \frac{6 \text{ k}}{119 \cdot 589 \text{ k}}$$

$$\Rightarrow \frac{i_o}{i_s} = 6.07$$

$$\text{now, } i_{o,a} R_L = (i_o - i_{o,a}) R_C$$

$$\frac{i_{o,a} \times 11}{i_s \times 10} = 6.07$$

$$\Rightarrow i_{o,a} (R_L + R_C) = i_o R_C$$

$$\Rightarrow i_{o,a} = i_o \times \frac{R_C}{R_L + R_C}$$

$$= i_o \times \frac{10}{11} \times \frac{(R_C \parallel R_L)}{R_C}$$

$$\Rightarrow \frac{i_{o,a}}{i_s} = \frac{6.07 \times 10}{11}$$


$$= 5.5$$

$$i_o = i_{o,a} \times \frac{11}{10}$$

$$\therefore a_{CL} = \frac{6.07}{1 + 6.07 \times \frac{1}{11}} = 3$$

## High frequency analysis

Consider a CS amplifier:

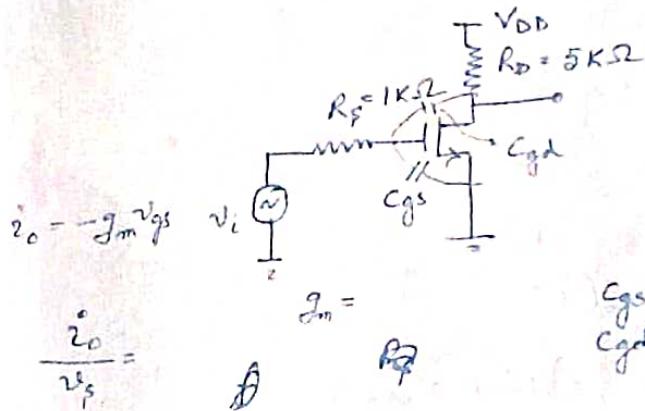

$$f_T = 400 \text{ MHz}$$


$f_T = \frac{\text{unity gain freq}}{\text{unity short ckt current gain frequency}}$

$$\frac{i_o}{v_i} = g_m$$

$$\begin{aligned} C_{gs} &= ? \\ C_{gd} &= 0.5 \text{ pF} \end{aligned}$$

$$\mu C_{ox} \frac{W}{L} = 100 \text{ mA/V}^2$$
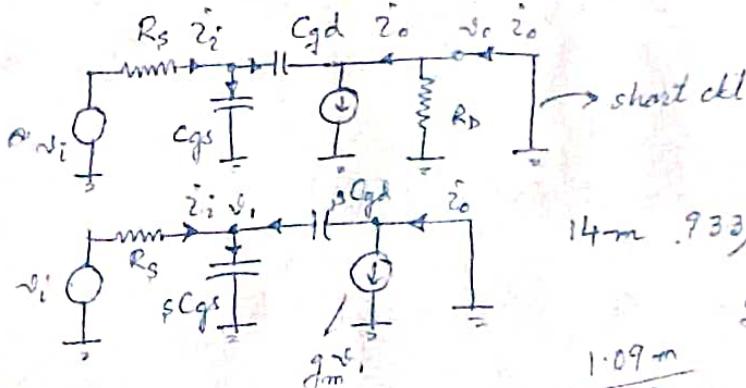
$$I_D = 1 \text{ mA}, \text{let } \lambda = 0$$



$$14 \text{ m } .933 \mu$$

$$g_m^2 \sqrt{2 \pi f_T (\mu C_{ox} \frac{W}{L})}$$

$$\frac{1.09 \text{ m}}{2\pi(5f)}$$

$$= \sqrt{2 \times 60 \times 10 \times 1 \text{ m}}$$

$$i_o = g_m v_i + (0 - v_i) \times s C_{gd}$$

$$= g_m v_i - v_i \cdot s C_{gd} = v_i (g_m - s C_{gd}) = \sqrt{ }$$

~~$$i_2 = v_i \times s C_{gs} + v_i$$~~

~~$$i_2 + v_i \times s C_{gd} = v_i (s C_{gs} + s C_{gd})$$~~

$$\Rightarrow i_2 = v_i (s C_{gs} - s C_{gd})$$

$$i_2 = v_i (s C_{gs} + s C_{gd})$$

$$\Rightarrow i_o = \frac{i_2 (g_m - s C_{gd})}{(s C_{gs} - s C_{gd})}$$

$$\Rightarrow i_o = \frac{g_m v_i}{g_m + s C_{gd}}$$

$$i_o + v_i C_{gd}s = g_m v_i$$

$$\Rightarrow i_o = (g_m - s C_{gd}) v_i$$

$$i_o = \frac{g_m - s C_{gd}}{s C_{gs} + s C_{gd}} \times i_2$$

$$\frac{i_o}{i_2} = \frac{\sqrt{g_m^2 + \omega^2 C_{gd}^2}}{\omega_T (C_{gs} + C_{gd})} = 1 \Rightarrow$$

$$= \frac{\sqrt{2 \times 10^{-4} + 1.58 \times 10^{-6}}}{2\pi f_T} = 5.65 \text{ pF}$$

$$\begin{aligned} g_{gm} &= 2\pi (C_{gs} + C_{gd}) \\ &= 2\pi (0.5 + 0.5) \\ &= 3.183 \text{ pF} \end{aligned}$$

$$s C_{gd} = \frac{g_m}{2\pi f_T} = \frac{100 \text{ mA/V}^2}{2\pi \times 500 \text{ MHz}} = 3.183 \text{ pF}$$

$$s C_{gs} = \frac{g_m}{2\pi f_T} = \frac{100 \text{ mA/V}^2}{2\pi \times 500 \text{ MHz}} = 3.183 \text{ pF}$$

$$s C_{gd} = \frac{g_m}{2\pi f_T} = \frac{100 \text{ mA/V}^2}{2\pi \times 500 \text{ MHz}} = 3.183 \text{ pF}$$


$$s C_{gs} = \frac{g_m}{2\pi f_T} = \frac{100 \text{ mA/V}^2}{2\pi \times 500 \text{ MHz}} = 3.183 \text{ pF}$$

$$C_{gs} + C_{gd} = \frac{\sqrt{g_m^2 + \omega^2 C_{gd}^2}}{2\pi f_T}$$

$$= \frac{\sqrt{2 \times 10^{-4} + (2\pi f_T)^2}}{2\pi f_T}$$

$$C_{gs} + C_{gd} = 5.65 \mu F$$

$$C_{gs} = 5.65 - 0.5 = 5.15 \mu F$$

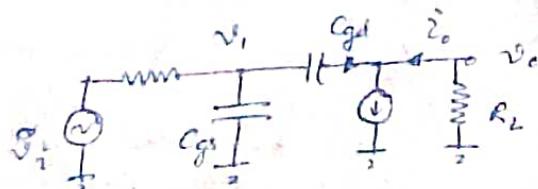

$$v_o = -i_o R_D \quad i_o = g_m v_i + \frac{(v_o - v_i)}{R_D}$$

$$i_o = -\frac{v_o}{R_D} \quad i_o + (v_i - v_o) s C_{gd} = g_m v_i$$

$$\Rightarrow i_o - v_o s C_{gd} = v_i (g_m s C_{gd})$$

$$\frac{v_i - v_o}{R_s} = v_i (s C_{gs} + s C_{gd})$$

$$\Rightarrow \frac{v_i}{R_s} = v_i \left\{ (s C_{gs} + s C_{gd}) + \frac{1}{R_s} \right\}$$

$$\Rightarrow v_i = \left\{ 1 + s R_s (C_{gs} + C_{gd}) \right\}^{-1} v_o$$

$$= \frac{v_o}{1 + s R_s (C_{gs} + C_{gd})}$$

$$\Rightarrow -\frac{v_o}{R_D} - v_o s C_{gd} = \frac{(g_m - s C_{gd}) v_i}{\{1 + s R_s (C_{gs} + C_{gd})\}}$$


$$\Rightarrow v_o (1 + s R_D C_{gd}) = - \frac{R_D (g_m - s C_{gd})}{\{1 + s R_s (C_{gs} + C_{gd})\}} v_i$$

$$\Rightarrow \frac{v_o}{v_i} = - \frac{R_D (g_m - s C_{gd})}{\{1 + s R_s (C_{gs} + C_{gd})\} (1 + s R_D C_{gd})}$$

$$\omega_Z = \frac{g_m}{C_{gd}} = \frac{14.14 m}{0.5 p} \Rightarrow f_Z = 4.5 \text{ GHz}$$

$$f_{P_1} = \frac{1}{R_s(C_{gs} + C_{gd}) \cdot 2\pi} = 28.17 \text{ MHz}$$
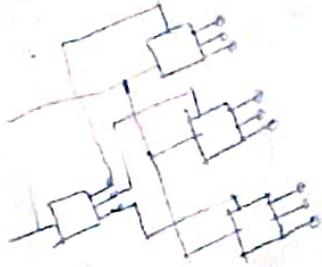
$$f_{P_2} = \frac{1}{2\pi R_D C_{gd}} = 63.6 \text{ MHz}$$



$$\begin{aligned} \frac{v_i - v_o}{R_s} &= v_i s C_{gs} + (v_i - v_o) s C_{gd} \\ &= v_i (s C_{gs} + s C_{gd}) - v_o s C_{gd} \end{aligned}$$

$$\Rightarrow v_i = v_o \left\{ 1 + s R_s (C_{gs} + C_{gd}) \right\} - v_o s R_s C_{gd}.$$

$$\Rightarrow v_i = \frac{v_i + v_o s R_s C_{gd}}{\left\{ 1 + s R_s (C_{gs} + C_{gd}) \right\}}$$

$$\Rightarrow -\frac{v_o (1 + s R_s C_{gd})}{R_D} = \frac{(g_m - s C_{gd})(v_i + v_o s R_s C_{gd})}{\left\{ 1 + s R_s (C_{gs} + C_{gd}) \right\}}$$

$$\Rightarrow -v_o \left\{ \frac{1}{R_D} + s C_{gd} + \frac{(g_m - s C_{gd}) s R_s C_{gd}}{\left\{ 1 + s R_s (C_{gs} + C_{gd}) \right\}} \right\} = \frac{(g_m - s C_{gd})}{\left\{ 1 + s R_s (C_{gs} + C_{gd}) \right\}}$$

$$\begin{aligned} \Rightarrow -v_o \left\{ \frac{1 + s R_s (C_{gs} + C_{gd}) + s^2 R_s C_{gd} (C_{gs} + C_{gd})}{R_D} \right. \\ \left. + \frac{s R_s C_{gd} g_m - s^2 R_s C_{gd}^2}{R_D} \right\} = g_m - s C_{gd}. \end{aligned}$$

$$\Rightarrow -v_o \left\{ 1 + s R_s (C_{gs} + C_{gd}) + s C_{gd} R_D + s^2 R_s C_{gd} (C_{gs} + s R_s C_{gd} R_D g_m) \right\} \\ = (g_m - s C_{gd}) R_D v_i$$

$$\Rightarrow v_o \left\{ 1 + s \{ R_s (C_{gs} + C_{gd}) + C_{gd} R_D + g_m R_s R_D C_{gd} \} + s^2 R_s R_D C_{gd} C_{gs} \right\} \\ = -(g_m - s C_{gd}) R_D$$

$$v_o \left\{ s^2 R_s R_D C_{gd} C_{gs} + s \{ R_s (C_{gs} + C_{gd}) + C_{gd} R_D + g_m R_s R_D C_{gd} \} + 1 \right\} = R_D (g_m - s C_{gd}) v_i$$

$$\Rightarrow v_o \left\{ s^2 \times 1.29 \times 10^{-17} + s \{ 4.35 \times 10^{-8} + 1 \} \right\} = R_D (g_m - s C_{gd}) v_i$$

$$s = \frac{-4.35 \times 10^{-8} \pm \sqrt{(4.35 \times 10^{-8})^2 - 4.129 \times 10^{-17}}}{2 \times 1.29 \times 10^{-17}}$$


$$= \frac{-4.35 \times 10^{-8} \pm 4.29 \times 10^{-8}}{2.58 \times 10^{-17}}$$


$$\Rightarrow v_o \left\{ s - 23.25 \times 10^6 \right\} \left\{ s - 3.34 \times 10^9 \right\} = R_D (g_m - s C_{gd}) v_i$$

$$\Rightarrow f_1 = \frac{23.25 \times 10^6}{2\pi} = 3.7 \text{ MHz}$$

$$f_2 = \frac{3.34 \times 10^9}{2\pi} = 531.5 \text{ MHz}$$
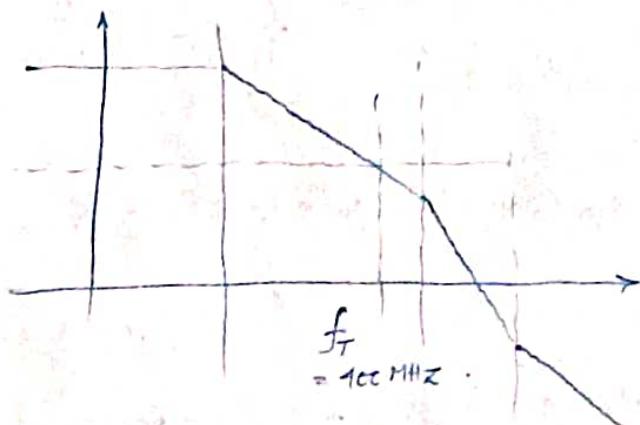
$$x_1 = \frac{g_m}{2\pi C_{gd}} = 4.5 \text{ GHz}$$



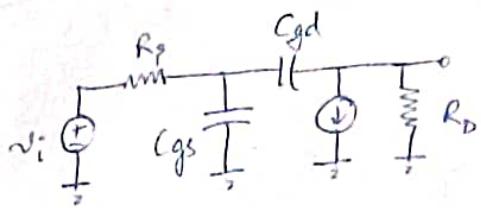

dominant pole:

Resistance associated with  $C_{gs}$ :  $R_g$

open  $C_{gd}$ ,

open cur.


short  $v_i$

Resistance associated with  $C_{gd}$ :  $(R_g + R_D)$

$\Rightarrow$

Time constant:

$$R_g C_{gs} + C_{gd}(R_g + R_D)$$

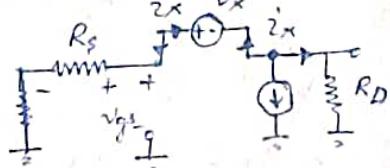

$$v_{gs} = i_x R_g$$

$$\frac{i_x R_g - v_x}{R_D} + g_m v_{gs} + i_x = 0$$

$$\Rightarrow i_x \frac{R_g}{R_D} - \frac{v_x}{R_D} + g_m R_g i_x + i_x = 0$$

$$\Rightarrow \frac{v_x}{R_D} = i_x \left( 1 + g_m R_g + \frac{R_g}{R_D} \right)$$

$$\Rightarrow \frac{v_x}{i_x} = R_D + g_m R_g R_D + R_g$$

$\Rightarrow$  time constant =


$$R_g C_{gs} + \left( R_D + g_m R_g R_D + R_g \right) C_{gd}$$

1.5 MHz

$$= 5.15 \times 10^{-9} + 3.835 \times 10^{-8} = 4.35 \times 10^{-8}$$

$$\Rightarrow f_{p1} = \frac{1}{2\pi \tau} = \frac{1}{2\pi \times 4.35 \times 10^{-8}} = 3.66 \text{ MHz}$$

short ckt & open ckt time constant

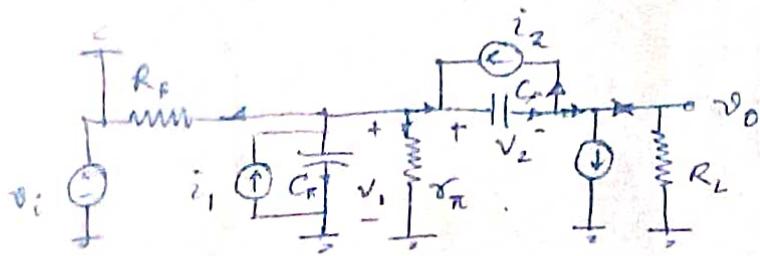

$$v_1 - v_2 = v_o$$

$$v_o = v_1 - v_2$$

$$i_1 = v_1 \cdot sC_n + \frac{v_1}{R_s} + \frac{v_1}{R_f} + v_2 \cdot sC_u$$

$$i_2 = v_2 \cdot sC_u +$$

$$v_2 \cdot sC_u + g_m v_1 \neq \frac{v_1 - v_2}{R_L} = i_2$$

$$\Rightarrow i_2 = v_2 \left( sC_u - \frac{1}{R_L} \right) + v_1 \left( g_m + \frac{1}{R_L} \right)$$

$$i_1 = v_1 \left( sC_n + \frac{1}{R_s} + \frac{1}{R_f} \right) + v_2 \cdot sC_u$$

$$i_2 = v_1 \left( g_m + \frac{1}{R_L} \right) + v_2 \left( sC_u - \frac{1}{R_L} \right)$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} sC_n + \frac{1}{R_s} + \frac{1}{R_f} & sC_u \\ g_m + \frac{1}{R_L} & sC_u - \frac{1}{R_L} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\Delta = \left( sC_n + \frac{1}{R_s} \right) \times \left( sC_u - \frac{1}{R_L} \right) - sC_u \left( g_m + \frac{1}{R_L} \right) = 0$$

$$\Rightarrow s^2 C_n C_u R_s R_L - s \frac{C_n}{R_L} + s \frac{C_u}{R_s} - s C_u g_m - s \frac{C_u}{R_L} - \frac{1}{R_s R_L} = 0$$

$$\Rightarrow \frac{s^2 C_n C_u R_s R_L - s C_n R_s + s C_u R_L - s C_u g_m R_s R_L - s C_u R_s - 1}{R_s R_L} = 0$$

$$\Rightarrow s^2 C_n C_u R_s R_L - s \{ C_n R_s + C_u R_L + g_m R_s R_L C_u + C_u R_s \} - 1 = 0$$

## Cascade amplifier

$$\begin{aligned}
 \Delta(s) &= k_3 s^3 + k_1 s^2 + k_2 s + k_0 \\
 &\Rightarrow k_3 \left( s^3 + \frac{k_1}{k_3} s^2 + \frac{k_2}{k_3} s + \frac{k_0}{k_3} \right) \\
 &= k_3 (s - p_1)(s - p_2)(s - p_3) \\
 &= k_3 \left\{ (s^2 - (p_1 + p_2)s + p_1 p_2)(s - p_3) \right\} \\
 &= k_3 \left\{ s^3 - s^2(p_1 + p_2) + s p_1 p_2 - s^2 p_3 + p_3(p_1 + p_2)s - p_1 p_2 p_3 \right\} \\
 &\Rightarrow k_3 \left\{ s^3 - s^2(p_1 + p_2 + p_3) + s(p_1 p_2 + p_2 p_3 + p_3 p_1) - p_1 p_2 p_3 \right\}
 \end{aligned}$$

Denominator :  $\Delta$

$$\Delta(s) = \left\{ s^2 R_f R_D C_{gd} C_{gs} + s \left\{ R_f (C_{gs} + C_{gd}) + C_{gd} R_D + g_m R_s R_D C_{gd} \right\} + 1 \right\} = 0$$

$$\Rightarrow s^2 + s \frac{\{ R_s C_{gs} + (R_s + R_D + g_m R_f R_D) C_{gd} \}}{R_s R_D C_{gd} C_{gs}} + \frac{1}{R_s R_D C_{gd} C_{gs}} = 0$$

$$\Rightarrow (s - p_1)(s - p_2) = 0 \rightarrow \text{if } p_1 \text{ non dominant pole}$$

$$\Rightarrow (1 - \frac{s}{p_1})(1 - \frac{s}{p_2}) = 0 \rightarrow \text{dominant pole}$$

$$1 + \frac{s^2}{p_1 p_2} - s \left( \frac{1}{p_1} + \frac{1}{p_2} \right) = 0 \Rightarrow \frac{1}{p_1 p_2} = R_s R_D C_{gd} C_{gs}$$



$$\Rightarrow p_2 = \frac{R_s C_{gs} + (R_s + R_D + g_m R_s R_D) C_{gd}}{R_s R_D C_{gd} C_{gs}}$$

$$\begin{aligned}
 \text{if } p_2 \gg p_1 \Rightarrow \frac{1}{p_1} &\approx R_s C_{gs} + (R_s + R_D + g_m R_s R_D) C_{gd} \\
 &= \sum R_i C_i
 \end{aligned}$$

for non dominant pole,

$$\begin{aligned}
 s^2 - s(p_1 + p_2) + p_1 p_2 &= 0 \Rightarrow p_2 \approx \frac{1}{R_D C_{gd}} + \frac{1}{C_{gs} \times \frac{R_2 R_D}{R_2 + R_D + g_m R_s R_D}} \\
 &= \frac{1}{R_D C_{gd}} + \frac{1}{C_{gs} \times \frac{(R_2 || R_D)}{1 + g_m R_s R_D}}
 \end{aligned}$$

short ckt time constant:

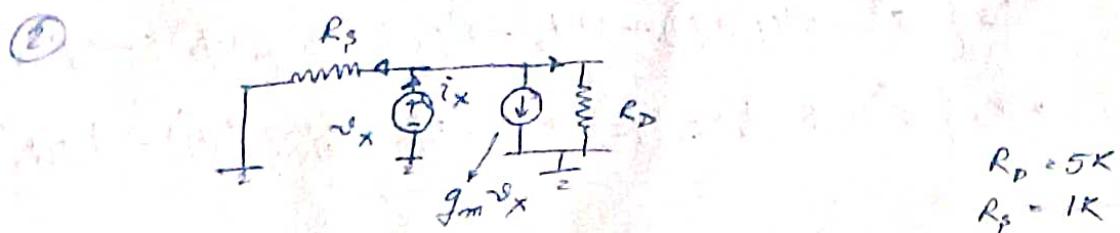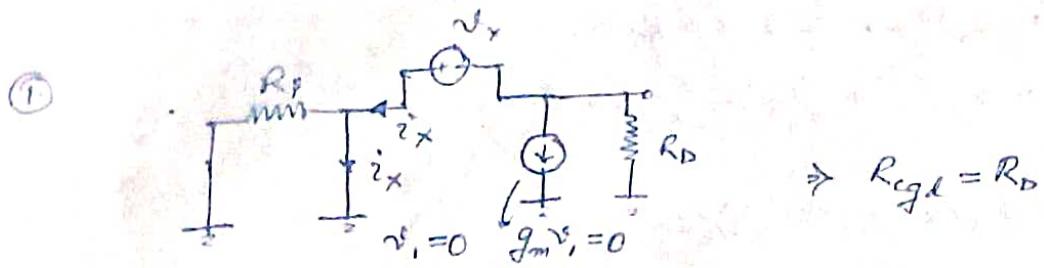

$$\begin{aligned} \dot{i}_x &= \frac{v_x}{R_p} + g_m v_x + \frac{v_x}{R_D} \\ &\approx v_x \left( \frac{2g_m R_p R_D + R_p + R_D}{R_p R_D} \right) \end{aligned}$$

$$g_m = 14.19 \text{ mA/V}$$

$$R_p \parallel R_D = 0.83K$$

$$\Rightarrow \frac{v_x}{i_x} = \frac{R_p \parallel R_D}{1 + g_m R_p \parallel R_D}$$

$$\Rightarrow f_2 = \text{non-dominant pole: } \sum \frac{1}{R_i C_i}$$

$$\Rightarrow f_2 = \frac{1}{R_D C_{gd}} + \frac{1}{C_{gd} \times \frac{R_p \parallel R_D}{1 + g_m R_p \parallel R_D}}$$

$$= \frac{1}{5K \times 0.5\mu} + \frac{1}{0.5 \cdot 1.5 \mu \times 65}$$


$$= \frac{1}{2.5 \text{ ns}} + \frac{1}{3.34 \times 10^{-10}}$$

$$\Rightarrow f_2 = \frac{1}{2\pi(R_p \parallel R_D)}$$

$$\Rightarrow f_2 = \frac{3.39 \times 10^9}{2\pi}$$

$$= 540 \text{ MHz}$$

CE stage with emitter degeneration.

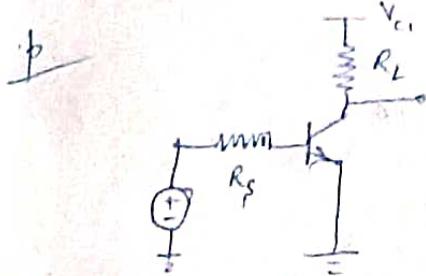

find  $\frac{V_o}{V_i}$

$f = 3 \text{ dB}$

$$K_n \frac{W}{L} = 10 \times 60 \mu$$

$$= 600 \mu$$

$$R_1 = 40 \text{ K}$$

$$R_2 = 20 \text{ K}$$

$$R_p = 10 \text{ K}\Omega$$

$$\frac{20}{60} = \frac{1}{3} \times 6 = 2 \text{ V}$$

$$R_L = 5 \text{ K}\Omega$$

$$I_D = \frac{1}{2} K_n \frac{W}{L} (V_{AS} - V_{TH})^2$$

$$= \frac{1}{2} 600 \mu \cdot 300 \text{ mV}^2$$

given  $\beta = 200$

$$f_T = 600 \text{ MHz}$$

$$I_C = 1 \text{ mA}$$

$$\left(\frac{V_o}{V_i}\right)_{n/p} = 192.5$$

$$C_A = 0.2 \text{ pF}$$

$$C_{je} = 2 \text{ pF} \approx C_\pi \quad \left(\frac{V_o}{V_i}\right)_n = 16.67$$

$$C_{ce} = 1 \text{ pF}$$

$$\Rightarrow 1 + af = 11.54$$

$$\frac{V_o}{V_i} = \frac{r_\pi + g_m h_e}{r_\pi + R_p} \times \frac{R_L}{R_E}$$

$$f_T = \frac{g_m}{2\pi(C_\pi + C_0)} = \frac{38.5 \text{ m}}{2\pi(C_\pi + 0.2 \text{ pF})}$$

$$g_m = 0.3 \text{ mA}$$

$$G = 0.3 \text{ mA} \times 10 \text{ K}$$

$$= 6 - 3 = 3 \text{ V}$$


$$= \frac{5.2 \text{ K}}{5.2 \text{ K} + 40 \text{ K}}$$

$$\Rightarrow \beta = 600 \text{ M} \rightarrow C_\pi + 0.2 \text{ pF} = \frac{38.5 \text{ m}}{2\pi \times 600 \text{ M}} = 10 \text{ pF} \quad 10 \cdot 2 \text{ pF}$$

$$= -EG / \text{w/o } R_E$$

$$\Rightarrow C_\pi = 10 \text{ pF} \cdot \sqrt{K_n \frac{W}{L} \times 0.3 \text{ m}} = \sqrt{2 \times 6 \cdot 3 \text{ m} \times 0.6 \text{ m}}$$
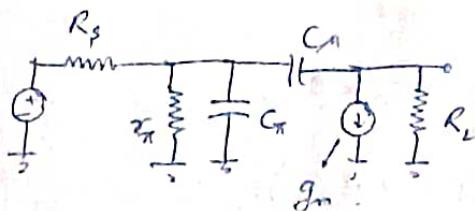
$$= \sqrt{0.6 \text{ m} \times 0.6 \text{ m}}$$



$$\gamma_\pi = \frac{\beta}{g_m} = \frac{200}{38.5 \text{ m}} = 0.6 \text{ mA/V}$$

$$= 5.2 \text{ K}$$

$$R_{C_\pi} = \gamma_\pi \parallel R_p = 10 \text{ K} \parallel 5.2 \text{ K}$$

$$= 3.42 \text{ K}$$

$$\Rightarrow R_{C_\pi} C_\pi = 3.42 \text{ K} \times 10 \text{ pF}$$

$$= 34.2 \text{ ns}$$

$$\begin{aligned} & \frac{40}{3} \text{ K} \\ & \frac{40}{3} \text{ K} \\ & 13.33 \text{ K} \end{aligned}$$

$$R_{C_\pi} = (R_p \parallel \gamma_\pi) + R_L + g_m R_L \times (R_p \parallel \gamma_\pi)$$

$$= 3.42 \text{ K} + 5 \text{ K} + 38.5 \text{ m} \times 5 \text{ K} \times 3.42 \text{ K}$$

$$= 666.77 \text{ K}$$

$$\Rightarrow R_{C_\pi} C_\pi = 666.77 \text{ K} \times 0.2 \text{ pF}$$

$$\Rightarrow f_{p_1} = \frac{1}{2\pi(34.2 \text{ n} + 133.35 \text{ n})} \Rightarrow 133.35 \text{ ns}$$

13.33 K

$$\begin{aligned} & (13.33 \text{ K} \times 100) \\ & + (13.33 \text{ K} \times 20) \end{aligned} \Rightarrow 949.9 \text{ kHz}$$

$$= 46.8 \text{ MHz}$$


$$\begin{aligned} & 13.33 \text{ K} \\ & + 10 \text{ K} \\ & + 6 \text{ K} \end{aligned} \Rightarrow 33 \text{ K}$$

$$\begin{aligned} & 2 \times 13.33 \text{ K} + 6 \times 13.33 \text{ K} \\ & = 26.66 \text{ K} + 79.98 \text{ K} = 106.64 \text{ K} \end{aligned}$$

with emitter degeneration:

$$R_s = ?$$

$$R_E = 300 \Omega$$

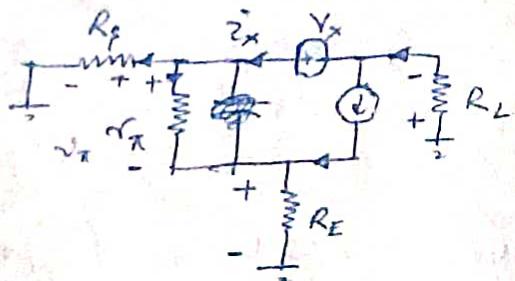

$$R_2 = 5K$$

$$R_E = 300 \Omega$$

$$G_1 = -\frac{R_L}{R_E} = -\frac{5K}{300} = -16.7$$

$$G_2 = -g_m R_L = -38.5m \times 5K$$

$$= 192.5$$

$$(i_x - \frac{v_\pi}{r_\pi}) R_s - v_\pi - (\frac{v_\pi}{r_\pi} + g_m v_\pi) R_E = 0 \Rightarrow$$

$$\Rightarrow i_x = v_\pi \left( \frac{R_s}{r_\pi} + 1 + \frac{R_E}{r_\pi} + \frac{g_m R_E}{r_\pi} \right)$$

$$= \frac{v_\pi}{r_\pi} \cdot (R_s + R_E + r_\pi + g_m R_E)$$

$$= v_\pi \frac{(10K + 0.3K + 3.42K + 38.5m \times 0.3K)}{3.42K}$$

also,  $\left( i_x - \frac{v_\pi}{r_\pi} \right) \cancel{R_s} \Rightarrow v_\pi = i_x \times 0.25$

also,  $v_\pi \left( \frac{1}{r_\pi} + g_m \right) R_E + v_x - v_x + (i_x + g_m v_\pi) R_L = 0$

$$i_x \times 0.25 \left( \frac{1}{r_\pi} + g_m \right) R_E + i_x \times 0.25 + i_x R_L + g_m i_x \times 0.25 \times R_L = v_x$$

$$\Rightarrow i_x \left\{ 4.4 + 0.25 + 5K + 48.125 \right\} = v_x$$

$$\Rightarrow \frac{v_x}{i_x} \approx 5K$$



X

$$f_{cav} = 5K \times 0.25$$

$$= 1.25$$

$$\Rightarrow f_{P1, max} = \frac{1}{2\pi 55.2 \mu} \approx 4.52 \text{ MHz}$$

Q)  $R_\pi = ?$

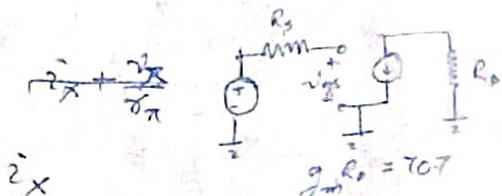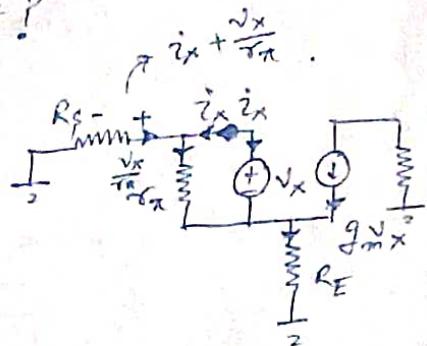

$$5^{\circ} \quad 14 \times 3 = 67$$

$$\Rightarrow \left( i_x + \frac{v_x}{R_\pi} \right) R_s - v_x = (g_m v_x + i_x) +$$

$$R_s \times i_x - v_x - (g_m v_x - i_x) R_E = 0$$

$$\Rightarrow i_x (R_s + g_m R_E) = (1 + g_m R_E) v_x$$

$$\Rightarrow \frac{v_x}{i_x} = \left( \frac{1 + g_m R_E}{R_s + R_E} \right)^{-1}$$

$$\Rightarrow R_\pi = v_x \parallel \frac{R_s + R_E}{1 + g_m R_E} = \frac{3.42K \parallel 820}{661\Omega} = 661\Omega$$

$$\Rightarrow R_\pi C_\pi = 10\text{pF} \times 661\Omega = 6.61\text{nS}$$

$$\Rightarrow f_p = \frac{1}{2\pi R_\pi C_\pi} = \frac{1}{2\pi \times 661\Omega \times 10^{-12}} = 20.9 \text{ MHz}$$

$$R_{cg1} = \frac{R_s + R_E}{1 + g_m R_E}$$

$$= 132$$

$$C_{gs} = 5.15\text{fF}$$

$$R_{cg2} =$$

$$R_s + R_D + G_m R_s R_D$$

$$G_m = \frac{g_m}{1 + g_m R_s} = 933\text{A}$$



$$= 1K + 5K + 4.67K = 10.67K$$

$$\tau = 6.8 \times 10^{-10} + 5.335 \times 10^{-9} = 6.015 \times 10^{-9}$$

$$\Rightarrow f_p = \frac{1}{2\pi 6.015 \times 10^{-9}}$$

$$\text{OR } \frac{2K}{1+1K}$$

Calculation of  $R_s$ :

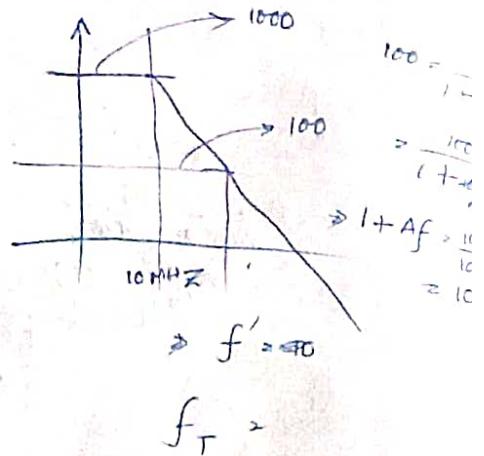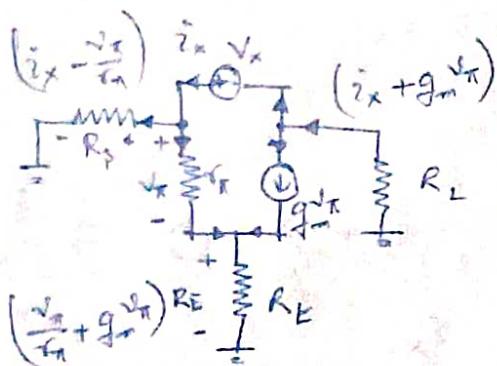

$$(i_x - \frac{v_\pi}{r_\pi}) R_s - v_x + (i_x + g_m v_\pi) R_L = 0$$

$$\Rightarrow i_x (R_s + R_L) - \left( \frac{v_\pi}{r_\pi} R_s - v_\pi - g_m v_\pi R_L \right) = v_x$$

$$i_x (R_s - \frac{v_\pi}{r_\pi} R_s + v_\pi) - (g_m v_\pi R_L) R_E = 0$$

$$\Rightarrow i_x R_s = v_\pi \left( \frac{R_s}{r_\pi} + 1 + \frac{(1 + g_m) R_E}{r_\pi} \right)$$

$$= v_\pi \left\{ \frac{R_s + r_\pi + (\beta + 1) R_E}{r_\pi} \right\}$$

$$\therefore v_\pi = \frac{R_s r_\pi \times i_x}{R_s + r_\pi + (\beta + 1) R_E}$$

$$\Rightarrow i_x (R_s + R_L) - v_\pi \left( \frac{R_s}{r_\pi} - g_m R_L \right) = v_x$$

$$\Rightarrow i_x (R_s + R_L) - \frac{R_s i_x}{R_s + r_\pi + (\beta + 1) R_E} \left( \frac{R_s - g_m R_L}{r_\pi} \right) = v_x$$


$$\Rightarrow \frac{(R_s + R_L)(R_s + r_\pi + (\beta + 1) R_E) - R_s (R_s - g_m R_L)}{R_s + r_\pi + (\beta + 1) R_E} = \frac{v_x}{i_x}$$

$$\Rightarrow \frac{\cancel{R_s^2} + R_s r_\pi + R_s R_E (\beta + 1) + R_L R_s + R_L r_\pi + R_L R_E (\beta + 1) - \cancel{R_s^2} - R_s R_L}{R_s + r_\pi + (\beta + 1) R_E} = \frac{v_x}{i_x}$$


$$\Rightarrow \frac{(\beta + 1)(R_s R_E + R_L R_s) + R_L R_s + R_L r_\pi + R_s r_\pi - \beta R_s R_L}{R_s + r_\pi + (\beta + 1) R_E} = \frac{v_x}{i_x}$$

$$i_x R_S - v_x + i_o R_D = 0$$
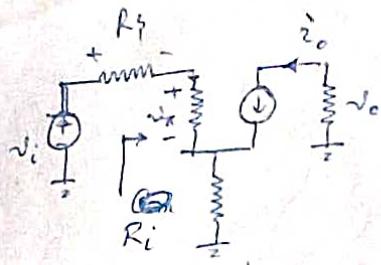
$$\Rightarrow i_x R_S - v_x + \left( i_x + \frac{g_m i_x R_F}{1 + g_m R_S} \right) R_D = 0$$



$$\frac{i_o}{v_i} =$$

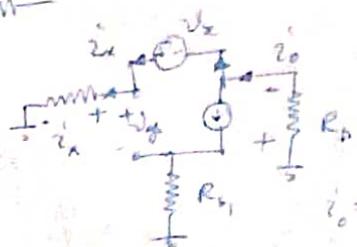

$$i_o = i_x + g_m v_x$$

$$i_o = g_m v_x$$

$$i_x R_F - v_{gs} - g_m v_{gs} R_S = 0$$

$$\Rightarrow v_{gs} (1 + g_m R_S) = i_x R_F \Rightarrow \frac{v_{gs}}{i_x} = \frac{i_x R_F}{(1 + g_m R_S)}$$

$$v_i - \left( \frac{v_x}{r_\pi} \right) R_S - v_\pi - \left( \frac{v_x}{r_\pi} + g_m v_x \right) R_E = 0$$

$$i_x R_S + i_x \left\{ \frac{1 + g_m R_S + g_m R_F}{1 + g_m R_S} \right\} R_D = v_x \Rightarrow v_i - v_\pi \left\{ \frac{R_F}{r_\pi} + 1 + \left( \frac{1}{r_\pi} + g_m \right) R_E \right\} = 0$$

$$\frac{v_x}{i_x} = R_S + \left\{ 1 + \frac{g_m R_F}{1 + g_m R_S} \right\} R_D \Rightarrow v_i = v_\pi \left\{ \frac{R_F + r_\pi + (\beta+1) R_E}{r_\pi} \right\}$$

$$= R_S R_D + \frac{g_m R_F R_D}{1 + g_m R_S}$$


$$\Rightarrow i_o \approx \frac{g_m \times r_\pi \times v_L}{R_S + r_\pi + \beta R_E}$$

$$\frac{i_o R_L}{v_i} = - \frac{g_m r_\pi R_L}{R_S + r_\pi + \beta R_E}$$

$$\frac{v_o}{v_i} = - \frac{g_m R_L}{1 + \frac{R_F}{r_\pi} + g_m R_E}$$

follow this procedure

$$\frac{v_o}{v_i} = G_m R_L$$

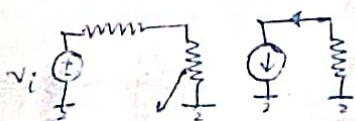


$$r_\pi + (\beta+1) R_E = R_i$$

$$= 5.2K + (20) \times 0.3K$$

$$= 65.5K$$

$$v_o = - g_m v_\pi R_L$$

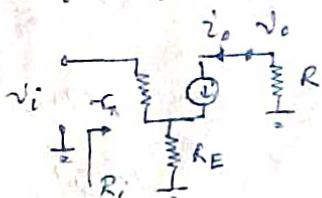


$$G_m \cdot v_i$$

$$= - g_m v_\pi R_L = - \frac{g_m R_L}{1 + g_m R_E}$$

$$= - \left( \frac{g_m}{1 + g_m R_E} \right) R_L$$

$$\Rightarrow G_m = \frac{38.5m}{1 + 38.5m \times 0.3K}$$

$$= 3.06mA/V$$

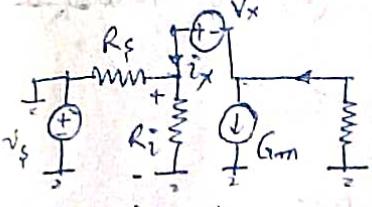


$$i_x (R_f \parallel R_i) - v_x + \left\{ i_x + \frac{G_m}{1 + g_m R_E} i_x (R_f \parallel R_i) \right\} R_L = 0$$

$$\Rightarrow v_x = i_x \left\{ R_f \parallel R_i + R_L + \frac{G_m}{1 + g_m R_E} R_L (R_f \parallel R_i) \right\}$$

$$\Rightarrow \frac{v_x}{i_x} = \left\{ 8.67K + 5K + \frac{3.06m}{38.5m \times 5K \times 8.67K} \right\}$$

$$= 146.92K$$

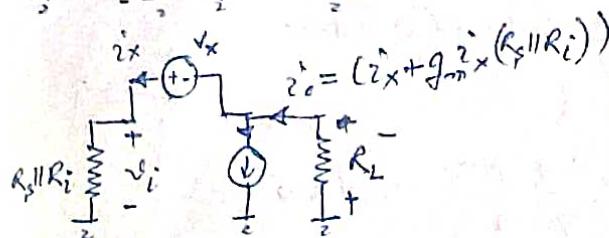

$$v_i = i_x (R_f \parallel R_i)$$

$$\Rightarrow R_A = 146.3 \text{ k}\Omega$$


$$C_A = 0.2 \mu\text{F}$$

$$\Rightarrow T_{\pi A} = R_A C_A = 29.3 \text{ ms}$$

$$\begin{aligned} \Rightarrow T_{\pi A} + T_{\pi} &= 6.61 \text{ ms} + 29.3 \text{ ms} \\ &\approx 36 \text{ ms} \end{aligned}$$

$$\Rightarrow f_{P_1} = \frac{1}{2\pi(T_{\pi A} + T_{\pi})} = 4.42 \text{ MHz}$$

Gain:

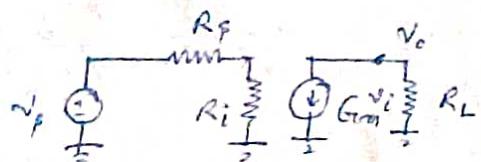

$$\begin{aligned} \Rightarrow \frac{v_o}{v_i} &= -G_m \times \frac{R_L}{R_i + R_F} \times R_L \\ &= -3.07 \text{ m} \times \frac{65.5}{75.5} \times 5 \text{ k} \\ &= -13.31 \end{aligned}$$

$$\left| \frac{v_o}{v_i} \right| = \frac{a}{5} = \frac{a}{1+af}$$

$$(a) = 70, 1+af = 7$$

-G<sub>m</sub>

$$\therefore a \approx -66 \quad \Rightarrow \quad T = 1+af = 4.96.$$

$$\Rightarrow \frac{f_{P_1, \text{no CE}}}{f_{P_1, \text{with CE}}} = \frac{4.42 \text{ MHz}}{949 \text{ kHz}} \approx 4.65$$




$$g_{m1} = \frac{10mA}{25mV} = 400 \text{ mS} \quad \beta_1, \beta_2 = 100$$

$$g_{m2} = \frac{0.1mA}{25mV} = 4 \text{ mS} \quad r_{\pi_1} = \frac{\beta_1 + 1}{g_{m1}} = \frac{100 + 1}{400} = 2.5K \quad r_{\pi_2} = \frac{\beta_2 + 1}{g_{m2}} = \frac{100 + 1}{4} = 25K$$

~~Frequency response of a Darlington pair~~

$$C_{\pi} = C_b + C_{je}$$

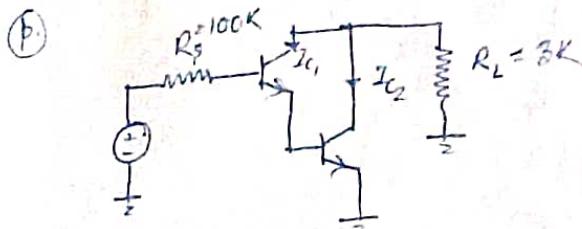

$$g_{m1} = \frac{10mA}{26mV} = 384 \mu A/V$$

$$\Rightarrow r_{\pi_1} = \frac{100}{g_{m1}} = 260K\Omega$$


$$g_{m2} = \frac{1}{26} = 38.4 \mu A/V$$

$$r_{\pi_2} = \frac{100}{g_{m2}} = 2.6K\Omega$$

$$f_T > \frac{g_m}{2\pi(C_n + C_{\pi})} = 500M \quad \text{with} \quad I_{C_1} = 10mA,$$

$$\Rightarrow \frac{1/26}{2\pi \times 500M} = C_n + C_{\pi} \Rightarrow C_n + C_{\pi}$$
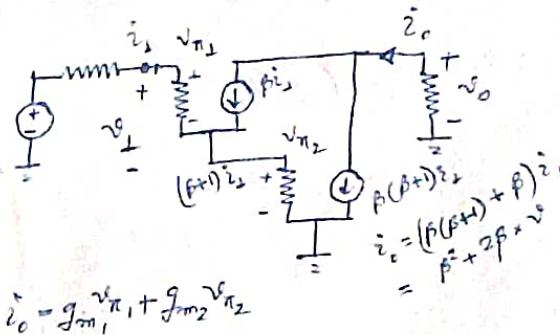
$$\Rightarrow C_{\pi} = 12.24p - 0.4p = \frac{3.84 \mu}{2\pi \times 500M} \Rightarrow C_{\pi} = 11.84 \mu F \Rightarrow C_n =$$



$$v_o = -i_o R_L \quad g_{m1} \neq g_{m2}$$

$$\dot{i}_o = g_{m1} v_{\pi_1} + g_{m2} v_{\pi_2}$$

$$v_{\pi_2} = \left( \frac{v_{\pi_1}}{r_{\pi_1}} + g_m v_{\pi_1} \right) r_{\pi_2}$$

$$= v_{\pi_1} \left( \frac{1}{r_{\pi_1}} + g_m \right) r_{\pi_2}$$

$$\Rightarrow \dot{i}_o = g_{m1} v_{\pi_1} + v_{\pi_1} \left( \frac{1}{r_{\pi_1}} + g_m \right) r_{\pi_2}$$

$$+ v_{\pi_1} \left\{ g_{m1} + g_{m2} \frac{(\beta+1) \times r_{\pi_2}}{r_{\pi_1}} \right\}$$

$$v_{\pi_1} + v_{\pi_2} = v_i$$

$$= \frac{\beta_0 + \beta_0 (\beta+1)}{r_{\pi_1} + (\beta+1) r_{\pi_2}}$$

$$+ v_{\pi_2} = \left( \frac{v_{\pi_1}}{r_{\pi_1}} + g_m v_{\pi_1} \right) r_{\pi_2}$$

$$= v_{\pi_1} \times \left( \beta+1 \right) \frac{r_{\pi_2}}{r_{\pi_1}}$$

$$+ v_{\pi_1} + v_{\pi_1} (\beta+1) \frac{r_{\pi_2}}{r_{\pi_1}} = v_i$$

$$\Rightarrow v_{\pi_1} \left( \frac{r_{\pi_1} + (\beta+1) r_{\pi_2}}{r_{\pi_1}} \right) = v_i$$

$$v_{\pi_1} = \frac{r_{\pi_1}}{r_{\pi_1} + (\beta+1) r_{\pi_2}} \cdot v_i$$

$$R_i = r_{\pi_1} + (\beta+1) r_{\pi_2}$$

$$= 260K + 101 \times 2.6K$$

$$= 523K\Omega$$

$$\Rightarrow \frac{v_o}{v_i} = - G_m \cdot R_L \times \frac{R_i}{R_i + R_S} = - 19.5m \times 3 \times \frac{523}{623} = - 49 V/V$$