

# Tutorial 12

EC103


(Multivibrators)

# Question 1 (GATE ECE 2016)

- Go the next page...
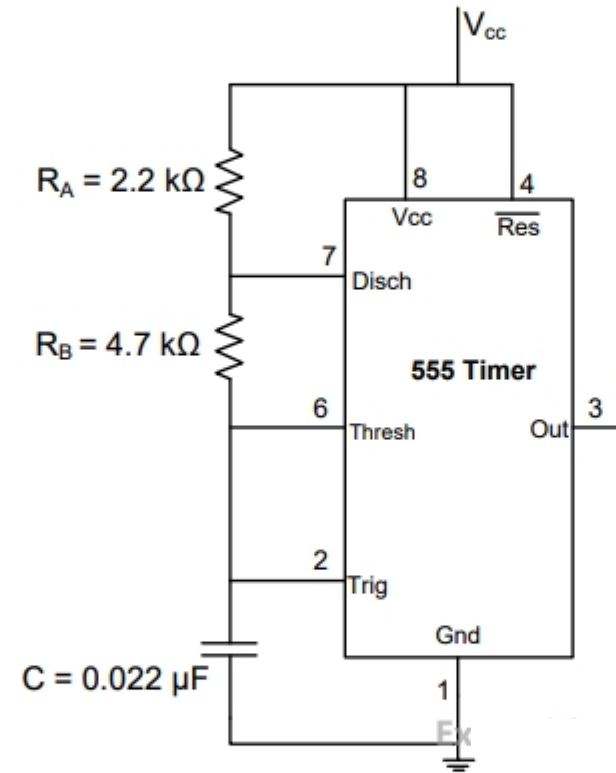
### GATE ECE 2016 Set 3

In the astable multivibrator circuit shown in the figure, the frequency of oscillation (in kHz) at the output pin 3 is



- Ans: **5.65**

# Question 2

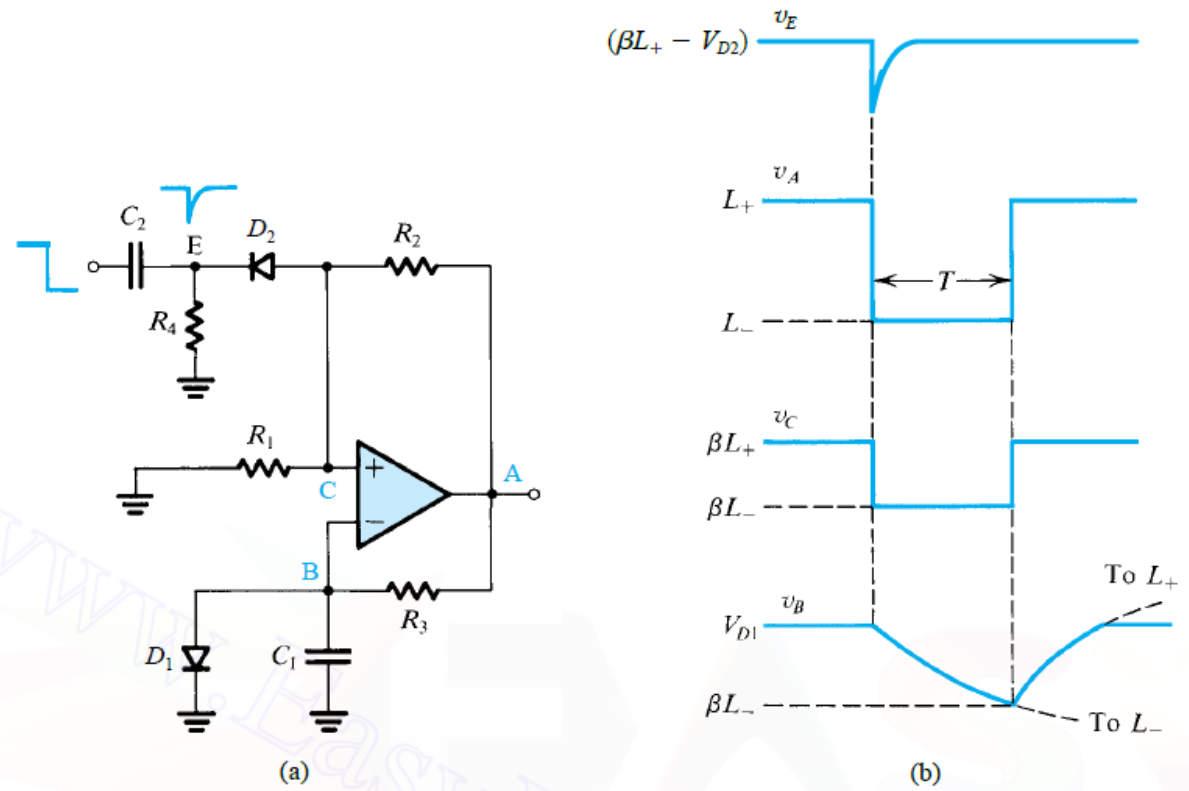


Figure 17.26 (a) An op-amp monostable circuit. (b) Signal waveforms in the circuit of (a).

## EXERCISES

**17.19** For the monostable circuit of Fig. 17.26(a), find the value of  $R_3$  that will result in a 100- $\mu$ s output pulse for  $C_1 = 0.1 \mu\text{F}$ ,  $\beta = 0.1$ ,  $V_D = 0.7 \text{ V}$ , and  $L_+ = -L_- = 12 \text{ V}$ .

## Question 2.

# Question 3

- Three NOT gates connected in cascade and out put of the last is fed back the input of the first making a closed loop.
- Can this whole circuit work as a multivibrator?
- If `No`, state the reason.
- If `Yes`, state the reason.





## Question 4 (GATE ECE 2001)

- Consider the following two statements.
  - **Statement 1:** Astable Multivibrator can be used for generating Square Wave.
  - **Statement 2:** Bistable Multivibrator can be used for storing binary information.
- 
- Options:
    - A: Statement 1 is correct
    - B: Statement 2 is correct
    - C: Both the statements are correct
    - D: None of the statements is correct.

# Answer


- c

## Question 5 (GATE ECE 1998)

- Go to the next page ...
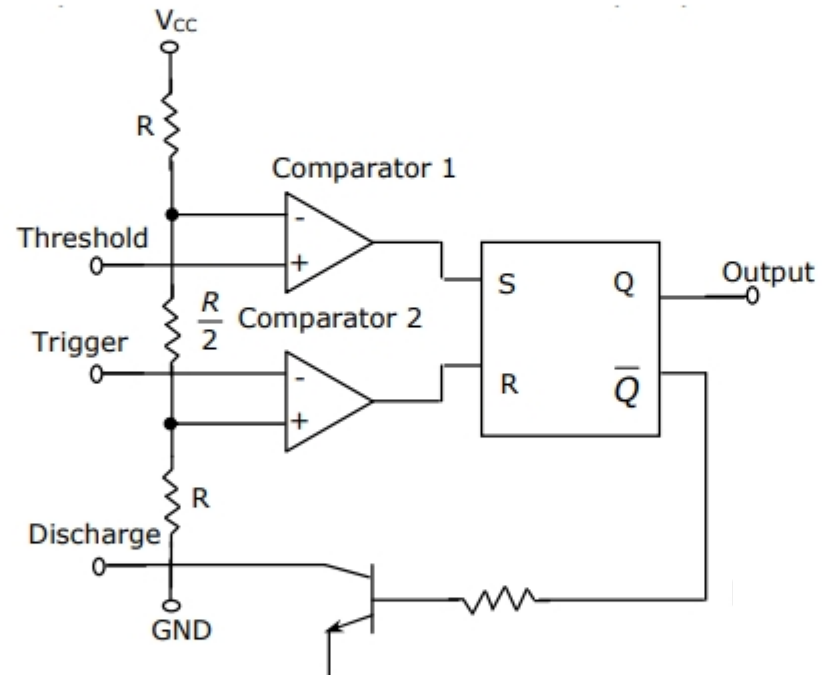
### GATE ECE 1998

Implement a monostable multivibrator using the timer circuit shown, in Fig. Also determine an expression for ON time  $T$  of the o/p pulse.





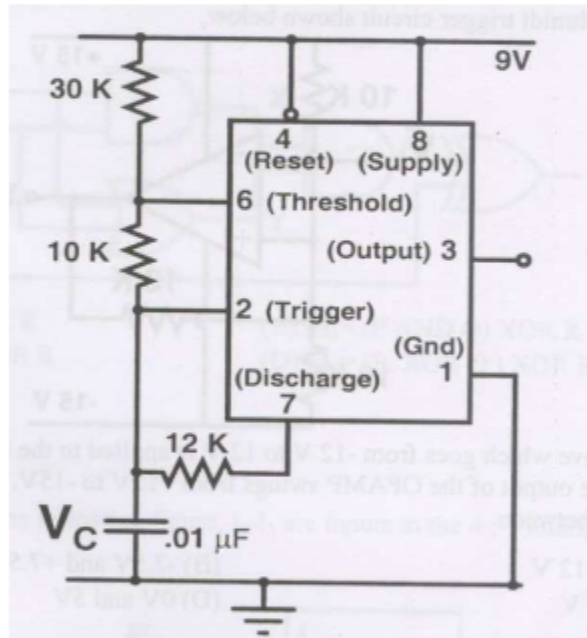
## Question 6 (GATE 2008)

- Go to the next page...

An astable multivibrator circuit using IC 555 timer is shown below. Assume that the circuit is oscillating steadily



The voltage  $V_C$  across the capacitor varies between


- (A) 3V to 5V    (B) 3V to 6V    (C) 3.6V to 6V    (D) 3.6V to 5V




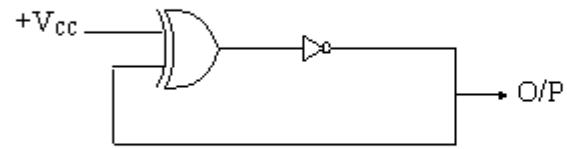
# Question 7

The figure given below shows the circuit of which one of the following is



- (A) Bi-stable multi-vibrator
- (B) Astable multi-vibrator
- (C) Mono stable multi-vibrator
- (D) None of these