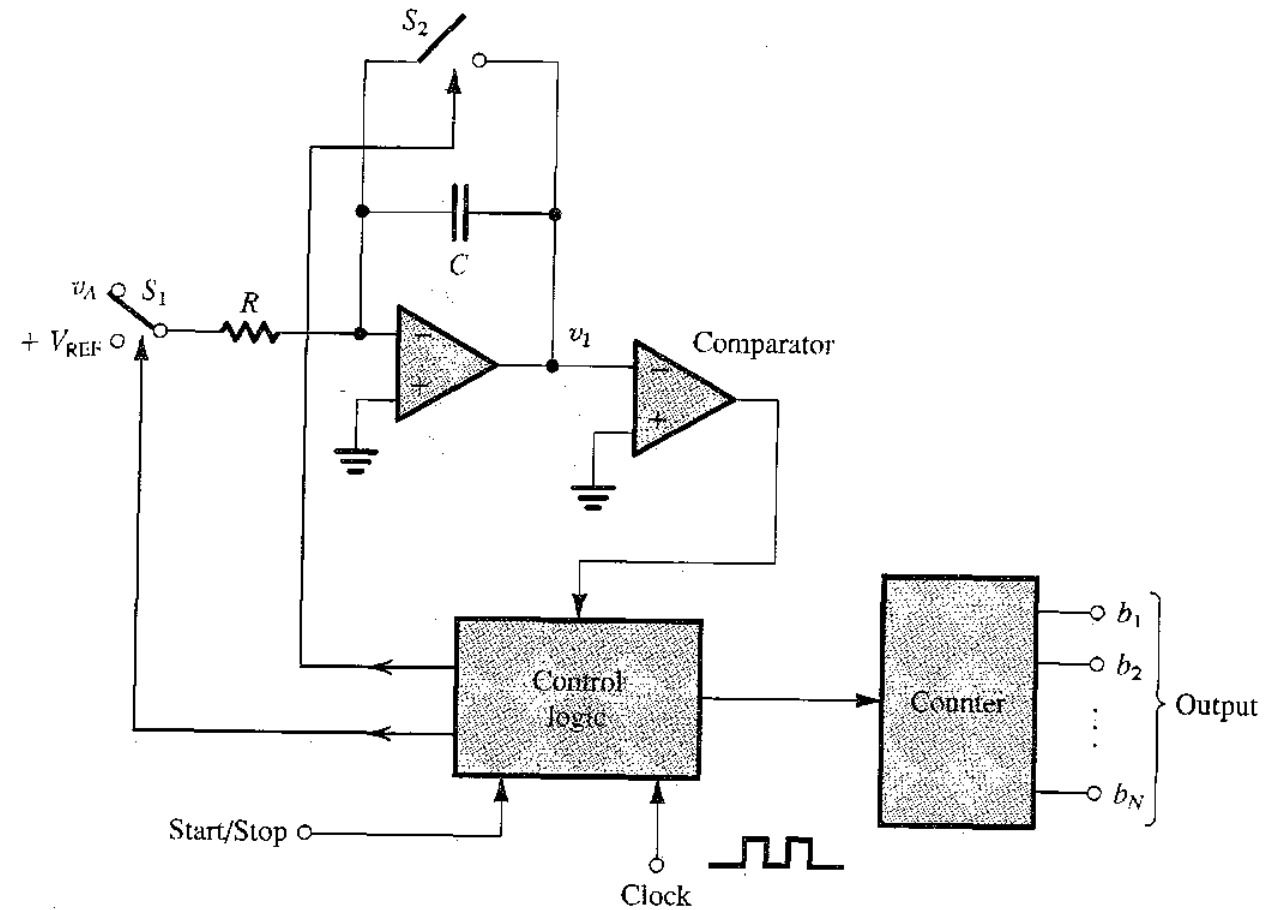


Lecture 28

EC103

Dual Slope ADC


- A very popular high resolution (12- to 14-bit) (but slow) ADC scheme is being shown.
- Below we describe its working principle:
 1. Assume that the input signal v_A is negative.
 2. Prior to start of the conversion cycle, the switch S_2 is closed, thus discharging the capacitor, and setting v_1 is zero.
 3. The conversion cycle begins with opening S_2 , and connecting the integrator input through the switch S_1 to the analog input.
 4. Since v_A is negative, a current will flow through R in the direction away from the Integrator.



Dual Slope ADC


Below we describe its working principle:

 1. Assume that the input signal v_A is negative.
2. Prior to start of the conversion cycle, the switch S_2 is closed, thus discharging the capacitor, and setting v_1 is zero.
3. The conversion cycle begins with opening S_2 , and connecting the integrator input through the switch S_1 to the analog input.
4. Since v_A is negative, a current $I = \frac{v_A}{R}$ will flow through R in the direction away from the Integrator.
5. Thus v_1 rises linearly with a slope $= \frac{I}{C} = \frac{v_A}{RC}$ as shown in the adjacent figure.



Dual Slope ADC

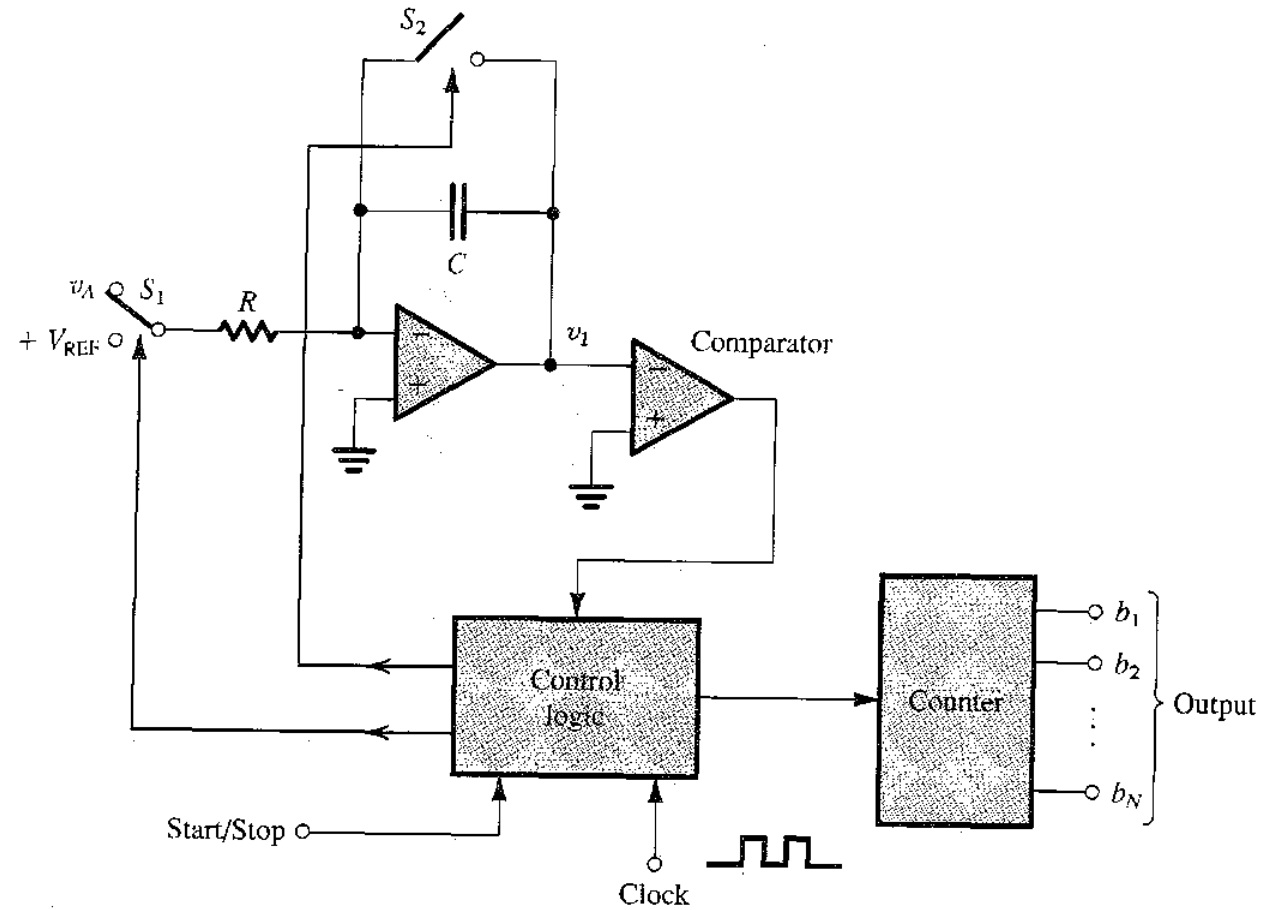6. Simultaneously, the counter is enabled, and it counts the pulses from a fixed-frequency clock.
7. This phase of conversion process continues for a fixed duration T_1 . It ends when the counter has accumulated a fixed count denoted N_{ref} . Usually, for a N -bit converter $N_{ref} = 2^N$.



Dual Slope ADC

6. Simultaneously, the counter is enabled, and it counts the pulses from a fixed-frequency clock.


7. This phase of conversion process continues for a fixed duration T_1 . It ends when the counter has accumulated a fixed count denoted N_{ref} .

Usually, for a N -bit converter $N_{ref} = 2^N$.

8. Denoting the peak voltage at the output of the integrator as V_{peak} , we can write by the reference to the adjacent figure:


$$\frac{V_{peak}}{T_1} = \frac{V_A}{RC} \quad \dots (i).$$

 9. At the end of this phase, the counter is reset to zero.




Dual Slope ADC

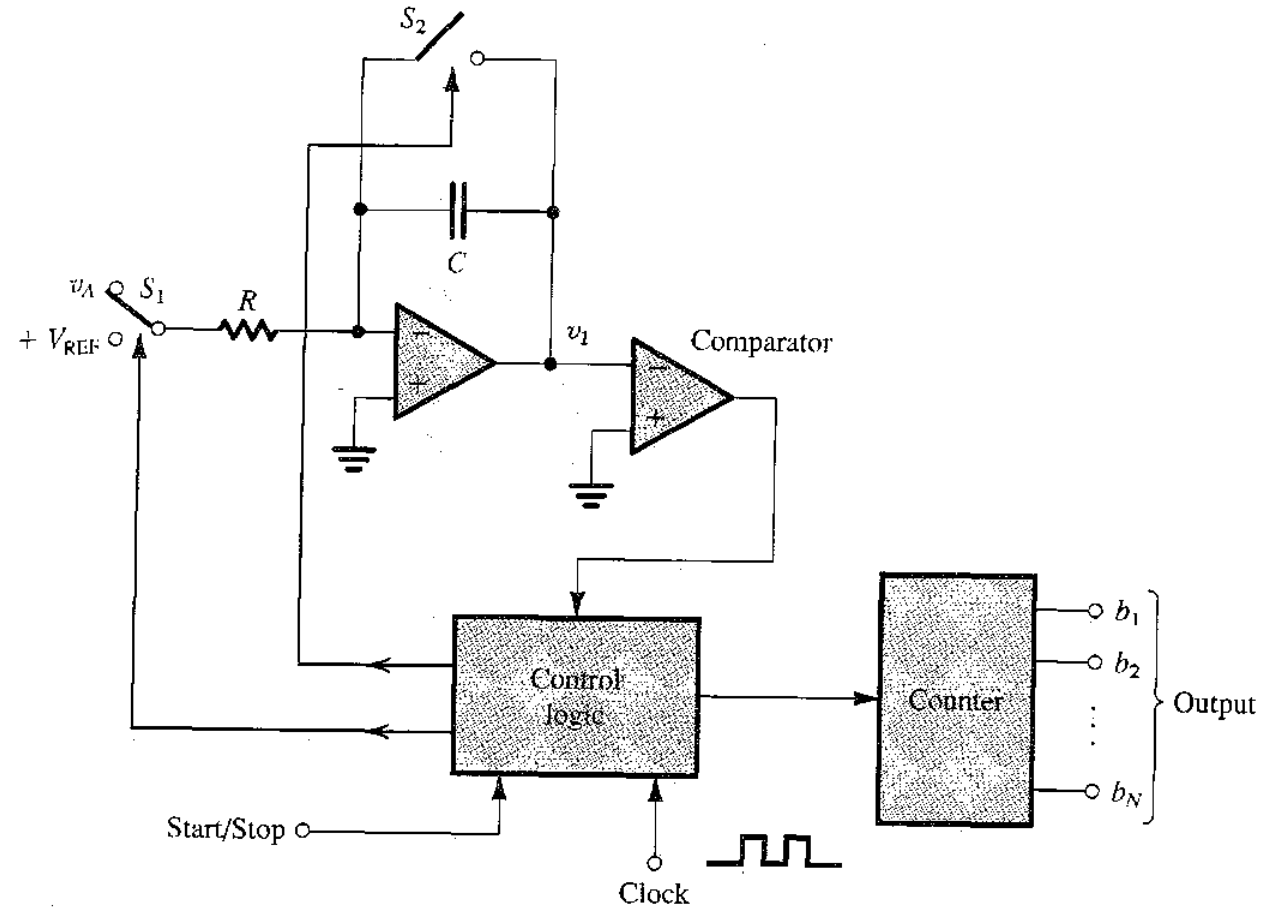10. Phase II of the conversion begins at $t = T_1$ by connecting the integrator input through the switch S_1 to the positive reference voltage V_{ref} .
11. The current into the integrator reverses direction and is equal to $\frac{V_{ref}}{R}$.



Dual Slope ADC

 10. Phase II of the conversion begins at $t = T_1$ by connecting the integrator input through the switch S_1 to the positive reference voltage V_{ref} .
11. The current into the integrator reverses direction and is equal to $\frac{V_{ref}}{R}$.
12. Thus v_1 decreases linearly with a slope of V_{ref}/RC .
13. Simultaneously, the counter is enabled, and it counts the pulses from the fixed-frequency clock.



Dual Slope ADC


14. When v_1 reaches zero volts, the comparator signals the control logic to stop the counter.

15. Denoting the duration of the phase II by T_2 , we can write by the reference to the adjacent figure:

$$\frac{V_{peak}}{T_2} = \frac{V_{ref}}{RC} \quad \dots (ii).$$

 16. Combining equations (i) and (ii), we get

$$T_2 = T_1 \left(\frac{v_A}{V_{ref}} \right) \quad \dots (iii).$$



Dual Slope ADC


17. We can also conclude from the equation (iii):

$$n = n_{ref} \left(\frac{v_A}{V_{ref}} \right) \quad \dots (iv),$$

where $\frac{n}{n_{ref}} = \frac{T_2}{T_1}$

as n_{ref} is the counter reading after T_1 interval,
And n is the counter reading after T_2 interval.

18. Thus the counter reading n gives digital equivalent to v_A .

 

Lecture 29


EC103

Example on Dual Slope ADC

- Consider a 8-bit dual-slope ADC with a 2 MHz clock and has $V_{ref} = -4\text{ V}$. The fixed interval T_1 is the time taken for the counter to accumulate a count of 2^N . What is the time required to convert an input voltage equal to 2 V.?
- Ans. 0.192 ms.


Single Slope ADC

- It uses a linear ramp generator to produce a constant-slope reference voltage.
- At the beginning of a conversion cycle, the counter is in the reset state, and the ramp generator output is 0 V.
- The analog input is greater than the reference voltage at this point. Hence, produces a high-level output from the comparator.
- This high level enables the clock to the counter, and starts the ramp generator.

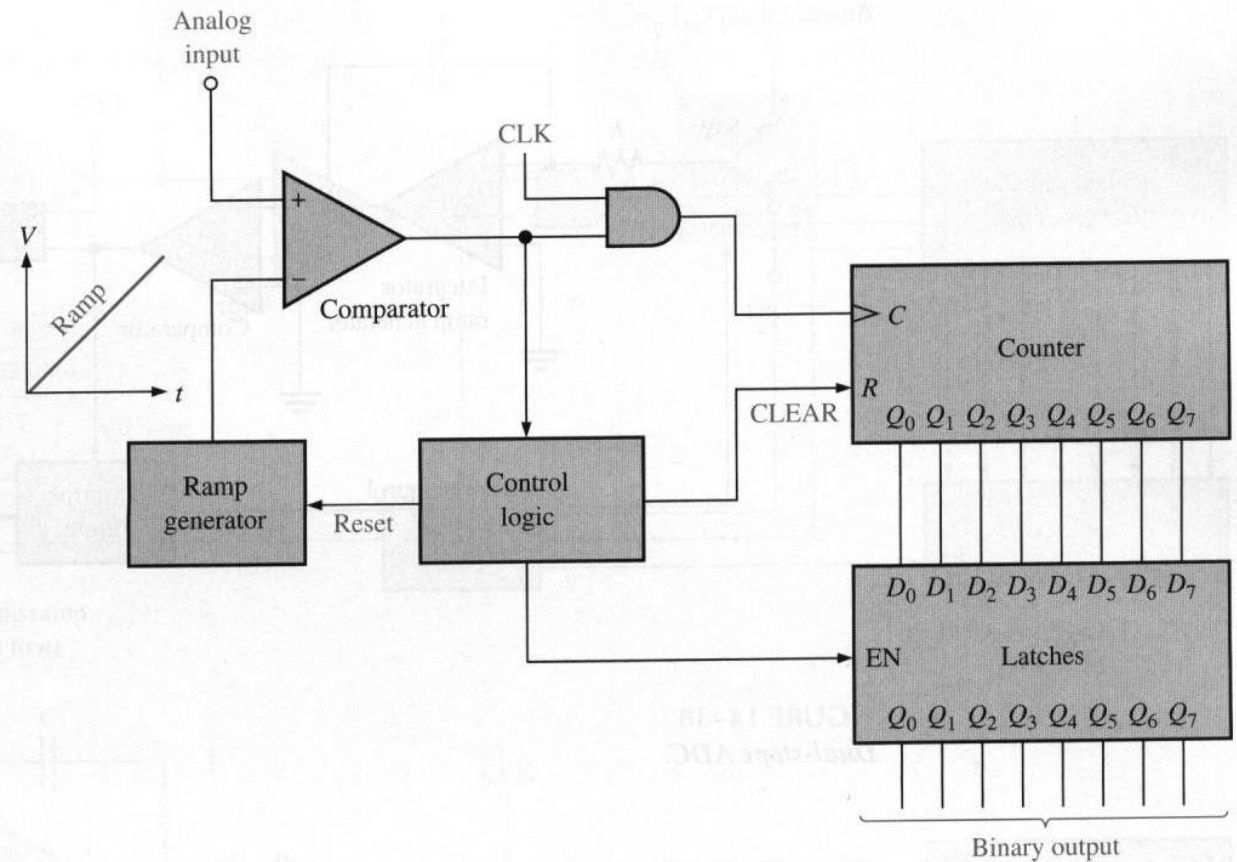

Single Slope ADC

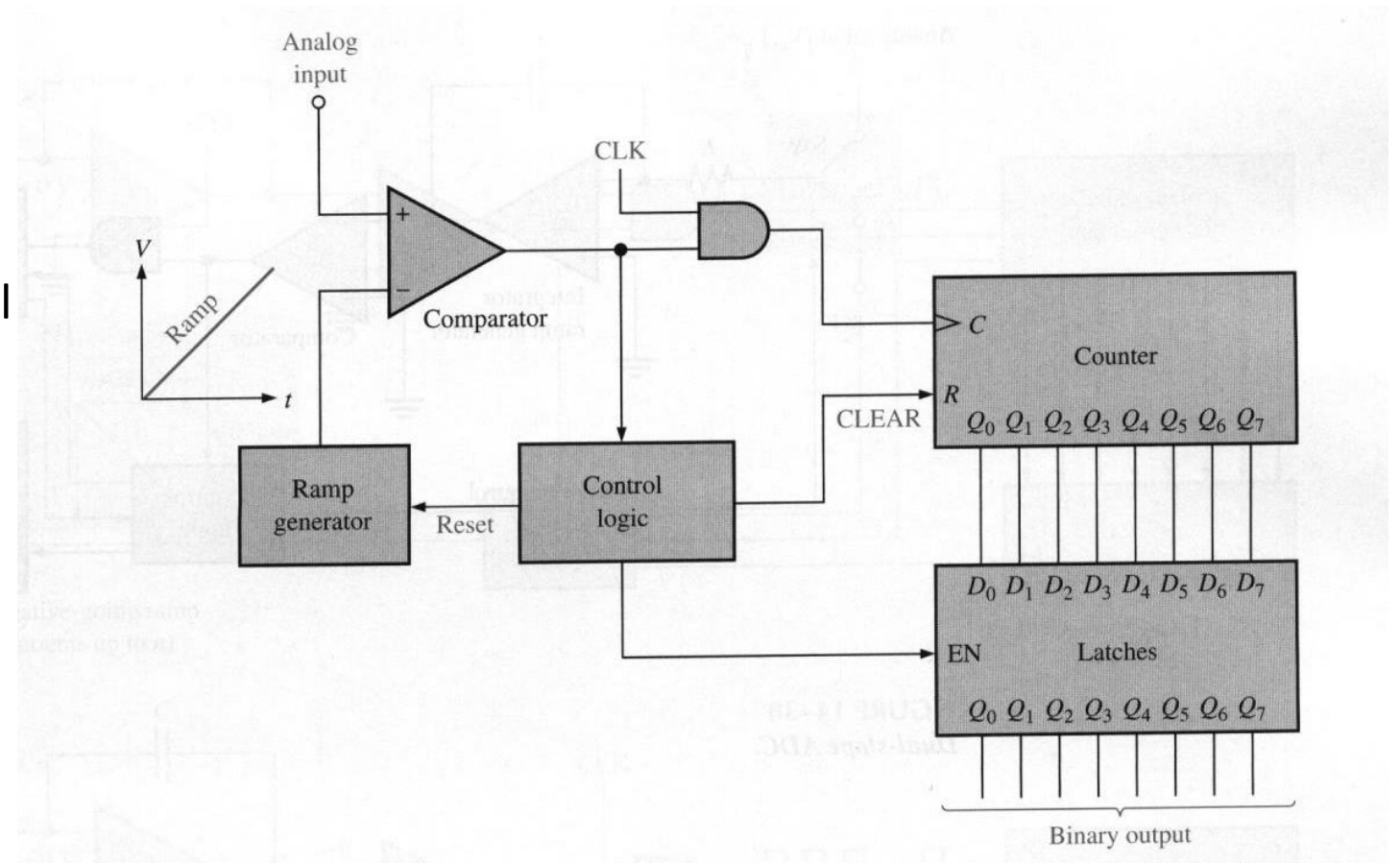- When the increasing ramp generator output attains a level equal to the analog input, the comparator produces a low-level output.
- At this point, the ramp is reset, and the binary count is stored in the latches by the control logic.
- This binary count is a digital Equivalent to the analog input.



Example on Single Slope ADC

- $R = 10\text{ k}\Omega$, $C = 0.1\text{ }\mu\text{F}$, $V_{ref} = 1\text{ V}$, *analog input* $= 2\text{ V}$, *clock frequency* $= 100\text{ kHz}$.
- What is the binary count after the conversion?
- Ans. **200**

