

Power Divider and Coupler

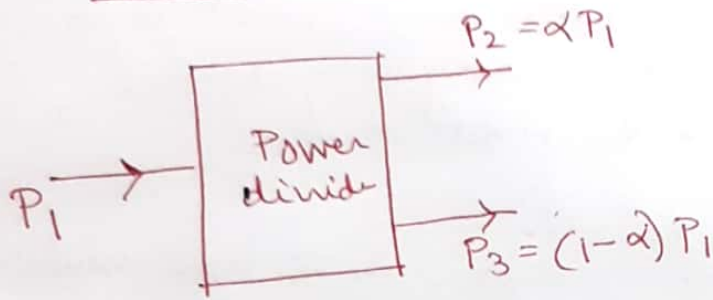


Fig: Power Division

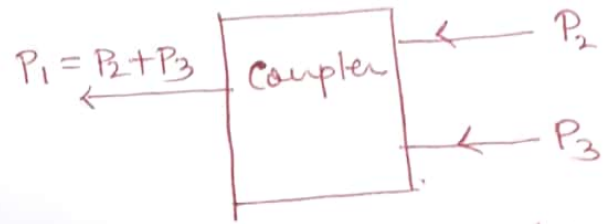


Fig: Power Combining

A three port network cannot be lossless, reciprocal and matched at all ports:
or

It is not possible to construct a perfectly matched, lossless, reciprocal 3-port junction. At least one of the reflection coefficients must be different from zero in the reciprocal case.

If all ports are matched, then $S_{ii} = 0$ & if the network is reciprocal then the S-matrix becomes,

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix} \quad \text{--- (2)}$$

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix} \quad \text{--- (1)}$$

If the network is also lossless then energy conservation requires that S-matrix be unitary,

$$|S_{12}|^2 + |S_{13}|^2 = 1 \quad \text{--- 3a}$$

$$|S_{12}|^2 + |S_{23}|^2 = 1 \quad \text{--- 3b}$$

$$|S_{13}|^2 + |S_{23}|^2 = 1 \quad \text{--- 3c}$$

$$S_{13}^* S_{23} = 0 \quad \text{--- 3d}$$

$$S_{23}^* S_{12} = 0 \quad \text{--- 3e}$$

$$S_{12}^* S_{13} = 0 \quad \text{--- 3f}$$

If any one of these three conditions is relaxed, then a physically realizable device is possible.

Eqn. 3(d-f) show that at least two of the three parameters (S_{12}, S_{13}, S_{23}) must be zero,

but this condition is always inconsistent with one of eqs (3a-c), implying that a 3 port network cannot be lossless, reciprocal, matched at all ports.

check whether it is possible to design a lossless and reciprocal T-junction with two of its ports being matched, while the third is not matched.

As For this assume that ports 1 & 2 are matched.
 \therefore S-matrix can be represented as follows:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix}$$

Since network is lossless; we can write the following equations;

$$a_{12} \quad S_{13} S_{23}^* = 0 \quad \text{_____ a}$$

$$a_{23} \quad S_{12}^* S_{13} + S_{23}^* S_{33} = 0 \quad \text{_____ b}$$

$$e_{3c_1} \quad S_{23}^* S_{12} + S_{33}^* S_{13} = 0 \quad \text{_____ c}$$

$$|S_{12}|^2 + |S_{13}|^2 = 1 \quad \text{_____ d } \checkmark$$

$$|S_{12}|^2 + |S_{23}|^2 = 1 \quad \text{_____ e } \checkmark$$

$$|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 = 1 \quad \text{_____ f } \checkmark$$

Eqs (d) & (e) reveal that

$$|S_{13}| = |S_{23}| \quad \text{_____ g}$$

by applying (a) in (g) proves ~~does~~ ~~real~~

$$S_{13} = S_{23} = 0 \quad \text{_____ h}$$

Again substituting h in eqs d, e, f given

$$|S_{12}| = |S_{33}| = 1 \quad \text{_____ i}$$

eqⁿ (g) - (i) ensure the network will have scattering matrix,

$$[S] = \begin{bmatrix} 0 & e^{j\theta} & 0 \\ e^{j\theta} & 0 & 0 \\ 0 & 0 & e^{-j\theta} \end{bmatrix}$$

∴ it is possible to design a 3-port reciprocal & lossless network with any of its two ports matched,

check whether it is possible to design a 3-port network with all its ports matched, provided the network is lossless but not reciprocal.

For such case 'S' matrix is represented as follow:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix}$$

network is still lossless,

1C ₂	∴ $S_{31}^* S_{32} = 0$	_____ a
2C ₃	$S_{12}^* S_{13} = 0$	_____ b
3C ₁	$S_{23}^* S_{12} = 0$	_____ c
	$ S_{12} ^2 + S_{13} ^2 = 1$	_____ d
	$ S_{21} ^2 + S_{23} ^2 = 1$	_____ e
	$ S_{31} ^2 + S_{32} ^2 = 1$	_____ f

Eq^{ns} (a) - (f) can be satisfied simultaneously if any one of the following two condition is satisfied:


$$S_{12} = S_{23} = S_{31} = 0 ; \quad |S_{21}| = |S_{32}| = |S_{13}| = 1$$

$$S_{21} = S_{32} = S_{13} = 0 ; \quad |S_{12}| = |S_{23}| = |S_{31}| = 1$$

$$\therefore [S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

So, it can be proved that a three port network with all its ports matched can be designed if the network is lossy.

S-matrix of 3-port H-plane Tee

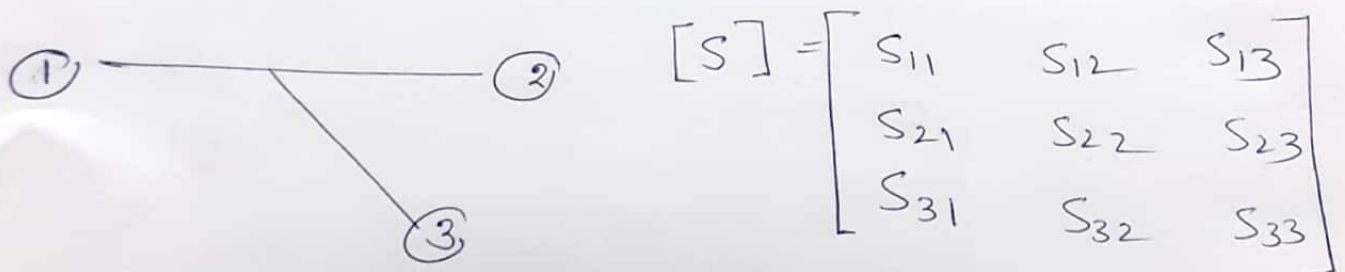

- junction scattering coefficient S_{13} and S_{23} must be ~~equal~~ to the plane of symmetry ;
 $\therefore S_{13} = S_{23}$
- From symmetric property $S_{ij} = S_{ji}$
 $\therefore S_{12} = S_{21}, S_{31} = S_{13}, S_{23} = S_{32}$
 $\quad \quad \quad = S_{13}$
- considering port 3 is perfectly matched
 reflection coefficient $S_{33} = 0$

$\therefore [S]$ matrix can be written as

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & S_{22} & S_{13} \\ S_{13} & S_{13} & 0 \end{bmatrix}$$

Now we have four unknowns,

\therefore by using unitary property,

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = 1 \quad \text{--- a}$$

$$|S_{12}|^2 + |S_{22}|^2 + |S_{13}|^2 = 1 \quad \text{--- b}$$

$$|S_{13}|^2 + |S_{13}|^2 = 1 \quad \text{--- c}$$

zero property

$$\hat{R}_1 \hat{R}_3 \quad S_{13} S_{11}^* + S_{13} S_{12}^* = 0 \quad \text{--- d}$$

from (c) $|S_{13}| = \frac{1}{\sqrt{2}}$

Comparing eqns (a) & (b);

$$S_{11} = S_{22}$$

from (d);

$$S_{13} (S_{11}^* + S_{12}^*) = 0$$

but $S_{13} \neq 0$, $\therefore S_{11}^* = -S_{12}^*$

$$\text{or } S_{11} = -S_{12}$$

$$\text{or } S_{12} = -S_{11}$$

using eqn (a)

$$|S_{11}|^2 + |S_{11}|^2 + \left(\frac{1}{\sqrt{2}}\right)^2 = 1$$

$$\Rightarrow S_{11} = \frac{1}{2}$$

$$\therefore S_{12} = -\frac{1}{2}$$

$$\& S_{22} = \frac{1}{2}$$

∴ S matrix x for H-plane tee;

$$[S] = \begin{bmatrix} \frac{1}{2} & -\frac{1}{2} & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & \frac{1}{2} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & 0 \end{bmatrix}$$

Again $[b] = [S][a]$

$$\therefore \begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & -\frac{1}{2} & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & \frac{1}{2} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix}$$

$$b_1 = \frac{a_1}{2} - \frac{a_2}{2} + \frac{a_3}{\sqrt{2}}$$

$$b_2 = -\frac{a_1}{2} + \frac{a_2}{2} + \frac{a_3}{\sqrt{2}}$$

$$b_3 = \frac{a_1}{\sqrt{2}} + \frac{a_2}{\sqrt{2}}$$

as port 3 is input, i.e. $a_3 \neq 0$,
 $a_1 = 0$, $a_2 = 0$

∴ eqns becom

$$b_1 = \frac{a_3}{\sqrt{2}}; \quad b_2 = \frac{a_3}{\sqrt{2}}, \quad b_3 = 0$$

$$\begin{aligned} \therefore \text{Power gain} &= 10 \log_{10} \left(\frac{P_1}{P_3} \right) \\ &= 10 \log_{10} \frac{P_1}{2 P_1} \\ &= -3 \text{ dB} \end{aligned}$$

∴ power coming out from port 1 and 2 is 3 dB less than input power at port 3.

For E-plane, Tee.

$$[S] = \begin{bmatrix} \frac{1}{2} & \frac{1}{2} & \frac{1}{\sqrt{2}} \\ \frac{1}{2} & \frac{1}{2} & -\frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & -\frac{1}{\sqrt{2}} & 0 \end{bmatrix}$$