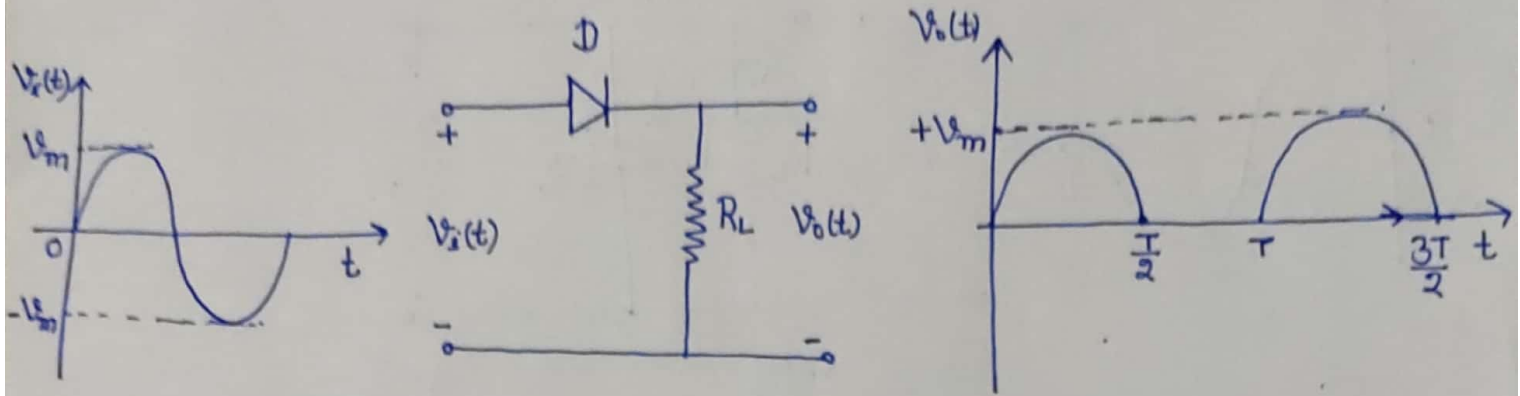


Rectifiers with Capacitive Filters




$V_i(t)$: Input Signal


Diode is ideal

$V_o(t)$: O/P Signal
(Pulsating DC Signal)




HWR With Capacitive filter

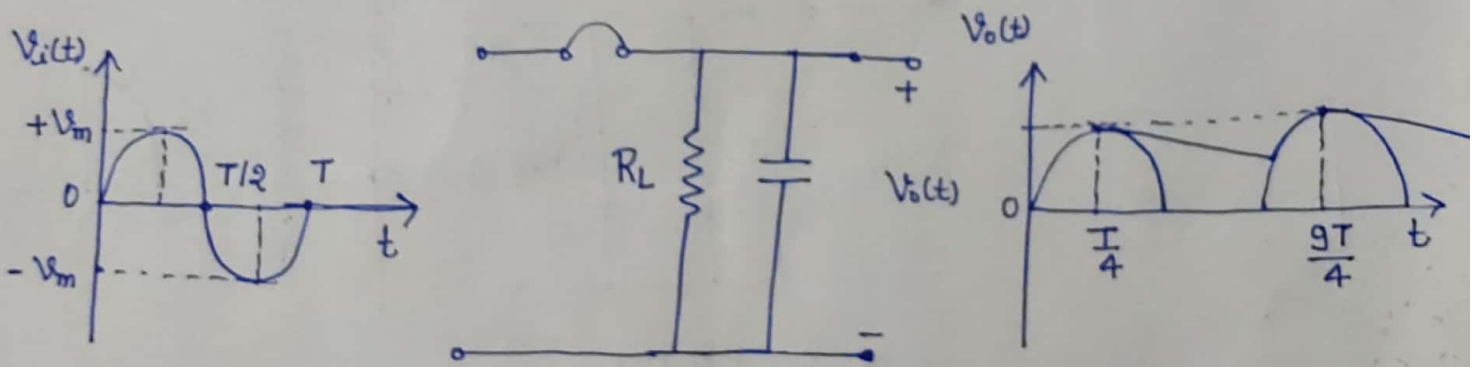




For $0 < t \leq \frac{T}{4}$

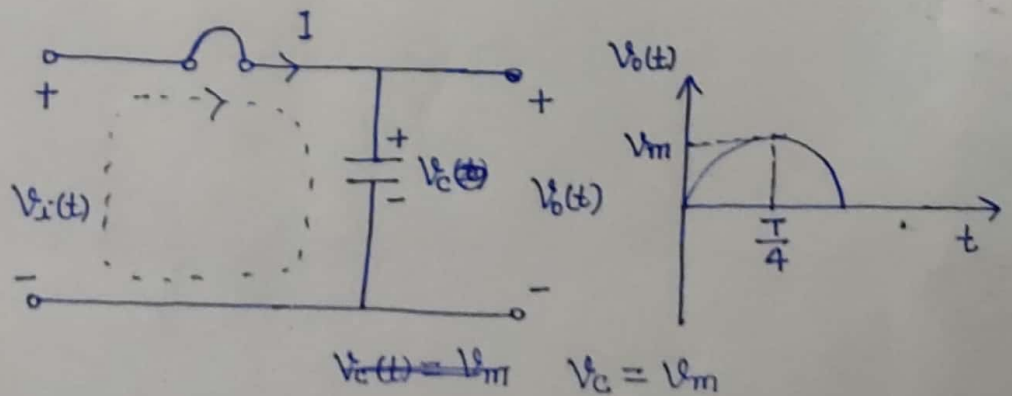

For $\frac{T}{4} \leq t \leq t'$

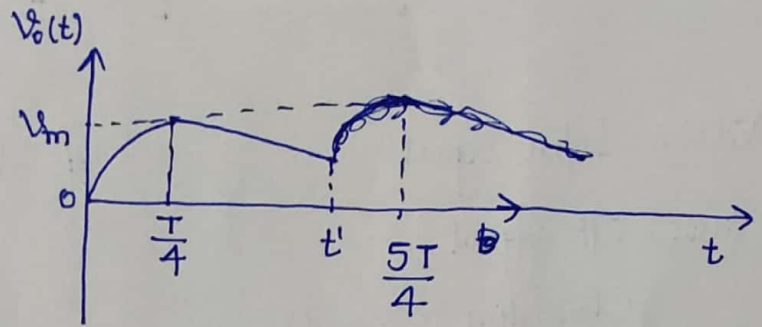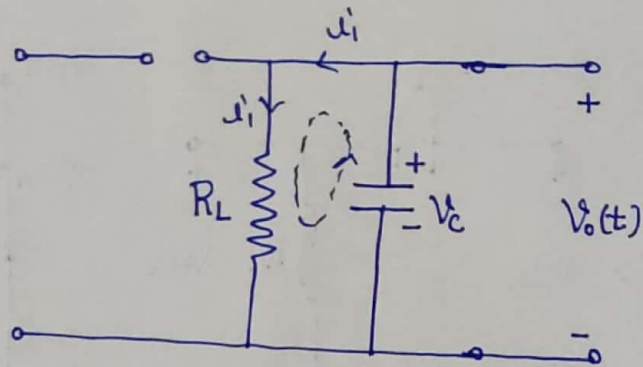
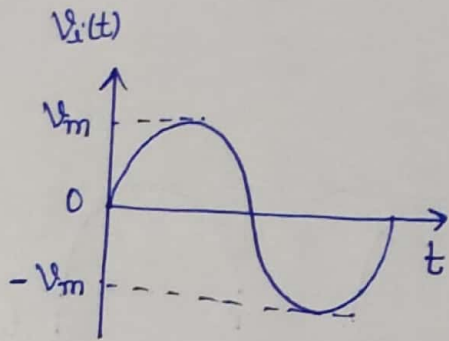


For $t' < t < \frac{5T}{4}$

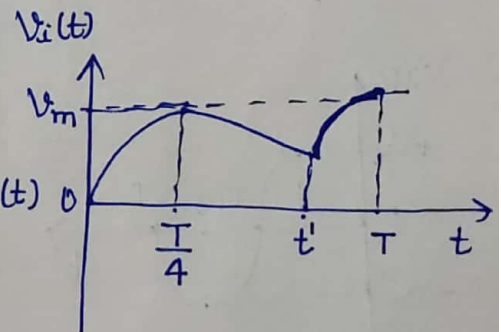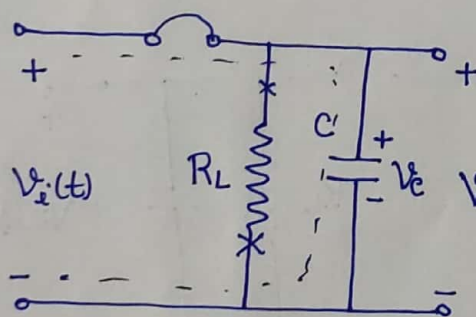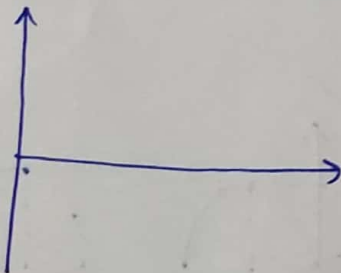


R_L Not effective
(By pass)

Output of HWR with Capacitive filter

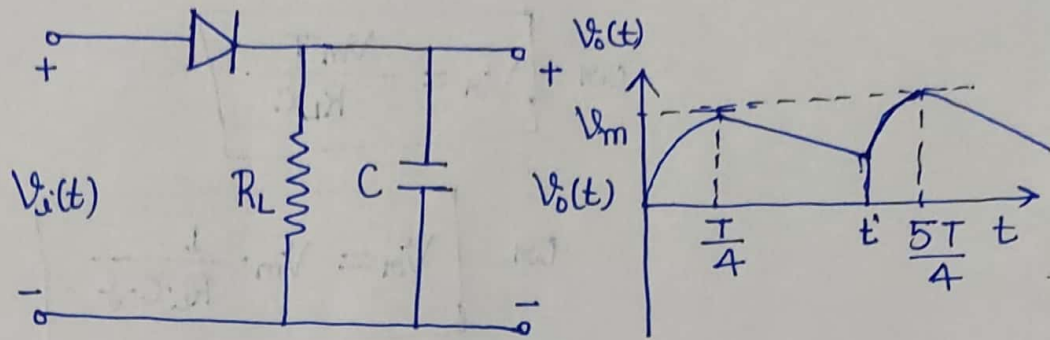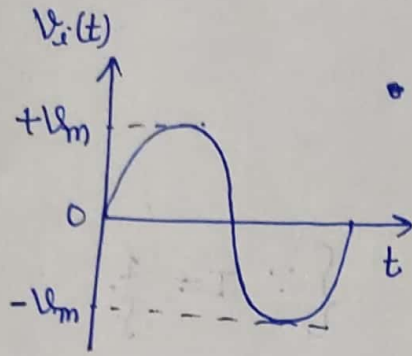

$V_i(t)$: Input AC Signal

$V_o(t)$: Pulsating DC Signal

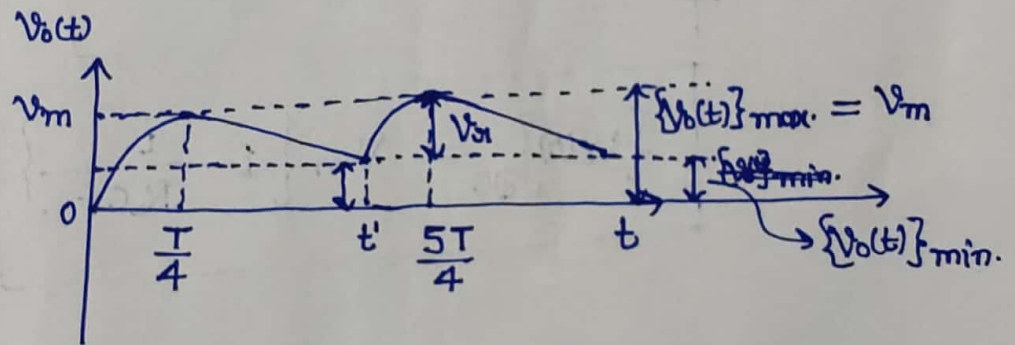

$$\{V_o(t)\}_{DC} = \frac{\{V_o(t)\}_{max} + \{V_o(t)\}_{min}}{2}$$

$$= \frac{V_m + (V_m - V_{s1})}{2}$$

$$= \frac{2V_m - V_{s1}}{2} = V_m - \frac{V_{s1}}{2}$$


Here, V_{s1} = ripple voltage

$$V_m - V_{s1} = V_m e^{-t'/R_L C}$$

$\therefore R_L C \gg T$, Therefore

$$t' \approx T$$
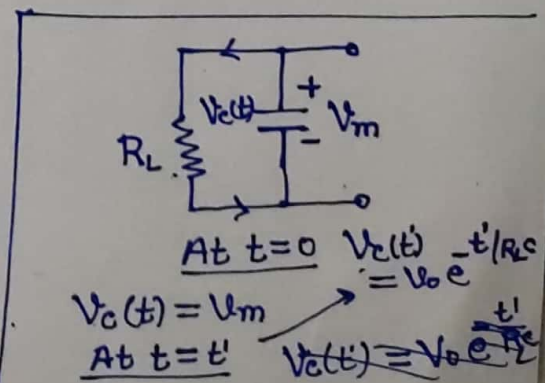
$$V_m - V_{s1} = V_m \cdot e^{-\frac{T}{R_L C}}$$



$$V_m - V_{o1} = V_m \cdot \left\{ 1 - \frac{T}{R_L C} \right\}$$

$$\left\{ \begin{array}{l} e^{-x} \approx 1-x \\ \text{if } x \ll 1 \end{array} \right.$$

$$V_m - V_{o1} = V_m - \frac{V_m T}{R_L C}$$

$$\text{or } V_{o1} = \frac{V_m T}{R_L C}$$

$$\text{or } V_{o1} = V_m \cdot \frac{1}{R_L \cdot C \cdot f}$$




$$\left\{ \because T = \frac{1}{f} \right.$$

For Small V_{o1}

- R_L should be large
- C " " "
- f " " "

$$\{V_o(t)\}_{DC} = V_m \left\{ 1 - \frac{1}{R_L C f} \right\}$$

Bridge Rectifier

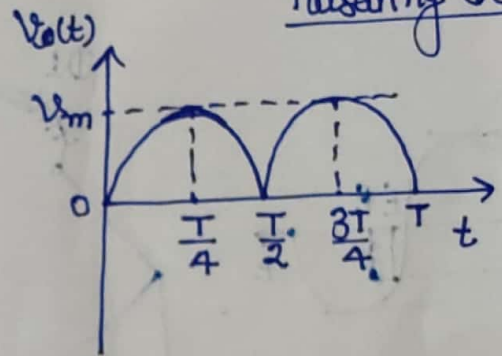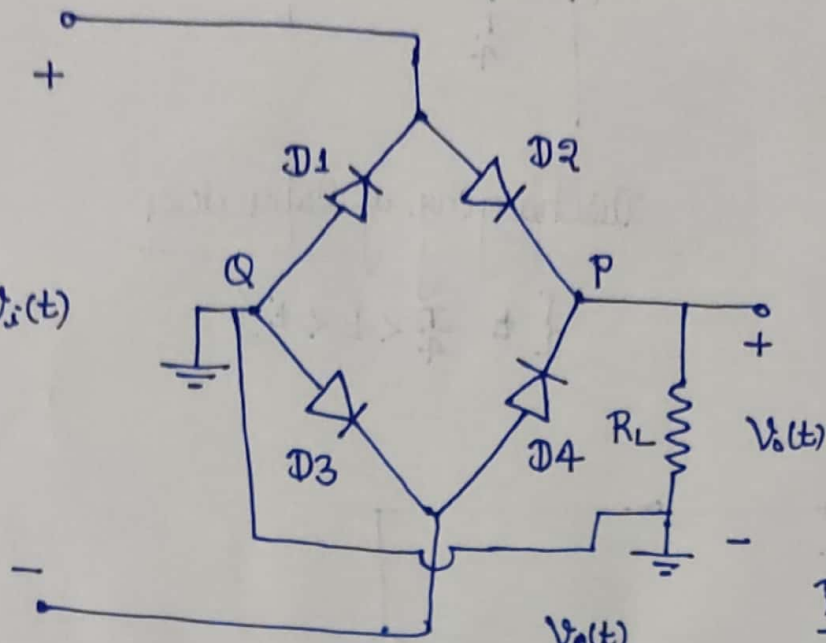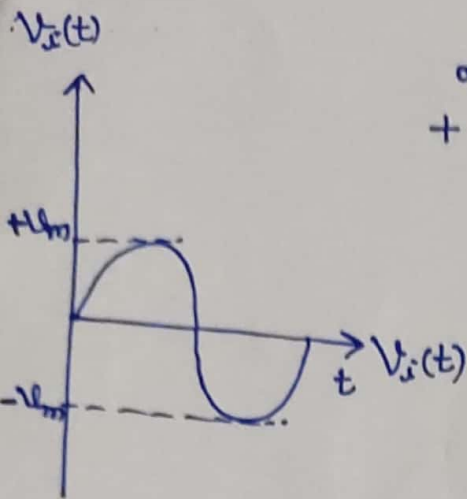


Pulsating DC

All diodes are ideal


FWR with Capacitive Filter


For $0 < t \leq \frac{T}{4}$

(Charging of Capacitor)

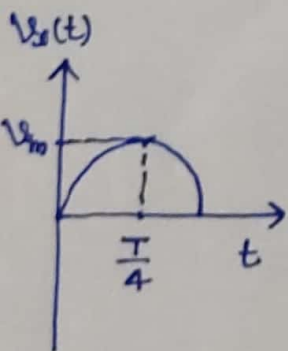


$V_i(t)$

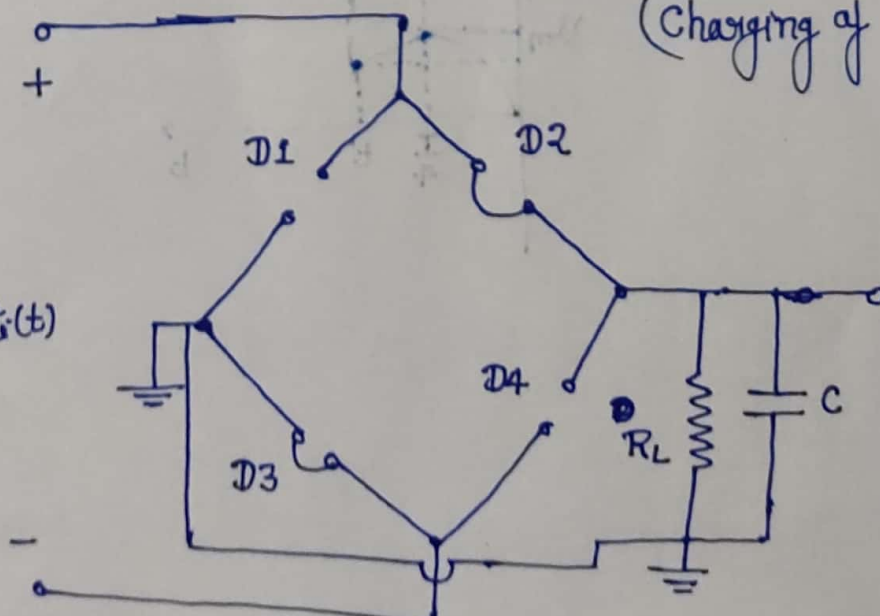

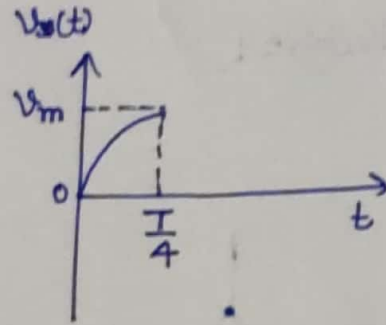


Discharging of Capacitor



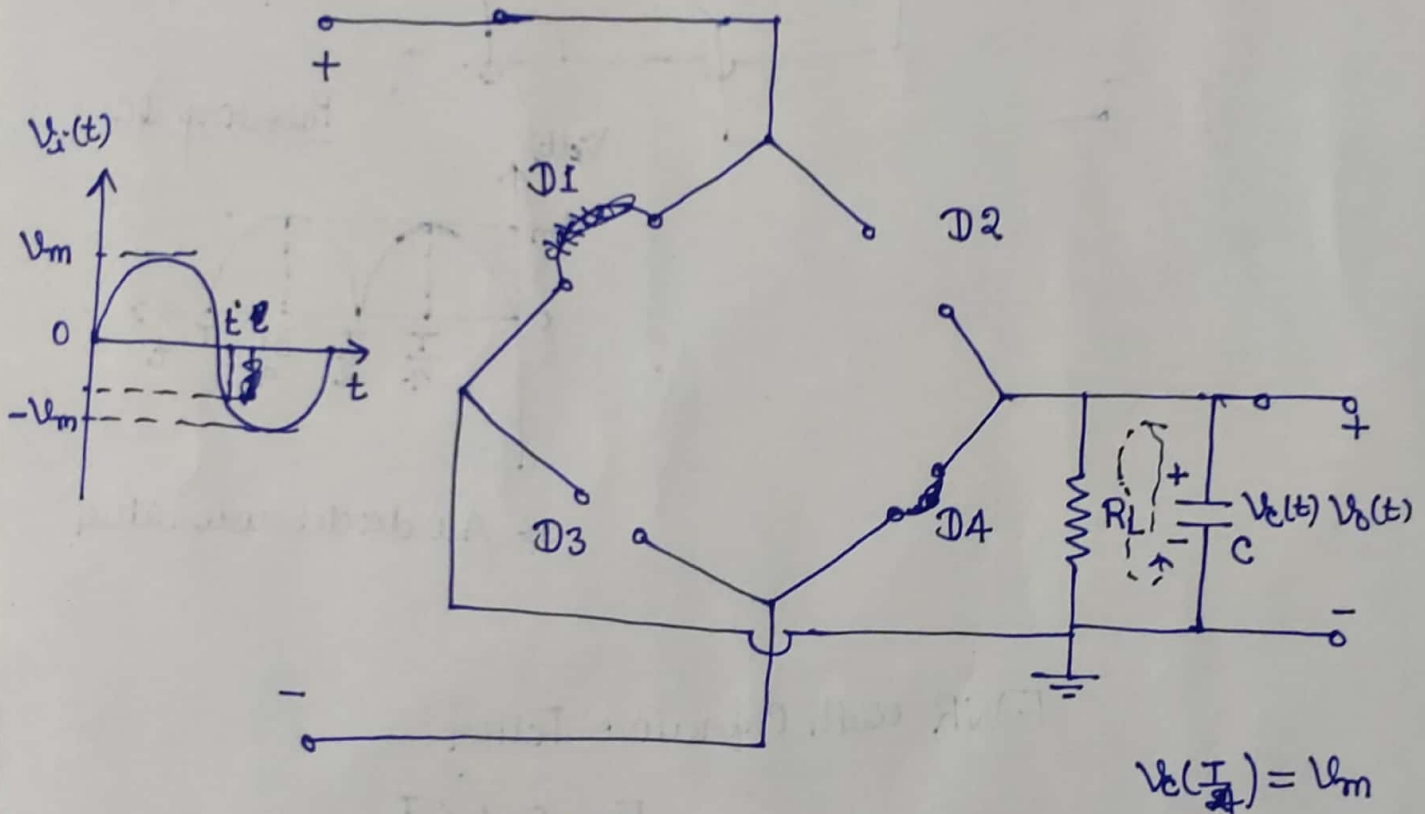
$$\left\{ \frac{T}{4} < t < t' \right\}$$




$$V_o\left(\frac{T}{4}\right) = V_m$$

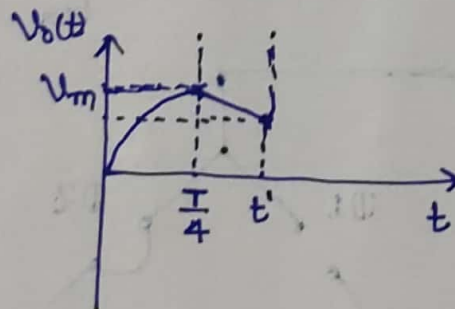

For $t' < t < \frac{3T}{4}$

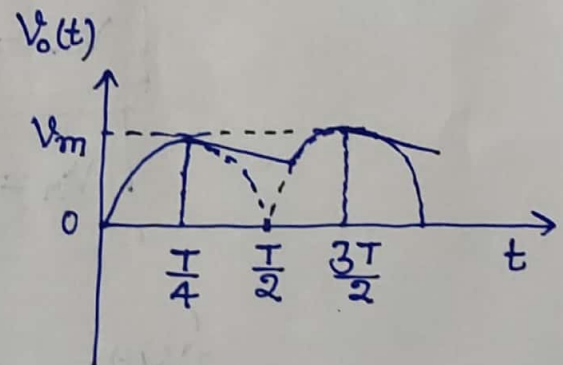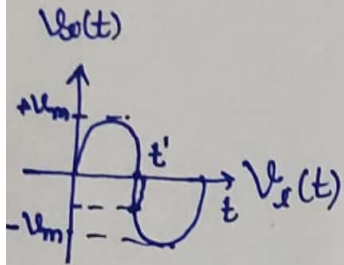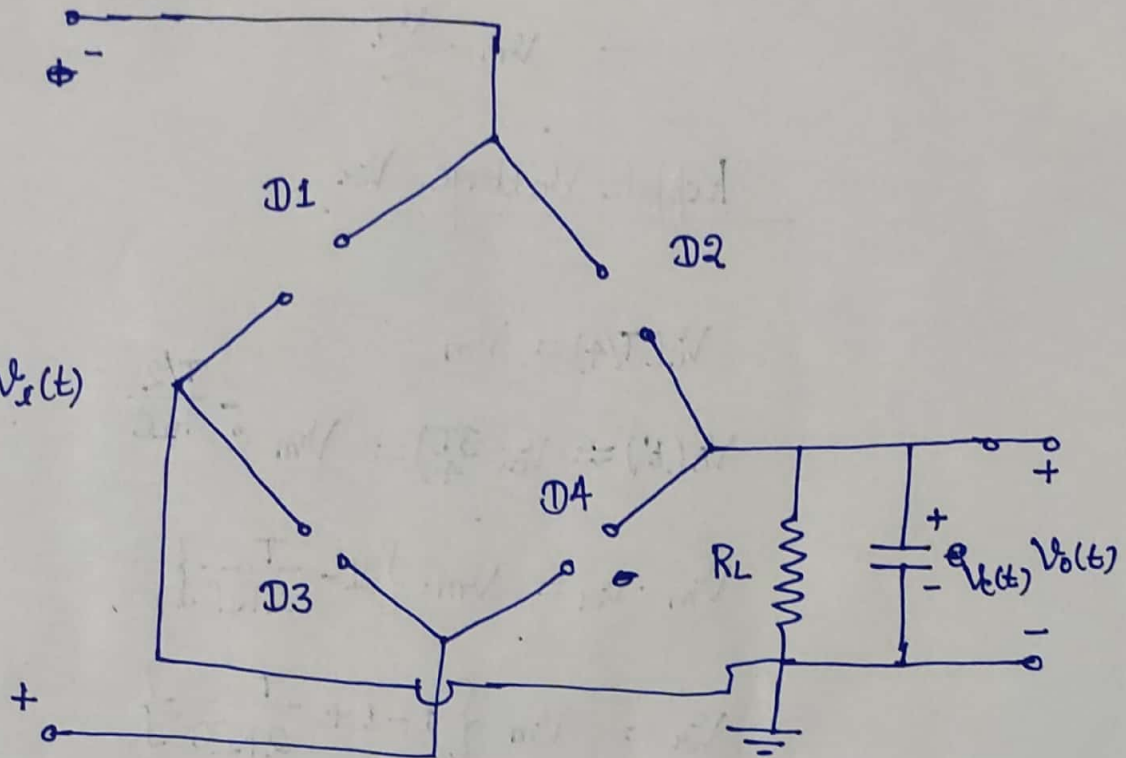

Output

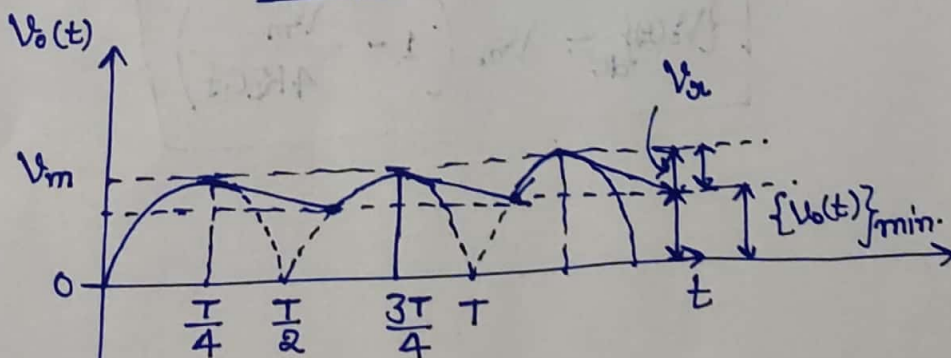

$$\{V_o(t)\}_{\min.} = \{V_o(t)\}_{\max.} - V_{or}$$

$$= V_m - V_{or}$$

$$\{V_o(t)\}_{\text{avg}} = \{V_o(t)\}_{\text{oc}} = \frac{\{V_o(t)\}_{\max.} + \{V_o(t)\}_{\min.}}{2}$$

$$\{V_o(t)\}_{dc} = \frac{V_m + V_m - V_{or}}{2}$$

$$= V_m - \frac{V_{or}}{2}$$

Ripple Voltage V_{or}

$$V_c(T/4) = V_m$$

$$V_c(t') \approx V_c\left(\frac{3T}{4}\right) = V_m e^{-\frac{T/2}{RC}}$$

$$V_m - V_{or} = V_m \cdot \left\{ 1 - \frac{T}{2RC} \right\}$$

$$V_{or} = V_m \left\{ 1 - 1 + \frac{T}{2RC} \right\}$$

$$V_{or} = V_m \frac{T}{2RC}$$

$$V_{or} = \frac{V_m}{2fRC}$$

$$\{V_o(t)\}_{dc} = V_m - \frac{1}{4} \frac{V_m}{fRC}$$

$$\{V_o(t)\}_{dc} = V_m \left(1 - \frac{V_m}{4fRC} \right)$$