


# Tutorial 11

EC103

(GATE Questions: ADC , DAC )
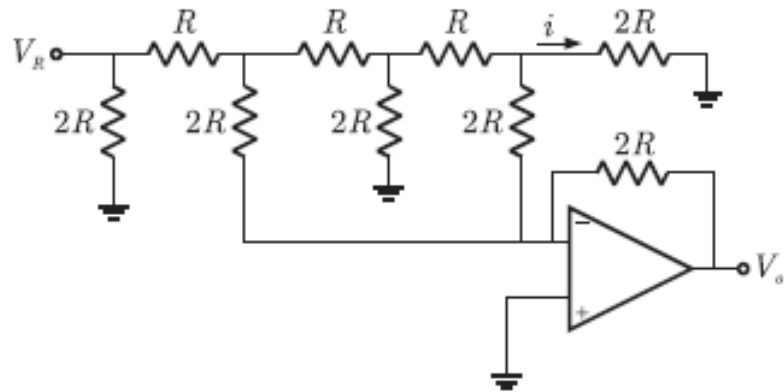
# Question 1 (GATE)

In the Digital-to-Analog converter circuit shown in the figure below,  
 $V_R = 10V$  and  $R = 10k\Omega$



The current is

(A)  $31.25\mu A$

(C)  $125\mu A$


(B)  $62.5\mu A$

(D)  $250\mu A$
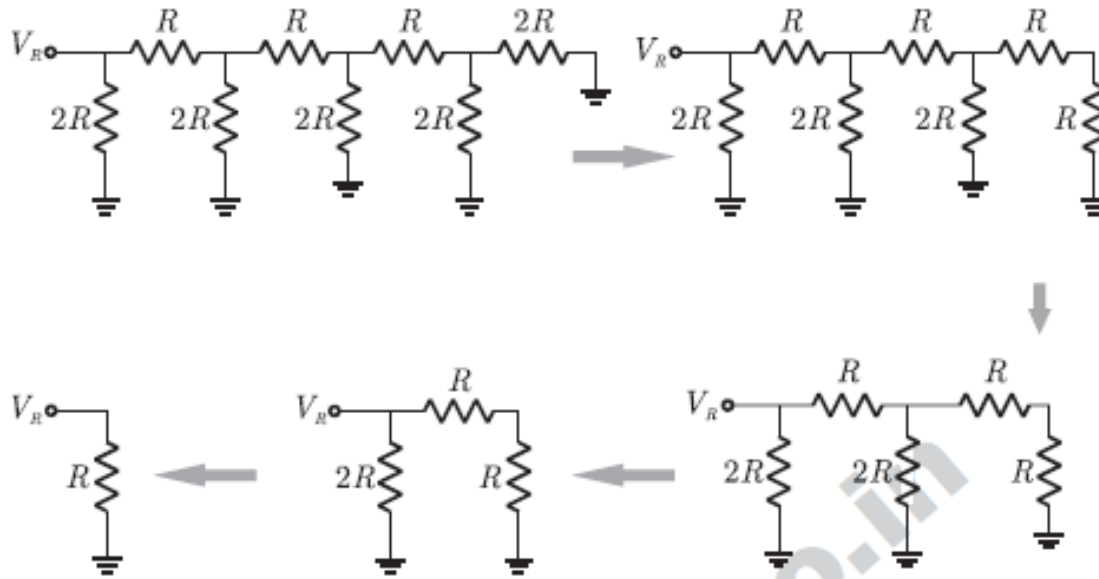
# Answer

Option (B) is correct.

Since the inverting terminal is at virtual ground the resistor network can be reduced as follows




The current from voltage source is

$$I = \frac{V_R}{R} = \frac{10}{10k} = 1 \text{ mA}$$
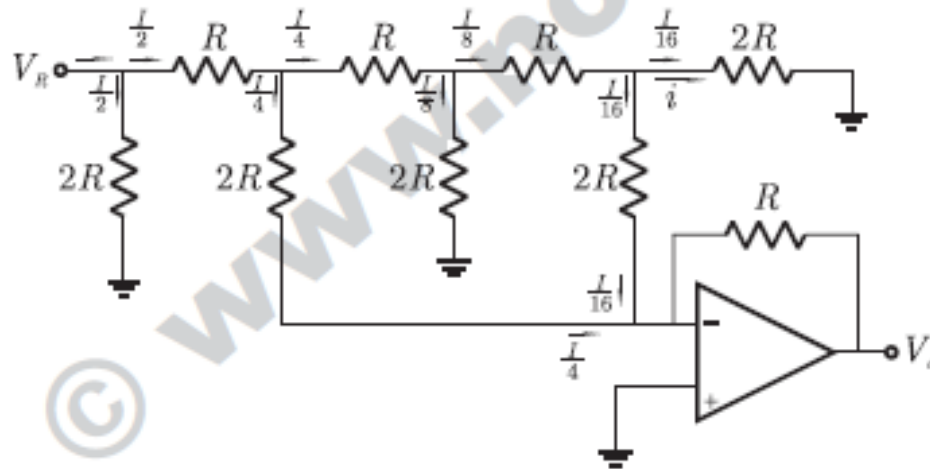
# Answer

This current will be divide as shown below




Now

$$i = \frac{I}{16} = \frac{1 \times 10^{-3}}{16} = 62.5 \mu A$$
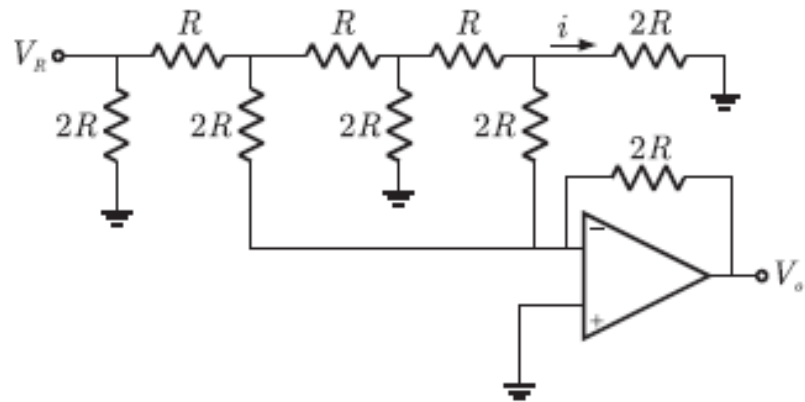
## Question 2 (GATE)

In the Digital-to-Analog converter circuit shown in the figure below,  
 $V_R = 10V$  and  $R = 10k\Omega$



The voltage  $V_o$  is

(A)  $-0.781 V$

(C)  $-3.125 V$

(B)  $-1.562 V$

(D)  $-6.250 V$

# Answer

Option (C) is correct.


The net current in inverting terminal of OP - amp is

$$I = \frac{1}{4} + \frac{1}{16} = \frac{5I}{16}$$

So that  $V_0 = -R \times \frac{5I}{16} = -3.125$
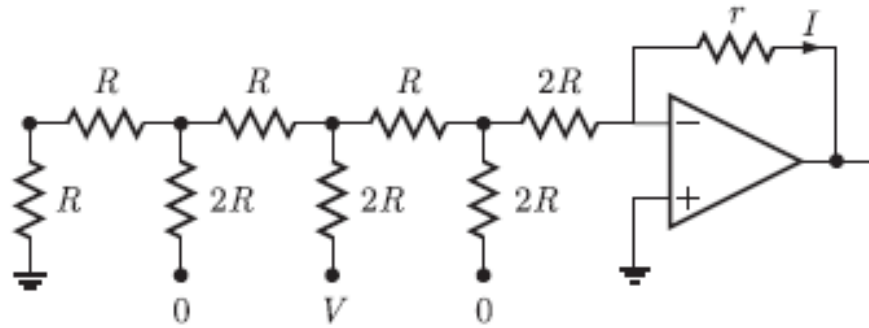
## Question 3 (GATE)

The current  $I$  through resistance  $r$  in the circuit shown in the figure is



(A)  $\frac{-V}{12R}$

(B)  $\frac{V}{12R}$

(C)  $\frac{V}{6R}$

(D)  $\frac{V}{3R}$


# Answer

- $V/12R$


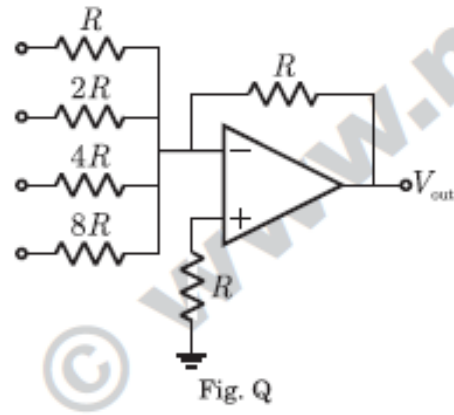
# Question 4 (GATE)

The circuit shown in the figure is a 4 bit DAC



The input bits 0 and 1 are represented by 0 and 5 V respectively. The OP AMP is ideal, but all the resistance and the 5 v inputs have a tolerance of  $\pm 10\%$ . The specification (rounded to nearest multiple of 5%) for the tolerance of the DAC is

- (A)  $\pm 35\%$
- (B)  $\pm 20\%$
- (C)  $\pm 10\%$
- (D)  $\pm 5\%$

# Answer

Option (A) is correct.

$$V_o = -V_1 \left[ \frac{R}{R} b_o + \frac{R}{2R} b_1 + \frac{R}{4R} b_2 + \frac{R}{4R} b_3 \right]$$

Exact value when  $V_1 = 5$ , for maximum output

$$V_{oExact} = -5 \left[ 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right] = -9.375$$

Maximum  $V_{out}$  due to tolerance

$$\begin{aligned} V_{o\max} &= -5.5 \left[ \frac{110}{90} + \frac{110}{2 \times 90} + \frac{110}{4 \times 90} + \frac{110}{8 \times 90} \right] \\ &= -12.604 \end{aligned}$$

Tolerance = 34.44% = 35%

in

## Question 5 (GATE)

The minimum number of comparators required to build an 8-bits flash ADC is


- (A) 8
- (B) 63
- (C) 255
- (D) 256

# Answer


- (C) 255
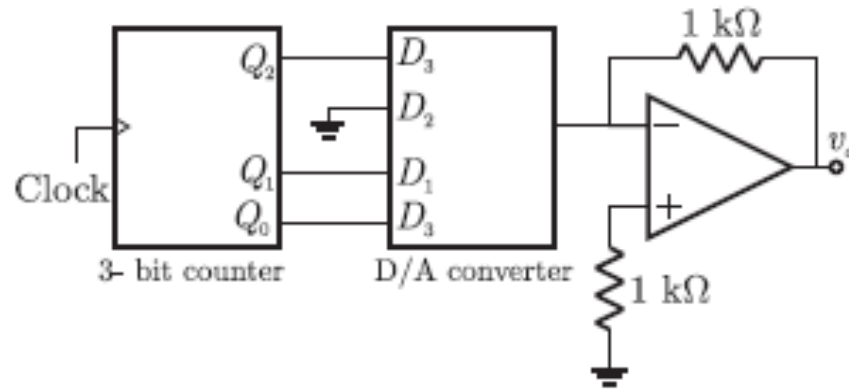
## Question 6 (GATE)

A 4 - bit DAC is connected to a free - running 3 - bit UP counter, as shown in the following figure. Which of the following waveforms will be observed at  $V_0$  ?



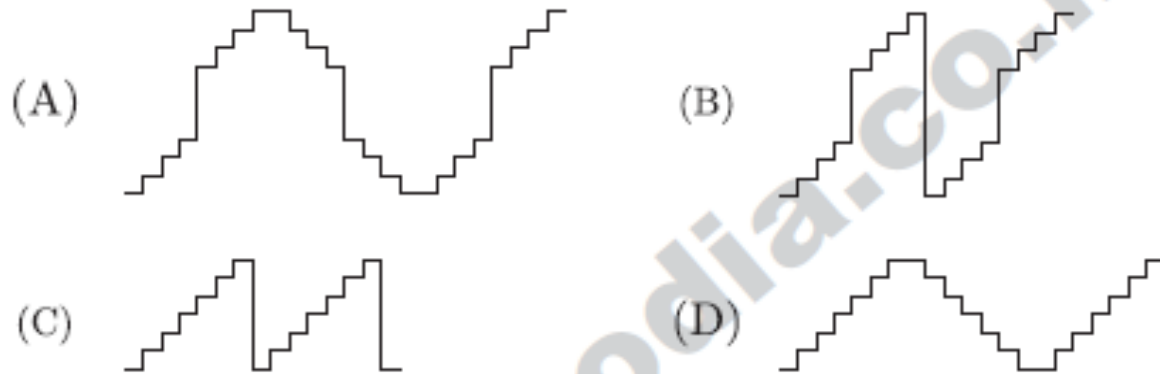In the figure shown above, the ground has been shown by the symbol  $\nabla$



# Answer

Option (B) is correct.

$Q_2Q_1Q_0$	$D_3 = Q_2$	$D_2 = 0$	$D_1 = Q_1$	$D_0 = Q_0$	$V_o$
000	0	0	0	0	0
001	0	0	0	1	1
010	0	0	1	0	2
011	0	0	1	1	3
100	1	0	0	0	8
101	1	0	0	1	9
110	1	0	1	0	10
111	1	0	1	1	11
000	0	0	0	0	0
001	0	0	0	1	1

## Question 7 (GATE)

The resolution of a 4-bit counting ADC is 0.5 volts. For an analog input of 6.6 volts, the digital output of the ADC will be

(A) 1011

(B) 1101

(C) 1100

(D) 1110






# Answer

- (B) 1101


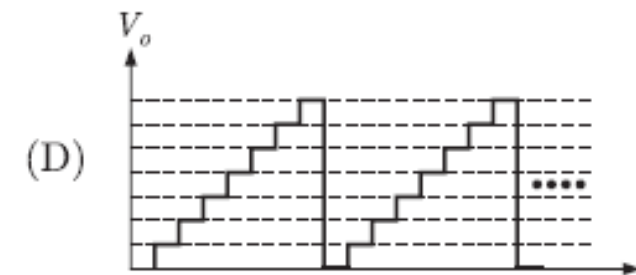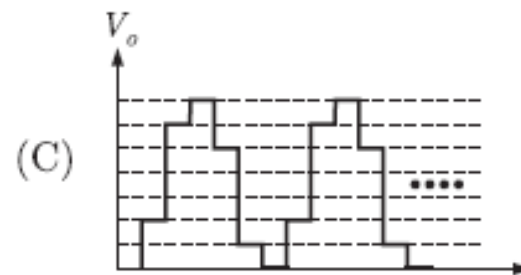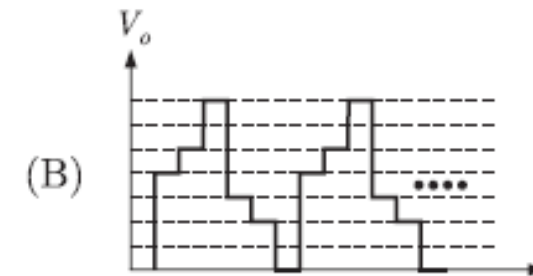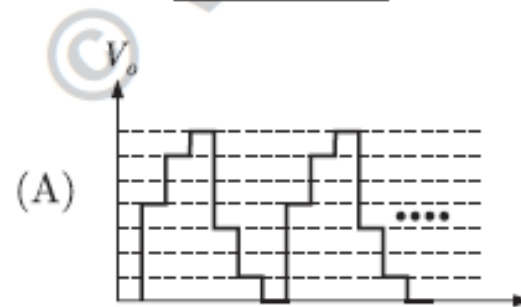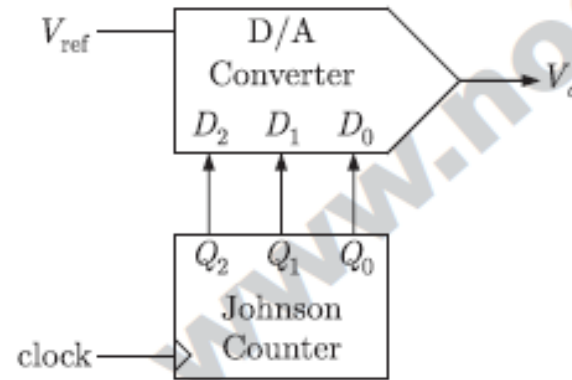
# Question 8 (GATE)


The output of a 3-stage Johnson (twisted ring) counter is fed to a digital-to-analog (D/A) converter as shown in the figure below. Assume all states of the counter to be unset initially. The waveform which represents the D/A converter output  $V_o$  is


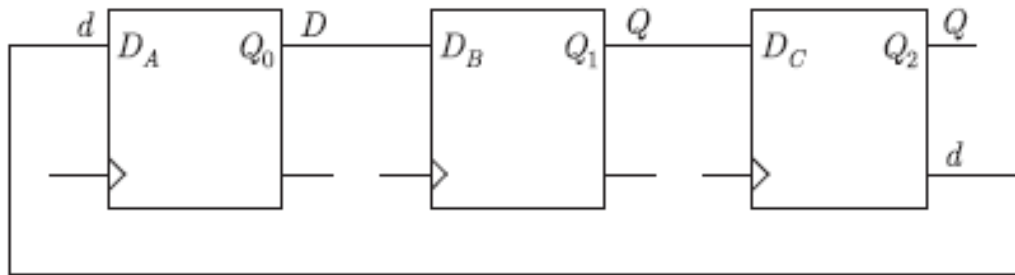
# Answer

Option (A) is correct.

All the states of the counter are initially unset.



State Initially are shown below in table :

$Q_2$	$Q_1$	$Q_0$	
0	0	0	0
1	0	0	4
1	1	0	6
1	1	1	7

## Question 9 (GATE)

The output  $Y$  of a 2-bit comparator is logic 1 whenever the 2-bit input  $A$  is greater than the 2-bit input  $B$ . The number of combinations for which the output is logic 1, is

(A) 4

(B) 6

(C) 8

(D) 10

# Answer

Option (B ) is correct.



$Y = 1$ , when  $A > B$

$$A = a_1a_0, B = b_1b_0$$

$a_1$	$a_0$	$b_1$	$b_0$	$Y$
0	1	0	0	1
1	0	0	0	1
1	0	0	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1

Total combination = 6