 



# Lecture 25

EC103

# Discrete (Digital) Points on an Analog Curve


 
# Digital Representation of an Analog curve



# Introduction

- \* Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.

# Introduction

- \* Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- \* Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.

# Introduction

- \* Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- \* Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.
- \* An ADC (Analog-to-Digital Converter) is used to convert an analog signal to the digital format.

# Introduction


- \* Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- \* Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.
- \* An ADC (Analog-to-Digital Converter) is used to convert an analog signal to the digital format.
- \* The reverse conversion (from digital to analog) is also required. For example, music stored in a DVD in digital format must be converted to an analog voltage for playing out on a speaker.

# Introduction


- \* Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- \* Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.
- \* An ADC (Analog-to-Digital Converter) is used to convert an analog signal to the digital format.
- \* The reverse conversion (from digital to analog) is also required. For example, music stored in a DVD in digital format must be converted to an analog voltage for playing out on a speaker.
- \* A DAC (Digital-to-Analog Converter) is used to convert a digital signal to the analog format.



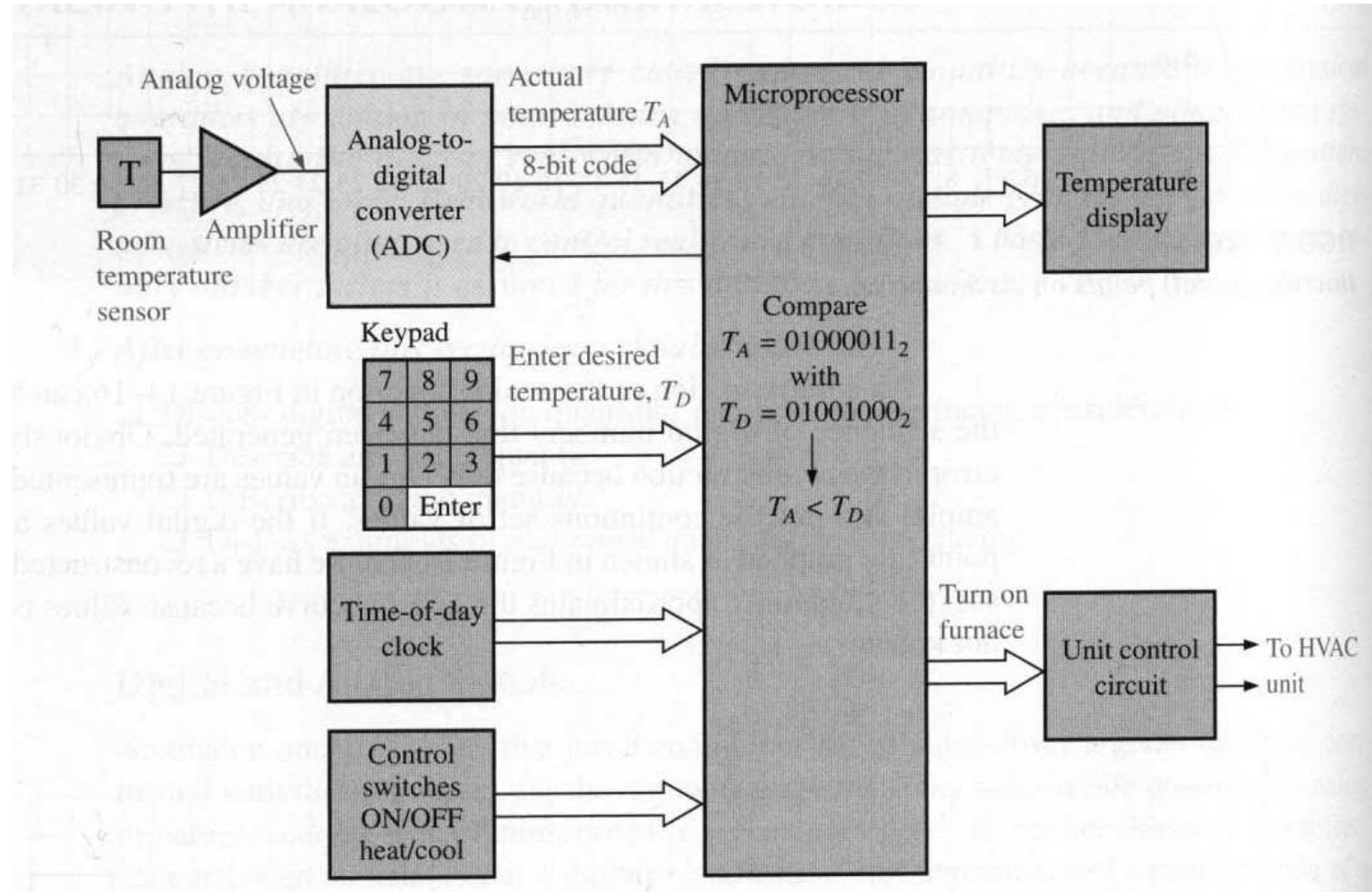
# Interfacing the Analog and Digital Worlds: Example 1: An Electronic Thermostat



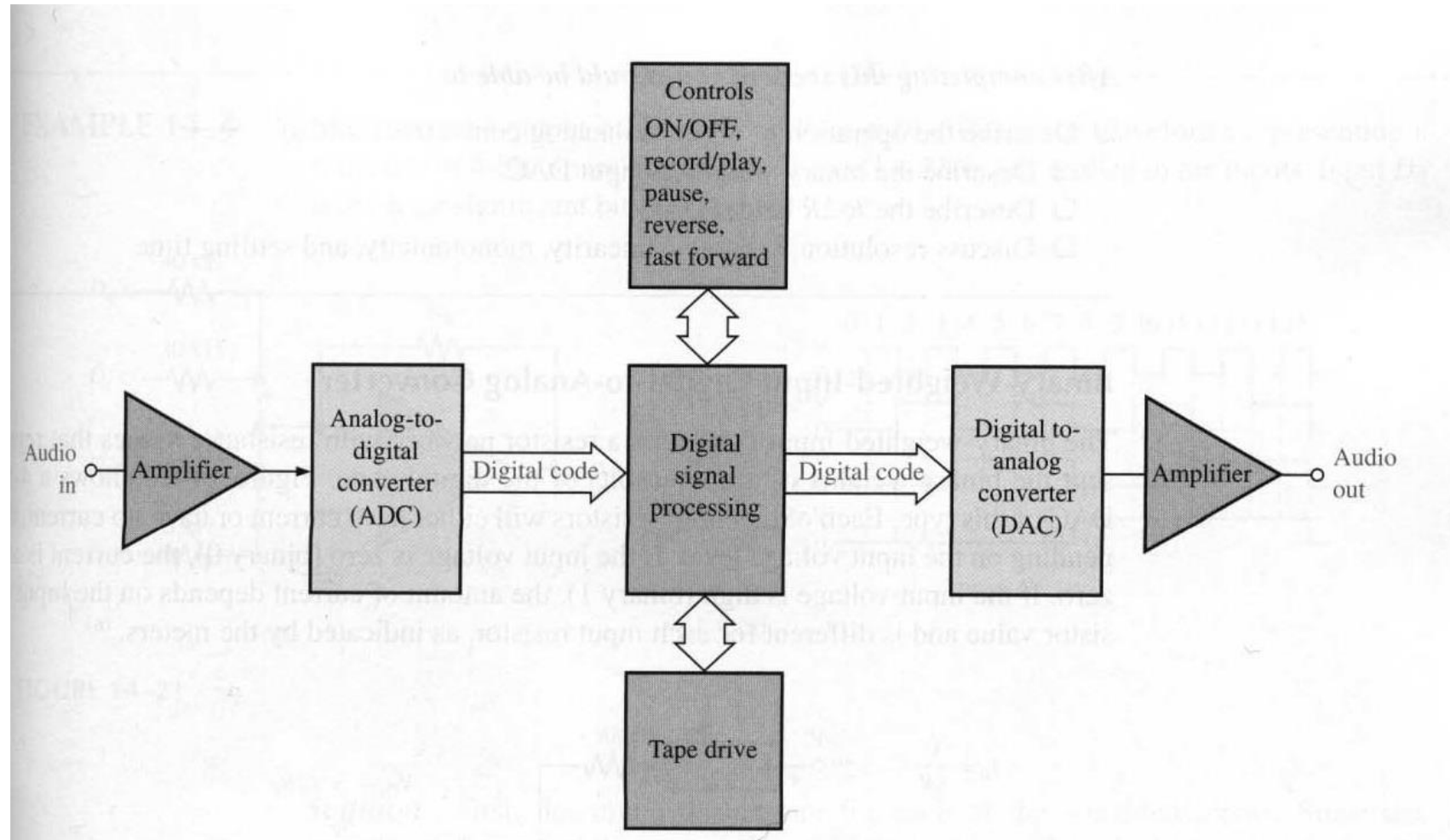
## Interfacing the Analog and Digital Worlds: Example 2: A Digital Audio Recorder/Player



# DAC

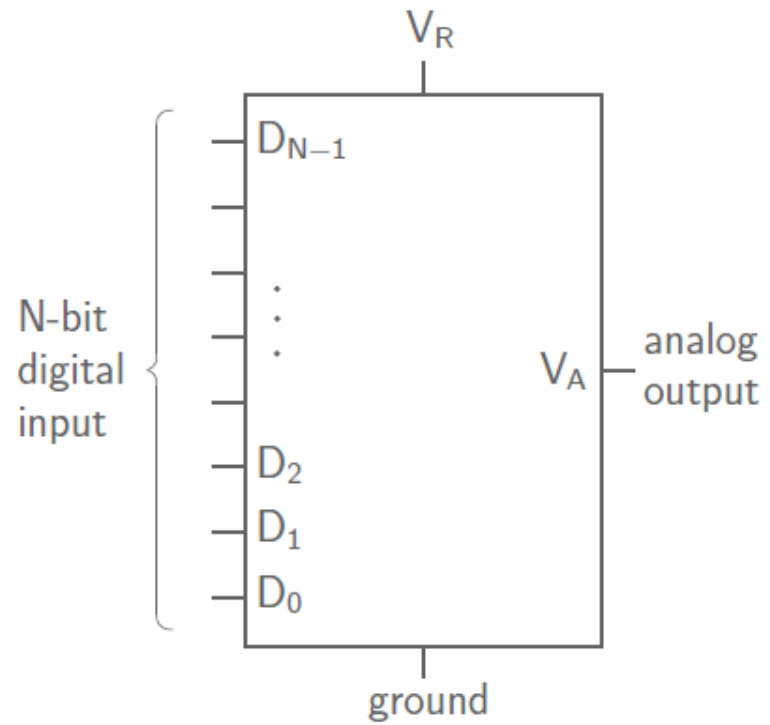


# DAC

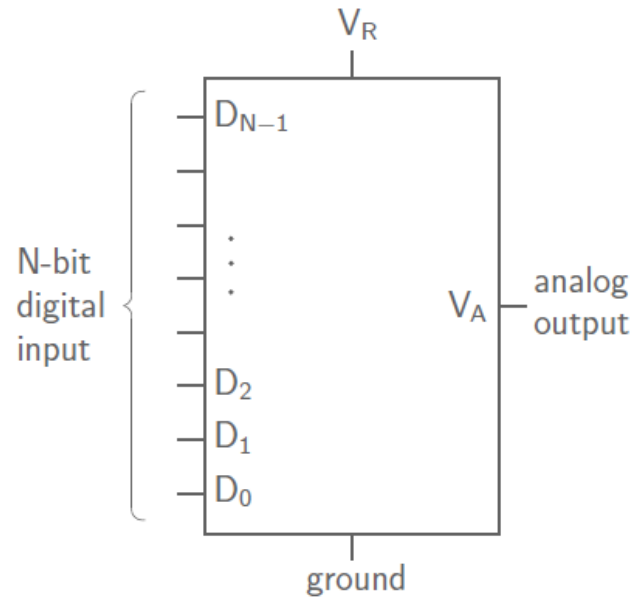


- \* For a 4-bit DAC, with input  $S_3 S_2 S_1 S_0$ , the output voltage is  $V_A = K [(S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0)]$ .  
In general,  $V_A = K \sum_{k=0}^{N-1} S_k 2^k$ .

# DAC

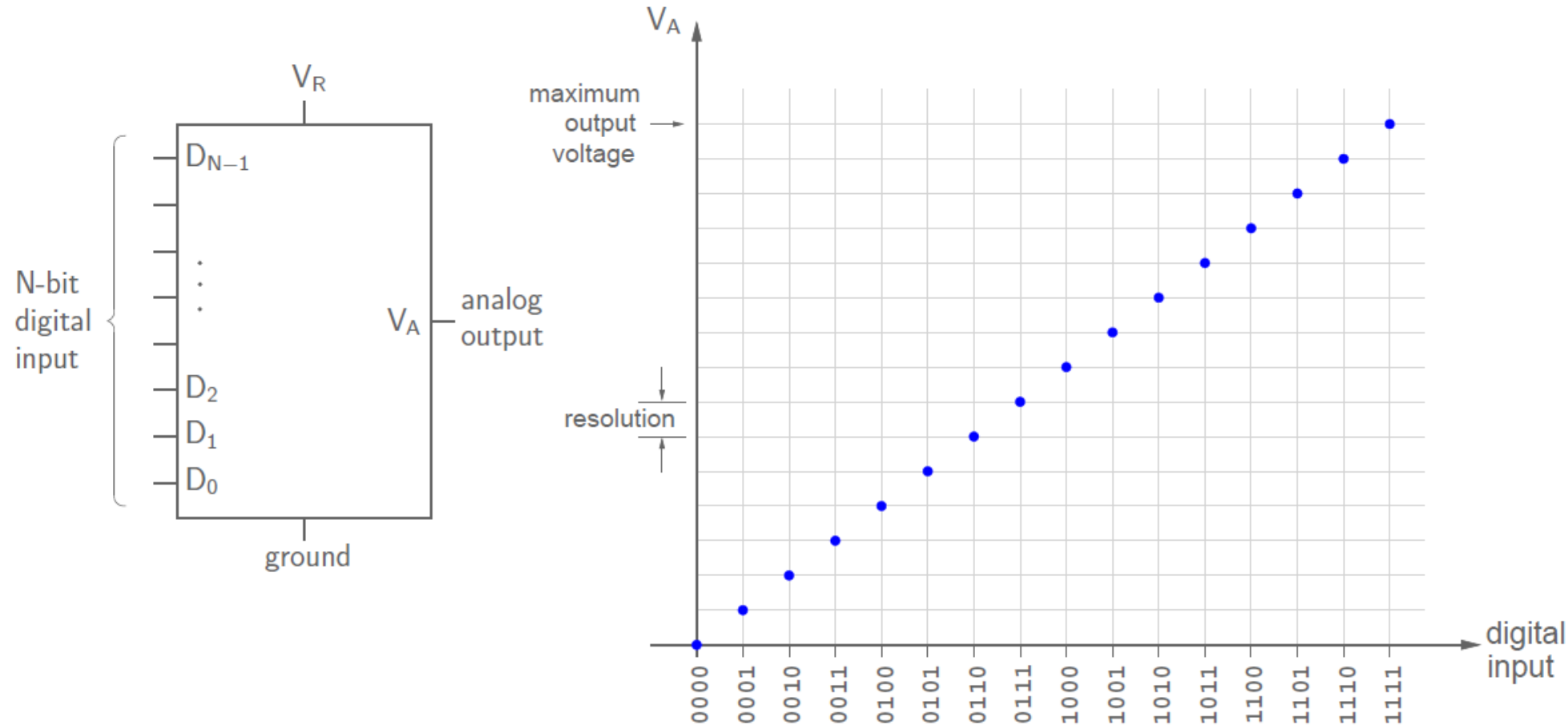



- \* For a 4-bit DAC, with input  $S_3S_2S_1S_0$ , the output voltage is 
$$V_A = K [(S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0)] .$$
 In general, 
$$V_A = K \sum_{k=0}^{N-1} S_k 2^k .$$

# DAC

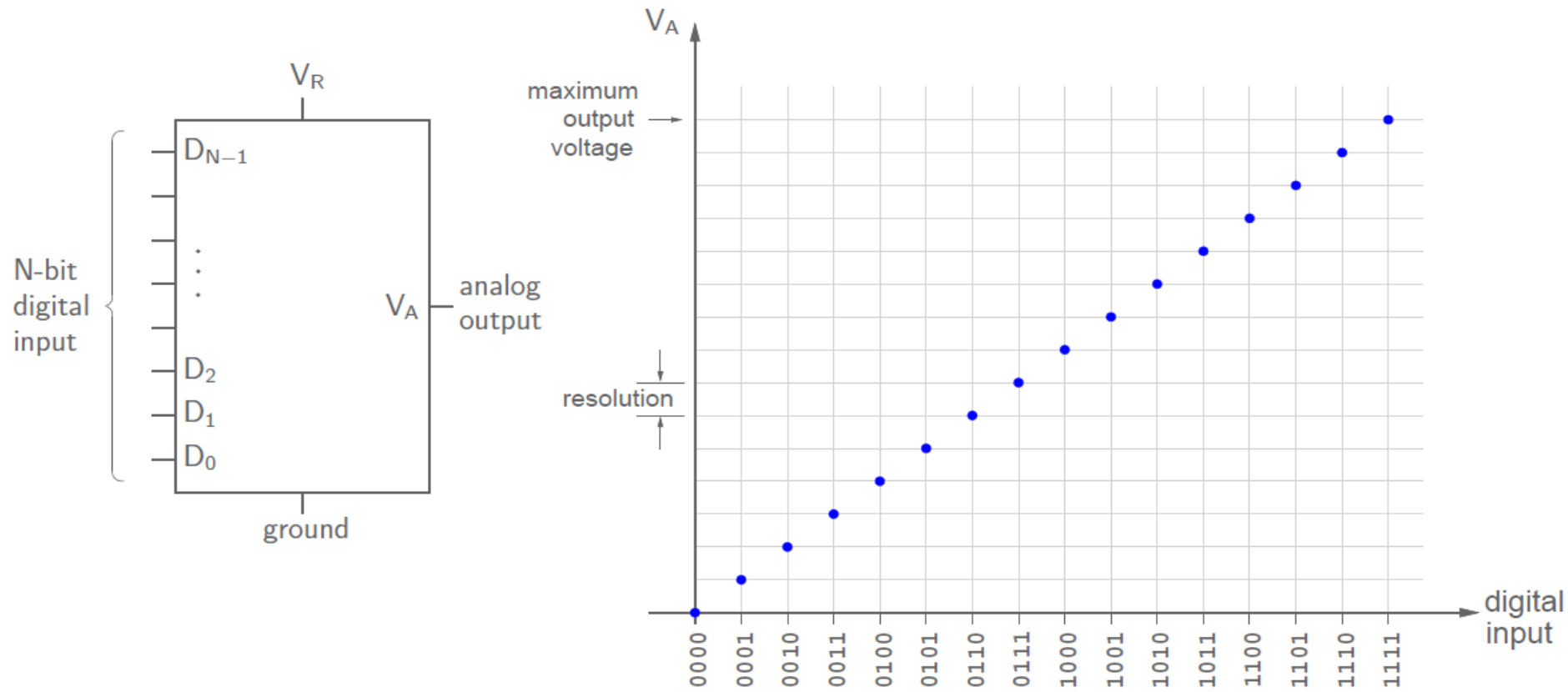


- \* For a 4-bit DAC, with input  $S_3S_2S_1S_0$ , the output voltage is  $V_A = K [(S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0)]$ .  
In general,  $V_A = K \sum_{k=0}^{N-1} S_k 2^k$ .
- \*  $K$  is proportional to the reference voltage  $V_R$ . Its value depends on how the DAC is implemented.

## DAC using binary-weighted resistors

  


## DAC using binary-weighted resistors

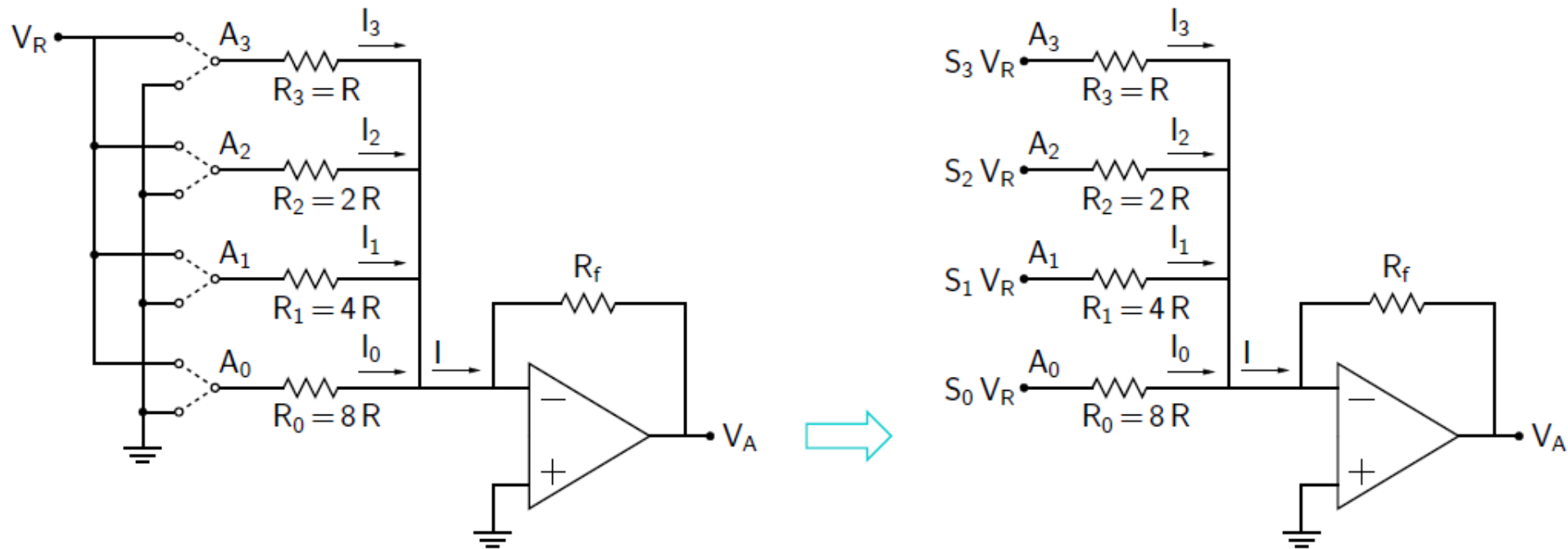

\* If the input bit  $S_k$  is 1,  $A_k$  gets connected to  $V_R$ ; else, it gets connected to ground.




## DAC using binary-weighted resistors

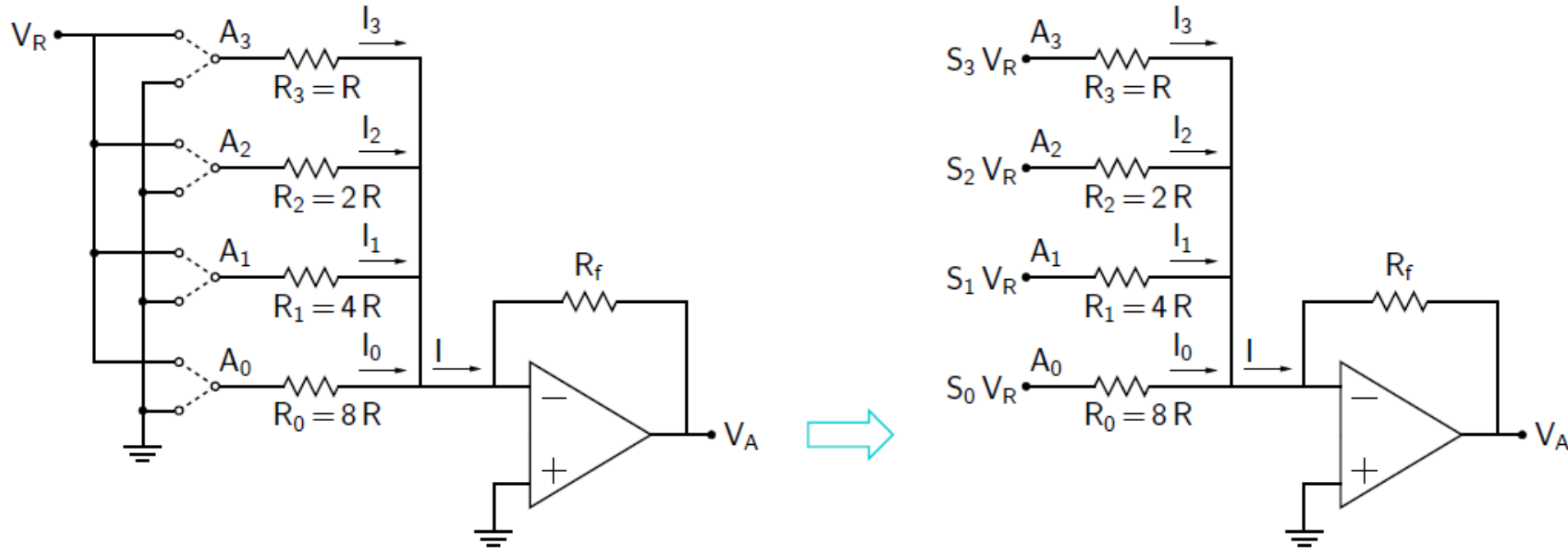

- \* If the input bit  $S_k$  is 1,  $A_k$  gets connected to  $V_R$ ; else, it gets connected to ground.  
→  $V(A_k) = S_k \times V_R$ .

## DAC using binary-weighted resistors

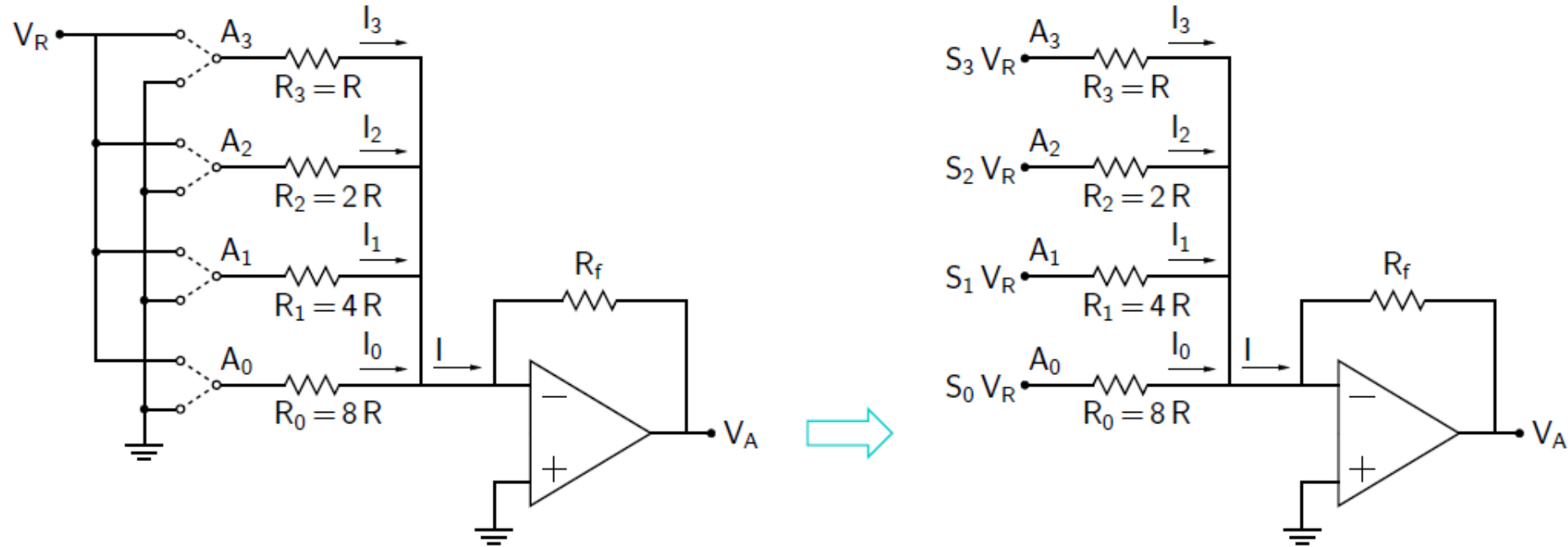


- \* If the input bit  $S_k$  is 1,  $A_k$  gets connected to  $V_R$ ; else, it gets connected to ground.

$$\rightarrow V(A_k) = S_k \times V_R.$$

- \* Since the inverting terminal of the Op Amp is at virtual ground,

$$I_k = \frac{V(A_k) - 0}{R_k} = \frac{S_k V_R}{R_k}.$$

## DAC using binary-weighted resistors

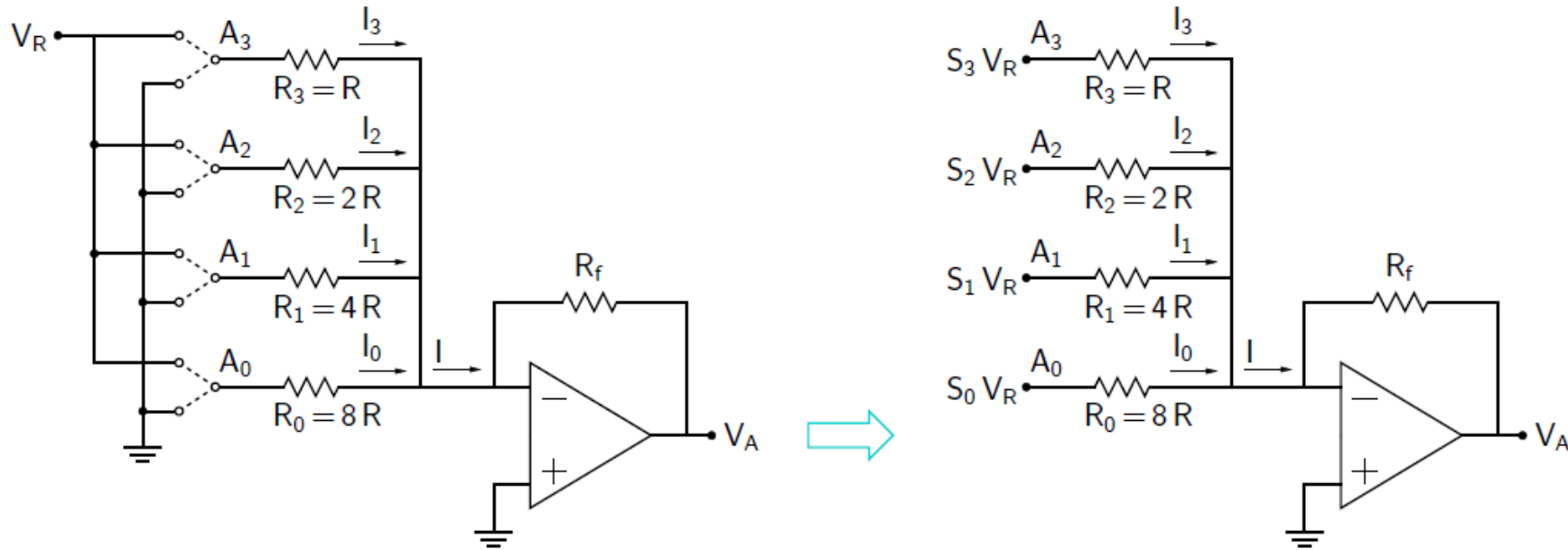

- \* If the input bit  $S_k$  is 1,  $A_k$  gets connected to  $V_R$ ; else, it gets connected to ground.


$$\rightarrow V(A_k) = S_k \times V_R.$$

- \* Since the inverting terminal of the Op Amp is at virtual ground,

$$I_k = \frac{V(A_k) - 0}{R_k} = \frac{S_k V_R}{R_k}.$$

- \* Using  $R_k = 2^{N-1} R / 2^k$ , we get  $I = \frac{V_R}{2^{N-1} R} \sum_{k=0}^{N-1} S_k \times 2^k$  ( $N = 4$  here).

## DAC using binary-weighted resistors

 

- \* If the input bit  $S_k$  is 1,  $A_k$  gets connected to  $V_R$ ; else, it gets connected to ground.  
 $\rightarrow V(A_k) = S_k \times V_R$ .

- \* Since the inverting terminal of the Op Amp is at virtual ground,  
$$I_k = \frac{V(A_k) - 0}{R_k} = \frac{S_k V_R}{R_k}.$$


- \* Using  $R_k = 2^{N-1} R / 2^k$ , we get  $I = \frac{V_R}{2^{N-1} R} \sum_0^{N-1} S_k \times 2^k$  ( $N = 4$  here).

- \* The output voltage is  $V_o = -R_f I = -V_R \frac{R_f}{2^{N-1} R} \sum_0^{N-1} S_k \times 2^k$ .


# Lecture 26

EC103
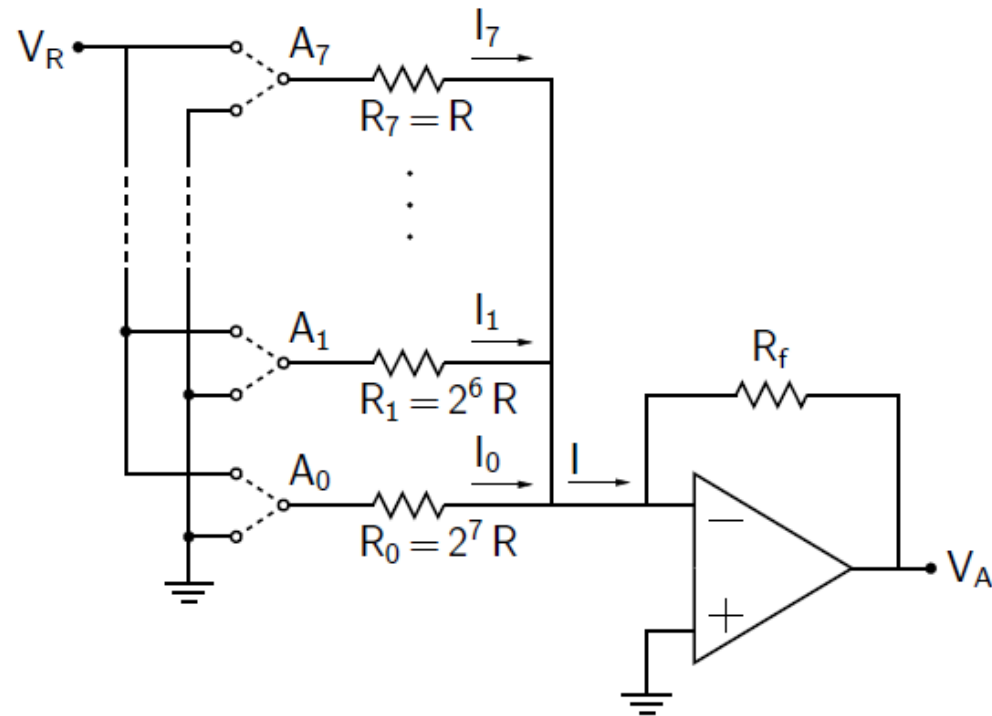
## DAC using binary-weighted resistors: Example




 - \* Consider an 8-bit DAC with  $V_R = 5\text{ V}$ . What is the smallest value of  $R$  which will limit the current drawn from the supply ( $V_R$ ) to 10 mA?



- \* Consider an 8-bit DAC with  $V_R = 5\text{ V}$ . What is the smallest value of  $R$  which will limit the current drawn from the supply ( $V_R$ ) to 10 mA?

 
Maximum current is drawn from  $V_R$  when the input is 1111 1111.



- \* Consider an 8-bit DAC with  $V_R = 5\text{ V}$ . What is the smallest value of  $R$  which will limit the current drawn from the supply ( $V_R$ ) to 10 mA?

 Maximum current is drawn from  $V_R$  when the input is 1111 1111.  
 $\rightarrow$  All nodes  $A_0$  to  $A_7$  get connected to  $V_R$ .






- \* Consider an 8-bit DAC with  $V_R = 5\text{ V}$ . What is the smallest value of  $R$  which will limit the current drawn from the supply ( $V_R$ ) to 10 mA?

Maximum current is drawn from  $V_R$  when the input is 1111 1111.

→ All nodes  $A_0$  to  $A_7$  get connected to  $V_R$ .
 
$$\begin{aligned} \rightarrow 10\text{ mA} &= \frac{V_R}{R} + \frac{V_R}{2R} + \dots + \frac{V_R}{2^7 R} = \frac{1}{2^7} \frac{V_R}{R} (2^0 + 2^1 + \dots + 2^7) \\ &= \frac{1}{2^7} \frac{V_R}{R} (2^8 - 1) = \frac{255}{128} \frac{V_R}{R} \end{aligned}$$



- \* Consider an 8-bit DAC with  $V_R = 5\text{ V}$ . What is the smallest value of  $R$  which will limit the current drawn from the supply ( $V_R$ ) to 10 mA?


Maximum current is drawn from  $V_R$  when the input is 1111 1111.

→ All nodes  $A_0$  to  $A_7$  get connected to  $V_R$ .


$$\rightarrow 10\text{ mA} = \frac{V_R}{R} + \frac{V_R}{2R} + \cdots + \frac{V_R}{2^7 R} = \frac{1}{2^7} \frac{V_R}{R} (2^0 + 2^1 + \cdots + 2^7)$$

$$= \frac{1}{2^7} \frac{V_R}{R} (2^8 - 1) = \frac{255}{128} \frac{V_R}{R}$$
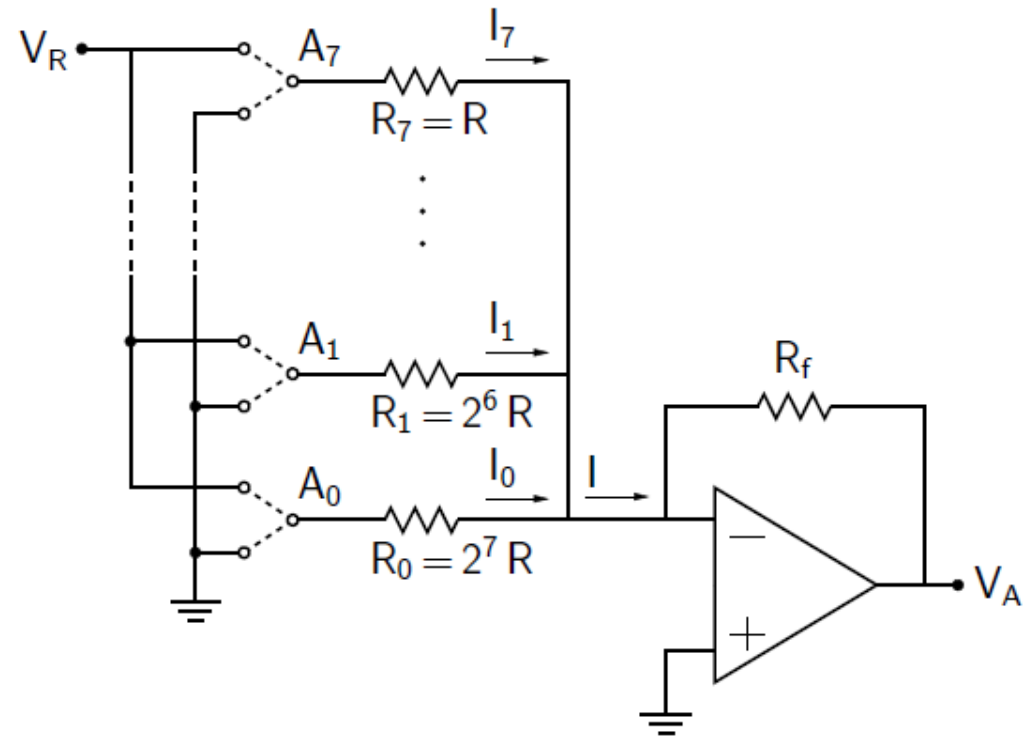
$$\rightarrow R_{\min} = \frac{5\text{ V}}{10\text{ mA}} \times \frac{255}{128} = 996\ \Omega.$$




 - \* If  $R_f = R$ , what is the resolution (i.e.,  $\Delta V_A$  corresponding to the input LSB changing from 0 to 1 with other input bits constant)?



- \* If  $R_f = R$ , what is the resolution (i.e.,  $\Delta V_A$  corresponding to the input LSB changing from 0 to 1 with other input bits constant)?
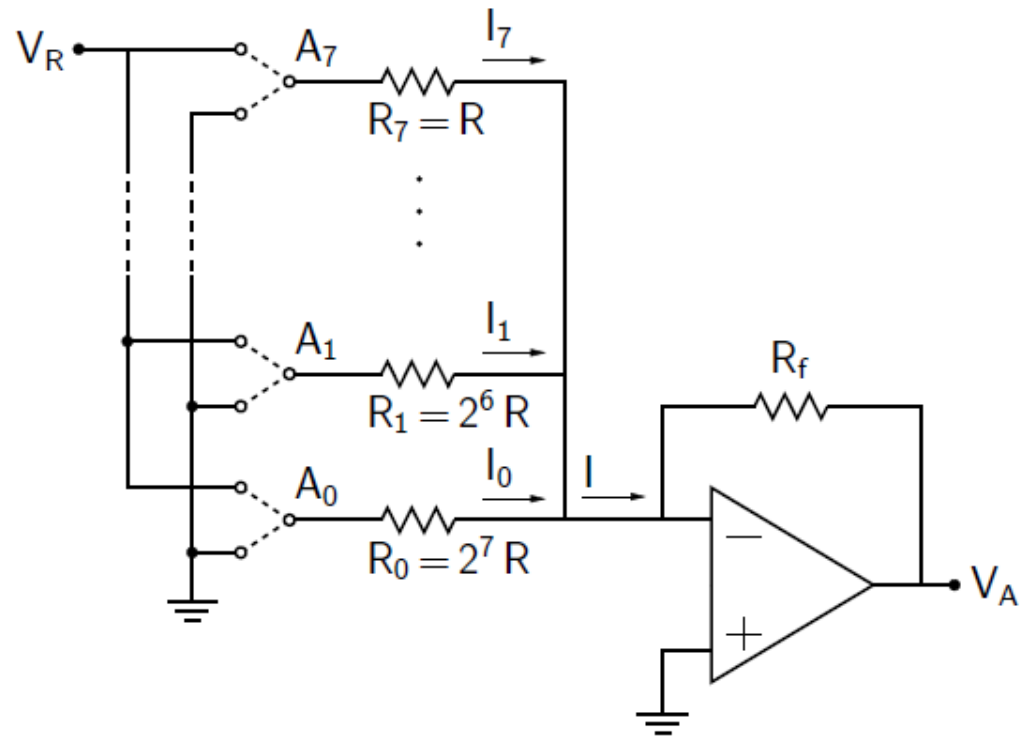
$$V_A = -V_R \frac{R_f}{2^{N-1}R} \left[ S_7 2^7 + \dots + S_1 2^1 + S_0 2^0 \right]$$




- \* If  $R_f = R$ , what is the resolution (i.e.,  $\Delta V_A$  corresponding to the input LSB changing from 0 to 1 with other input bits constant)?

$$V_A = -V_R \frac{R_f}{2^{N-1}R} \left[ s_7 2^7 + \dots + s_1 2^1 + s_0 2^0 \right]$$


$$\rightarrow \Delta V_A = \frac{V_R}{2^{N-1}} \frac{R_f}{R} = \frac{5 \text{ V}}{2^{8-1}} \times 1 = \frac{5}{128} = 0.0391 \text{ V}.$$

## R-2R ladder network

 


Node  $A_k$  is connected to  $V_R$  if input bit  $S_k$  is 1; else, it is connected to ground.

## R-2R ladder network

 


Node  $A_k$  is connected to  $V_R$  if input bit  $S_k$  is 1; else, it is connected to ground.

The original network is equivalent to

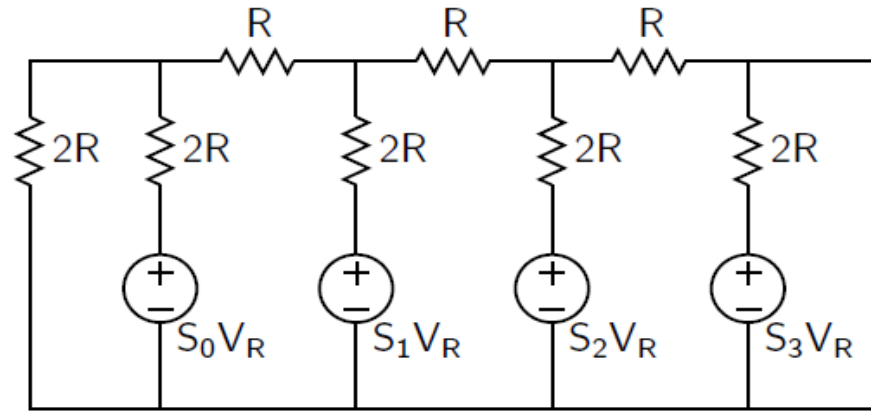

 
## R-2R ladder network: Thevenin resistance






 
## R-2R ladder network: Thevenin resistance



 
## R-2R ladder network: Thevenin resistance



 
## R-2R ladder network: Thevenin resistance



 
## R-2R ladder network: Thevenin resistance



 
## R-2R ladder network: Thevenin resistance



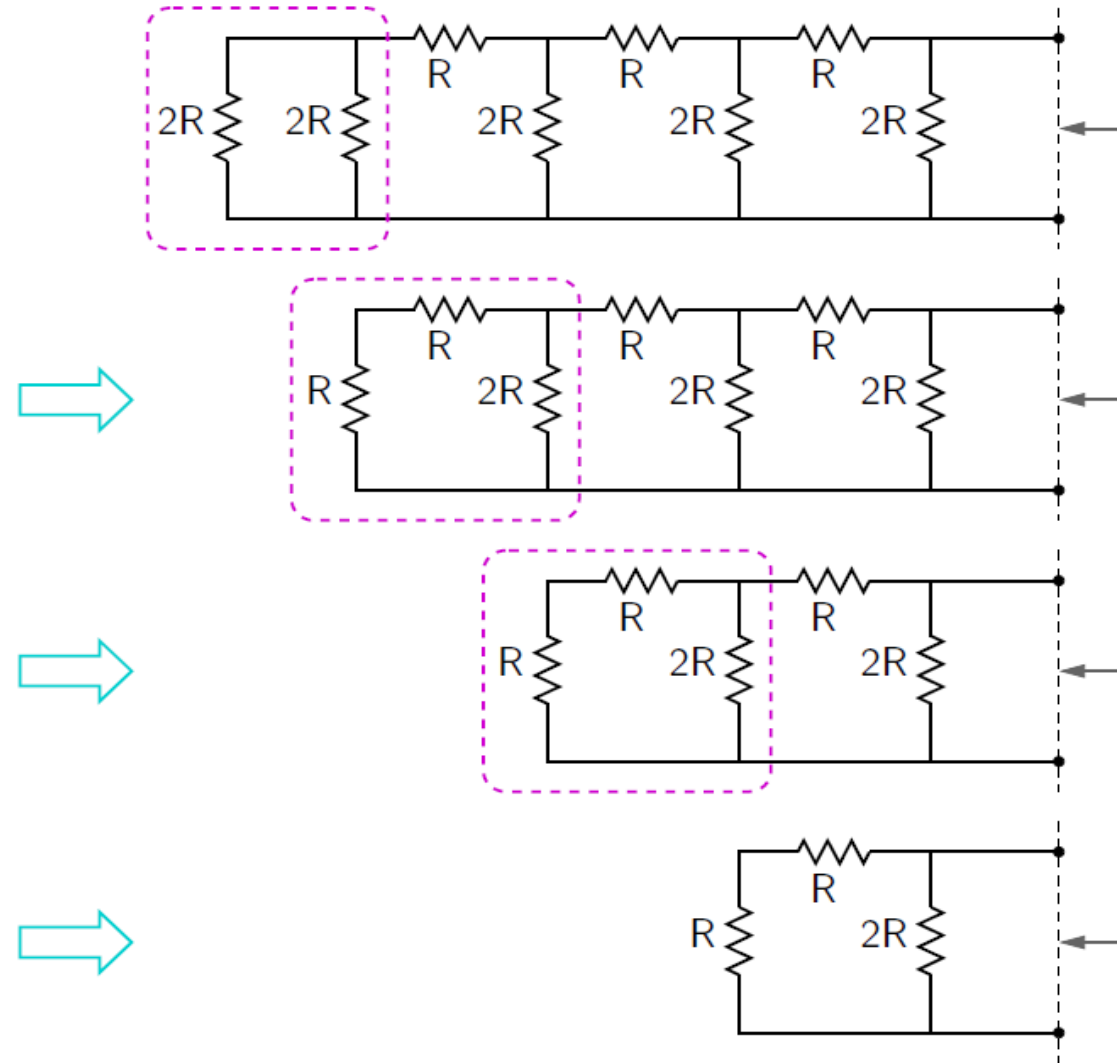
## R-2R ladder network: Thevenin resistance


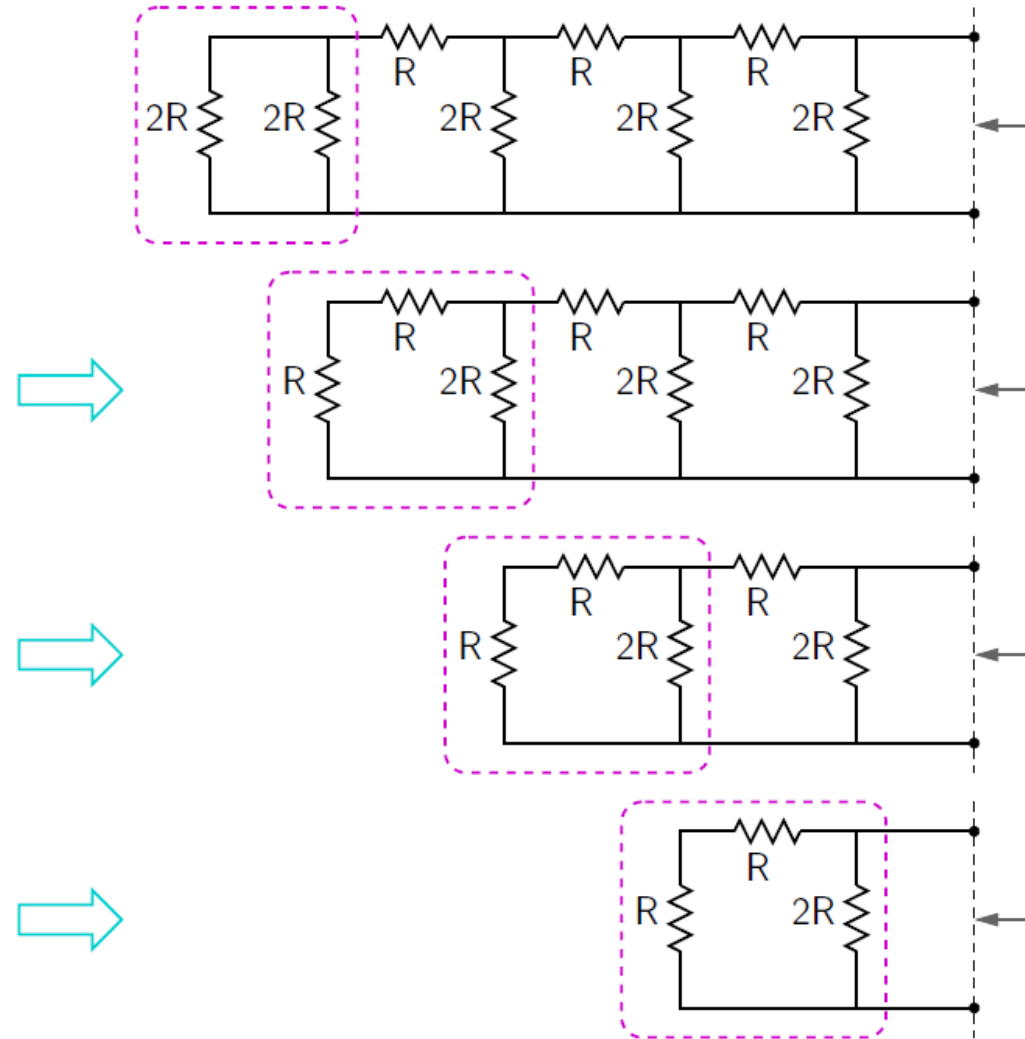
## R-2R ladder network: Thevenin resistance



 
## R-2R ladder network: Thevenin resistance






 
R-2R ladder network:  $V_{Th}$  for  $S_0 = 1$



 
R-2R ladder network:  $V_{Th}$  for  $S_0 = 1$





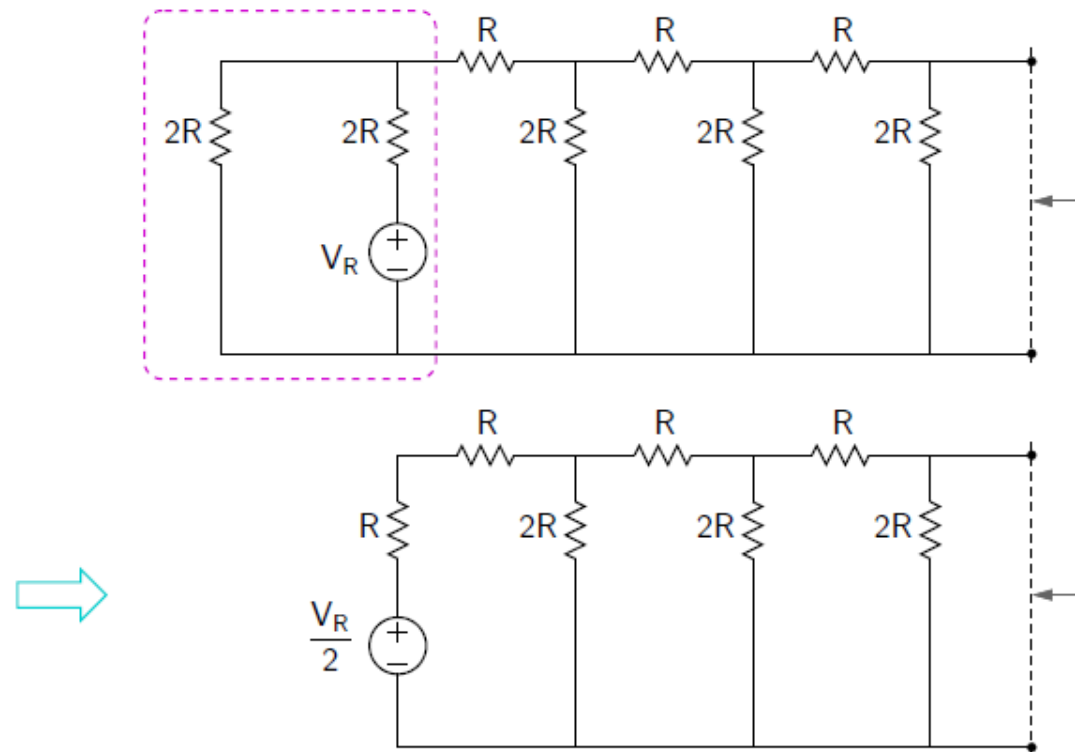
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$





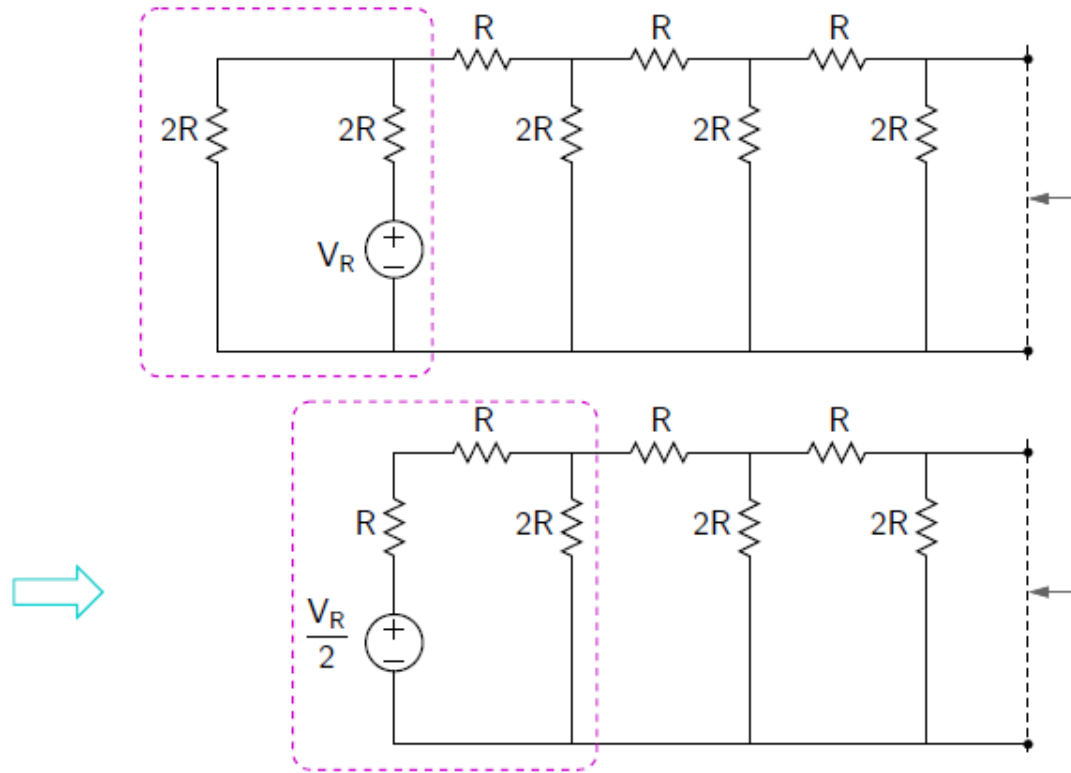
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$



   
## R-2R ladder network: $V_{Th}$ for $S_0 = 1$



   
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$


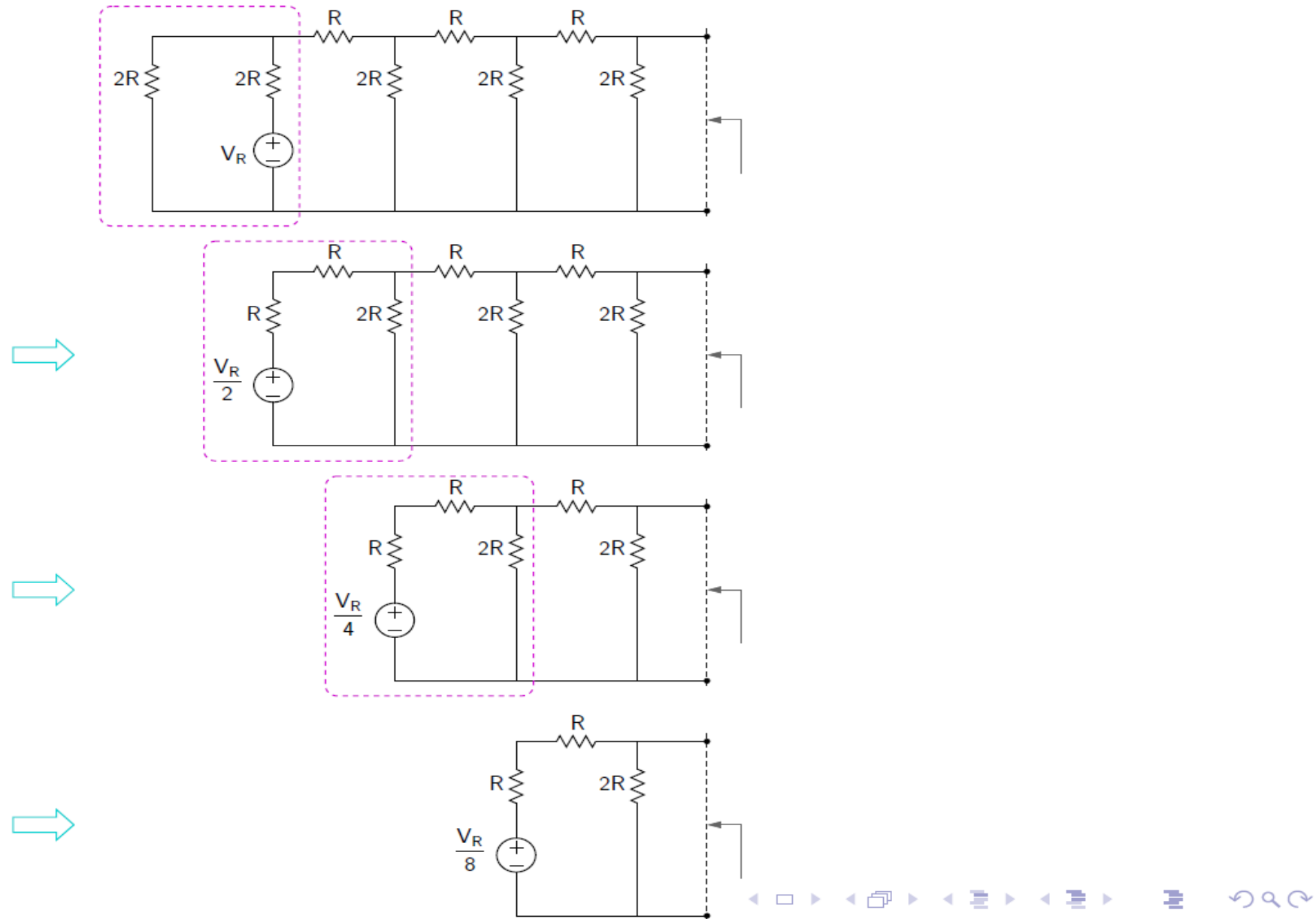
## R-2R ladder network: $V_{Th}$ for $S_0 = 1$



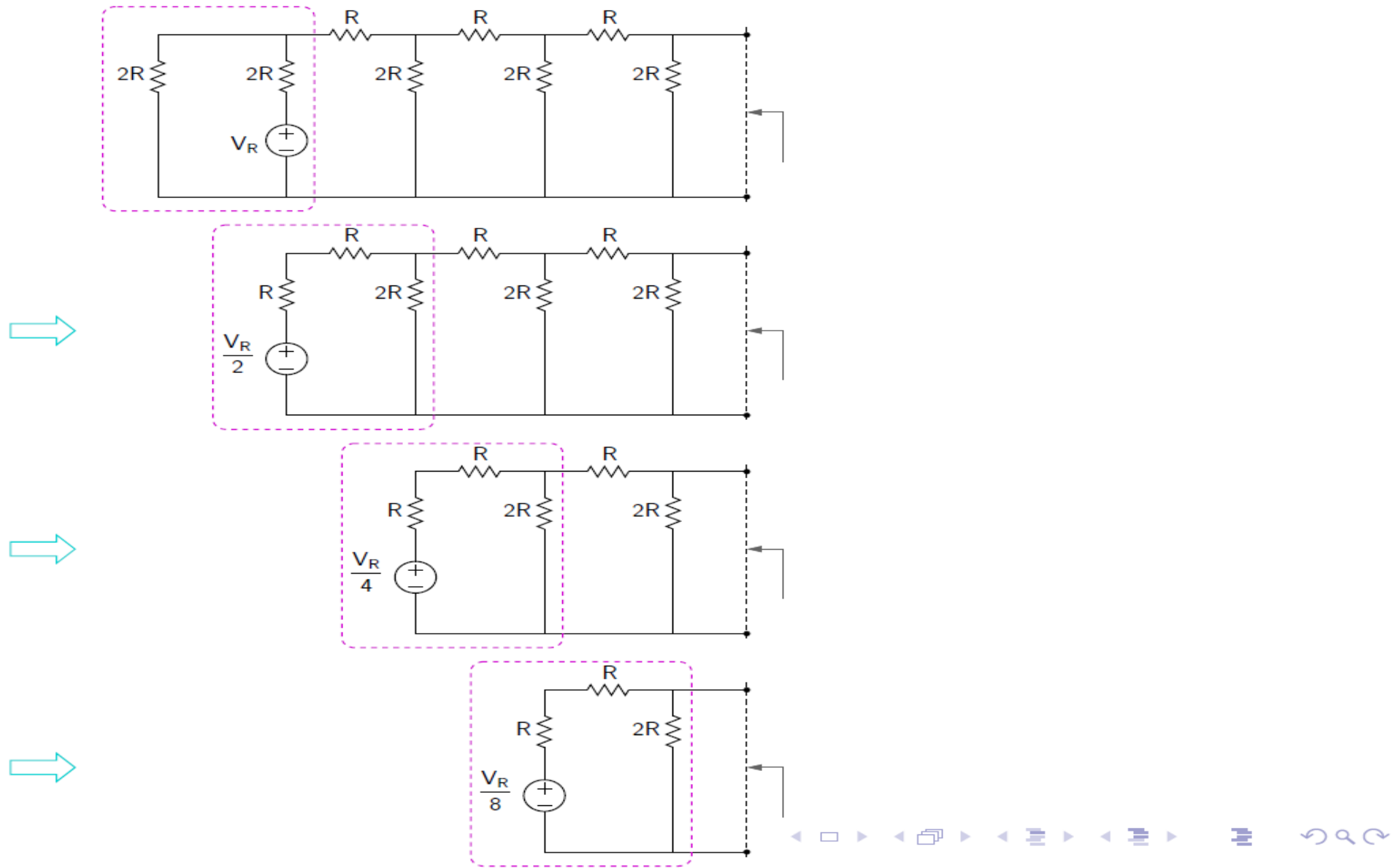
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$






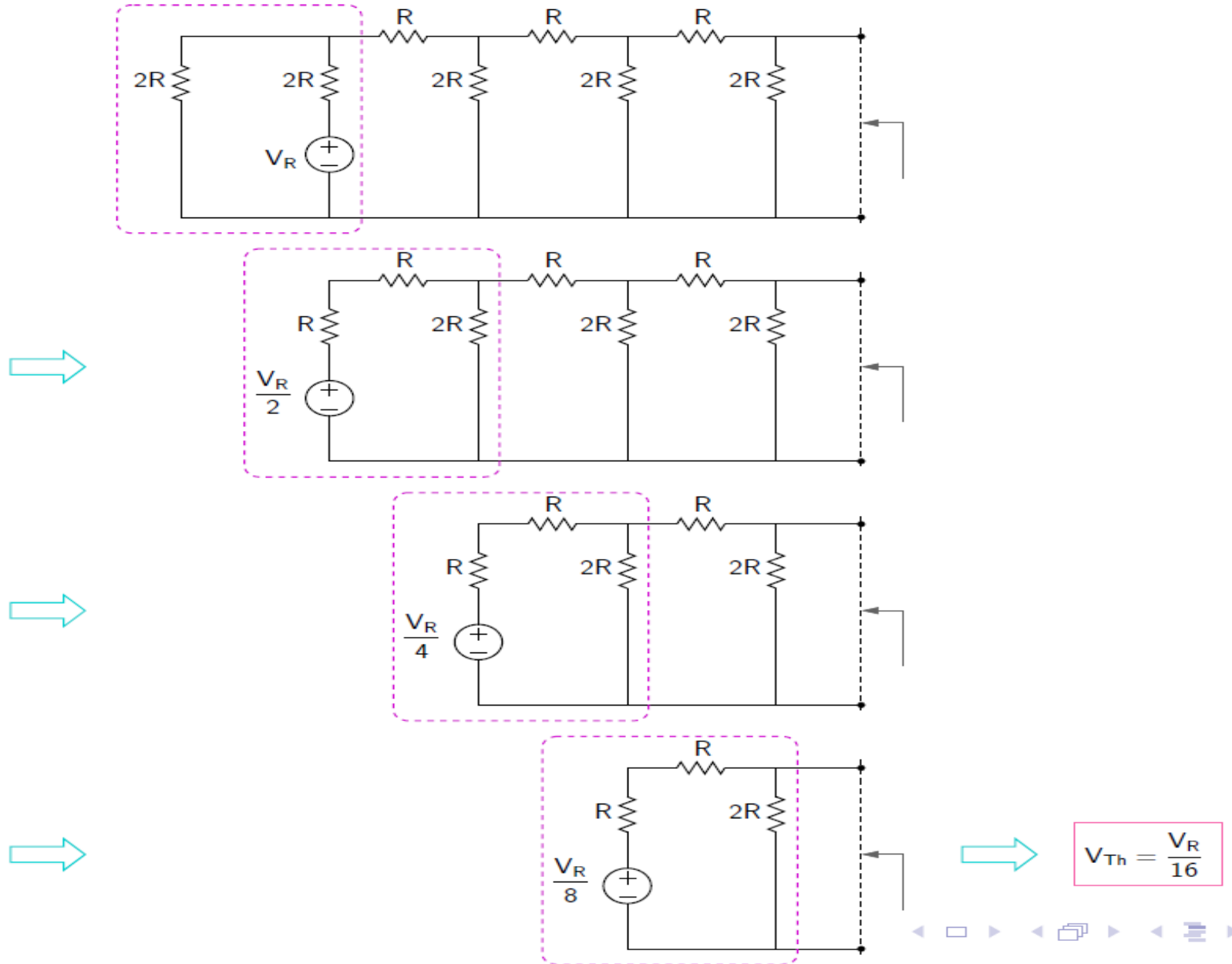
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$



 
R-2R ladder network:  $V_{Th}$  for  $S_1 = 1$




 
R-2R ladder network:  $V_{Th}$  for  $S_1 = 1$


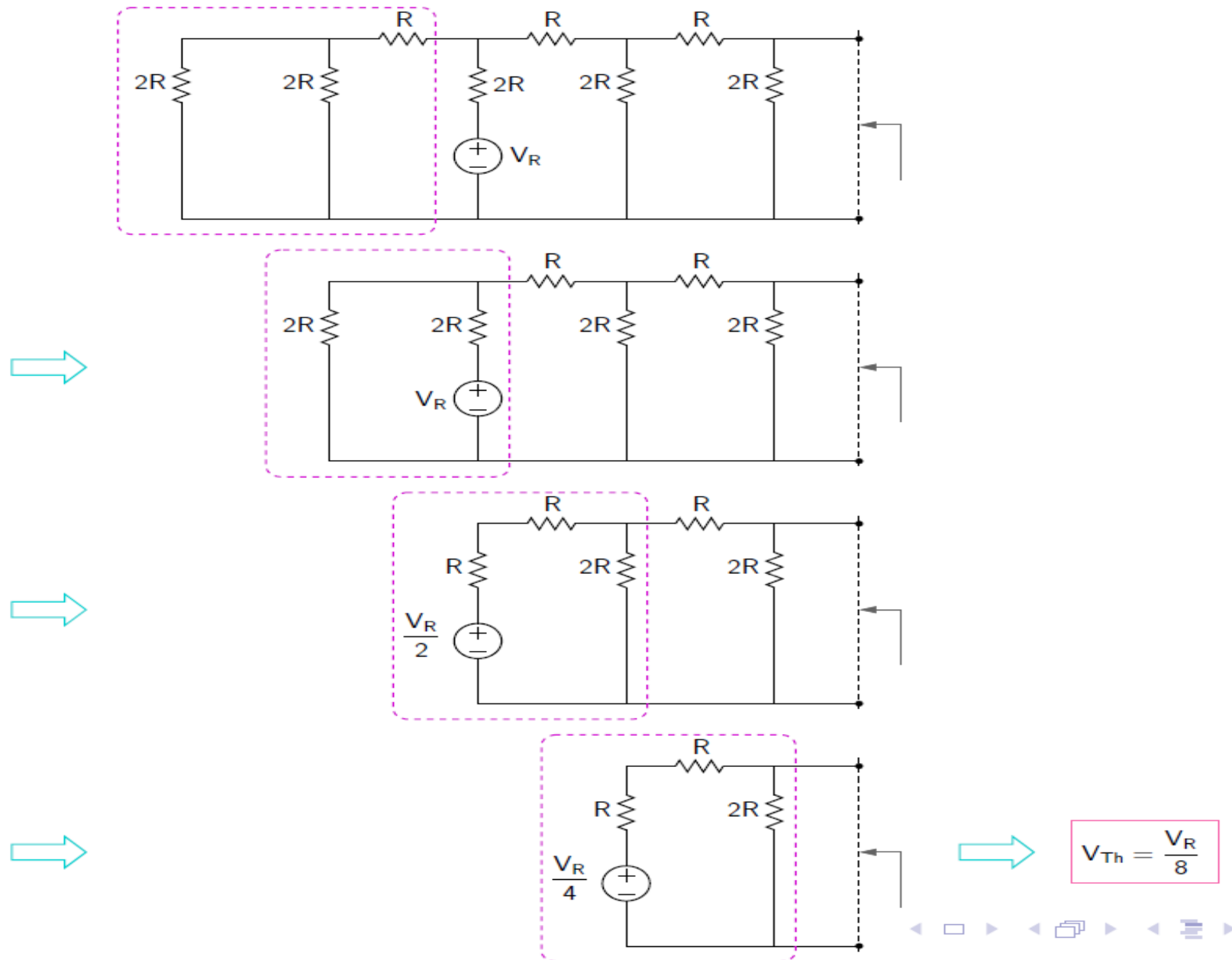
# R-2R ladder network: $V_{Th}$ for $S_1 = 1$



  
# R-2R ladder network: $V_{Th}$ for $S_3 = 1$




$$V_{Th} = \frac{V_R}{2}$$
 
## R-2R ladder network: $R_{Th}$ and $V_{Th}$



- \*  $R_{Th} = R$ .
- \*  $V_{Th} = V_{Th}^{(S_0)} + V_{Th}^{(S_1)} + V_{Th}^{(S_2)} + V_{Th}^{(S_3)}$   
$$= \frac{V_R}{16} \left[ S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3 \right] .$$
- \* We can use the  $R$ - $2R$  ladder network and an Op Amp to make up a DAC  $\rightarrow$  next slide.

## DAC with R-2R ladder

 

$$* V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{16} \left[ S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3 \right] .$$

$$* \text{ For an } N\text{-bit DAC, } V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_0^{N-1} S_k 2^k .$$



- \* 6- to 20-bit DACs based on the R-2R ladder network are commercially available in monolithic form (single chip).
- \* Bipolar, CMOS, or BiCMOS technology is used for these DACs.

# Lecture 27

EC103





## DAC: settling time

 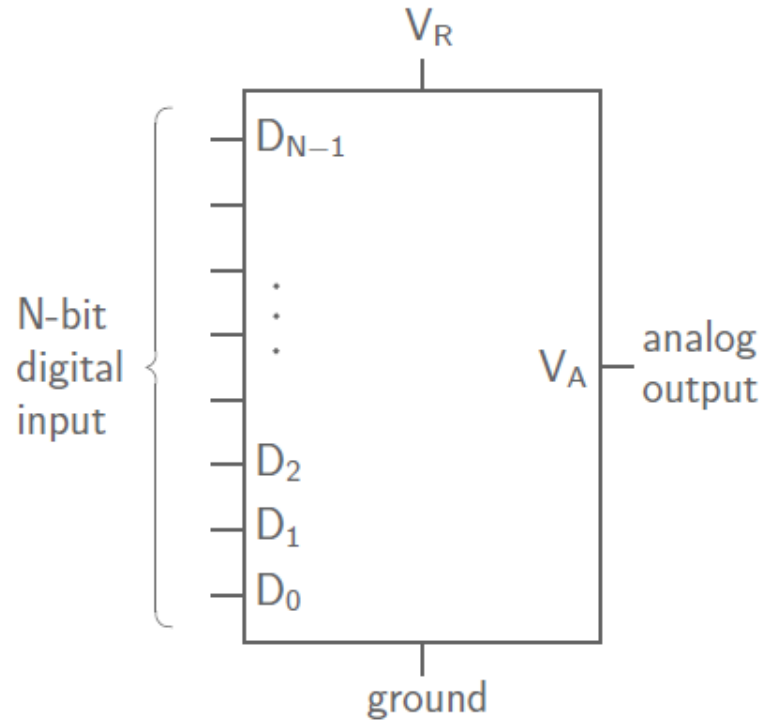

- \* When there is a change in the input binary number, the output  $V_A$  takes a finite time to settle to the new value.

## DAC: settling time

 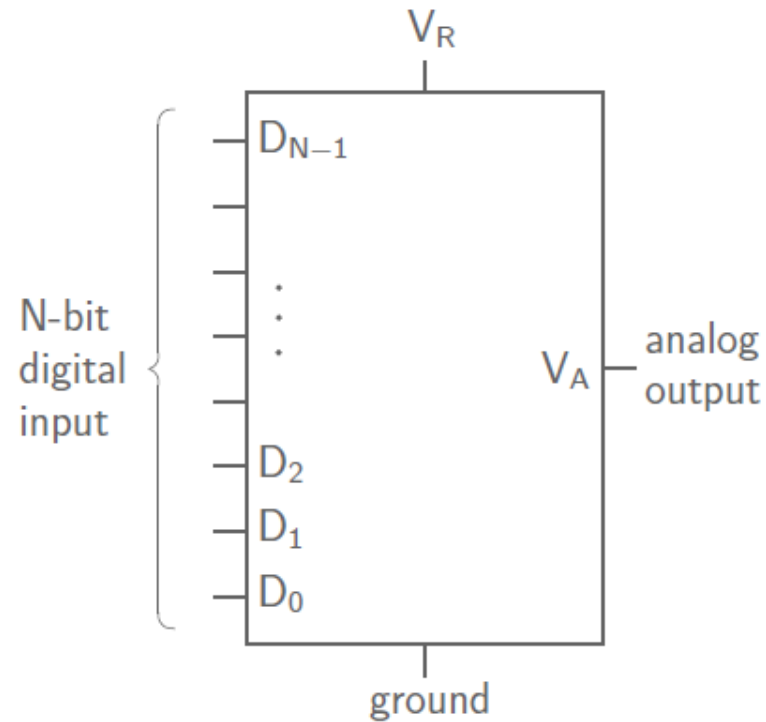

- \* When there is a change in the input binary number, the output  $V_A$  takes a finite time to settle to the new value.
- \* The finite settling time arises because of stray capacitances and switching delays of the semiconductor devices used within the DAC chip.



# DAC: Resolution:

- The resolution of a DAC is the reciprocal of the maximum number of discrete steps in the output.
- Resolution, of course, is dependent on the number of input bits.
- For example, a 4-bit DAC has a resolution of one part in fifteen, i.e.,  $1/15$ . That is  $100/15\% = 6.67\%$ .
- The total number of discrete steps equals to  $2^n - 1$ , where  $n$  is the number of bits.
- Resolution can also be expressed as the number of bits that are converted.


# DAC: Accuracy

- Accuracy is a comparison of the actual output of a DAC with the expected output.
- It is expressed as a percentage of a full-scale, or maximum, output voltage.
- For example, if a DAC has a full-scale output of 10 V, and the accuracy is  $\pm 0.1\%$ , then the maximum error for any output voltage is  $10\text{V} \times 0.001 = 10\text{ mV}$ .
- Ideally, the accuracy should be no worse than  $\pm 0.5$  of an LSB.
- For a 8-bit converter, the LSB is 0.39% of the full scale. The accuracy should be approximately  $\pm 0.2\%$ .

# ADC: introduction

 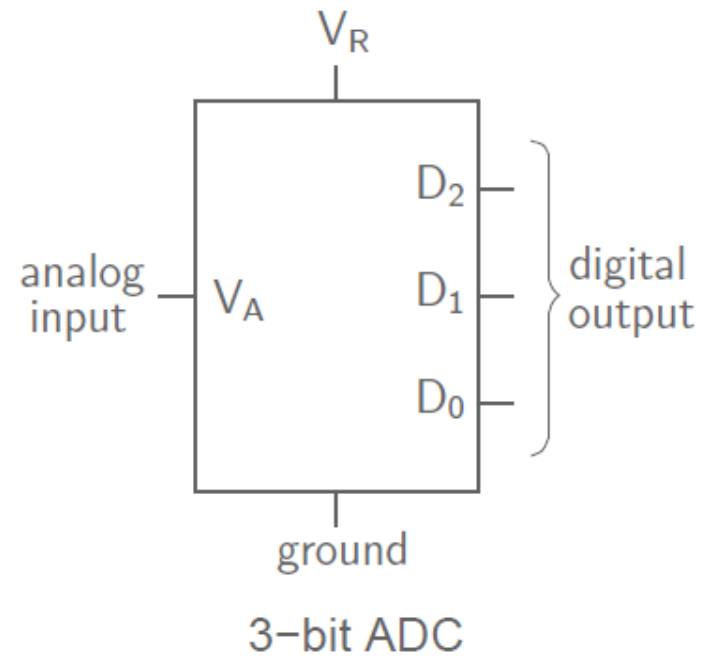


## ADC: introduction

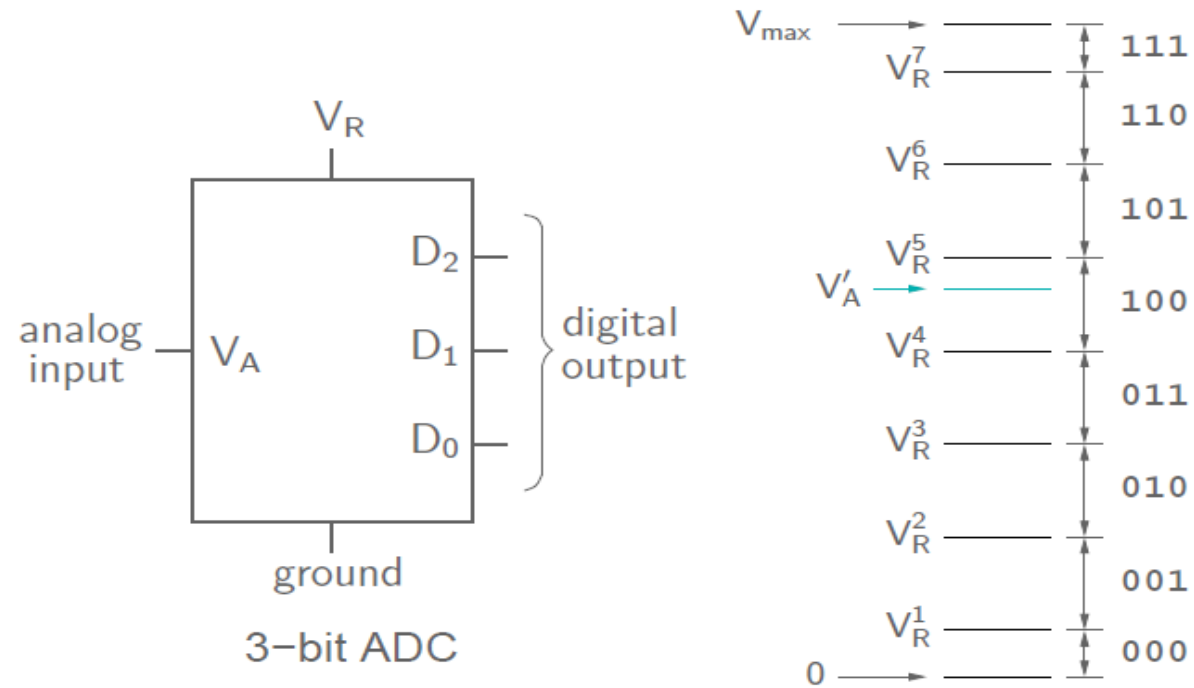


- \* If the input  $V_A$  is in the range  $V_R^k < V_A < V_R^{k+1}$ , the output is the binary number corresponding to the integer  $k$ . For example, for  $V_A = V'_A$ , the output is 100.

## ADC: introduction

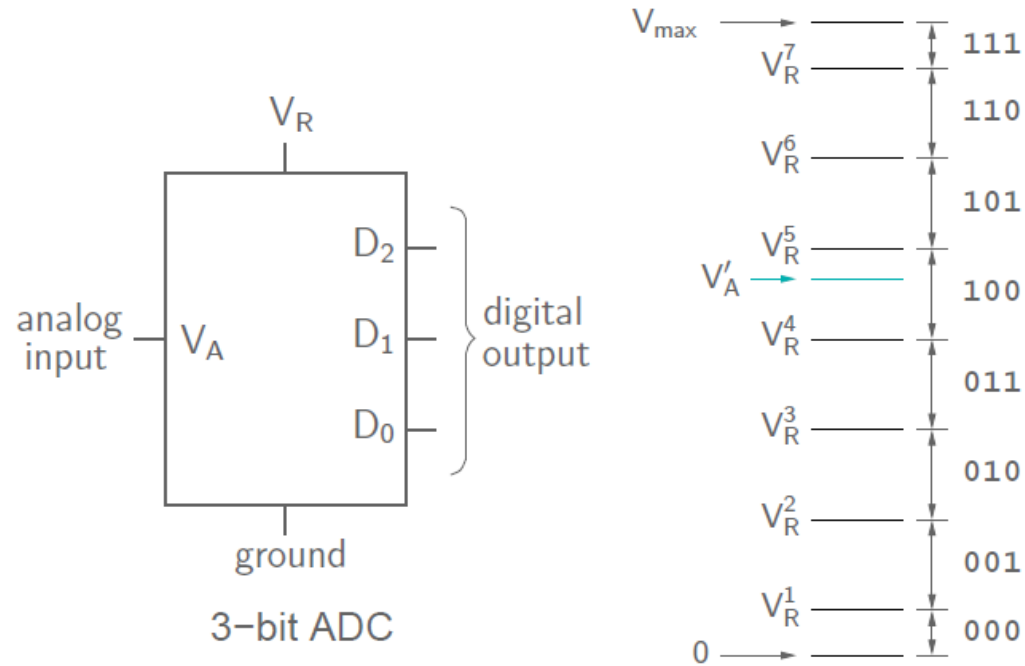

- \* If the input  $V_A$  is in the range  $V_R^k < V_A < V_R^{k+1}$ , the output is the binary number corresponding to the integer  $k$ . For example, for  $V_A = V'_A$ , the output is 100.
- \* We may think of each voltage interval (corresponding to 000, 001, etc.) as a "bin." In the above example, the input voltage  $V'_A$  falls in the 100 bin; therefore, the output of the ADC would be 100.


## ADC: introduction

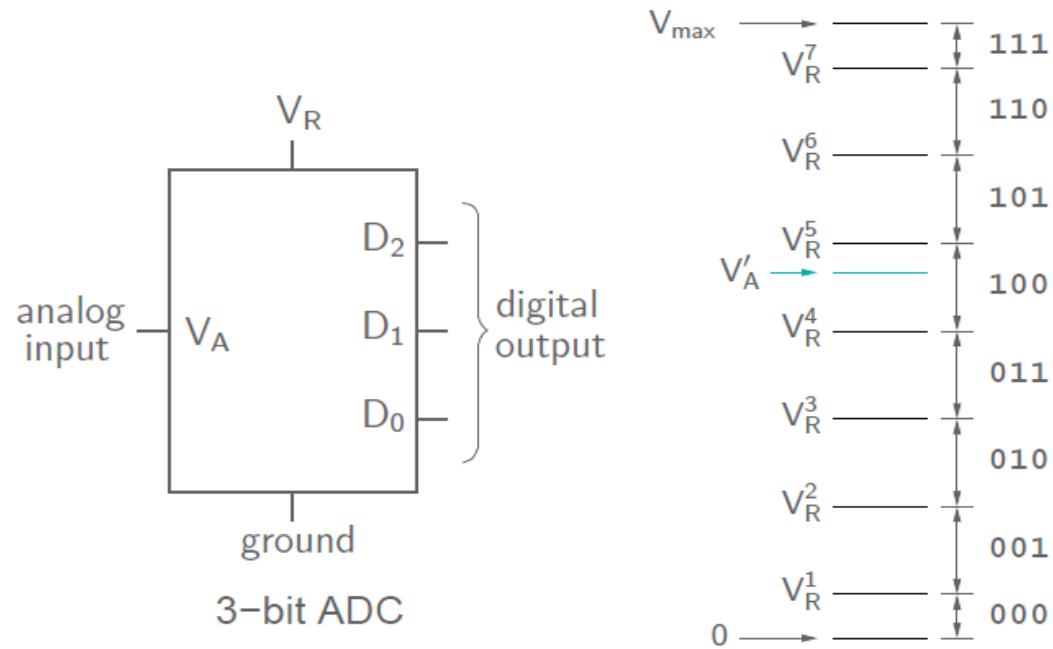

- \* If the input  $V_A$  is in the range  $V_R^k < V_A < V_R^{k+1}$ , the output is the binary number corresponding to the integer  $k$ . For example, for  $V_A = V'_A$ , the output is 100.
- \* We may think of each voltage interval (corresponding to 000, 001, etc.) as a "bin." In the above example, the input voltage  $V'_A$  falls in the 100 bin; therefore, the output of the ADC would be 100.
- \* Note that, for an N-bit ADC, there would be  $2^N$  bins.




## ADC: introduction

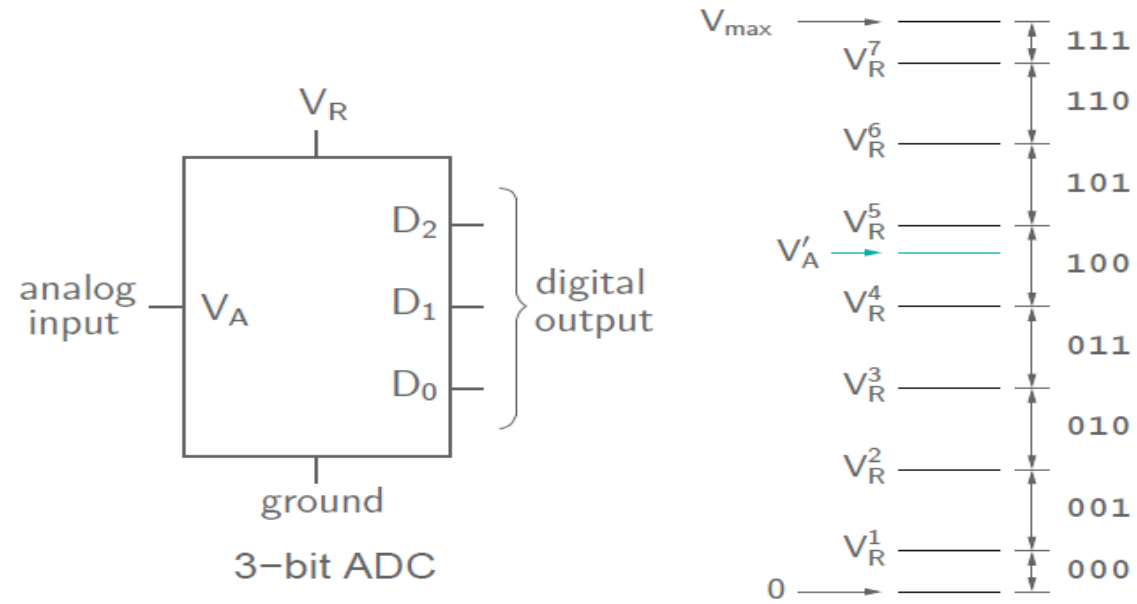

\* The basic idea behind an ADC is simple:


## ADC: introduction

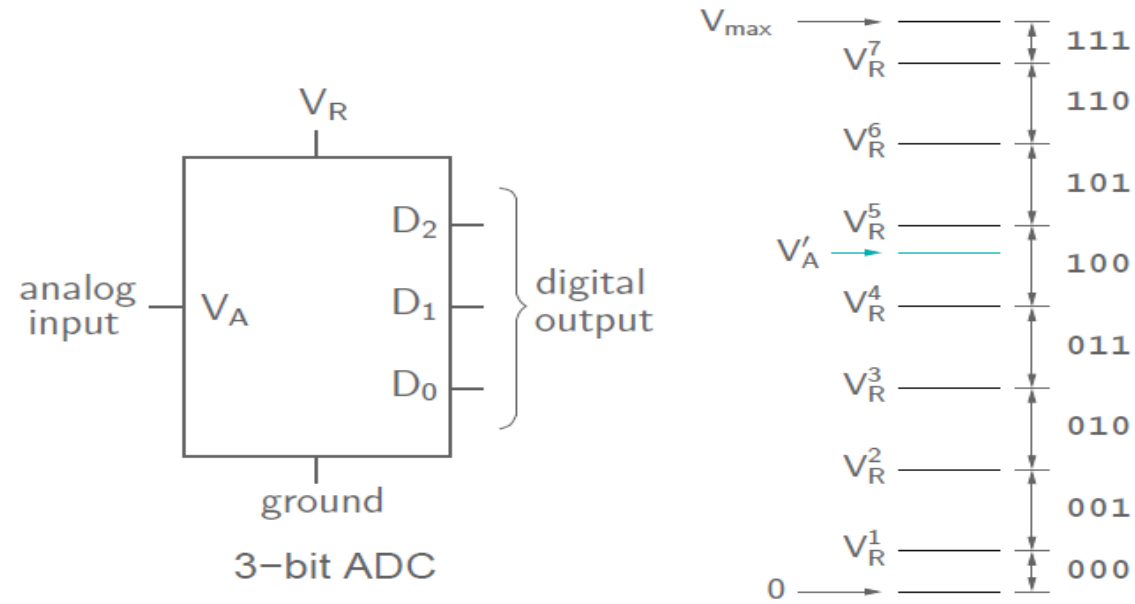

\* The basic idea behind an ADC is simple:

- Generate reference voltages  $V_R^1$ ,  $V_R^2$ , etc.


## ADC: introduction

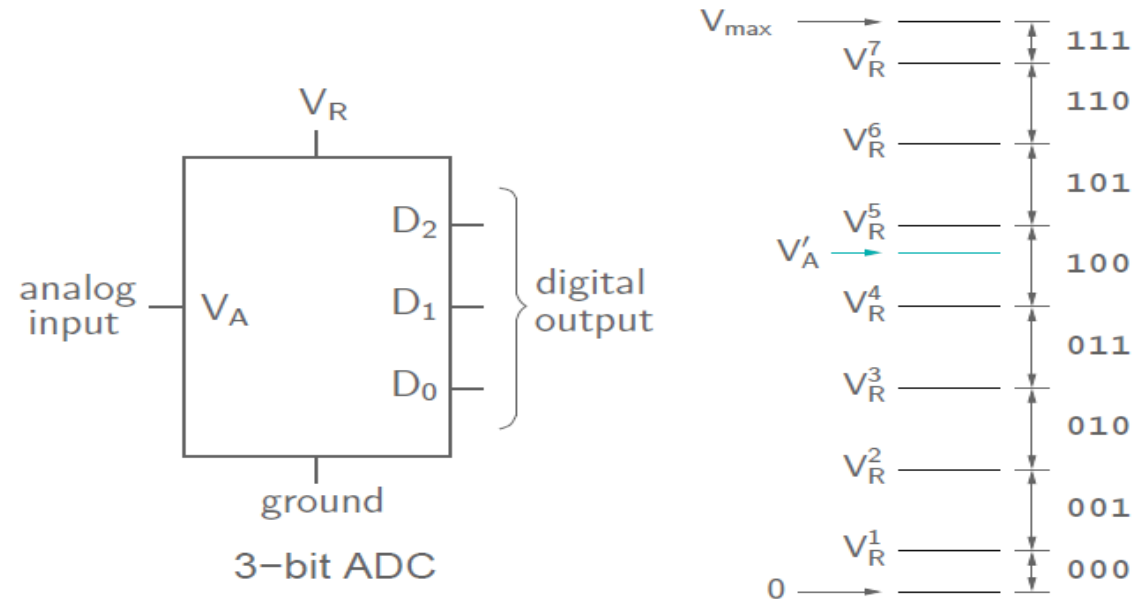

\* The basic idea behind an ADC is simple:

- Generate reference voltages  $V_R^1, V_R^2$ , etc.
- Compare the input  $V_A$  with each of  $V_R^i$  to figure out which bin it belongs to.


## ADC: introduction

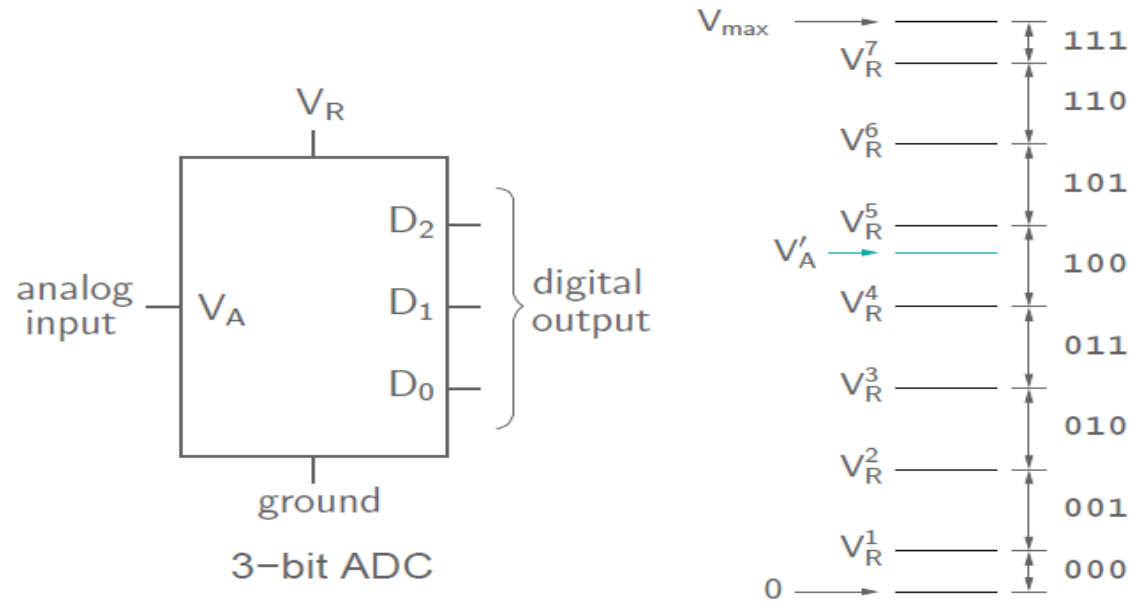

\* The basic idea behind an ADC is simple:

- Generate reference voltages  $V_R^1, V_R^2$ , etc.
- Compare the input  $V_A$  with each of  $V_R^i$  to figure out which bin it belongs to.
- If  $V_A$  belongs to bin  $k$  (i.e.,  $V_R^k < V_A < V_R^{k+1}$ ), convert  $k$  to the binary format.

## ADC: introduction



 


\* The basic idea behind an ADC is simple:


- Generate reference voltages  $V_R^1, V_R^2$ , etc.
- Compare the input  $V_A$  with each of  $V_R^i$  to figure out which bin it belongs to.
- If  $V_A$  belongs to bin  $k$  (i.e.,  $V_R^k < V_A < V_R^{k+1}$ ), convert  $k$  to the binary format.

\* A "parallel" ADC does exactly that → next slide.

## 3-bit parallel (flash) ADC

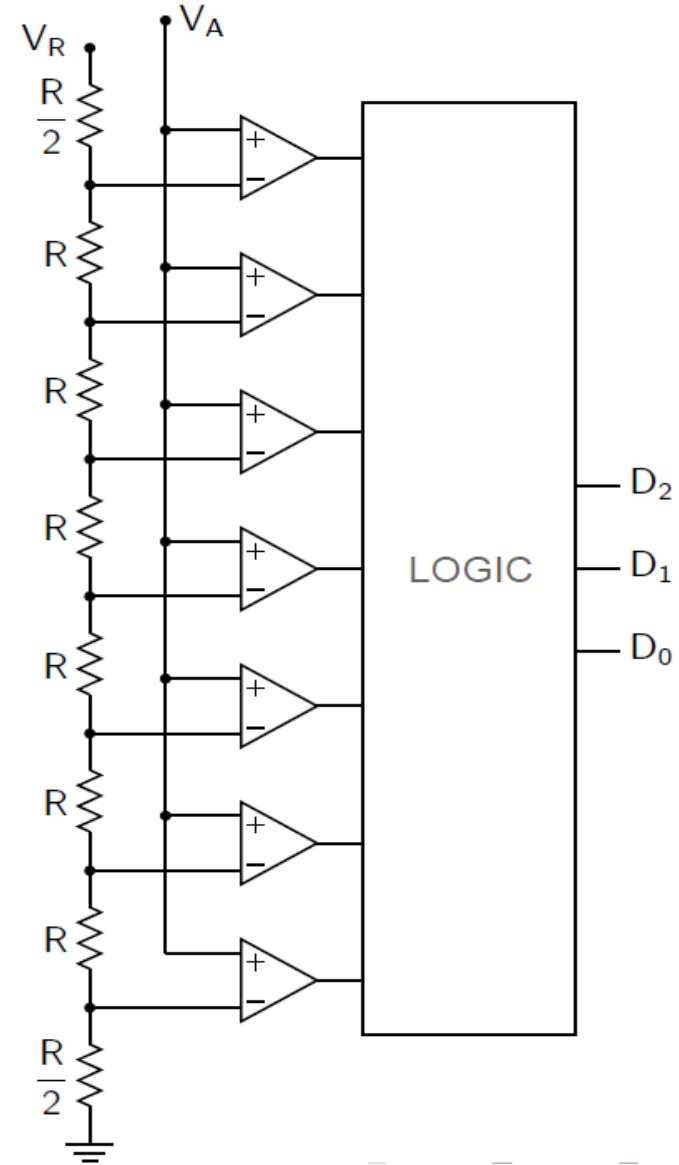  


## 3-bit parallel (flash) ADC

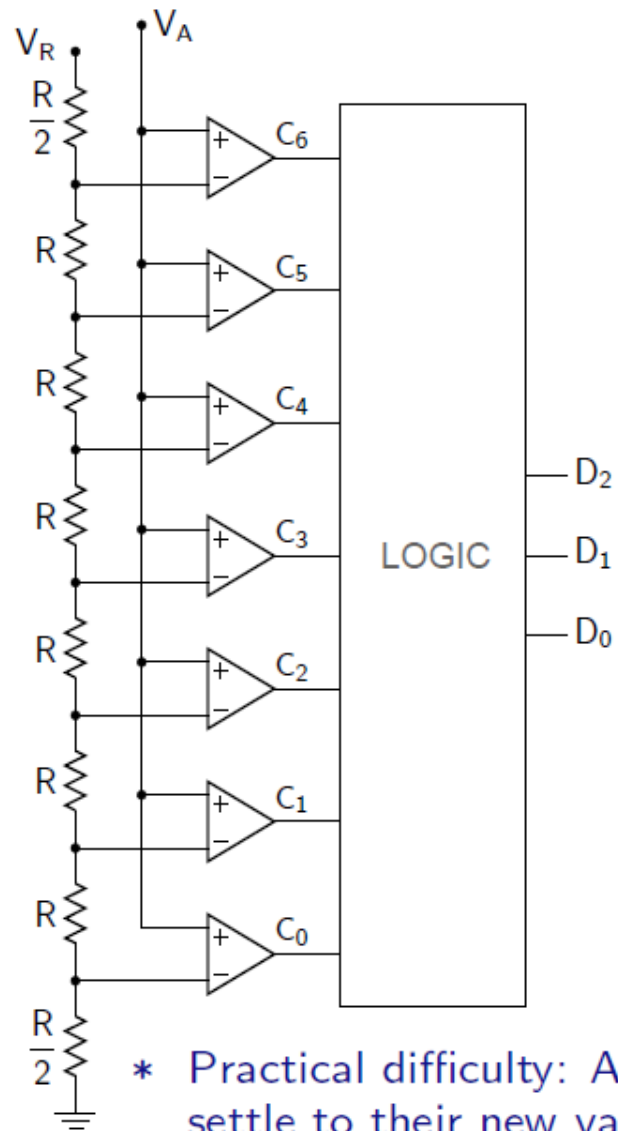

- \* Practical difficulty: As the input changes, the comparator outputs ( $C_0$ ,  $C_1$ , etc.) may not settle to their new values at the same time.  
→ ADC output will depend on when we sample it.



## 3-bit parallel (flash) ADC

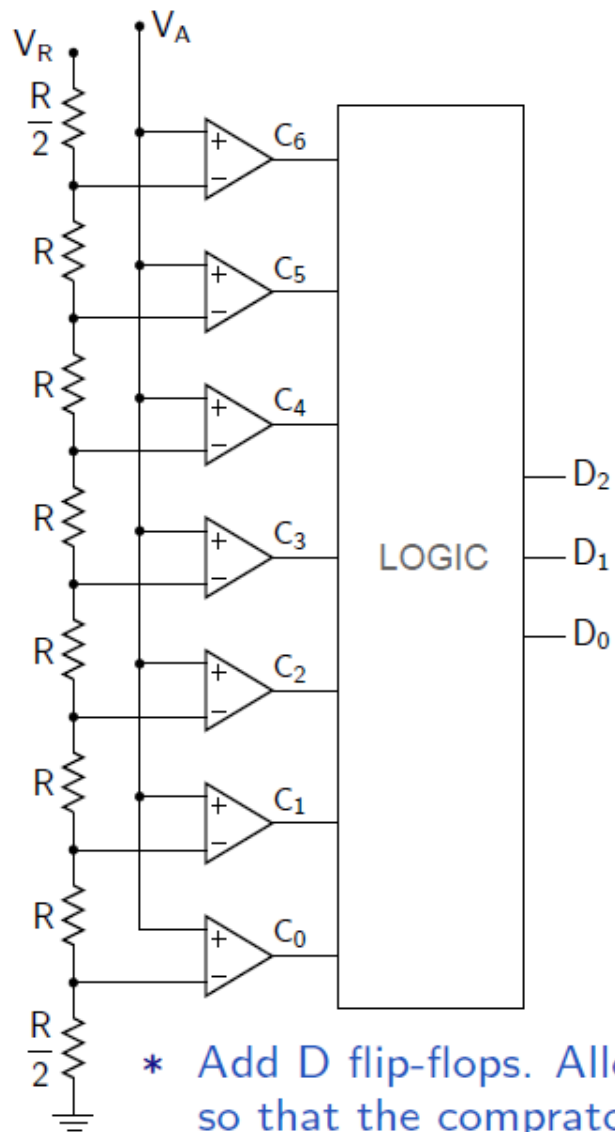

\* Add D flip-flops. Allow sufficient time (between the change in  $V_A$  and the active clock edge) so that the comparator outputs have already settled to their new values before they get latched in.



## 3-bit parallel (flash) ADC

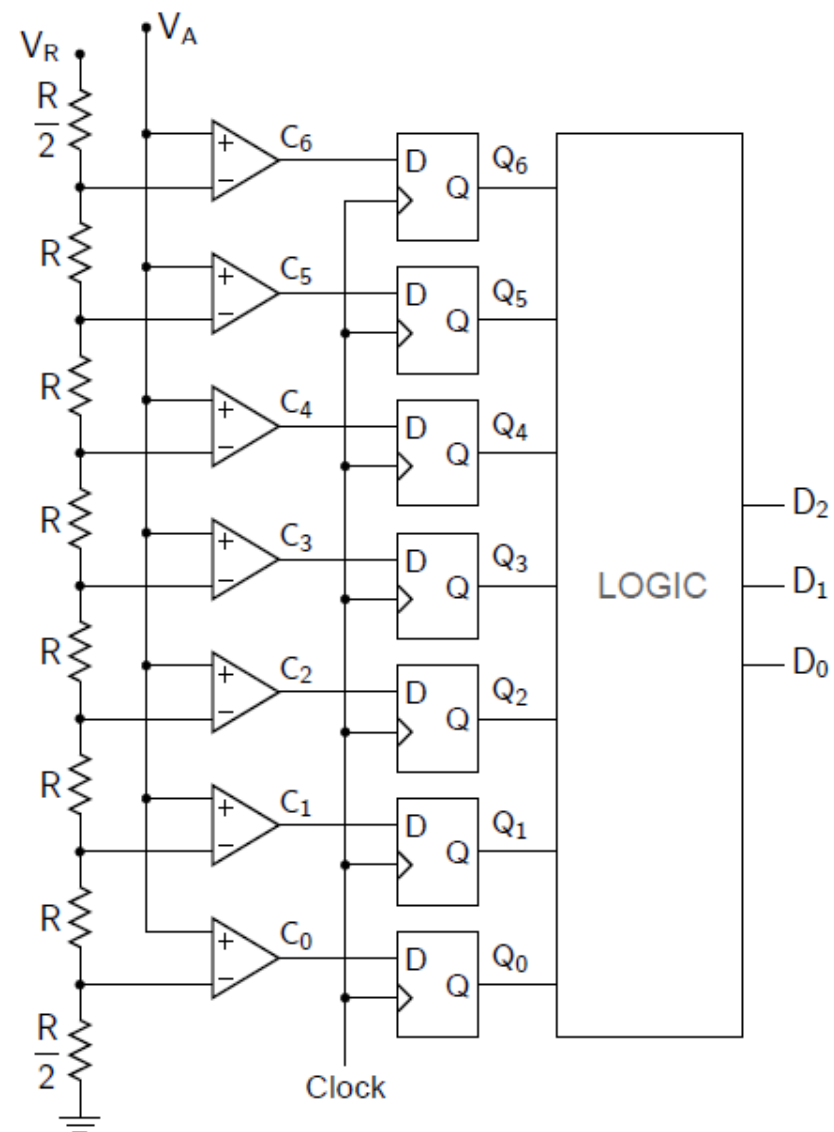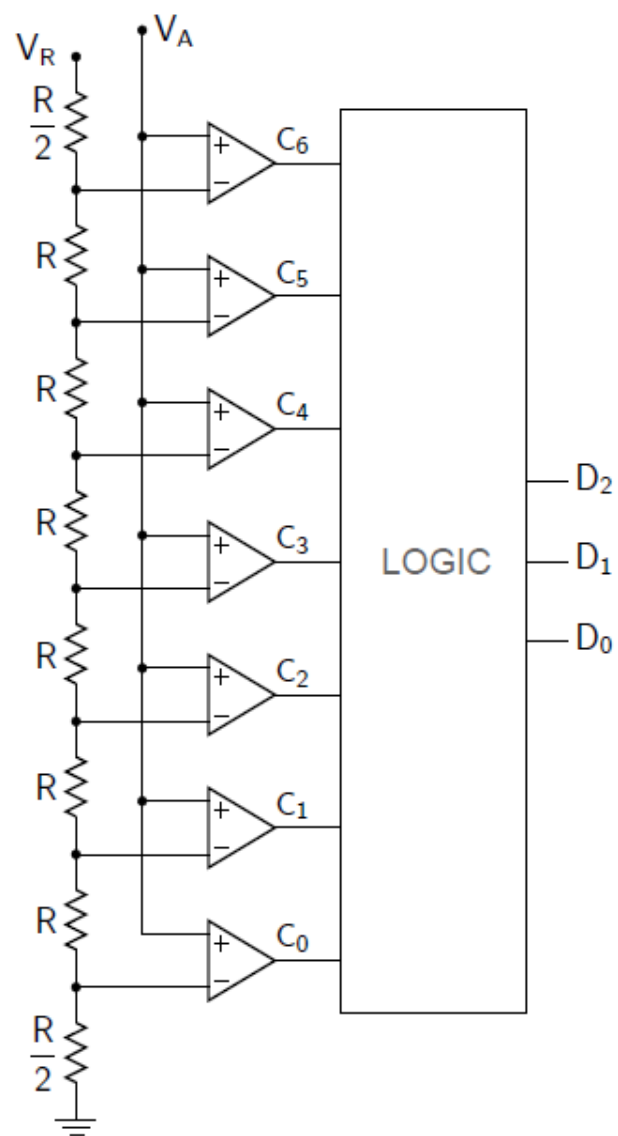

## Parallel (flash) ADC

- \* In the parallel (flash) ADC, the conversion gets done “in parallel,” since all comparators operate on the same input voltage.


## Parallel (flash) ADC

- \* In the parallel (flash) ADC, the conversion gets done “in parallel,” since all comparators operate on the same input voltage.
- \* Conversion time is governed only by the comparator response time → fast conversion (hence the name “flash” converter).
- \* Flash ADCs to handle 500 million analog samples per second are commercially available.




## Parallel (flash) ADC

- \* In the parallel (flash) ADC, the conversion gets done “in parallel,” since all comparators operate on the same input voltage.
- \* Conversion time is governed only by the comparator response time → fast conversion (hence the name “flash” converter).
- \* Flash ADCs to handle 500 million analog samples per second are commercially available.
- \*  $2^N$  comparators are required for N-bit ADC → generally limited to 8 bits.
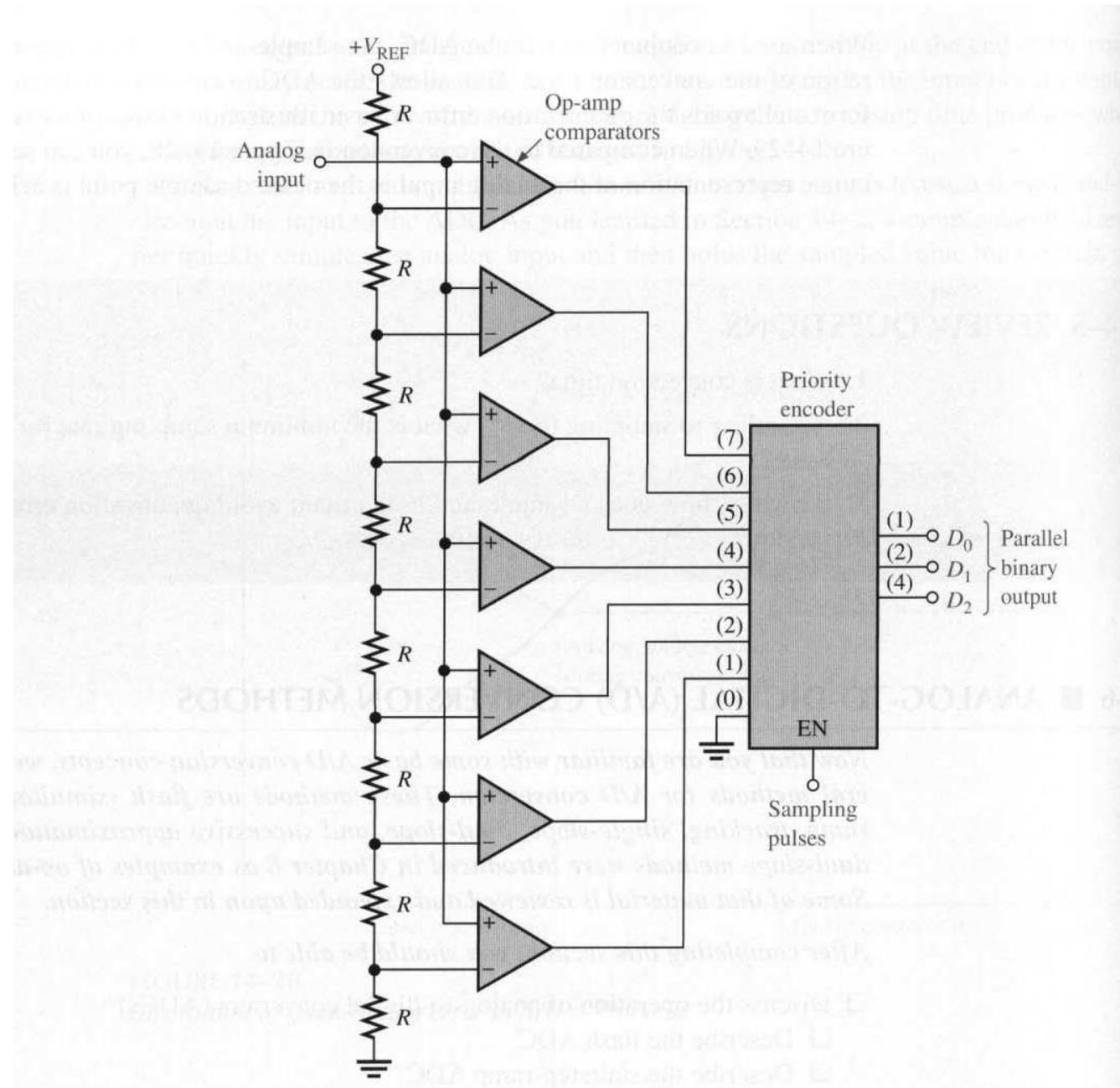
## Alternative Structure for a 3-bit Parallel (Flash) ADC




## ADC: sampling of input signal

 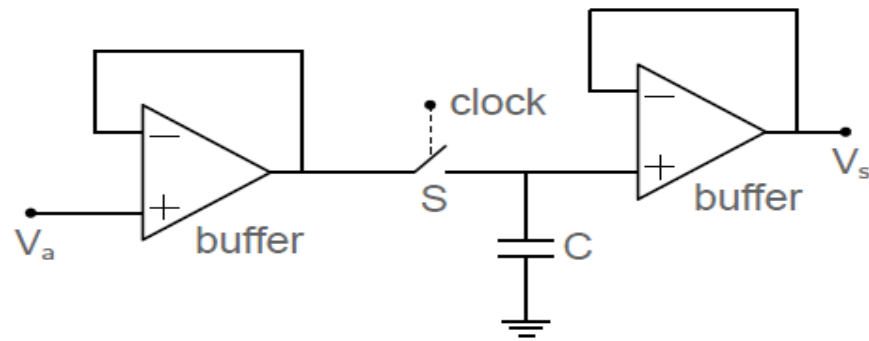 


- \* An ADC typically operates on a “sampled” input signal ( $V_s(t)$  in the figure) which is derived from the continuously varying input signal ( $V_a(t)$  in the figure) with a “sample-and-hold” (S/H) circuit.
- \* The S/H circuit samples the input signal  $V_a(t)$  at uniform intervals of duration  $T_c$ , the clock period.
- \* When the clock goes high, switch  $S$  (e.g., a FET or a CMOS pass gate) is closed, and the capacitor  $C$  gets charged to the signal voltage at that time. When the clock goes low, switch  $S$  is turned off, and  $C$  holds the voltage constant, as desired.

# Successive Approximation ADC

 

- \* Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
  - Start with  $D_3D_2D_1D_0 = 0000$ ,  $I = 3$ .


# Successive Approximation ADC

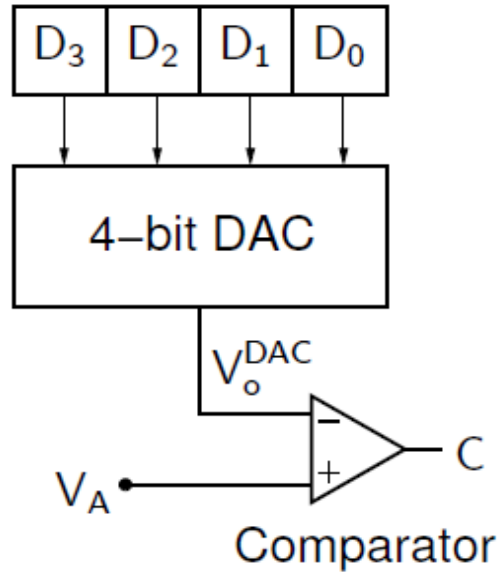

- \* Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
  - Start with  $D_3D_2D_1D_0 = 0000$ ,  $I = 3$ .
  - Set  $D[I] = 1$  (keep other bits unchanged).




# Successive Approximation ADC

 


- \* Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
  - Start with  $D_3D_2D_1D_0 = 0000$ ,  $I = 3$ .
  - Set  $D[I] = 1$  (keep other bits unchanged).
  - If  $V_o^{DAC} > V_A$  (i.e.,  $C = 0$ ), set  $D[I] = 0$ ; else, keep  $D[I] = 1$ .

# Successive Approximation ADC

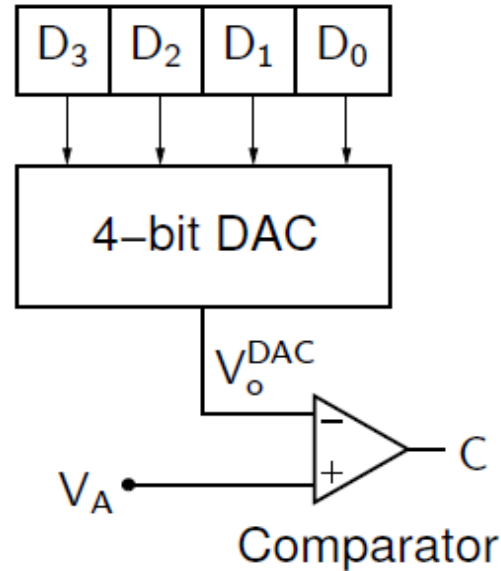


- \* Suppose we have a 4-bit DAC. We can use it to perform A-to-D conversion by successively setting the four bits as follows.
  - Start with  $D_3D_2D_1D_0 = 0000$ ,  $I = 3$ .
  - Set  $D[I] = 1$  (keep other bits unchanged).
  - If  $V_o^{DAC} > V_A$  (i.e.,  $C = 0$ ), set  $D[I] = 0$ ; else, keep  $D[I] = 1$ .
  - $I \leftarrow I - 1$ ; go to step 1.

# Successive Approximation ADC

 


- \* At the end of four steps, the digital output is given by  $D_3D_2D_1D_0$ .  
Example → next slide.

# Successive Approximation ADC

 


\* At the end of the 5<sup>th</sup> step, we know that the input voltage corresponds to 10110.

# Successive Approximation ADC

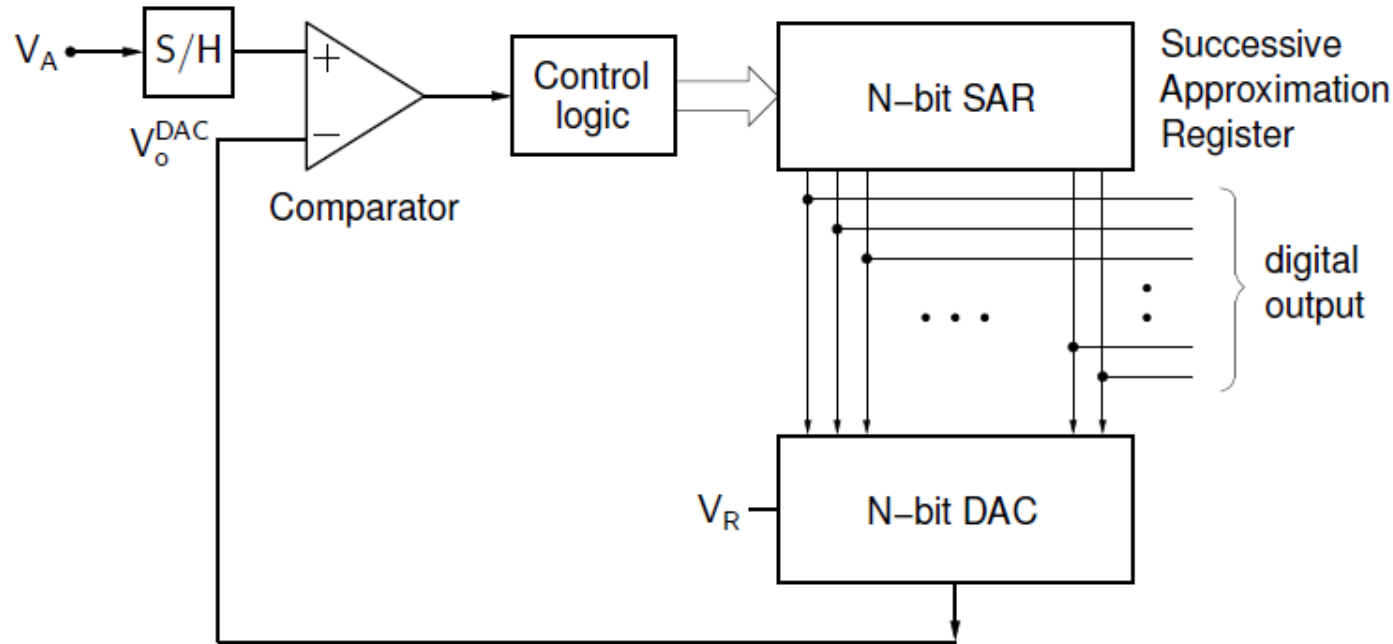



- \* Each step (setting SAR bits, comparison of  $V_A$  and  $V_o^{DAC}$ ) is performed in one clock cycle  
→ conversion time is  $N$  cycles, irrespective of the input voltage value  $V_A$ .
- \* S. A. ADCs with built-in or external S/H (sample-and-hold) are available for 8- to 16-bit resolution and conversion times of a few  $\mu\text{sec}$  to tens of  $\mu\text{sec}$ .
- \* Useful for medium-speed applications such as speech transmission with PCM.

# Counting ADC

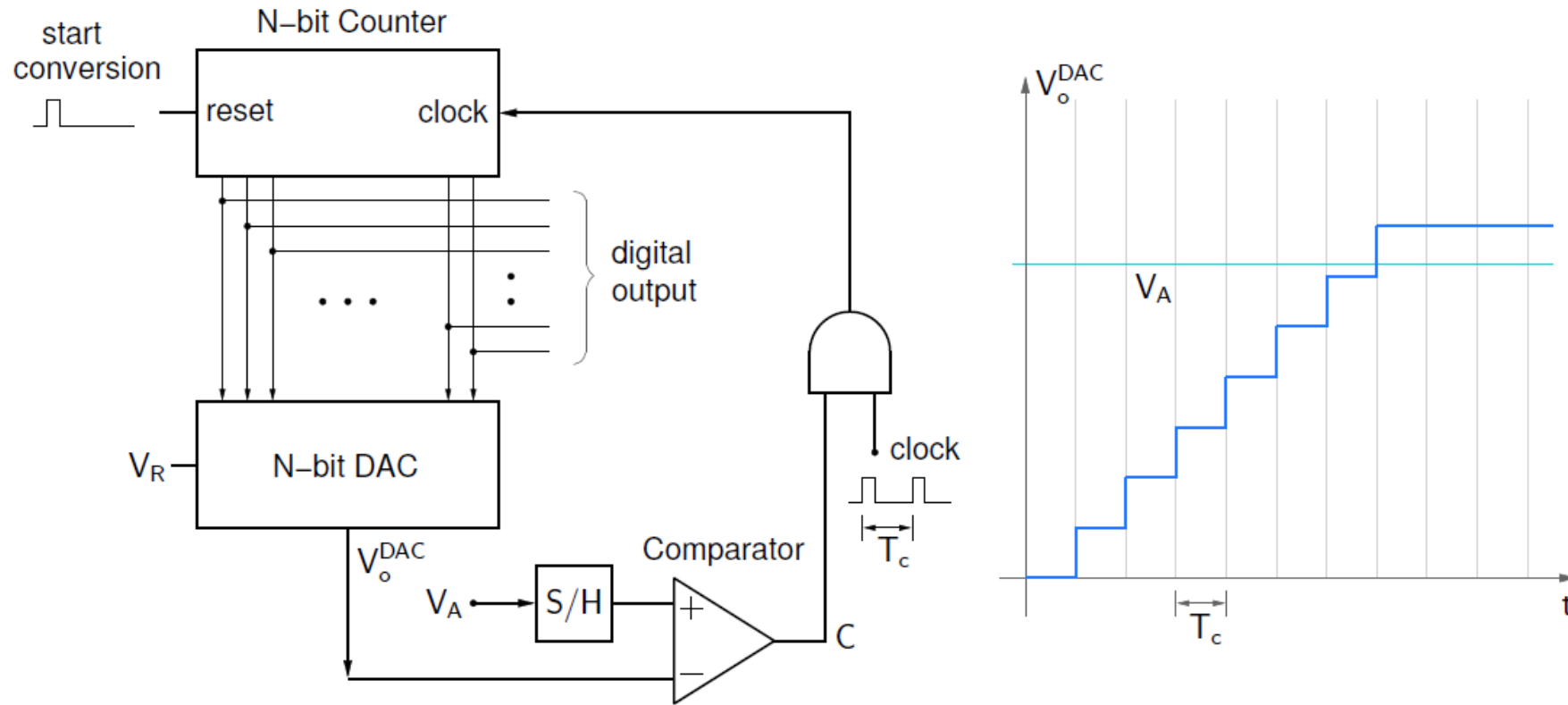

- \* The “start conversion” signal clears the counter; counting begins, and  $V_o^{DAC}$  increases with each clock cycle.
- \* When  $V_o^{DAC}$  exceeds  $V_A$ ,  $C$  becomes 0, and counting stops.
- \* Simple scheme, but (a) conversion time depends on  $V_A$ , (b) slow (takes  $2^N$  clock cycles in the worst case) → tracking ADC (next slide)

# Tracking ADC

 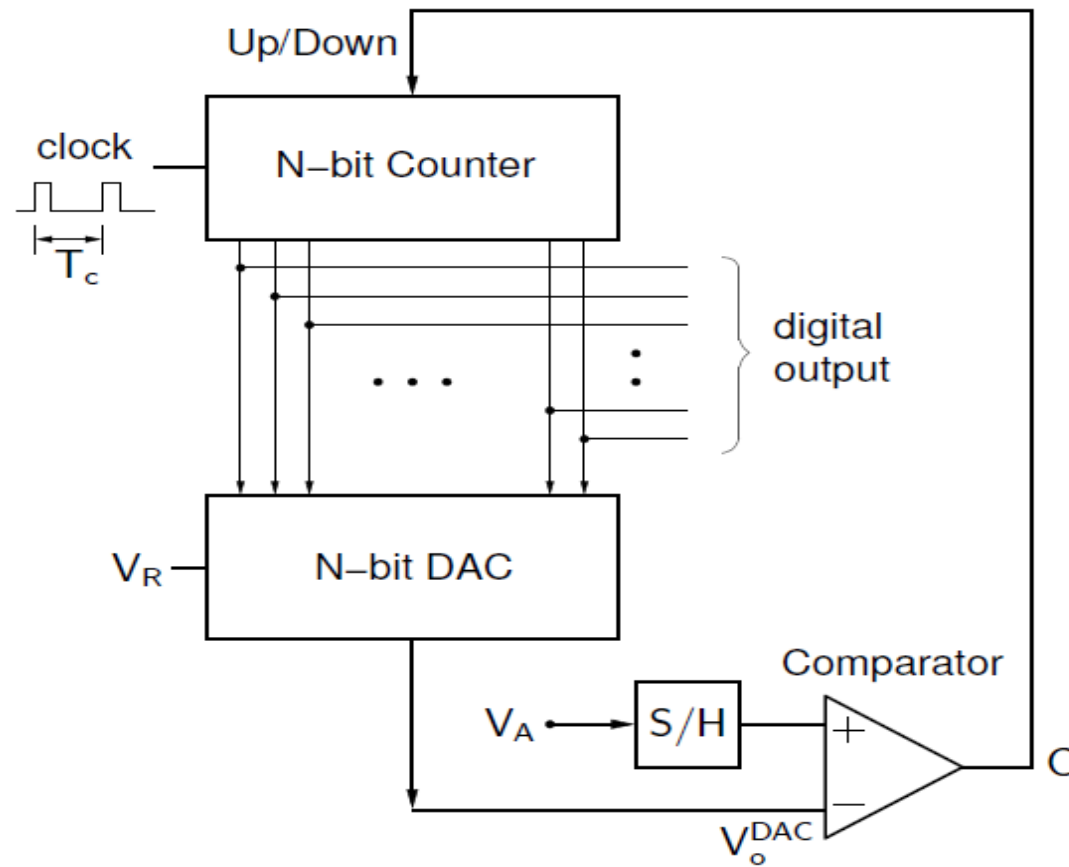

- \* The counter counts up if  $V_o^{DAC} < V_A$ ; else, it counts down.
- \* If  $V_A$  changes, the counter does not need to start from 000...0, so the conversion time is less than that required by a counting ADC.
- \* used in low-cost, low-speed applications, e.g., measuring output from a temperature sensor or a strain gauge