
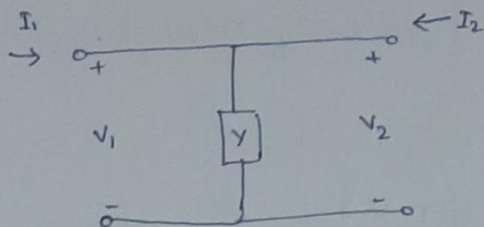


ABCD parameter for Shunt Admittance

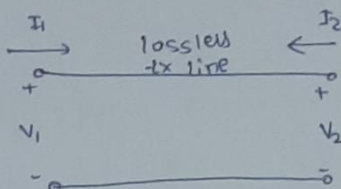


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$




$$\begin{bmatrix} \cos \beta l & j Z_0 \sin \beta l \\ j Y_0 \sin \beta l & \cos \beta l \end{bmatrix}$$

e.g.

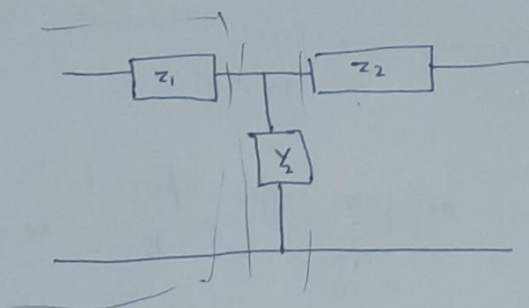


A x
B Ω
C V
D x

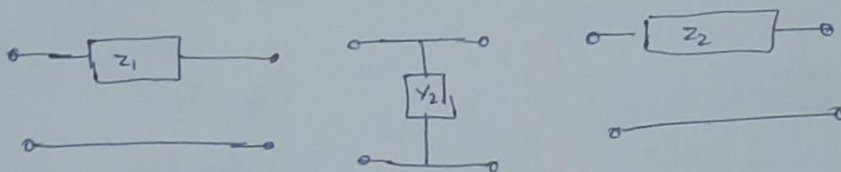

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \times \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \times \begin{bmatrix} A_3 & B_3 \\ C_3 & D_3 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \times \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix} \times \begin{bmatrix} 1 & Z_2 \\ 0 & 1 \end{bmatrix}$$
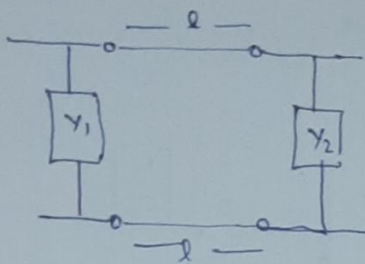
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + Z_1 Y_2 & Z_1 + Z_2 + Z_1 Y_2 Z_2 \\ Y_2 & 1 + Z_1 Y_2 \end{bmatrix} \quad \text{if } Z_1 = Z_2$$



lossless fx wire

$$\begin{bmatrix} \cos \beta l & j Z_0 \sin \beta l \\ j Y_0 \sin \beta l & \cos \beta l \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ Y_1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix}$$

ABCD \rightarrow S-parameter.

S-parameter

S_{11} - reflection co-efficient at Port 1

S_{22} - " " " " port 2

S_{12} - measure of gain or loss from Port 1 to Port 2

S_{21} - " " " " Port 2 to Port 1

for N-port Network

$$\begin{aligned} b_1 &= S_{11} a_1 + S_{12} a_2 + \dots + S_{1N} a_N \\ b_2 &= S_{21} a_1 + S_{22} a_2 + \dots + S_{2N} a_N \\ &\vdots \\ b_N &= S_{N1} a_1 + S_{N2} a_2 + \dots + S_{NN} a_N \end{aligned}$$

Properties

For Symmetrical Network;

" loss-less network:

$$[S] = [S]^T$$

$$[S] [S]^H = I$$

1. Unitary Property : $\sum_{i=1}^N S_{ij} S_{ij}^* = \sum_{i=1}^N |S_{ij}|^2 = 1 ;$

for $j=1$ $|S_{11}|^2 + |S_{21}|^2 + \dots + |S_{N1}|^2 = 1.$

$$\left| \frac{b_1}{a_1} \right|^2 + \left| \frac{b_2}{a_1} \right|^2 + \dots + \left| \frac{b_N}{a_1} \right|^2 = 1$$

$$\underbrace{|b_1|^2 + |b_2|^2 + \dots + |b_N|^2}_{\text{Sum of outgoing power}} = |a_1|^2$$

Input power

2) Orthogonal property :

$$\sum_{i=1}^N S_{ij} S_{ik}^* = 0 \quad \text{where } j \neq k$$

for $j=1 \neq k=2$, $S_{11} S_{12}^* + S_{21} S_{22}^* + \dots + S_{N1} S_{N2}^* = 0.$

To check

Network reciprocal

$$[S]^T = [S]$$

lossless

-(unitary property)

Return loss at port 1?

$$RL = -20 \log(|S_{11}|)$$

Insertion loss and phase delay between port 2 and port 1

$$RL = -20 \log(|S_{23}|)$$

phase delay = -phase of S_{23} .

ABCD to S-parameter

Y-adding
Ø YOKAD
Y / 10

$$S_{11} = \frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$$

$$S_{12} = \frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$$

$$S_{21} = \frac{2}{A + B/Z_0 + CZ_0 + D}$$

$$S_{22} = \frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$$

$$Z_{in} = Z + Z_0$$


$$\Gamma_{in} = S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{Z}{2Z_0 + Z}$$

6 $|S_{11}|^2 + |S_{21}|^2 = 1$ valid only if Z is lossless.


$$|S_{21}|^2 = 1 - |S_{11}|^2 = 1 - \left| \frac{Z}{2Z_0 + Z} \right|^2$$

$$S_{21} = \frac{2Z_0}{2Z_0 + Z}$$

Power Divider and coupler

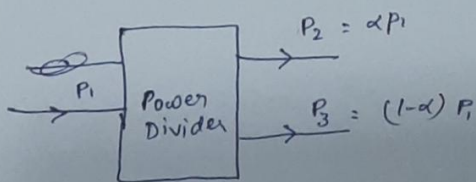

Power division
(1-Terminal)

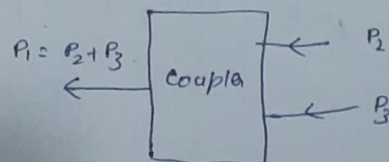

Power combination
(2-Terminal)

A three port network cannot be lossless, reciprocal and matched at all ports.

or

It is not possible to construct a perfectly matched, lossless, reciprocal 3-port junction. At least one of the reflection coefficients must be different from zero in the reciprocal case,

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

Reciprocal $S = S^T$

$$\begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

Unitary :-

$$R_1: |S_{12}|^2 + |S_{13}|^2 = 1$$

$$R_2: |S_{12}|^2 + |S_{23}|^2 = 1$$

$$R_3: |S_{13}|^2 + |S_{23}|^2 = 1$$

Orthogonal :-

$$S_{13} S_{23}^* = 0$$

$$S_{12} S_{13}^* = 0$$

$$S_{23} S_{12}^* = 0$$

Assume $S_{13} = 0$

$$S_{23} \neq 0$$

$$S_{12} \neq 0$$

Contradiction in unitary and
orthogonality

Q. check whether it is possible to design a lossless and reciprocal T-junction with two of its ports being matched while third is not matched.

T-joint

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

Assume $S_{11} = 0$, $S_{22} = 0$ (\because Port 1 & 2 is matched)

Reciprocal $[S] = [S]^T$

$$\begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix}$$

Unitary:

R1: $|S_{12}|^2 + |S_{13}|^2 = 1$

R2: $|S_{12}|^2 + |S_{23}|^2 = 1$

R3: $|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 = 1$

Orthogonal

$\checkmark \checkmark$ $S_{13} S_{23}^* = 0$

\checkmark $S_{12}^* S_{13} + S_{23}^* S_{33} = 0$

$S_{23}^* S_{12} + S_{33}^* S_{13} = 0$

Assume $S_{23} = 0$
 $S_{13} = 0$




$S_{12} = 1$

$S_{33} = 1$

$$S = \begin{bmatrix} 0 & 1 & 0 \\ 1 & 0 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

S-matrix of 3-port H-plane Tee

TE₁₀ - dominant mode

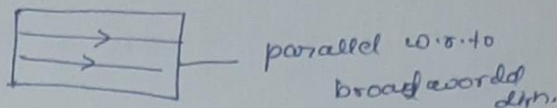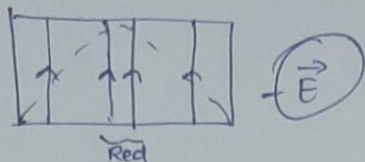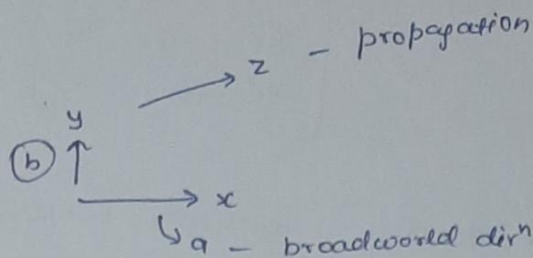


- practically dominant mode can propagate.

No. of modes
can propagate
- cut-off
freq.


Transmission coefficient S_{12} S_{21}
cut-off frequency (After 0 dB)
freq at which line cross.

TE₁₀ →
E → $\pm \pi$ to 'a'
H → $\pm \pi$ to 'a'


Side-arm (H-direction)
→ H-plane Tee

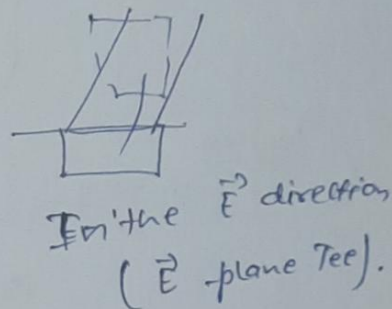

H-plane Tee

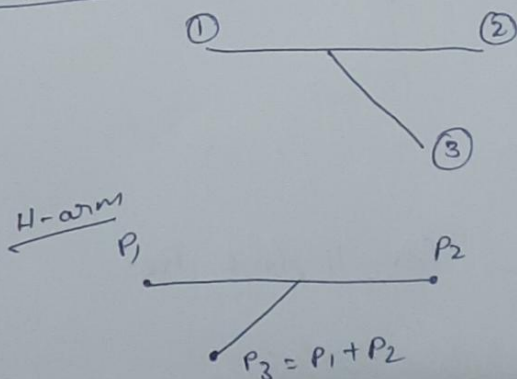

E-arm

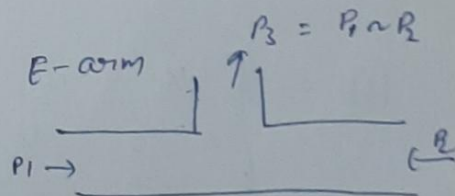

H-plane Tee

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

- junction scattering coefficient S_{13} and S_{23} must be equal to the plane of symmetry

$$\therefore S_{13} = S_{23}$$

- From symmetry property, $S_{ij} = S_{ji}$

$$\therefore S_{12} = S_{21}, S_{31} = S_{13}, S_{23} = S_{32} = S_{13}$$

- considering port 3 is perfectly matched, reflection coefficient $S_{33} = 0$.

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & S_{22} & S_{13} \\ S_{13} & S_{13} & 0 \end{bmatrix}$$

lossless

unitary :-

$$R1: |S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = 1 \quad \text{--- a}$$

$$|S_{12}|^2 + |S_{22}|^2 + |S_{13}|^2 = 1 \quad \text{--- b}$$

$$|S_{13}|^2 + |S_{13}|^2 = 1 \quad \text{--- c}$$

$$\Rightarrow S_{13} = \frac{1}{\sqrt{2}}$$

Apply Ortho

$$[S] = \begin{bmatrix} \frac{1}{2} & -\frac{1}{2} & \frac{1}{\sqrt{2}} \\ -\frac{1}{2} & \frac{1}{2} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & 0 \end{bmatrix} \quad \text{--- for H-plane Tee}$$

$$\{b\} = [S] \{a\}$$

$$b_1 = \frac{a_1}{2} - \frac{a_2}{2} + \frac{a_3}{\sqrt{2}}$$

$$b_2 = -\frac{a_1}{2} + \frac{a_2}{2} + \frac{a_3}{\sqrt{2}}$$

$$b_3 = \frac{a_1}{\sqrt{2}} + \frac{a_2}{\sqrt{2}}$$

as port 3 is input i.e. $a_3 \neq 0$

$$a_1 = 0 \quad a_2 = 0$$

$$b_1 = \frac{a_3}{\sqrt{2}}$$

$$b_2 = \frac{a_3}{\sqrt{2}}$$

$$b_3 = 0$$

$$\begin{aligned} \text{Power gain} &= 10 \log_{10} \left(\frac{P_1}{P_3} \right) \\ &= 10 \log_{10} \left(\frac{P_1}{2P_1} \right) \\ &= \underline{\underline{-3 \text{ dB}}} \end{aligned}$$

- ~~Power coming out~~

Input Impedance

$$Z_A = R_A + jX_A$$

Reflection coefficient

$$\Gamma = \frac{Z_A - Z_0}{Z_A + Z_0}$$

$$VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Transmission Line:

R = series resistance per unit length, for both conductor in Ω/m .

L = " inductance " " " for both conductors in H/m

G = shunt conductance per unit length in S/m

C = shunt capacitance per unit length in F/m

For Sinusoidal Steady-state condition,

$$\frac{dV(z)}{dz} = -(R + j\omega L) I(z)$$

$$\frac{dI(z)}{dz} = -(G + j\omega C) V(z)$$

↓
wave propagation in Tx line.

$$\frac{d^2 V(z)}{dz^2} + \gamma^2 V(z) = 0$$

$$\frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0$$

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

↳ complex propagation constant

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

$e^{-\gamma z}$ - wave propagating in $+z$ dirⁿ

$e^{\gamma z}$ - " " " $-z$ "

$$I(z) = \frac{\gamma}{R + j\omega L} (V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z})$$

$$Z_0 = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\frac{V_0^+ e^{-\gamma z}}{I_0^+} = Z_0 = - \frac{V_0^- e^{\gamma z}}{I_0^-}$$

$$\lambda = \frac{2\pi}{\beta} \quad ; \quad v_p = \frac{\omega}{\beta} = df$$

phase
velocity

ii) Lossless line

$$R=0, G=0$$

$$\boxed{\gamma = j\omega \sqrt{LC}}$$

$$\alpha = 0$$

$$\beta = \omega \sqrt{LC}$$

$$\boxed{\gamma = \alpha + j\beta}$$

$$\boxed{Z_0 = \frac{R + j\omega L}{\gamma} = \frac{j\omega L}{j\omega \sqrt{LC}} = \sqrt{\frac{L}{C}}}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$

$$\boxed{\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega \sqrt{LC}}}$$

$$\boxed{v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}}$$

phase
velocity

$$P_{avg} = \frac{1}{2} \frac{|V_0|^2}{Z_0} (1 - |\Gamma|^2) \quad - \text{Shows that average power flow is constant at any point on the line}$$

$$RL = -20 \log |\Gamma| \text{ dB.}$$

$$\frac{V}{\Gamma} = 0$$

$$P_{avg} = P_{total}$$

$$= \frac{1}{2} \frac{|V_0|^2}{Z_0}$$

$$Z_{in} = \frac{V(-l)}{I(-l)} = \frac{V_0^+ (e^{j\beta l} + \Gamma e^{-j\beta l})}{V_0^+ (e^{j\beta l} - \Gamma e^{-j\beta l})}$$

$$= \frac{1 + \Gamma e^{-2j\beta l}}{1 - \Gamma e^{-2j\beta l}} Z_0$$

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$$

Lossless

$$Z_L = 0$$

$$Z_{in} = j Z_0 \tan \beta l$$

Smith Chart

Voltage reflection coefficient, Γ

$$\Gamma = |\Gamma| e^{j\theta}$$

- Magnitude $|\Gamma|$ is plotted as radius from the centre of the chart
- ' θ ' is measured counterclockwise from right-hand side of horizontal diameter.

$$\bar{Z} = \frac{Z}{Z_0} \quad - \text{normalized Impedance.}$$

$$\Gamma = \frac{\bar{z}_L - 1}{\bar{z}_L + 1} = |\Gamma| e^{j\theta}$$

$$\text{or, } \bar{z}_L = \frac{1 + |\Gamma| e^{j\theta}}{1 - |\Gamma| e^{j\theta}}$$

$$x_L + j x_L = \frac{1 + \Gamma_r + j \Gamma_i}{(1 - \Gamma_r) - j \Gamma_i}$$

$$\Gamma_r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad ; \quad x_L = \frac{2 \Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad \text{--- (2)}$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L} \right)^2 = \left(\frac{1}{x_L} \right)^2$$

Smith chart L.

$$Z_L = 40 + j 70 \Omega$$

$$l = 0.3 \lambda$$


$$Z_0 = 100 \Omega$$

$$\bar{z}_L = \frac{Z_L}{Z_0} = 0.4 + j 0.7$$

Directional Coupler

- consists of two transmission line or waveguides coupled by fringing fields.

i/p	d/p	c/p	iso/p
1	2	3	4
2	1	4	3
3	4	1	2
4	3	2	1

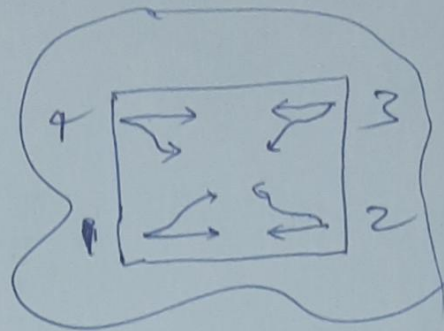

Parameters

(9) Directivity (D)

$$D = 10 \log \frac{P_3}{P_4} \text{ dB}$$

- Ratio of power coupled to the auxiliary arm to the power flowing in the uncoupled auxiliary arm
- expressed in dB.

Coupling factor:-

$$C_{dB} = 10 \log_{10} \frac{i/p}{c/p}$$

Input power → i/p
Coupled power → c/p

$$C_{dB} = 10 \log_{10} \frac{P_1}{P_3}$$

↓
ratio of power (entering) to the power coupled at the output in auxiliary arm.

WR 37


$$a = 7.3 \text{ inch}$$

$$a = 0.9 \text{ inch}$$

two last digit represent

WR 37

dimension of waveguide =

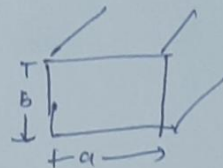

$a = 2b$ TE₁₀ is dominant mode.

Insertion Loss :-



loss arises due to insertion of component over a line. It specifies the total output power from all ports relative to the input power.

$$IL = 10 \log \frac{P_2 + P_3 + P_4}{P_1} \text{ dB.}$$

Isolation

Another way of specifying directivity and it is equal to the sum of directivity and coupling.
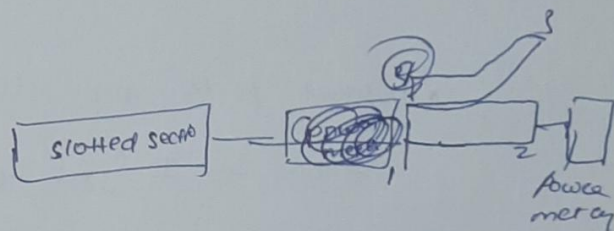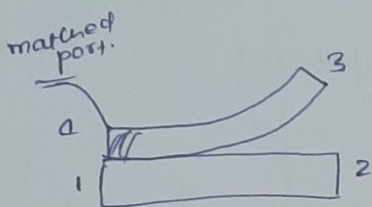
$$Isolation = 10 \log \frac{P_1}{P_4} \text{ dB.}$$



∴ we are measuring power at port 2, all the other ports should be shorted.

S-matrix

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

It is possible to match all ports as it is not
 case in power divider.

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{21} & 0 & S_{23} & S_{24} \\ S_{31} & S_{32} & 0 & S_{34} \\ S_{41} & S_{42} & S_{43} & 0 \end{bmatrix}$$

reciprocal $\Rightarrow [S] = [S]^T$

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix}$$

no power flow from
 port 1 to port 4

S_{41}

Input = 1
 but

Adjacent ports are isolated from input port,

$$S_{14} = S_{23} \neq S_{32} = S_{41} = 0.$$

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix}$$

↓
 Apply unitary and orthogonal property.

$$[S] = \begin{bmatrix} 0 & P & jZ & 0 \\ P & 0 & 0 & jZ \\ jZ & 0 & 0 & P \\ 0 & jZ & P & 0 \end{bmatrix}$$

Bothe hole (Single hole)

Q. The input power = 1mW

$$C = 15 \text{ dB}$$

$$D = 30 \text{ dB}$$

Calculate the power at all port.

$$15 = 10 \log_{10} \frac{10^{-3}}{P_B}$$

$$15 = \frac{+30}{2} \log_{10} P_B$$

$$0.5 = \log_{10} P_B$$

$$P_B = (10)^{0.5}$$

$$= 3.16 \text{ W}$$

$$G_{dBm} = 10 \log_{10} \frac{P}{1 \text{ mW}}$$

Q. $[S] = \begin{bmatrix} 0.2 \angle 0^\circ & 0.6 \angle 90^\circ \\ 0.6 \angle 90^\circ & 0.1 \angle 0^\circ \end{bmatrix}$



(a) Prove that the network is reciprocal but not lossless

(b) Find the return loss at Port 1 when Port-2 is short circuited.

$$[S] = \begin{bmatrix} 0.2 & +j0.6 \\ j0.6 & 0.1 \end{bmatrix}$$

$$RL = -20 \log |1|$$

E-arm

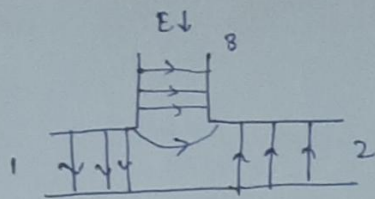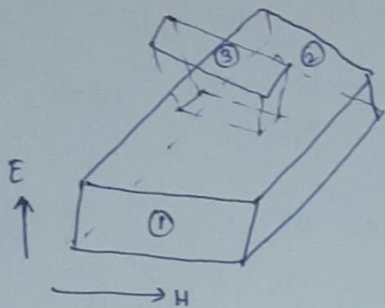

$$S_{13} = -S_{23} \quad \text{[out of phase]}$$

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

Port -3

Input

port 3 is matched the $S_{33} = 0$.

① port 1 & 2 are out of phase

$$S_{13} = -S_{23}$$

② Symmetry property

$$S_{12} = S_{21}, \quad S_{13} = S_{31}, \quad S_{23} = S_{32}$$

Apply unitary

$$[S] = \begin{bmatrix} 1/2 & 1/2 & 1/\sqrt{2} \\ 1/2 & 1/2 & -1/\sqrt{2} \\ 1/\sqrt{2} & -1/\sqrt{2} & 0 \end{bmatrix}$$

$$[b] = [S][a]$$

$$b_1 = 1/2 a_1 + 1/2 a_2 + 1/\sqrt{2} a_3$$

$$b_2 = 1/2 a_1 + 1/2 a_2 - 1/\sqrt{2} a_3$$

$$b_3 = 1/\sqrt{2} a_1 - 1/\sqrt{2} a_2$$

$$\text{if } a_1 = a_2 = 0 \quad \neq a_3 \neq 0$$


$$\text{then, } b_1 = \frac{1}{\sqrt{2}} a_3 \quad \& \quad b_2 = -\frac{1}{\sqrt{2}} a_3$$

Output power at port 2 & port 1 is $\frac{1}{2}$ power at port 3.

→ an i/p power in port 3 divides equally between port 1 & 2 but 180° out of phase with each other.

Thus, E-plane Tee acts as a 3dB splitter.

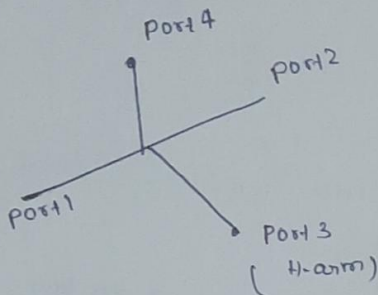Microwave Hybrid Circuit:- / Magic Tee (Both \vec{E} and \vec{H} arm, =



For H-plane Tee
 $S_{43} = 0$ — no output

$S_{23} = S_{13}$, $S_{33} = 0$
 ↳ it should be matched

For E-plane Tee

$S_{34} = 0$ — isolated

$S_{14} = -S_{24}$, $S_{44} = 0$
 ↳ it should be matched

~~EST~~ ~~port~~
 i(3) — input at port 3.
 $\begin{matrix} 0_{13} \\ 0_{23} \\ 0_{43} \end{matrix}$

(S) =

$$\begin{pmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{pmatrix}$$

Co-axial Cable

$$C = \frac{2\pi\epsilon_0\epsilon_r}{\ln D/d} \quad (\text{F/m})$$

d - inner diameter
 D - outer diameter

$$L = 0.2 \ln \frac{D}{d} \quad (\mu\text{H/m})$$

$$Z_0 = \sqrt{\frac{L}{C}}, \quad Z_0 = \frac{60}{\sqrt{\epsilon_r}} \ln \frac{D}{d} \quad (\Omega/\text{m})$$

Attenuation

dB/100 m

1.5 m
4 feet

2 dB/100 m

100 m

1

1.5

2 dB logs


$\frac{2}{100}$

$$\frac{1.5 \times 2}{100} = 0.03 \text{ dB logs}$$

Lab exam

$$a = 22$$
$$b = 10$$

thickness 1mm

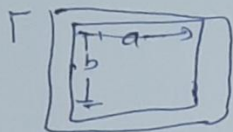

frequency c ?

Material '✓' (provided).

formulae for f_c (cut-off freq)

$b \sim \frac{a}{2}$ (TE_{10} is dominant mode).

$$f_c |_{TE_{10}} = 7.6 \text{ GHz}$$

5 to 10

- study dominant no

{ mode - 1 only }

cut-off freq - ~~S_2~~ S_2 or S_{21} [S-parameter]

0-dB crossing frequency.

$S_{12} (1)$
mode number.

Q2.

Two modes

\hookrightarrow ~~two~~ $S_{12} (1)$
 $S_{21} (1)$

$S_{12} (2)$
 $S_{21} (2)$

{ upper freq - high }.

Q3.

\rightarrow Identify the modes

\vec{E} .

propagating and non-propagating dominant mode


\hookrightarrow \vec{E} pattern with
better :

transmission coefficient
(S-parameter)

Background \rightarrow Normal

Microstrip Line
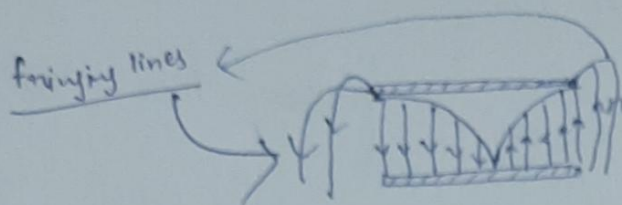
$$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \left(\frac{1}{\sqrt{1 + 10 \frac{d}{w}}} \right)$$




$$Z_0 = \begin{cases} \frac{60}{\sqrt{\epsilon_e}} \ln \left(\frac{8d}{w} + \frac{w}{4d} \right) & ; \text{ for } \frac{w}{d} \leq 1 \\ \frac{120\pi}{\sqrt{\epsilon_e} \left[\frac{w}{d} + 1.393 + 0.667 \ln \left(\frac{w}{d} + 1.444 \right) \right]} & ; \text{ for } \frac{w}{d} \gg 1 \end{cases}$$

Planar Transmission lines

planar power divider

2-way equal power divider

I/p Port should be matched
 $S_{11} = 0$

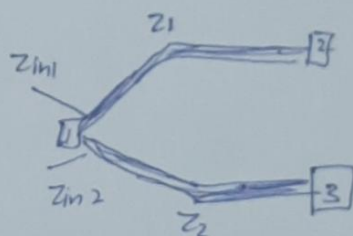

$$Z_{in1} = 100$$

$$Z_{in2} = 100$$


$$Z_{in1} = \frac{|Z_L|^2}{Z_L}$$

$$|Z_L|^2 = Z_{in1} \cdot Z_L$$

For equal power division ad loss-less network,

$$S_{21} = S_{31} = -j\frac{1}{\sqrt{2}} = S_{12} = S_{13}$$

Coupled line Directional Coupler (CLDC)

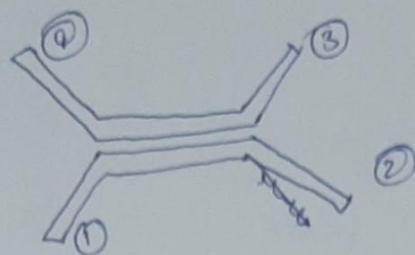

- ① - input port
- ② - Directly coupled port or Through port

① Transmission line

Z_{in}

SWR

Γ

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Smith chart
(Example)

Fundamental formula Equation

- plot of current / voltage (graph)
- draw voltage profile and current profile for short and open circuit. (plot if R is given)
- Z_{in} - for short & open ckt. } conductive or Inductive.

② Application

- ① calculate Unknown Impedance (Smith chart). By

- ② Quarter-wave transformer (Design)
Diagram