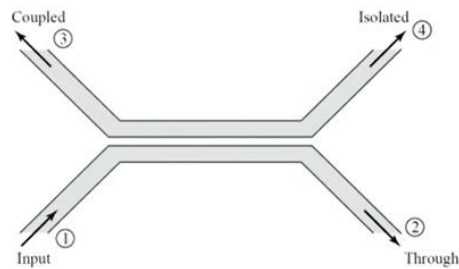


Coupled Line Directional Coupler (CLDC)



For Input at Port 1:

Port 2 is Directly Coupled Port or Through Port

Port 3 is Coupled Port ($|S_{31}|$ may be -10 dB to -30 dB)


Port 4 is Isolated Port ($|S_{41}|$ should be as large as possible)





S

CLDC – Even and Odd Modes

Even Mode Excitation

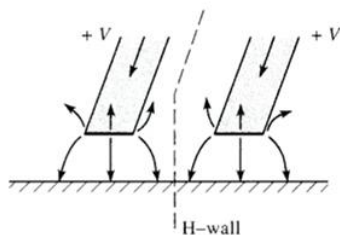

Odd Mode Excitation

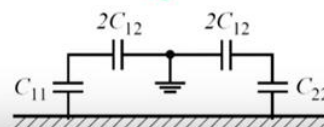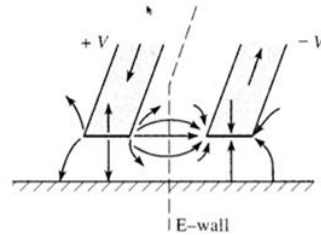

CLDC – Analysis and Design

Coupling (C) is maximum for $l = \lambda/4$. For desired C:

$$Z_{0e} = Z_0 \sqrt{\frac{1+C}{1-C}}$$

$$Z_{0o} = Z_0 \sqrt{\frac{1-C}{1+C}}$$

$$Z_0 = \sqrt{Z_{0e} \times Z_{0o}}$$


For $Z_0 = 50 \Omega$

Coupling C (dB)	Numeric value of C	Z_{0e} (Ω)	Z_{0o} (Ω)
-6	0.5	86.6	28.9
-10	0.316	69.4	36.0
-20	0.1	55.3	45.2
-30	0.0316	51.6	48.4

Where Z_{0e} and Z_{0o} are even and odd mode characteristic impedances.



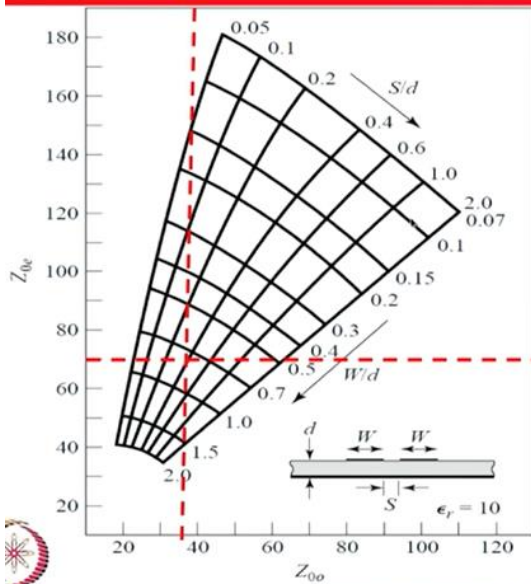Coupled Microstrip Line - Z_{0e} and Z_{0o}



Plot for Z_{0e} and Z_{0o} for
 $Z_0 = 50 \Omega$ and $\epsilon_r = 10$

As s/d increases,


Z_{0e} decreases and Z_{0o} increases

As w/d increases, both Z_{0e} and Z_{0o} decrease.

For 10 dB coupling, $Z_{0e} = 69.4 \Omega$ and
 $Z_{0o} = 36 \Omega$.

From graph: $w/d = 0.75$ and $s/d = 0.4$

Coupled Microstrip Line – Even Mode ϵ_e

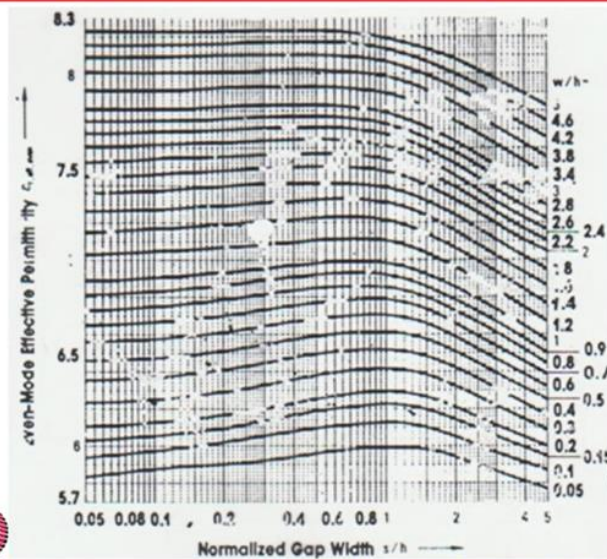

Plot for Even Mode ϵ_e
for $\epsilon_r = 9.6$

As w/h increases,
 ϵ_e increases.

As s/h increases,
 ϵ_e decreases.

Microstrip Line CLDC ($C = -20$ dB)



$f = 800 - 1000$ MHz

$\epsilon_r = 4.4$, $h = 0.8$ mm, $\tan\delta = 0.02$

Length $l = \lambda/4 = 46$ mm

Width = 1.5 mm, Gap = 1 mm

Coupling is max. for $l = \lambda/4$ and $3\lambda/4$ and min. for $l = 2\lambda/4 = \lambda/2$

$$|S_{11}| \leq -35 \text{ dB}$$

$$|S_{21}| \approx -0.2 \text{ dB}$$

$$|S_{31}| = C \approx -20.6 \text{ dB}$$



$|S_{41}| = I = -23$ dB at 900 MHz. Directivity = $|C - I|$ is very poor.

