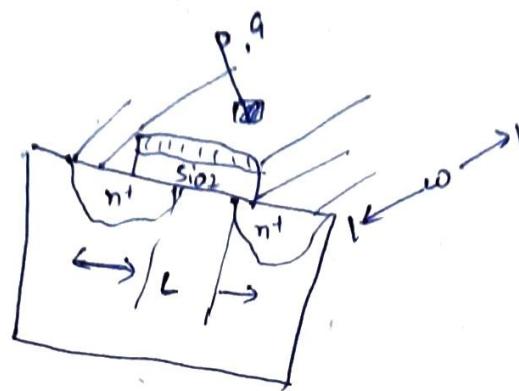





12/19/23

High frequency Analysis




D-S ~ capacitor is
not there.

$$C = \frac{\epsilon_0 A}{d}$$

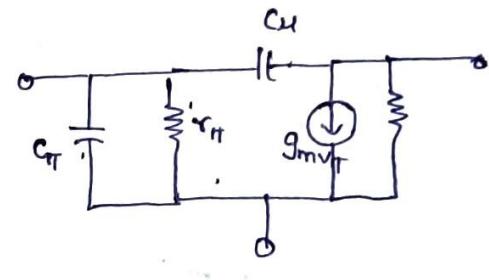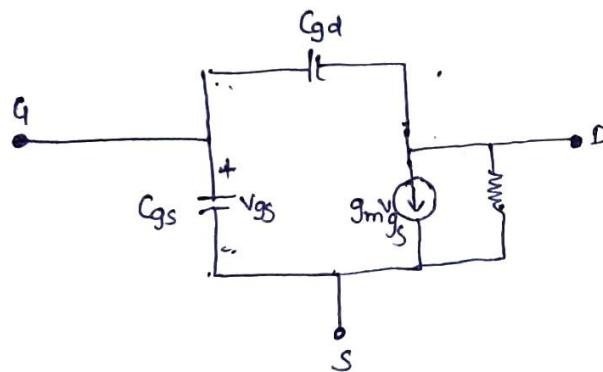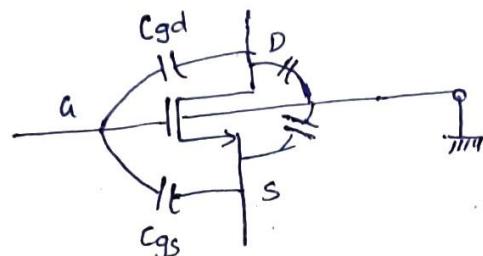


BJT



Hybrid - T - high frequency model

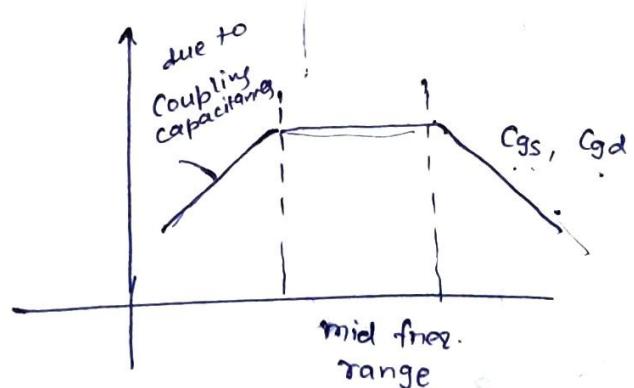

$$\frac{1}{j\omega C_{D-G}}$$

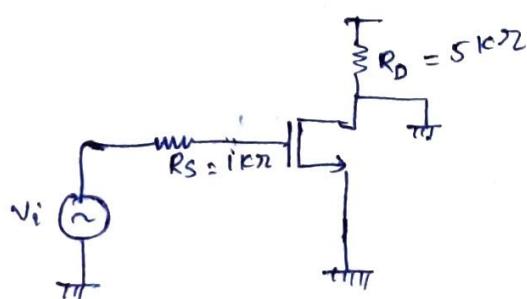

f_T = unity current gain frequency.

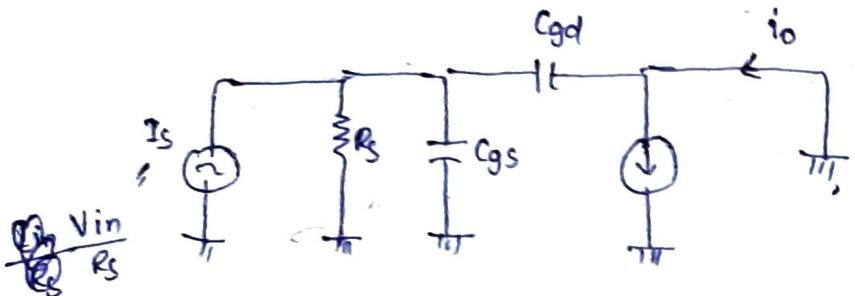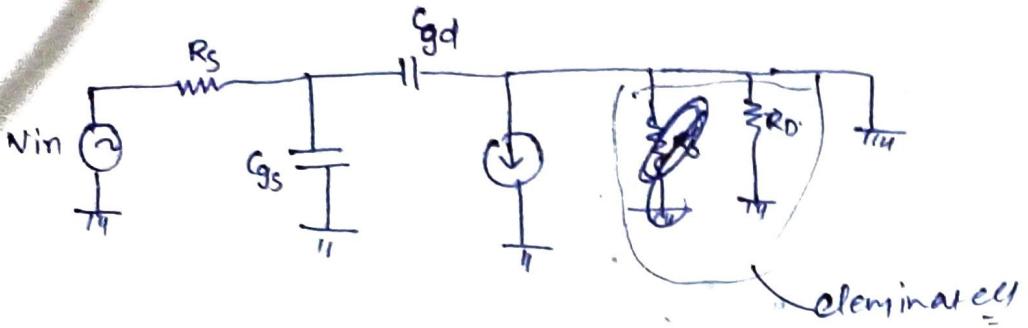

$$i_s = \frac{v_{gs}}{R_s} - \underbrace{\frac{v_{gs} \cdot s \cdot C_{gs}}{R_s}}_{= v_{gs} \cdot s \cdot C_{gd}} = 0$$

$$i_o = g_m v_{gs} - s C_{gd} v_{gs}$$

$$i_s = v_{gs} \left(\frac{1}{R_s} + s C_{gs} + s C_{gd} \right)$$

$$= \frac{i_o}{g_m - s C_{gd}} \left(\frac{1}{R_s} + s C_{gs} + s C_{gd} \right)$$

~~$$i_s = \frac{g_m}{R_s} \left(\frac{1}{R_s} + s C_{gs} + s C_{gd} \right)$$~~

$$\frac{i_o}{i_s} = \frac{(g_m - s C_{gd}) R_s}{1 + s R_s (C_{gs} + C_{gd})}$$

$$\left| \frac{i_o}{i_s} \right|_{s=j\omega} = \frac{(g_m - j\omega C_{gd}) R_s}{1 + j\omega R_s (C_{gs} + C_{gd})}$$

$$\left| \frac{i_o}{i_s} \right|_{s=j\omega} = \frac{R_s \sqrt{g_m^2 + \omega^2 C_{gd}^2}}{\sqrt{1 + \omega^2 R_s^2 (C_{gs} + C_{gd})^2}}$$

eq.

$$\left| \frac{i_o}{i_s} \right|_{\omega=\omega_T} = 1$$

$$R_s^2 \left(g_m^2 + \omega^2 C_{gd}^2 \right) = 1 + \omega^2 R_s^2 (C_{gs} + C_{gd})^2$$

$$g_m^2 \gg \omega^2 C_{gd}^2$$

$$\frac{R_s g_m}{\sqrt{1 + g_m^2 R_s^2 (C_{gs} + C_{gd})^2}} \approx 1$$

$$g_m^2 R_s^2 = 1 + \omega^2 R_s^2 (C_{gs} + C_{gd})^2$$

$$g_m^2 = \frac{1}{R_s^2} + \omega^2 (C_{gs} + C_{gd})^2$$


Generally
Rs value is
very high as it
is connected in
parallel to current.

$$g_m^2 = \omega^2 (C_{gs} + C_{gd})^2$$

$$f_T = \frac{g_m}{2\pi (C_{gs} + C_{gd})}$$

unity gain
current frequency.

Output is shorted

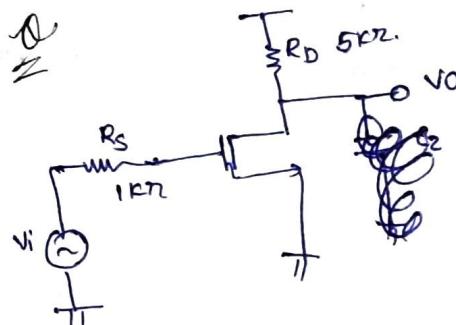


$$M_n COX \frac{W}{L} = 100 \text{ mA/V}^2$$

$$C_{gd} = 0.5 \text{ pF}$$

$$C_{gs} = 5.15 \text{ pF}$$

$$I_D = 1 \text{ mA}$$

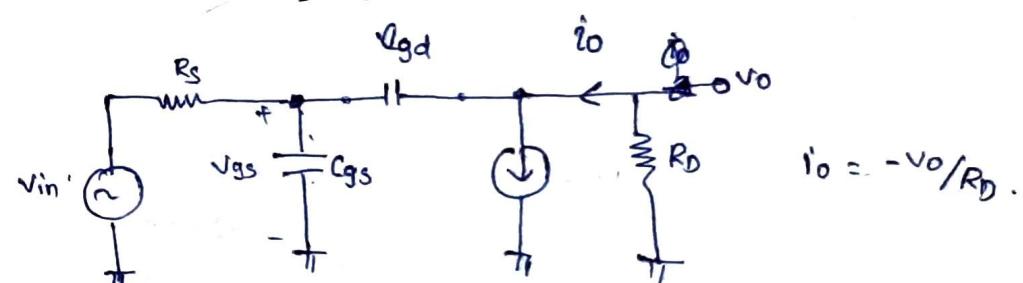

$$i_D = -V_0 / R_D$$

$$\frac{V_{in} - V_{gs}}{R_s} = V_{gs} \cdot s C_{gs} + (V_{gs} - V_0) s C_{gd} \quad (i)$$


$$\frac{-V_0}{R_D} - g_m V_{gs} + (V_{gs} - V_0) s C_{gd} = 0 \quad (ii)$$

f_{nom} eq (i) \Rightarrow (iii),

$$\frac{V_o}{V_{in}} = -\frac{(g_m - sC_{gd}) R_D}{S^2 R_S R_D C_{GS} C_{gd} + S \{ R_S (C_{GS} + C_{gd}) + C_{gd} R_D + g_m R_S R_D C_{gd} \} + 1} \quad (i)$$

At $\omega = \omega_L$


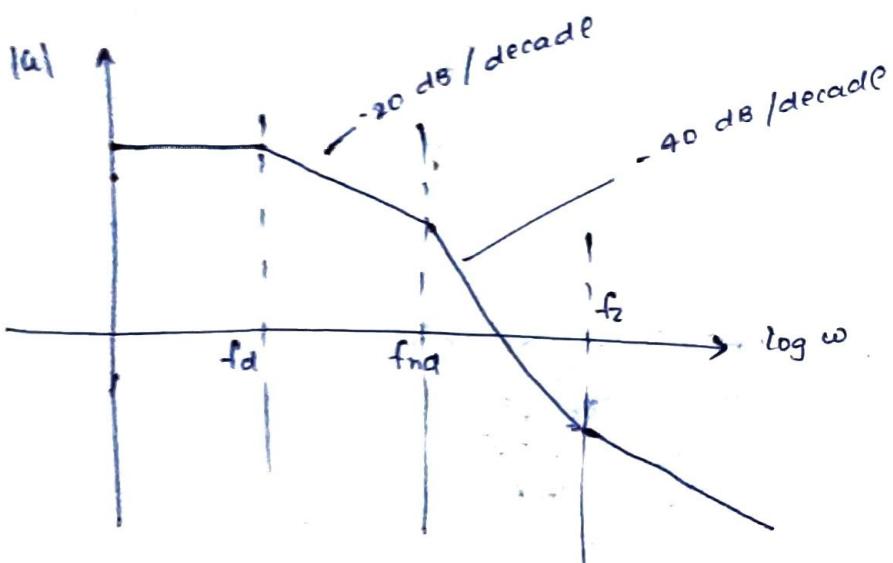
$$\begin{aligned} g_m &= \sqrt{2 \times n COX \omega_L / I_D} \\ &= \sqrt{2 \times 100 \times 10^{-3} \times 1 \times 10^{-3}} \\ &= \sqrt{2 \times 10^{-6}} \\ &= \sqrt{2} \times 10^{-3} = 14.14 \times 10^{-3}. \end{aligned}$$



f_d = dominant pole
 f_{nd} = non-dominant pole.

$$\begin{aligned} R_S R_D C_{GS} C_{gd} &= 1 \times 5 \times 10^6 \times 0.5 \times 5.15 \\ &= 12.875 \times 10^{-24+6} \\ &= 12.875 \times 10^{-18} \end{aligned}$$
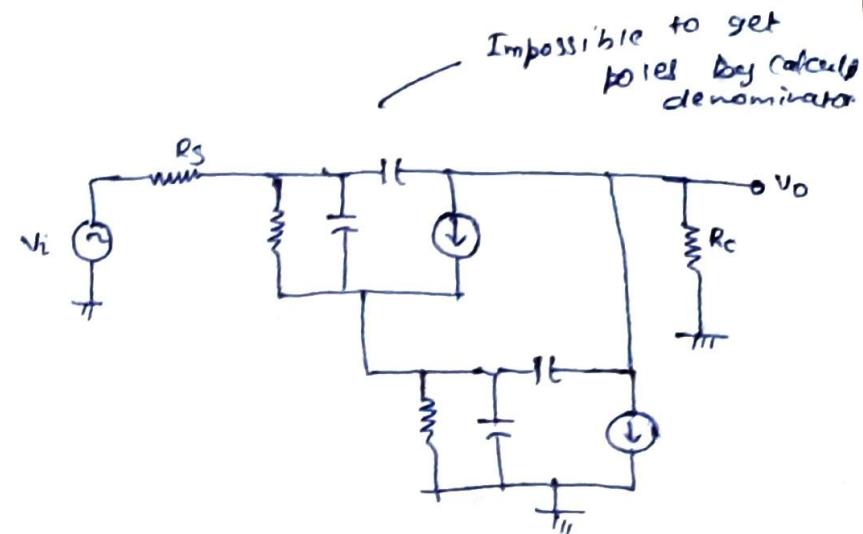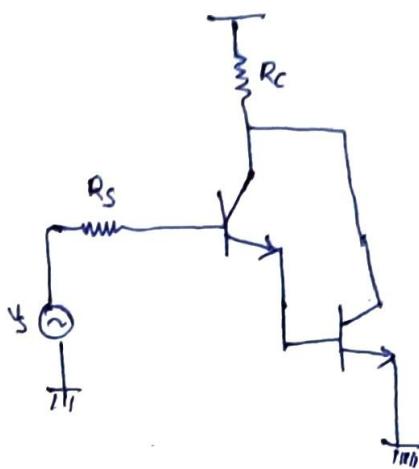
$$\begin{aligned} R_S (C_{GS} + C_{gd}) + C_{gd} R_D + g_m R_S R_D C_{gd} &= \\ &= 1 \times 10^3 (5.65) \times 10^{-12} + 0.5 \times 10^{-12} + 14.41 \times 10^{-3} \\ &\quad \times 5 \times 10^6 \end{aligned}$$



dominant pole \rightarrow using
non-dominant pole \rightarrow using

open circuit time constant.
Short circuit time constant.

↳ Denominator of eq (i) = 0

$$\left(\frac{s}{P_1} + 1\right) \left(\frac{s}{P_2} - 1\right) = 0$$

Calculation:

Make,
Ind. Voltage - short
Ind. current - open point.

$$\frac{1}{P_1} = \sum C_i R_i$$

$$P_1 = \frac{1}{\sum C_i R_i}$$

$P_1 \gg P_2$ are widely apart.

Assumption:-

$$P_1 = d.p.
P_2 = n.d.p.$$

During C_{GS} consideration
Open circuit C_{GD} and
calculate Resistance
across them.

from eq (i)

$$\frac{1}{P_1 P_2} = \underbrace{R_S R_D C_{GS} C_{GD}}$$

$$\frac{1}{P_1} + \frac{1}{P_2} = R_S C_{GS} + C_{GD} \left(R_S + R_D + g_m R_S R_D \right)$$

$$\therefore \frac{1}{P_1} \approx R_S C_{GS} + C_{GD} \left(R_S + R_D + g_m R_S R_D \right)$$


During C_{GD} consideration,
open circuit C_{GS} and
calculate equivalent
resistance across
them.

$$V_D - i_T - g_m i_T R_S - \frac{i_T R_S}{R_D} + \frac{V_D}{R_D} = 0$$

$$- R_D i_T - g_m R_S R_D i_T - i_T (R_S) = - V_D$$

Considering for C_{gd}
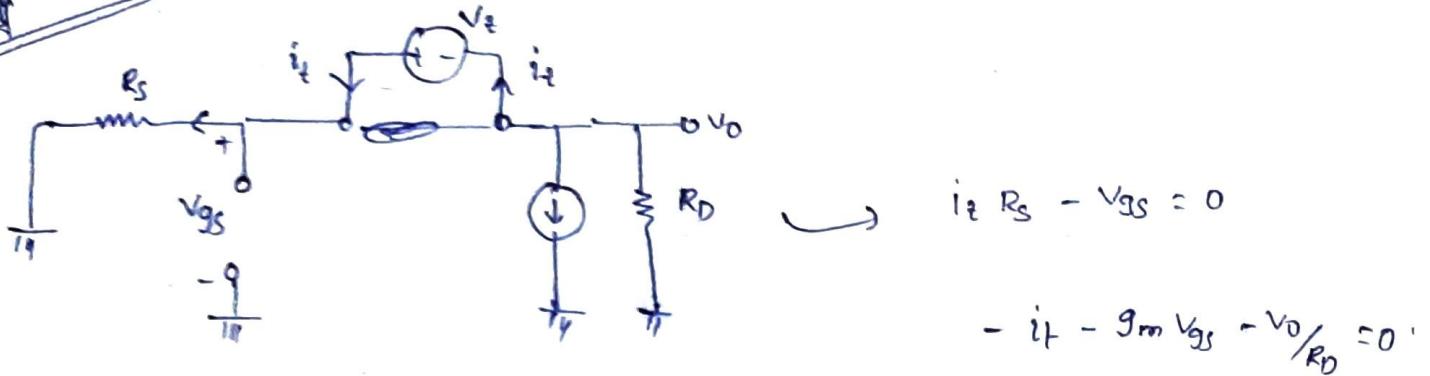
$$\frac{V_D}{i_T} = (R_D + R_S + g_m R_S R_D)$$



$$s^2 + s \frac{\{ R_S (c_{gs} + c_{gd}) + C_{gd} R_D + g_m R_S R_D C_{gd} \}}{R_S R_D c_{gs} c_{gd}} + \frac{1}{R_S R_D c_{gs} c_{gd}} = 0$$


$$(s - p_1)(s - p_2) = 0$$

$$p_1 + p_2 = \frac{1}{c_{gd}} \frac{1}{R_D} + \frac{1}{c_{gs}} \left(\frac{1}{R_D} + \frac{1}{R_S} + g_m \right).$$

$$p_2 = \sum \frac{1}{R_i C_i}$$


non-dominant pole determination.

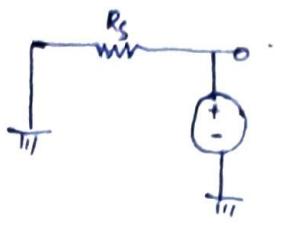In this case, we have to short circuit the other capacitor and determine the equivalent resistance.



Short circuit T_{short} time const.


(for Dominant pole)

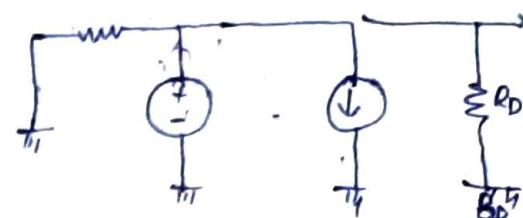

Short circ. T.C.

(for Non-Dominant pole)

BJT

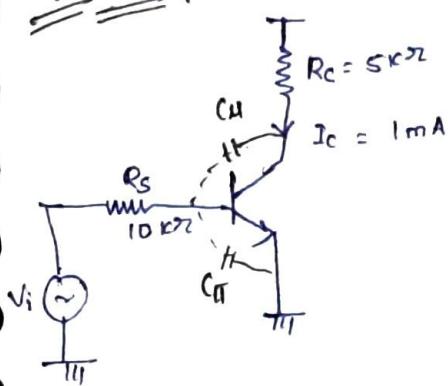

$$C_{ui} = 0.2 \text{ pF}$$

$$f_T @ 1 \text{ mA} = 600 \text{ MHz}$$

$$\beta = 200$$

$$g_m = \frac{I_c}{V_T}$$

$$= \frac{1 \text{ mA}}{25 \text{ mV}} = \frac{1}{25}$$

$$f_T = \frac{g_m}{2\pi(C_{pi} + C_{ui})} = \frac{1/25}{2\pi(C_{pi} + C_{ui})} = 600 \times 10^6$$



$Q \parallel e$



$$(C_{pi} + C_{ui})$$

$$= \frac{1}{50 \times \pi \times 600} \times 10^{-6}$$


$$= \frac{1}{3\pi} \times 10^{-10}$$

$$= 1.0471 \times 10^{-10}$$

~~$$= 1.0471 \times 10^{-12}$$~~

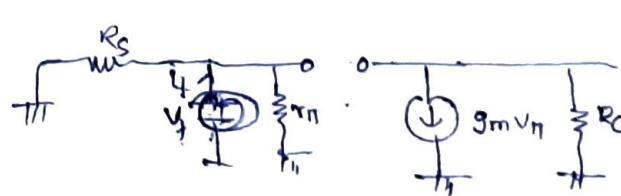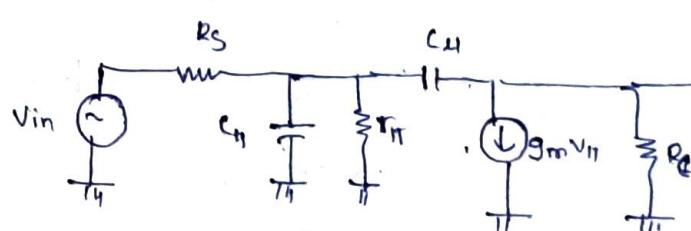


$$R_{pi} = R_S \parallel Y_{pi}$$

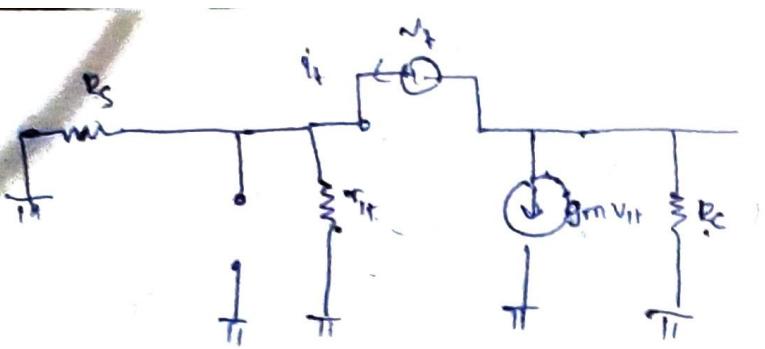


equivalent
Resistance
across U_e.

$$R_{\text{eq}} = R_S \parallel r_{\pi} + R_C + g_m (R_S \parallel r_{\pi}) \cdot R_C$$

14/09/23

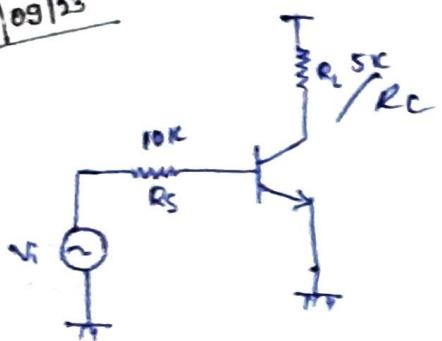

CE without
emitter degeneration.


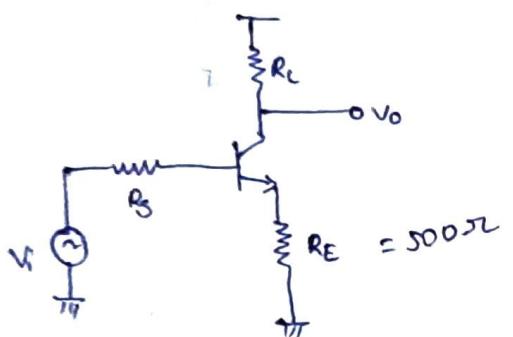



CE stage with
emitter degeneration

$$g_m = 38 \text{ mV/V}$$

$$r_{\pi} = 5.22 \text{ k}\Omega$$

$$\beta = 200$$

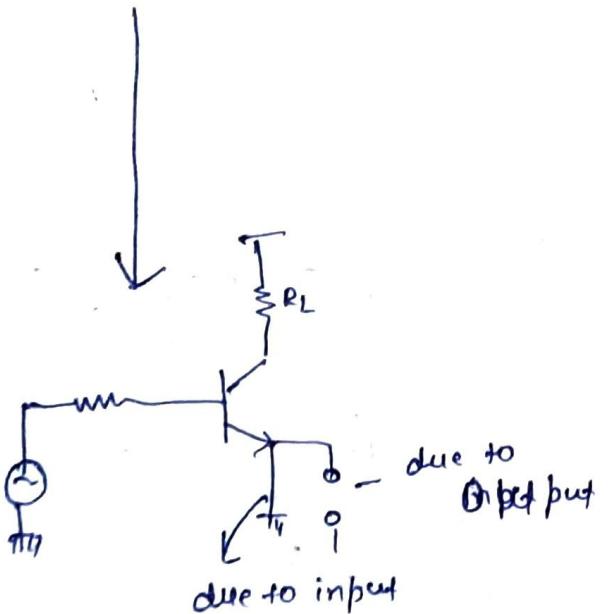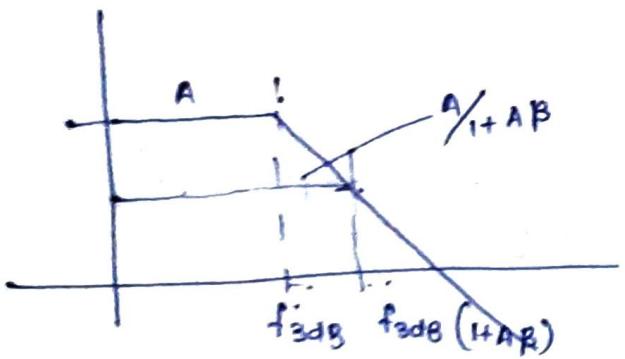

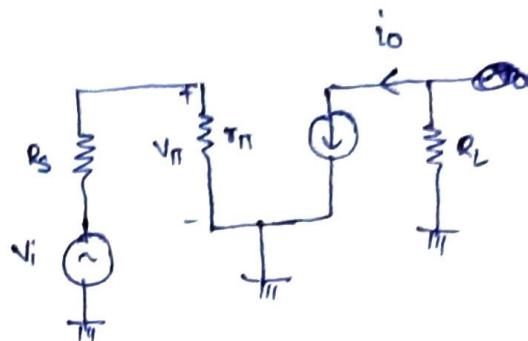

$$v_{o^-} = +g_m v_i \\ = +g_m \times \frac{r_{pi}}{r_{pi} + R_s} \times v_i$$

$$\frac{i_o}{v_i} = \frac{+g_m r_{pi}}{r_{pi} + R_s}$$

$$f = R_E$$


$$\left| \frac{i_o}{v_i} \right|_{CL} = \frac{\frac{+g_m r_{pi}}{r_{pi} + R_s} + +g_m r_{pi} R_E}{1 + R_E \left(\frac{+g_m r_{pi}}{r_{pi} + R_s} \right)}$$

$$\left| \frac{i_o}{v_i} \right|_{OL} = + \frac{38 \times 10^{-3} \times 5.22 \times 10^3}{15.22 \times 10^3} = \frac{198.36}{15.22} \\ \Rightarrow \cancel{30.6} \times \cancel{6.5} \\ = 13.032 \times 10^3.$$

$$\left| \frac{i_o}{v_i} \right|_{CL} = \frac{13.033 \times 10^{-3}}{1 + 13.033 \times 10^{-3} \times 0.5 \times 10^3} \\ = \frac{13.033 \times 10^{-3}}{17.515} = 1.734 \times 10^{-3}$$

$$1 + AB =$$
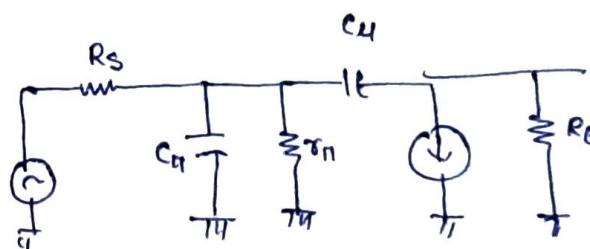
$$1 + 13.033 \times 0.5 = \cancel{6.5} 7.97$$



for Bandwidth determination, we determine
only dominant pole

→ Short circuit

After short circuit

$$R_{\pi} = R_s \parallel r_{\pi} = 3.43 \text{ k}\Omega$$

$$R_H = (R_s \parallel r_{\pi}) + R_C + g_m (R_s \parallel r_{\pi}) R_C$$

$$= 3.43 \times 10^3 + 5 \times 10^3 + 38 \times 10^{-5} \times 3.43 \times 10^3 \times 5 \times 10^3$$

$$= 10^3 (8.43 + 651.7)$$


$$= 660 \text{ k}\Omega$$


$$f_{3dB} = \frac{1}{2\pi (R_H C_H + R_C C_H)}$$

$$= \frac{1}{2\pi (3.43 \times 10^3 \times 9.8 \times 10^{-12} + 660 \times 10^3 \times 10^{-12})}$$

$$= \frac{1}{(33.614 + 660) \times 10^{-9}}$$

$$= 0.96 \text{ MHz.}$$

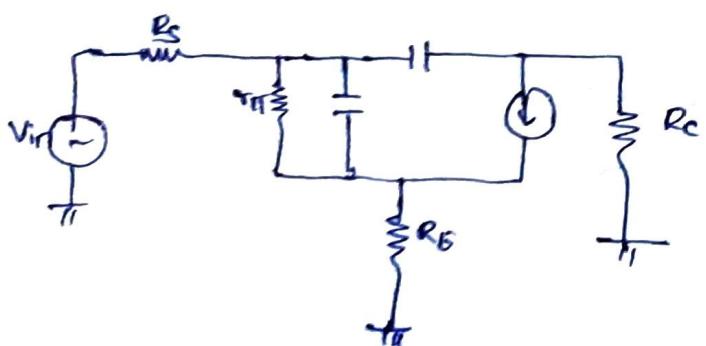

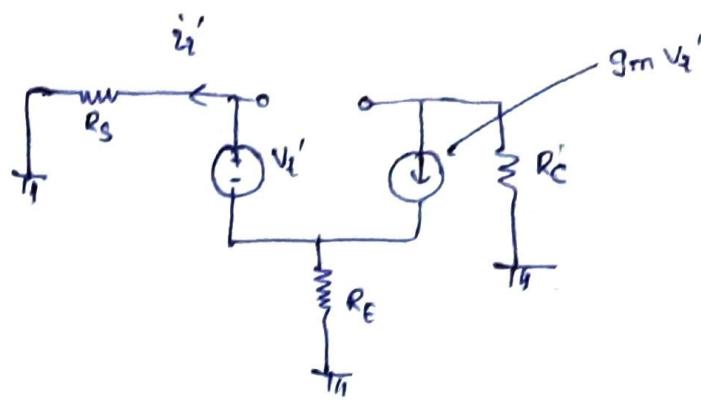

$$i_1' R_S - v_i' - (g_m v_i' - i_1') R_E = 0$$

$$i_1' (R_S + R_E) = v_i' (1 + g_m R_E)$$

$$\frac{v_i'}{i_1'} = \frac{R_S + R_E}{1 + g_m R_E}$$

$$\frac{v_i}{i_1} = \frac{R_S + R_E}{1 + g_m R_E} \parallel r_{\pi}$$


$$\frac{v_i'}{i_1'} = \frac{(5 + 0.5) \times 10^3}{1 + 38 \times 0.5}$$


$$= \cancel{55} \\ = 0.275 \times 10^3$$

$$= 275$$

$$r_{\pi} = \frac{r_{\pi} \times \frac{R_S R_E}{1 + g_m R_E}}{r_{\pi} + \frac{R_S R_E}{1 + g_m R_E}}$$
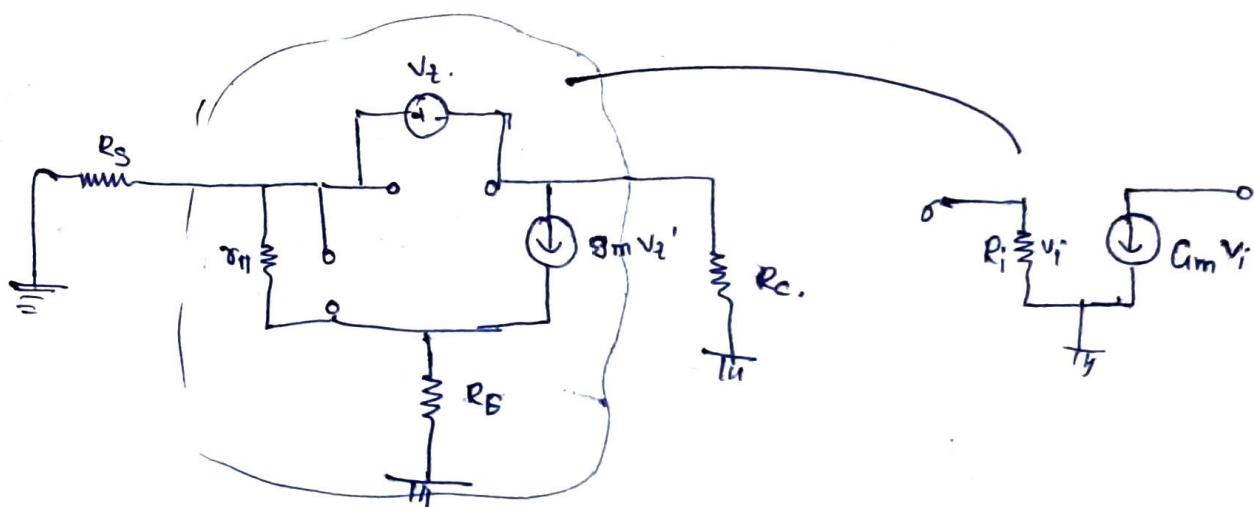
$$\frac{v_t}{i_1} = \frac{275 \times 5.22 \times 10^3}{275 + \dots} = \frac{1435.5 \times 10^3}{5495}$$



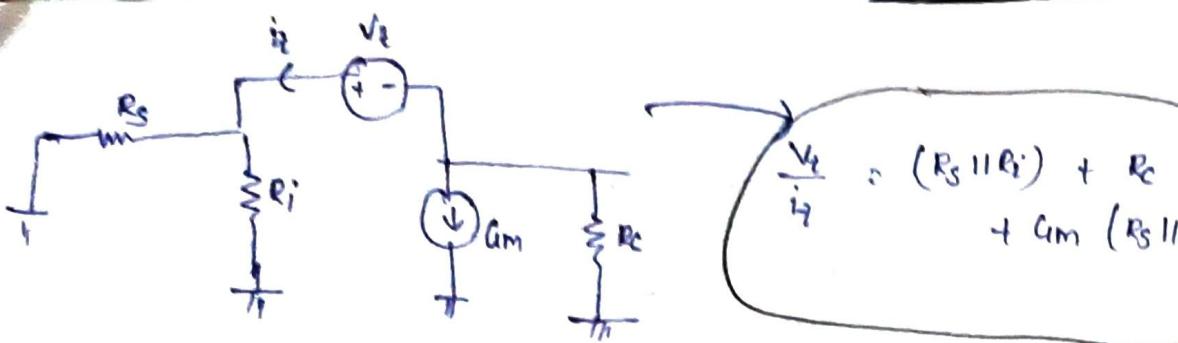

$$\frac{V_t}{i} = (R_s + R_i) + R_L + G_m (R_s + R_i) R_L$$

$$R_i = r_\pi + (\beta + 1) g_m$$

$$\frac{V_i}{i} = R_i$$

$$v_\pi = i v_\pi$$

$$v_{\pi} = \frac{V_i}{R_i} \times r_\pi$$

$$G_m = \frac{i_o}{v_i}$$

$$G_m = \frac{g_m v_\pi}{R_i}$$

~~$$G_m = \frac{g_m \times v_i}{R_i \times R_i}$$~~

~~$$= \frac{g_m v_i}{R_i^2}$$~~

$$r_i = r_\pi + (\beta + 1) g_m = 105.7 \text{ k}\Omega$$

$$G_m = \frac{g_m r_\pi}{R_i} = 1.88 \times 10^{-3}$$

$$R_s + R_i$$

$$= \frac{10 + 105.7}{115.7}$$

$$\frac{V_t}{i} = g_m \times 10^3 + 5 \times 10^3 + \frac{1.88 \times 10^{-3}}{x 9.14 \times 10^3 \times 5 \times 10^3} = 9.14 \text{ k}\Omega$$

$$= (9.14 + 5 + 85.916) \times 10^3$$



$$= 100.056 \times 10^3$$

$$R_H = 480 \Omega$$

$$R_H = 100 \text{ k}\Omega$$

$$\begin{aligned} f_{3dB} &= \frac{1}{2\pi} \sqrt{480 \times 9.8 \times 10^{-12} + 10^5 \times 0.2 \times 10^{-12}} \\ &= \frac{10^{12}}{(4704 + 20000) \times 2\pi} \\ &= \underline{\underline{6.44 \times 10^6 \text{ MHz}}} \end{aligned}$$

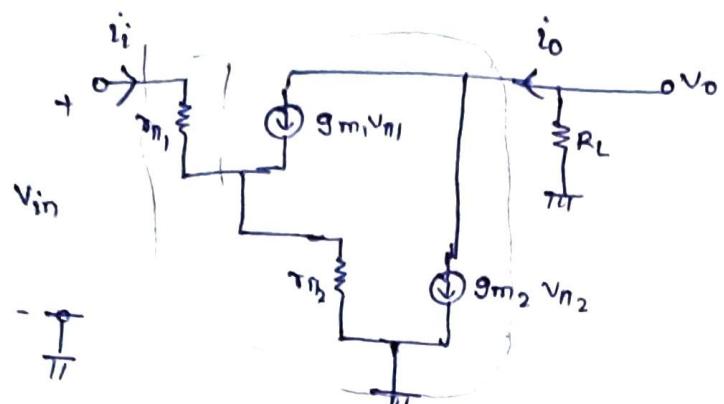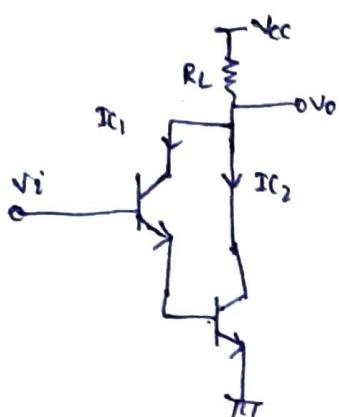Darlington pair $\xrightarrow{\text{freq. Analysis}}$



$V_A \rightarrow \infty$

$$R_{in} = \tau_{\eta_1} + (\beta_1 + 1) \tau_{\eta_2}$$

$$G_m = \frac{i_0}{V_i}$$

$$i_0 = g_{m_2} v_{\eta_2} + g_{m_1} v_{\eta_1}$$

$$v_i = v_{\eta_1} + v_{\eta_2}$$

$$v_{\eta_2} = v_i - i_1 \tau_{\eta_1}$$

$$i_0 = g_{m_2} (v_i - i_1 \tau_{\eta_1}) + g_{m_1} i_1 \tau_{\eta_1}$$

$$= g_{m_2} v_i - (g_{m_2} \tau_{\eta_1} + g_{m_1} \tau_{\eta_1}) i_1$$

$$= g_{m_2} v_i - (g_{m_2} \tau_{\eta_1} + g_{m_1} \tau_{\eta_1}) \frac{V_i}{R_{in}}$$

$$\frac{i_0}{V_i} = \frac{g_{m_2} R_{in} - g_{m_2} \tau_{\eta_1} - g_{m_1} \tau_{\eta_1}}{R_{in}}$$

$$G_m = \frac{g_{m_2} (\tau_{\eta_1} + (\cancel{g_{m_1} \tau_{\eta_1} + 1}) \tau_{\eta_2}) - g_{m_2} \tau_{\eta_1} - g_{m_1} \tau_{\eta_1}}{R_{in}}$$

$$= g_{m_2} \tau_{\eta_1} + g_{m_1} g_{m_2} \tau_{\eta_1} \tau_{\eta_2} + g_{m_2} \tau_{\eta_2} - g_{m_2} \tau_{\eta_1} - g_{m_1} \tau_{\eta_1}$$

$$G_m = \frac{g_{m_1} + g_{m_2} \tau_{\pi_1} \tau_{\pi_2} + g_{m_2} \tau_{\pi_2} - g_{m_1} \tau_{\pi_1}}{R_{in}}$$

$$G_m = \frac{\beta_1 \beta_2 + \beta_2 - \beta_1}{R_{in}}$$

$$\frac{V_o}{V_i} = -G_m R_L = - \frac{(\beta_1 \beta_2 + \beta_2 - \beta_1) \times R_L}{R_{in}}$$

Q. $I_{C_1} = 1mA$ $R_L = 5k\Omega$

$I_{C_2} = 100 \mu A$

$\beta_1 = 100 = \beta_2$


km

$$R_{in} = r_{\pi_1} + (\beta_1 + 1) \tau_{\pi_2}$$

$$\frac{1}{25} + \frac{100 \times 4 \times 10}{100} = 0.404 + 0.04 = 0.444$$

$$G_m = \frac{100 \times 100}{24.75} = 0.404$$

$$V_o = -24.75 \times 5 \times 10^3$$

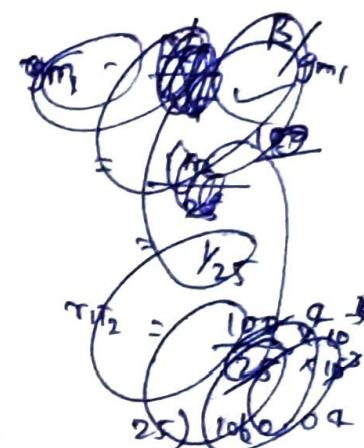

$$g_{m_1} = \frac{I_c}{V_T}$$

$$= \frac{1}{25}$$

$$= 0.04$$

$$g_{m_2} = \frac{100 \times 10^{-3}}{25 \times 10^{-3}}$$


$$\tau_{\pi_1} = \frac{\beta}{g_{m_1}} = \frac{100 \times 25}{1} = 25 \times 10^2 = 4 \times 10^3$$

$$\tau_{\pi_2} = \frac{\beta_2}{g_{m_2}} = \frac{100 \times 25}{25} = 25 \times 10^3$$

$$R_{in} = 2500 + 101 \times 25 \times 10^3$$

$$= 2.53 \times 10^6$$
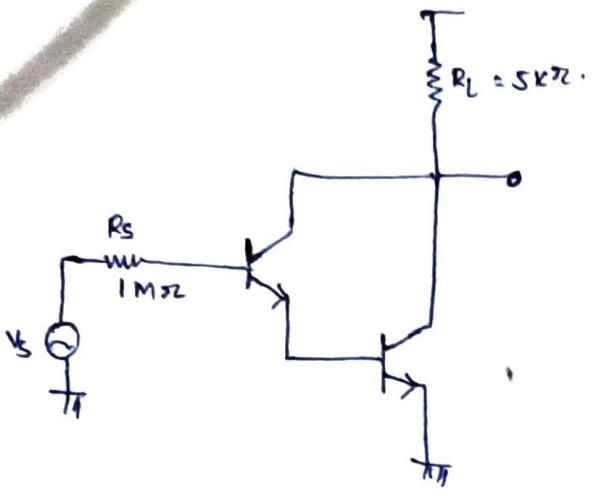
$$\frac{V_o}{V_i} = \sim 3.9 \times 50 \approx -20 \text{ V/V}$$




$$f_T = 600 \text{ MHz} @ 1 \text{ mA}$$

$$f_T = 4.00 \text{ MHz} @ 1.00 \mu\text{A.}$$

$$C_{\pi} = 10 \text{ pF.}$$

$$R_s = 1M\Omega.$$

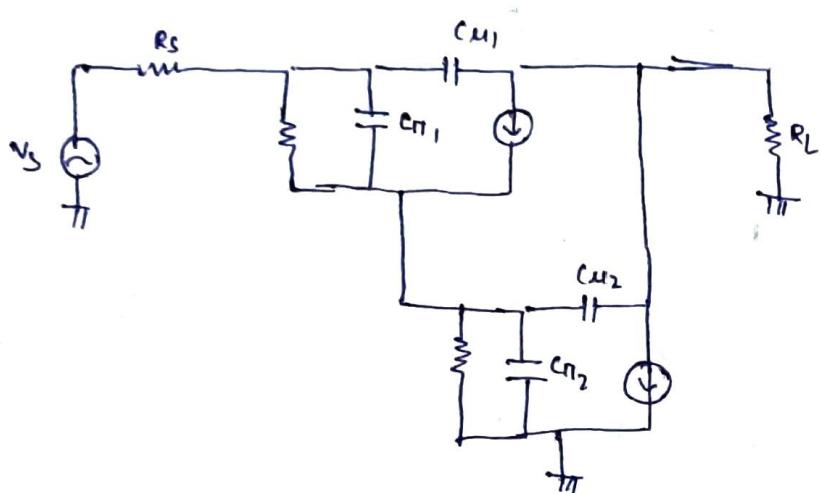

$$\begin{aligned} g_m &= \frac{\partial I}{\partial V_T} \\ &= \frac{600}{25} \\ &= 0.04. \end{aligned}$$

$$f_T = \frac{g_m}{2\pi(C_{\pi} + C_{\mu})} = 600 \text{ MHz.}$$

$$C_{\pi} + C_{\mu} = \frac{0.04 \times 10^{-6}}{2\pi \times 600} = 0.01097 \times 10^{-9} = 1.097 \mu\text{F.}$$

$$11 C_{\mu} = 1.097 \mu\text{F.}$$

$$C_{\mu} = 1.097 = 0.095 \mu\text{F.}$$

$$C_{\pi} = 0.95 \mu\text{F.}$$


$$f_{T_2} = \frac{g_{m_2}}{2\pi(C_{\pi} + C_{\mu})} \xrightarrow{g_{m_2} = 4 \times 10^{-3}} 4 \times 10^{-3} \text{ Hz}$$

$$\begin{aligned} g_{m_2} &= \frac{100 \times 10^{-3}}{25 \times 10^3} \\ &\approx 4 \times 10^{-3} \end{aligned}$$

$$C_{\pi} + C_{\mu} = \frac{4 \times 10^{-3}}{2\pi \times 400} \times 10^{-6}$$


$$C_{\pi} = 1.4 \text{ pF}$$

$$C_{\mu} = 0.14 \text{ pF.}$$

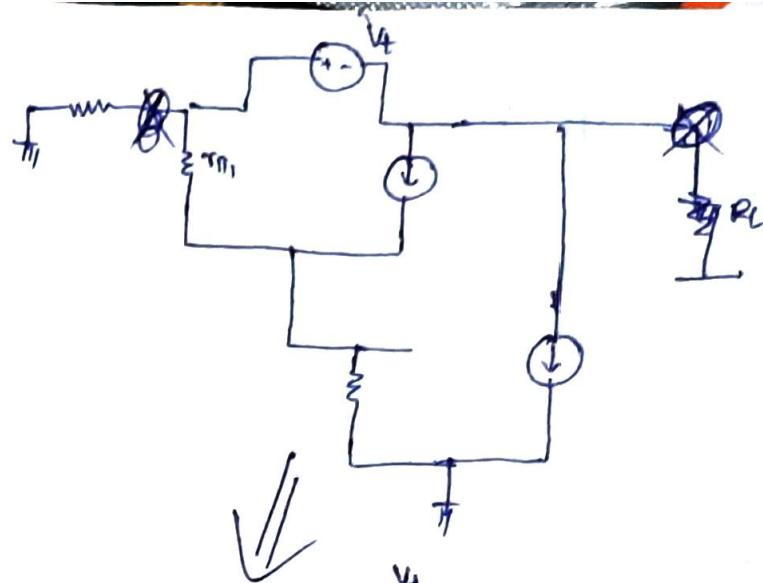

$$R_{in} = 2.57 \text{ M}\Omega$$

$$R_S = 1 \text{ M}\Omega$$

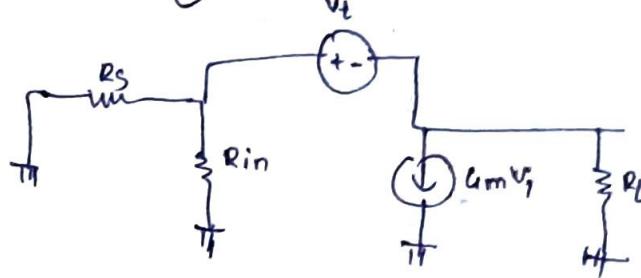


$$\frac{V_t}{i_t} = R_S \parallel R_{in} + R_L + g_m (R_S \parallel R_{in}) R_L$$

$$= \frac{2.57 \times 1}{2.57} + 5 \times 10^3 + 3.9 \times 10^6 \times 0.72 \times 10^6 \times 5 \times 10^3$$

$$= 0.72 \times 10^6 + 5 \times 10^3 + 14.09 \times 10^6$$

$$= 14.76 \times 10^6 + 500$$
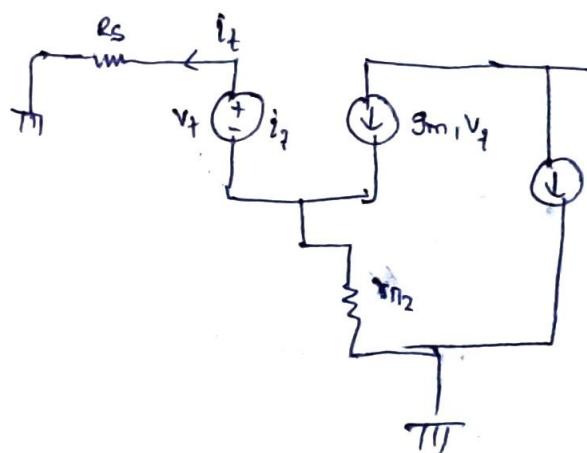
$$R_{in} = \underline{14.765 \text{ M}\Omega}$$



$$i_t R_S - V_t - (g_m V_t - i_t) \tau_{n2} = 0$$

$$i_t (R_S + \tau_{n2}) = V_t (1 + g_m \tau_{n2})$$


$$\frac{V_t}{i_t} = \frac{(R_S + \tau_{n2})}{1 + g_m \tau_{n2}}$$

$$R_{in} = \frac{(R_S + \tau_{n2})}{1 + g_m \tau_{n2}} \parallel \tau_{n1}$$

$$R_{\pi_1} = \frac{10^6 + 25 \times 10^3}{1 + 0.04 \times 25 \times 10^3} \text{ II } \infty$$

$$= 1024 \text{ II } 2500$$

$$= 726.45 \Omega.$$

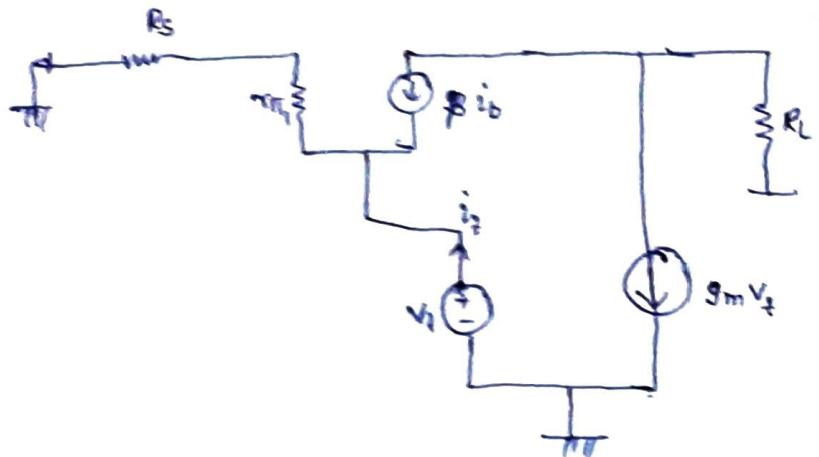

$$-i_e = i_b + \beta_1 i_b$$

$$\Rightarrow i_b = -\frac{i_e}{\beta_1 + 1}$$

$$-i_b R_S - i_b r_{\pi_1} - V_T = 0$$

$$V_T = -i_b (R_S + r_{\pi_1})$$


$$V_T = \frac{i_e}{\beta_1 + 1} (R_S + r_{\pi_1})$$

$$R_{\pi_2} = \frac{V_T}{i_e} = \frac{R_S + r_{\pi_1}}{(\beta_1 + 1)} \text{ II } r_{\pi_2},$$


$$= \frac{10^6 + 25 \times 10^3}{(101)} \text{ II } 25 \times 10^3$$

$$\downarrow 99.25.74$$

$$= 7.1 \text{ k}\Omega.$$

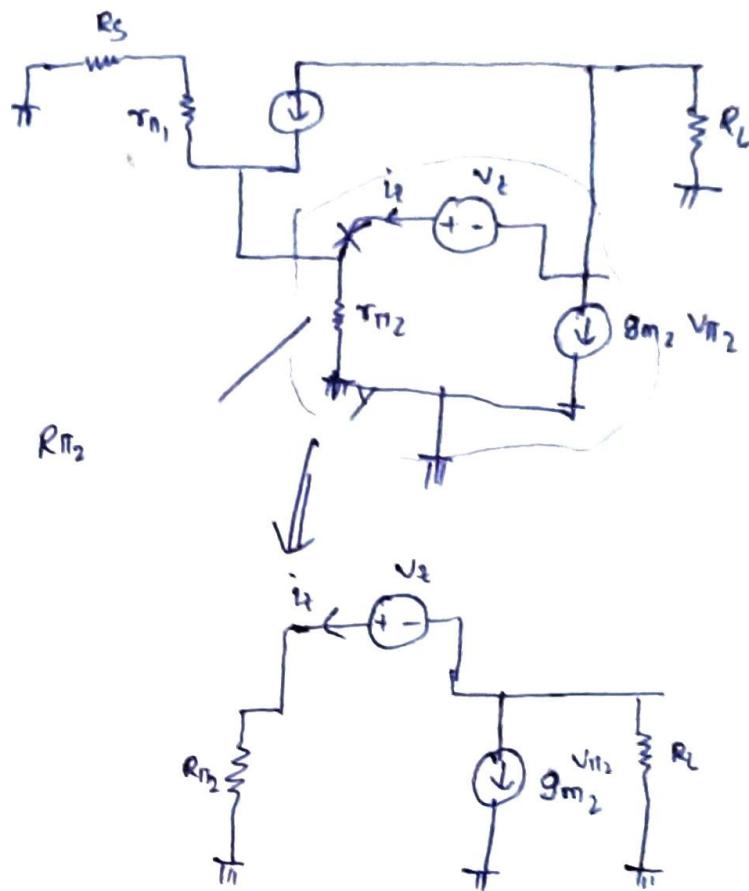
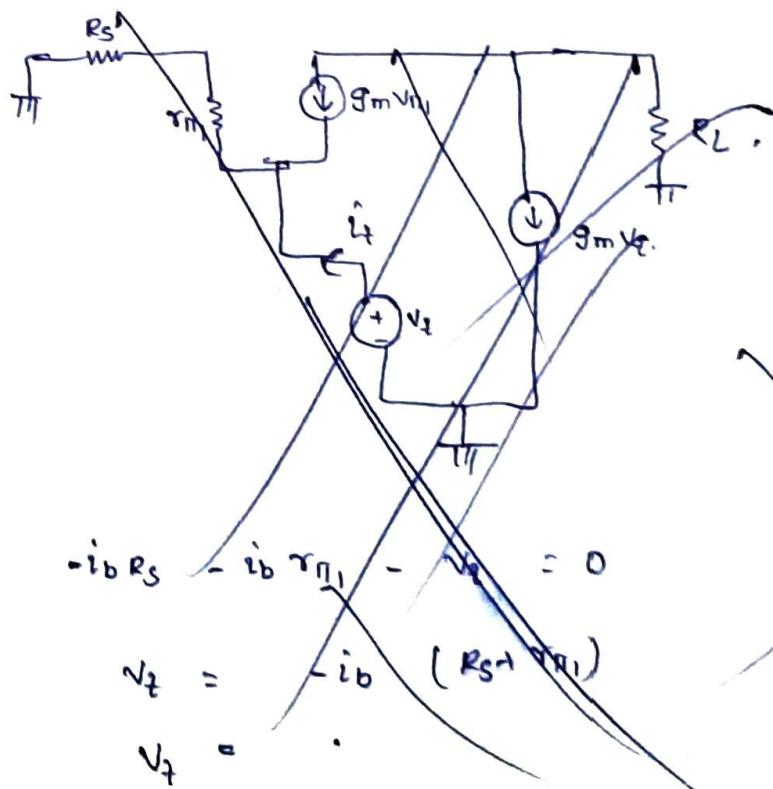
$$\begin{aligned}
 R_{42} &= \frac{V_t}{i_2} = R_{\pi 2} + R_L + g_{m2} R_{\pi 2} \times R_L \\
 &= 25 \times 10^3 + 5 \times 10^3 + 4 \times 10^5 \times 25 \times 10^3 \times 5 \times 10^3 \\
 &\quad 30 \times 10^3 + 105 \times 10^3 \\
 &= 185 \text{ k}\Omega
 \end{aligned}$$



$$-i_b = i_o + \beta_1 i_b$$

$$i_o = \frac{-i_b}{\beta_1 + 1}$$

$$-i_b R_S - i_b R_{\pi 1} - V_t = 0$$

$$V_t = -i_b (R_S + R_{\pi 1})$$

$$V_t$$

$$f_{3-\text{dB}} = \frac{1}{2\pi (C_{n_1} R_{n_1} + C_{n_2} R_{n_2} + C_{u_1} R_{u_1} + C_{u_2} R_{u_2})}$$

$$C_{n_1} = 9.2 \text{ pF}$$

$$R_{n_1} = 726.45 \Omega$$


$$C_{u_1} = 0.92 \text{ pF}$$

$$R_{n_2} = 7.1 \text{ k}\Omega$$

$$C_{n_2} = 1.4 \text{ pF}$$


$$R_{u_1} = 14.765 \text{ M}\Omega$$

$$C_{u_2} = 0.24 \text{ pF}$$

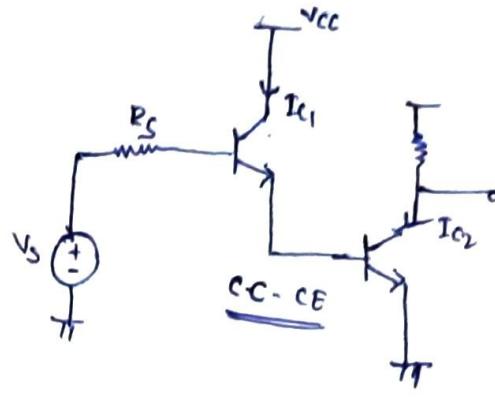

$$I_{C_1} = 1 \text{ mA}$$

$$I_{C_2} = 100 \mu\text{A}$$

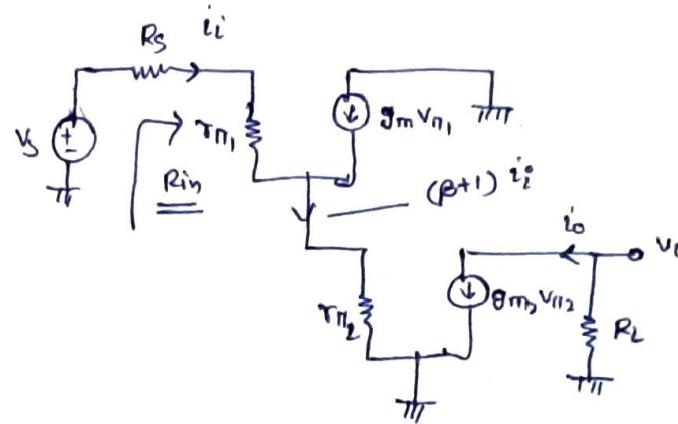

$$R_{in} = r_{T1} + (\beta+1) r_{T2}$$


$$\begin{aligned} i_o &= g_{m_2} v_{T2} \\ &= g_{m_2} i_i (\beta+1) r_{T2} \end{aligned}$$

$$i_o = g_{m_2} (\beta+1) r_{T2} \times \frac{V_i}{R_{in}}$$

$$\frac{i_o}{V_i} = g_m = \frac{\beta_2 (\beta_1 + 1)}{R_{in}} = \frac{100 \times 10^3}{2.53 \times 10^6}$$

$$= 3992.09 \times 10^{-8}$$


$$= 3.99 \times 10^{-3}$$

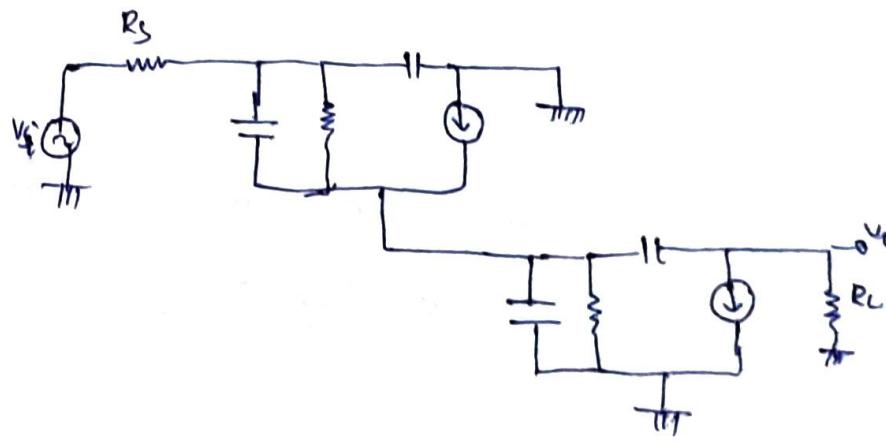

$$R_{M1} = 0.71 \text{ k}\Omega$$


Circuit resembles same as earlier discussed.

~~R_{M1}~~

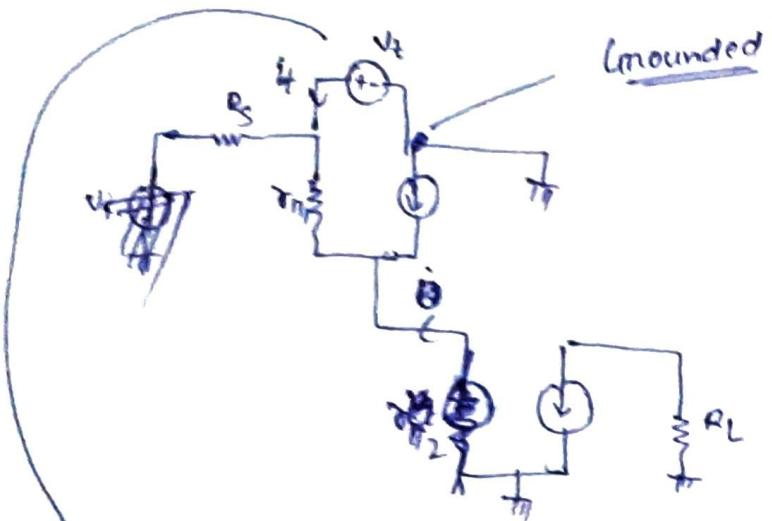


equivalent resistance will be R_{in} .
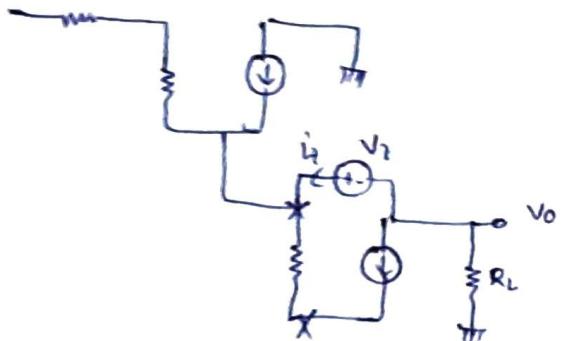
$$R_{M1} = R_{in} = 2.5 \text{ M}\Omega.$$



$$R_{M2} = \cancel{152} \text{ k}\Omega.$$

$$R_{in2} = 7 \text{ k}\Omega.$$

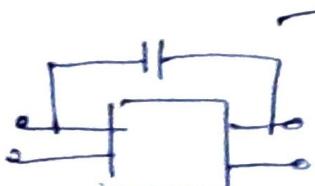

in 2nd circuit


$R_{M2} \rightarrow$ lower than earlier (darlington pair).

Miller capacitance C_M present in darlington pair

Slow in nature.

If we remove it, we can achieve higher Bandwidth.

Miller capacitance

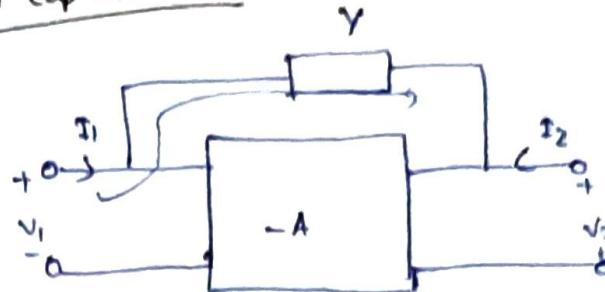

$$\frac{v_2}{v_1} = -A$$

$$v_1 - \frac{I}{Y} - v_2 = 0$$




$$v_1 - \frac{I}{Y} + Av_1 = 0$$



$$v_1(1+A) = \frac{I}{Y}$$

$$Y(I+A) = \frac{I}{v_1}$$

$$Y' = Y(1+A)$$

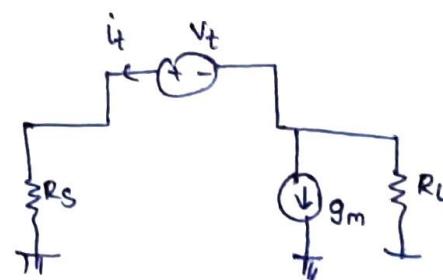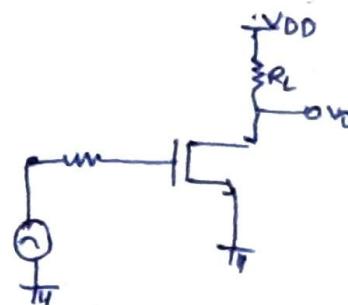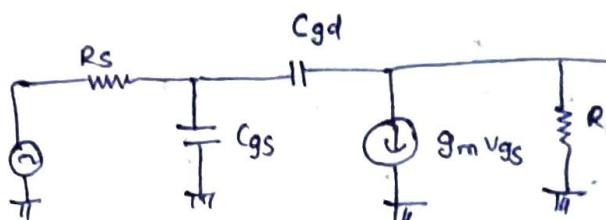

$$V_D = -g_m R_L$$



$$\begin{aligned}\frac{V_D}{i_D} &= R_S + R_L + g_m R_S R_L \\ &= R_S (1 + g_m R_L) + R_L\end{aligned}$$

$$f_{3dB} = \frac{1}{2\pi \sqrt{C_{gd}(R_S(1+g_m R_L) + R_L) + C_{gs} R_S}}$$


$$= \frac{1}{2\pi \sqrt{\frac{C_{gd}(1+g_m R_L) R_S}{C_{gd} R_S + C_{gd} R_L + C_{gs} R_S}}}$$

Miller capacitance


Miller capacitance

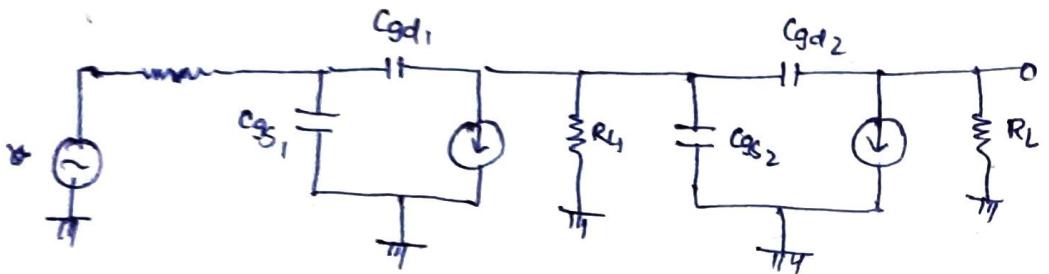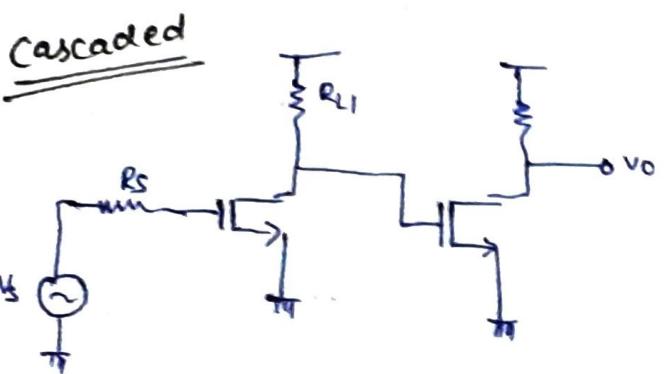

Cascode

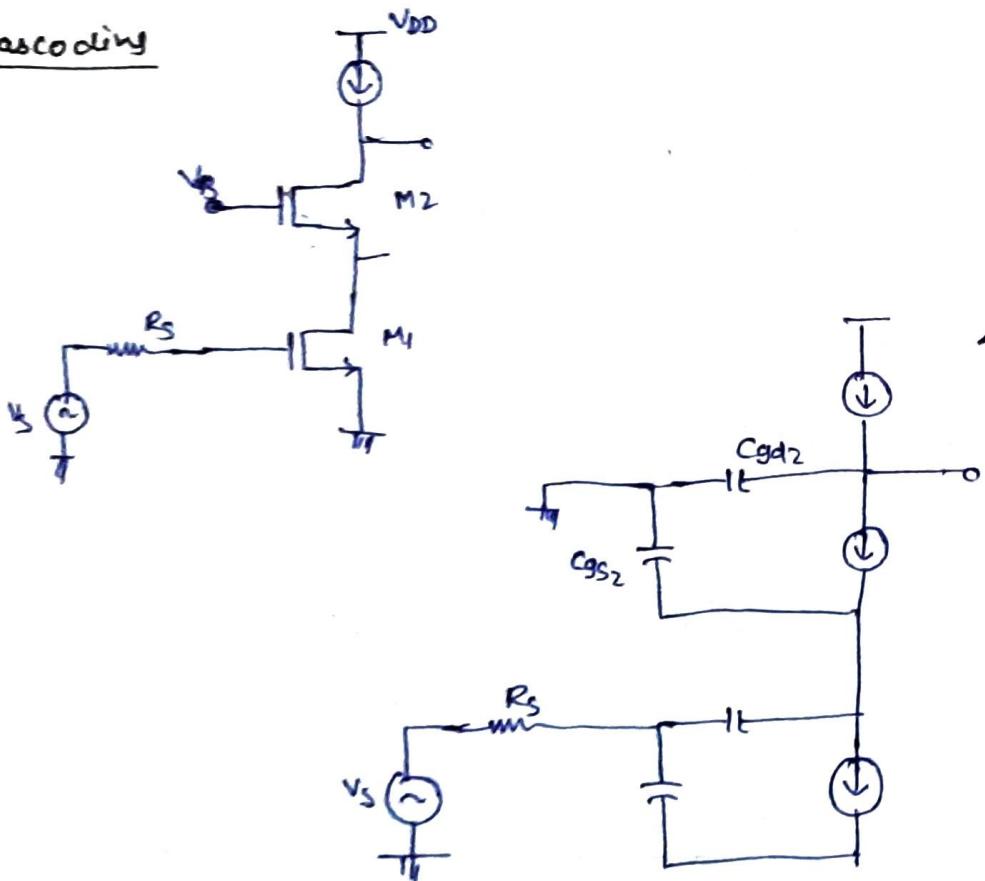

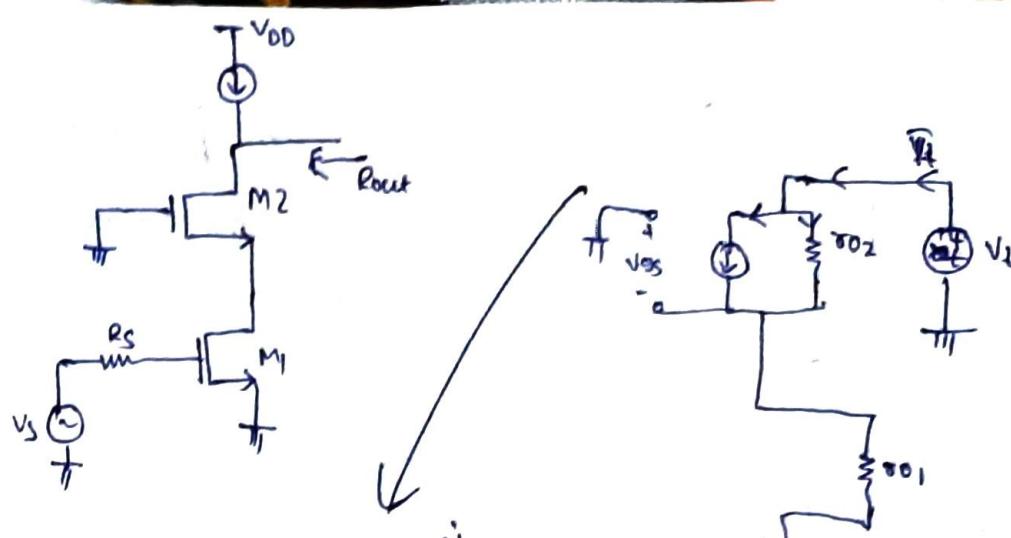No miller capacitance
b/w op. p.
bandwidth will be improved
increased



Only gate is
connected to
ground
not source.

$$-v_{gs2} - i_t \tau_{o1} = 0$$

$$-v_{gs2} - g_{m2} v_{ds2} = 0$$

$$\textcircled{1}$$

$$- \frac{(V_t - i_t \tau_{o1})}{\tau_{o2}} = 0$$

\textcircled{2}

$$i_t + g_{m2} i_t \tau_{o1} - \frac{V_t}{\tau_{o2}} + i_t \frac{\tau_{o1}}{\tau_{o2}} = 0$$


$$\frac{V_t}{\tau_{o2}} = i_t \left(1 + g_{m2} \tau_{o1} + \frac{\tau_{o1}}{\tau_{o2}} \right)$$

$$\frac{V_t}{i_t} = \tau_{o2} \left(1 + g_{m2} \tau_{o1} + \frac{\tau_{o1}}{\tau_{o2}} \right)$$



$$\frac{V_t}{i_t} = \tau_{o2} + g_{m2} \tau_{o1} \tau_{o2} + \tau_{o1}$$

$$\frac{V_t}{i_t} \approx (g_{m2} \tau_{o2}) \tau_{o1}$$

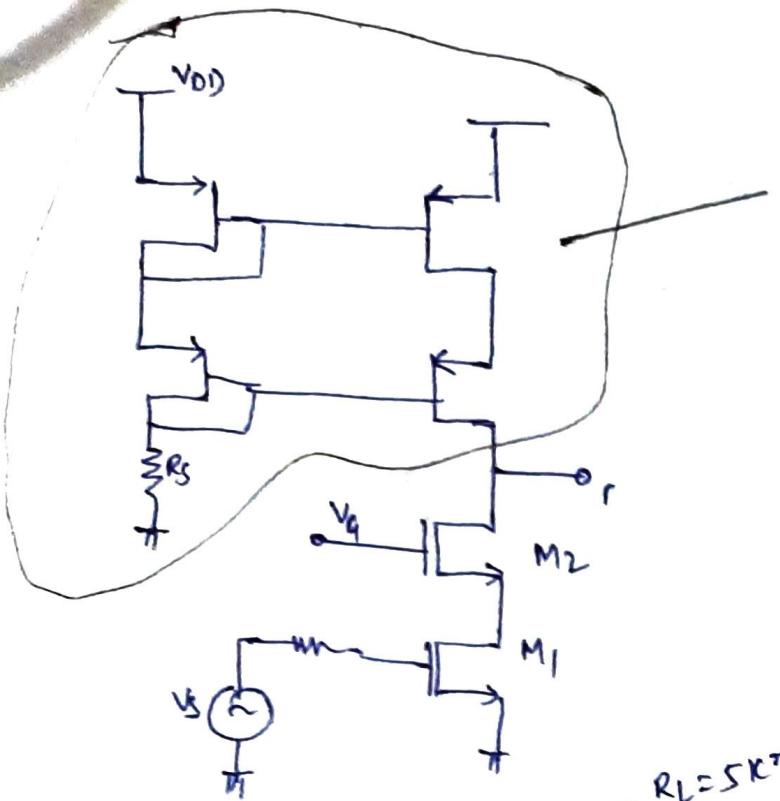To preserve gain
we must have
 R_L of the
order $(g_{m2} \tau_{o2}) \tau_{o1}$



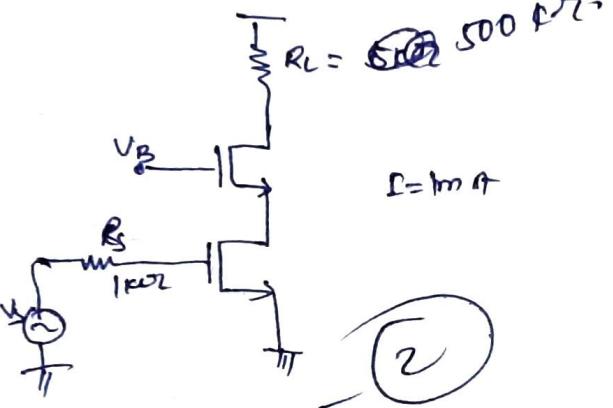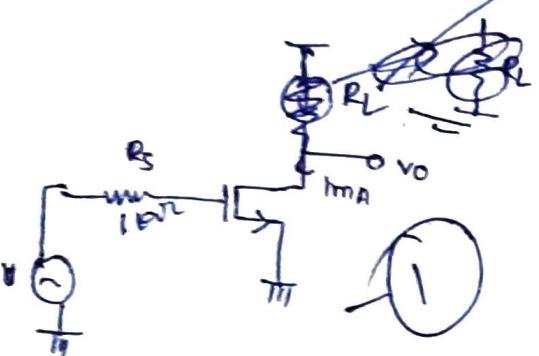design to preserve
the gain of cascoding
circuit.



$$\frac{w}{L} = 100$$

$$2 \mu_n C_{ox} = 60 \mu A/V^2$$

$$(g_{m2} r_{o2}) r_{o1}$$

$$c_{gs} = 100 \text{ fF}$$

$$r_{o1} = r_{o2} = 10 k\Omega$$

$$c_{gd} = 200 \text{ pF}$$

$$g_{m2} = \sqrt{2 \mu_n C_{ox} \frac{w}{L} \times I}$$

$$= \sqrt{2 \times 60 \times 10^{-6} \times 100 \times 10^{-3}}$$

$$= \sqrt{12 \times 10^{-6}}$$

$$= 3.46 \times 10^{-3}$$

$$(g_{m2} r_{o2}) r_{o1} = 3.46 \times 10^{-3} \times 10 \times 10 \times 10^6$$

$$346 \times 10^3$$


$$346 k\Omega$$

$$f_{3dB} = \frac{1}{2\pi \left\{ C_{GS} R_{GS} + C_{GD} R_{GD} \right\}}$$

for circuit ①.

$$f_{3dB} = \frac{1}{2\pi \left\{ C_{GS} R_S + C_{GD} (R_S + R_L + g_m R_S R_L) \right\}}$$

for circuit -2

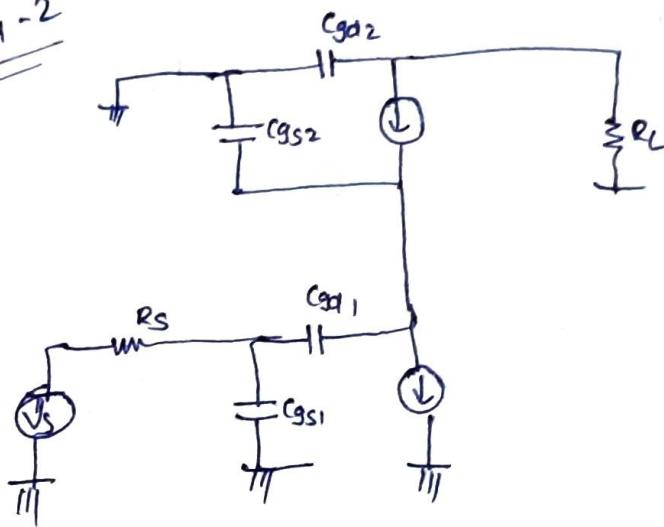


$$= \frac{1}{2\pi \left(\frac{100 \times 10^{-15}}{10^3} + \frac{20 \times 10^{-15}}{(1+5+\frac{3.96 \times 10^{-12}}{23.3 \times 10^3}) \times 1 \times 5} \right)}$$

$$= \frac{1}{2\pi \left(10^{-10} + 4.66 \times 10^{-12} \right)}$$

$$= \frac{1}{2\pi \times 5.66} \times 10^{10}$$

$$= 0.2775 \times 10^{10}$$

$$= 2.78 \times 10^9$$

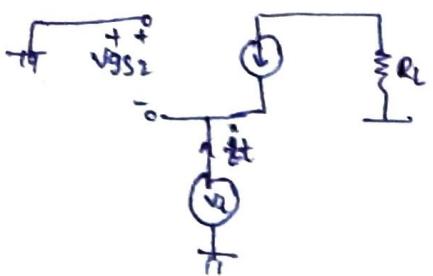

$$i_2 = -g_{m2} V_{gs2}$$


$$-V_{gs} - V_2 = 0$$

$$\frac{V_2}{i_2} = \frac{1}{g_{m2}}$$

$$\underline{\underline{V_2}} = -g_{m1} V_S \times \frac{1}{g_{m2}}$$

Gain of cascoding
amplifier.
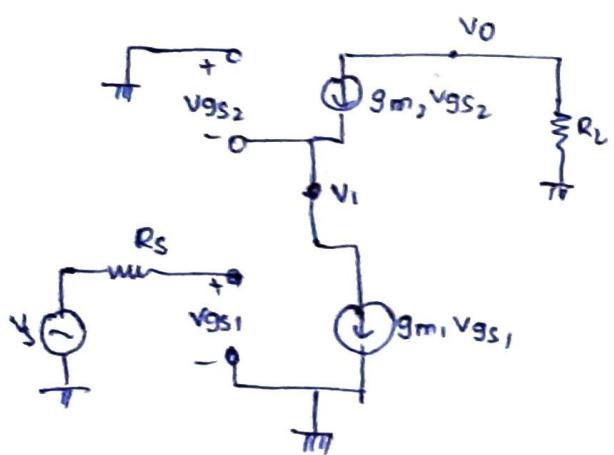
$$\frac{V_1}{V_S} = -\frac{g_{m1}}{g_{m2}} = -1$$



$$V_{gs2} = -V_1$$



$$V_0 = -R_L g_{m2} V_{gs2}$$

$$V_0 = -R_L g_{m2} \times (-V_1)$$

$$\frac{V_0}{V_1} = R_L g_{m2}$$

$$\boxed{\frac{V_0}{V_S} = \frac{V_1}{V_S} \times \frac{V_0}{V_1} = -1 \times g_{m2} R_L = -g_{m2} R_L}$$

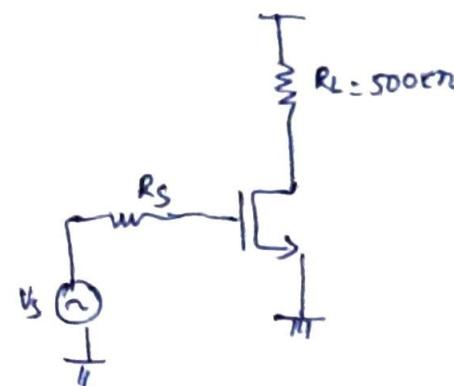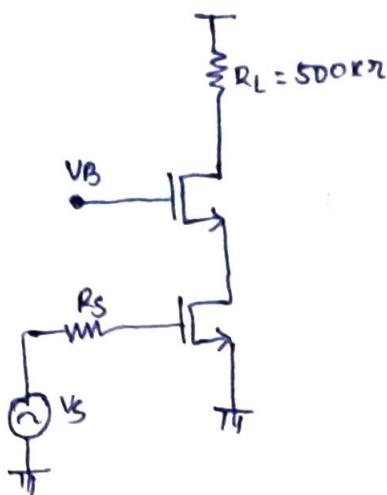Both cascoding and CS gain are $-g_m R_L$



$$f_{3-dB} = \frac{1}{2\pi \left\{ C_{GS} R_S + C_{GD} (R_S + R_L + g_m R_S R_L) \right\}}.$$

$$= \frac{1}{2\pi \left[\frac{100 \times 10^{-15} \times 10^3}{x 10^3} + 20 \times 10^{-15} \left\{ 1 + 500 + \frac{3.46 \times 10^3}{1 \times 500} \right\} \right]}.$$

$$= \frac{1}{2\pi \left[10^{-10} + 2 \times 10^{-11} [2231] \right]}.$$




$$= \frac{10^{10}}{2\pi [1 + 0.2 \times 2231]}.$$

$$= \frac{10^{10}}{2\pi \times 447.2}.$$

$$= 0.003512 \times 10^{10}$$

$$\therefore = 35.12 \times 10^6.$$

$$\therefore = 3.5 \text{ MHz}.$$

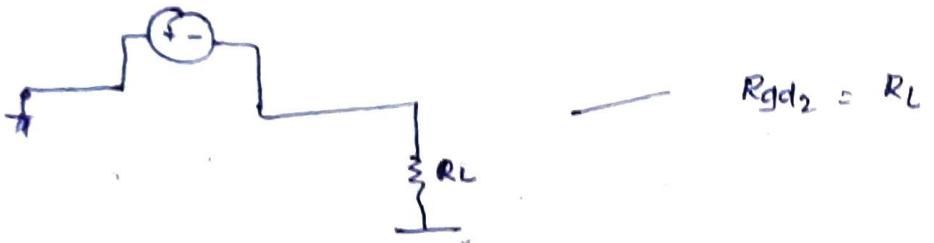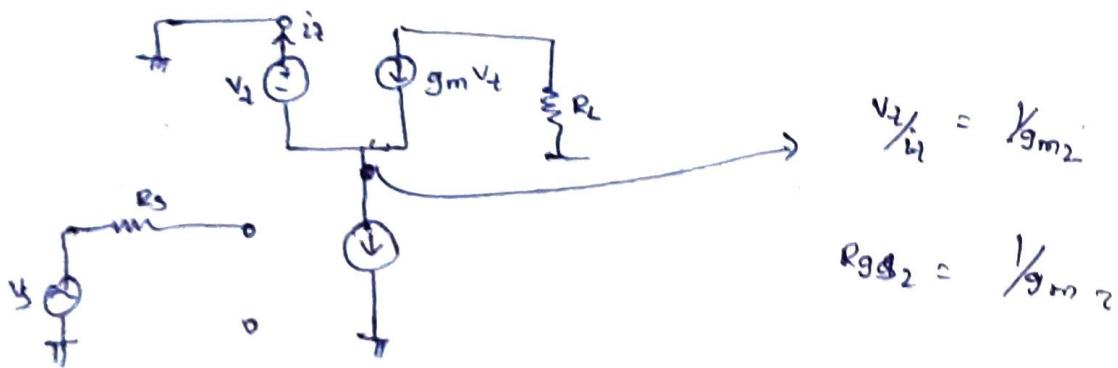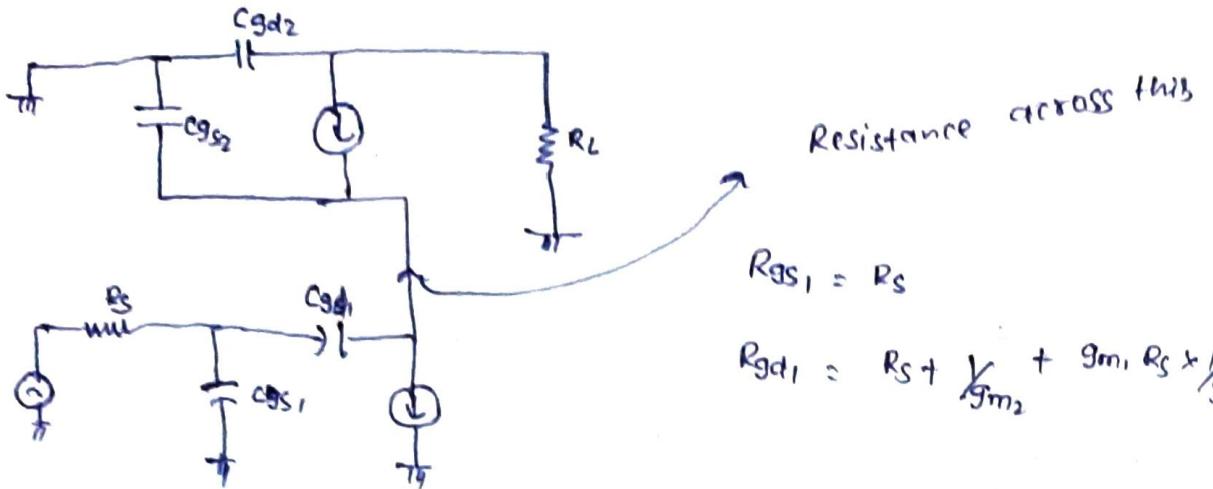


$$f_{3dB} = \frac{1}{2\pi \left\{ C_{GS1} R_S + C_{GD1} R_{GD1} + C_{GS2} \times \frac{1}{g_{m2}} + C_{GD2} R_L \right\}}$$

$$= \frac{1}{2\pi \left\{ C_{GS1} \left\{ R_S + \frac{1}{g_{m2}} \right\} + C_{GD1} \left\{ 2R_S + \frac{1}{g_{m2}} + R_L \right\} \right\}}$$

$$2 \frac{2\pi}{10^{-10} \times 1.289 + 2 \times 10^{-11} [2 + \frac{1}{3.46} + 500]} = 1004.578 \times 10^{-11}$$

$$= \frac{10^{10}}{2\pi \sqrt{1.289 + 100.4578}} = 15.6 \text{ MHz}$$

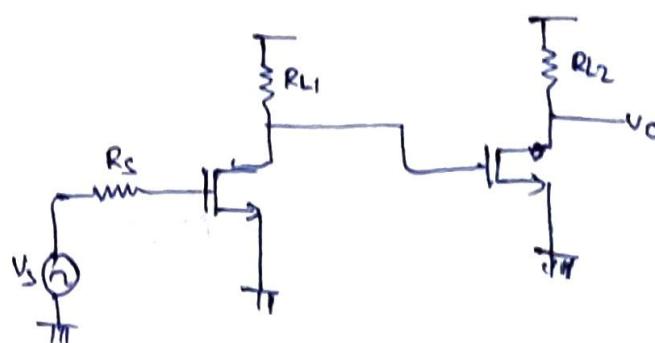
b) Cascading design with more component is faster than simple CS Amplifier having same gain.



$$\begin{aligned} \frac{V_o}{V_s} &= (g_{m1} \times R_{L1}) (g_{m2} \times R_{L2}) \\ &= 3.46 \text{ m} (1) \quad 3.46 (1) \end{aligned}$$

$$R_{L1} = R_{L2} = 12k\Omega$$

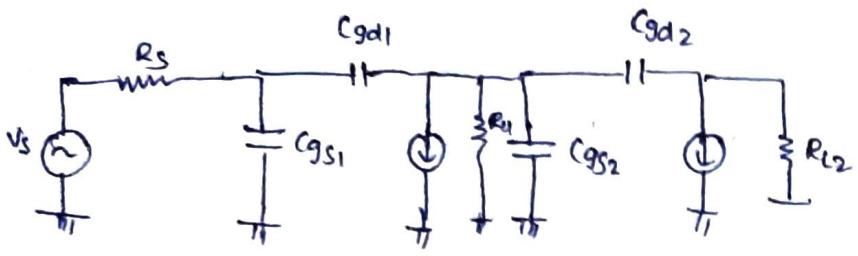to match the gain of above discussed amplifier.



$$R_{gg} = R_s$$

$\text{LK}\Omega$

$$R_{gd_1} = R_s + R_{L1} + g_m R_s R_{L1}$$

$$R_{gs_2} = R_{L1}$$

$$R_{gd_2} = R_{L1} + R_{L2} + g_{m2} R_{L1} R_{L2}$$

$$R_{gd_1} = 10^3 + 12 \times 10^3 + 3.46 \times 10^{-3} \times 1 \times 12 \times 10^3 \times 10^3$$

$$= 54.52 \text{ K}\Omega$$

$$R_{gs_2} = 12 \text{ K}\Omega$$

$$R_{gd_2} = 24 \text{ K} + 3.46 \times 10^{-3} \times 144 \times 10^3$$

$$= 522.24 \text{ K}\Omega$$

$$f_{3dB} =$$

$$\frac{1}{2\pi \left\{ C_{gs} \times 1\text{K} + C_{gd_1} \times 54.52 \text{K} + C_{gs_2} \times 12 \text{K} + R_{gd_2} \times 522.24 \text{K} \right\}}$$

$$= \frac{1}{2\pi \left\{ 100 \times 10^{-15} \times 13 \times 10^3 + 20 \times 10^{-15} \times 10^3 \times 522.24 \right\}},$$

$$= \frac{1}{2\pi \times \left\{ 13 \times 10^{-10} + 1.15352 \times 10^{-10} \right\}}$$

$$= \frac{10^{10}}{2 \times 3.14 \times 128.352}$$

$$f_{3dB} = 1.3 \text{ MHz}$$

for 0 Miller capacitor

$$f_{3dB} = 15.6 \text{ MHz}$$

for 1 Miller capacitor


$$f_{3dB} = 3.56 \text{ MHz}$$

for 2 Miller capacitance

$$f_{3dB} = 1.3 \text{ MHz}$$

5/10/23

Stability of \times feedback amplifier

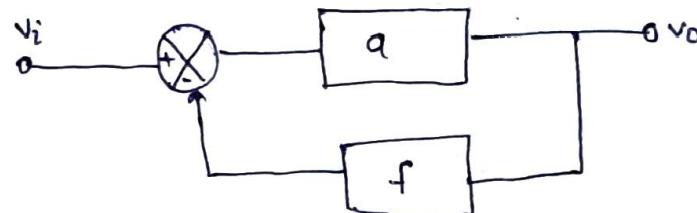

$a_f \rightarrow$ loop gain
 $a \rightarrow$ O.L. gain

$$\frac{v_o}{v_i} = \frac{a}{1 + af}$$

C.L. gain

$$= \frac{a(j\omega)}{1 + a(j\omega)f}$$

$$\frac{v_o}{v_i} = \frac{a(j\omega)}{1 + |a(j\omega)| \angle a(j\omega) f}$$

$$T(j\omega) = a(j\omega) f$$


i) if $|T(j\omega)| = 1$
 $\angle T(j\omega) = 180^\circ$

$\rightarrow v_o$ becomes oscillatory.

(ii) if $|T(j\omega)| > 1$


$$\angle T(j\omega) = 180^\circ$$

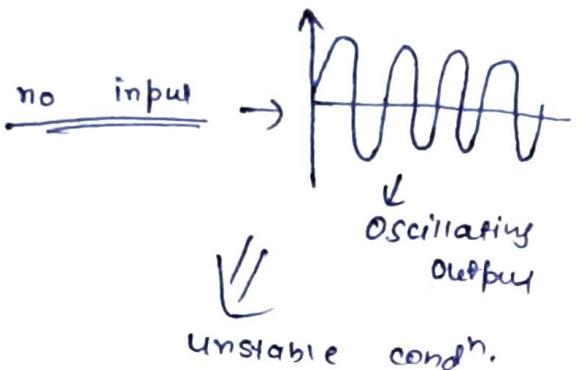$\rightarrow V_o \rightarrow \text{unstable}$



In practical, amplitude & parameter doesn't vary with time

due to practical nature of ref.

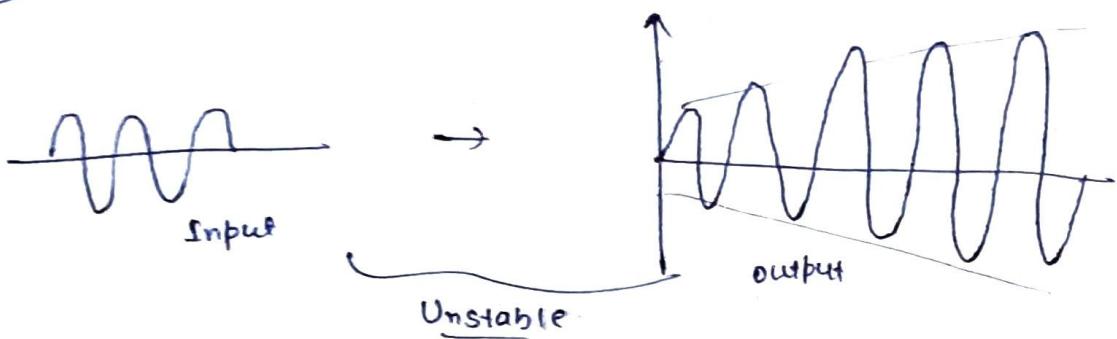

(iii) if $|T(j\omega)| < 1$

$$\text{and } \angle T(j\omega) = 180^\circ$$

} $\rightarrow \text{Stable.}$

These three conditions are

Barkhausen's criterion

2 pole amplifier

$$a(s) = \frac{a_0}{(s+p_1)(s+p_2)}$$

$$= \frac{a_0'}{(1+s/p_1)(1+s/p_2)}$$

All poles are widely apart

$$p_2 \gg p_1$$



$$p_2 > 10p_1$$

p_1 & p_2 are widely apart.

$$|a(j\omega)| = \frac{a_0'}{\sqrt{1 + (\frac{\omega}{p_1})^2} \sqrt{1 + (\frac{\omega}{p_2})^2}}$$

$$|a(j\omega)|_{dB} = 20 \log \left(\frac{a_0'}{\sqrt{1 + (\frac{\omega}{p_1})^2} \sqrt{1 + (\frac{\omega}{p_2})^2}} \right)$$

$$20 \log |a(j\omega)| = 20 \log a_0 - 20 \log \sqrt{1 + \left(\frac{\omega}{P_1}\right)^2} - 20 \log \sqrt{1 + \left(\frac{\omega}{P_2}\right)^2}.$$

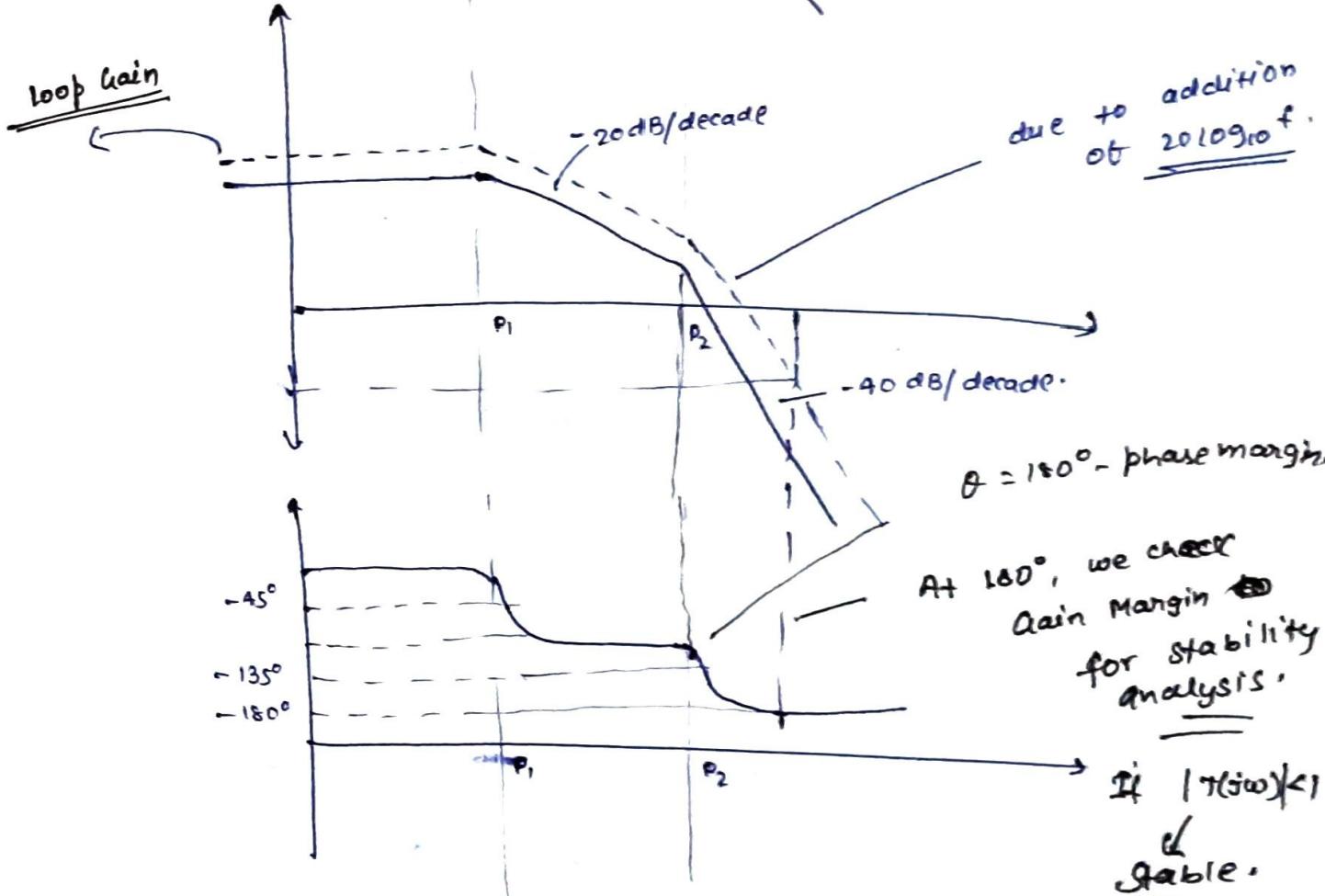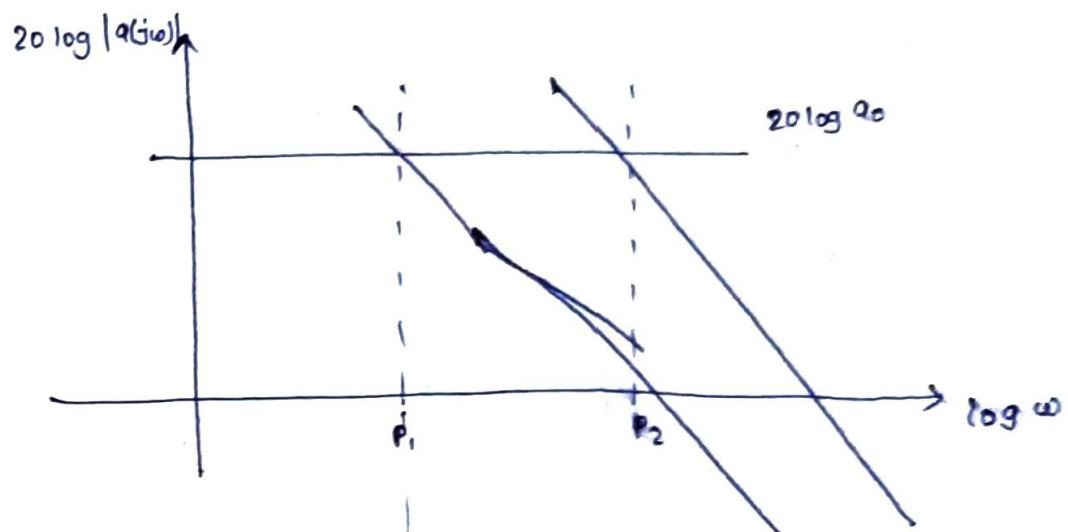

At ~~corner~~ loop gain = 1,

If phase margin $< 180^\circ$, \rightarrow Stable

Greater than 180° \rightarrow Unstable.

Phase = 180°

\hookrightarrow Check GM for Stability.

Q. An amplifier with low freq. feed gain $40K V/V$

-ve real poles are 2kHz , 200kHz , 4MHz . It is connected in feedback with β -constant.

Close loop gain of the circuit ≈ 900 .

Find out the phase margin?

Solⁿ:

$$\begin{aligned} A(j\omega) &= \frac{a_0 \beta}{\left(1 + j\frac{\omega}{P_1}\right) \left(1 + j\frac{\omega}{P_2}\right) \left(1 + j\frac{\omega}{P_3}\right)} \\ &= \frac{a_0 \beta}{\left(1 + j\frac{f}{A}\right) \left(1 + j\frac{f}{P_2}\right) \left(1 + j\frac{f}{P_3}\right)} \\ &= \frac{40K \beta}{\left(1 + j\frac{f}{2\pi}\right) \left(1 + j\frac{f}{200K}\right) \left(1 + j\frac{f}{4M}\right)} \end{aligned}$$

$$\frac{a_0}{1 + a_0 \beta} = 400$$

$$\frac{96 \times 10^3}{1 + 40K \beta} = 960 \quad 100 = 1 + 40 \times 10^3 \times \beta$$

$$\beta = \frac{99 \times 10^{-3}}{40}$$

$$= 2.475 \times 10^{-3}$$

$$a_0 \beta = 2.475 \times 10^{-3} \times 40 \times 10^3$$

∴ $\beta = 99.$

$$a(j\omega) \beta = \frac{100}{\left(1 + \frac{jf}{2k}\right) \left(1 + \frac{jf}{200k}\right) \left(1 + \frac{jf}{4M}\right)}.$$

$$|a(j\omega) \beta| = 1$$

$$\frac{100}{\sqrt{1 + \left(\frac{f_c}{2k}\right)^2} \sqrt{1 + \left(\frac{f_c}{200k}\right)^2} \sqrt{1 + \left(\frac{f_c}{4M}\right)^2}} = 1$$

$$\text{at } f = 2k$$

$$\frac{100}{\sqrt{2}} \approx 1$$

$$\text{at } f = 200k.$$

$$f_{p_1} < f_c < f_{p_2}$$

$$\frac{100}{100 \times \sqrt{2} \times 1} = \frac{1}{\sqrt{2}} < 1$$

$$f_{p_1} < f_c < f_{p_2} \quad \rightarrow \quad p_3 \text{ terms can be ignored.}$$


$$100^2 = \left(1 + \frac{f_c^2}{(2k)^2}\right) \left(1 + \frac{f_c^2}{(200k)^2}\right)$$

$$\Rightarrow \frac{f_c^4}{(2k)^2 (200k)^2} + f_c^2 \underbrace{\left(\frac{1}{(2k)^2} + \frac{1}{(200k)^2}\right)}_{2.5 \times 10^{-7}} - 100^2 = 0.$$

$$\frac{x^2}{9 \cdot 6} + x \times \left(\frac{1}{a} + \frac{1}{b}\right) - 100^2 = 0.$$

$$x = \frac{-\left(\frac{1}{a} + \frac{1}{b}\right) \pm \sqrt{\left(\frac{1}{a} + \frac{1}{b}\right)^2 - 4 \cdot 10^4 \cdot \frac{1}{ab}}}{2 \frac{1}{ab}}$$

$$f_c = \frac{457.230}{X 10^3}$$

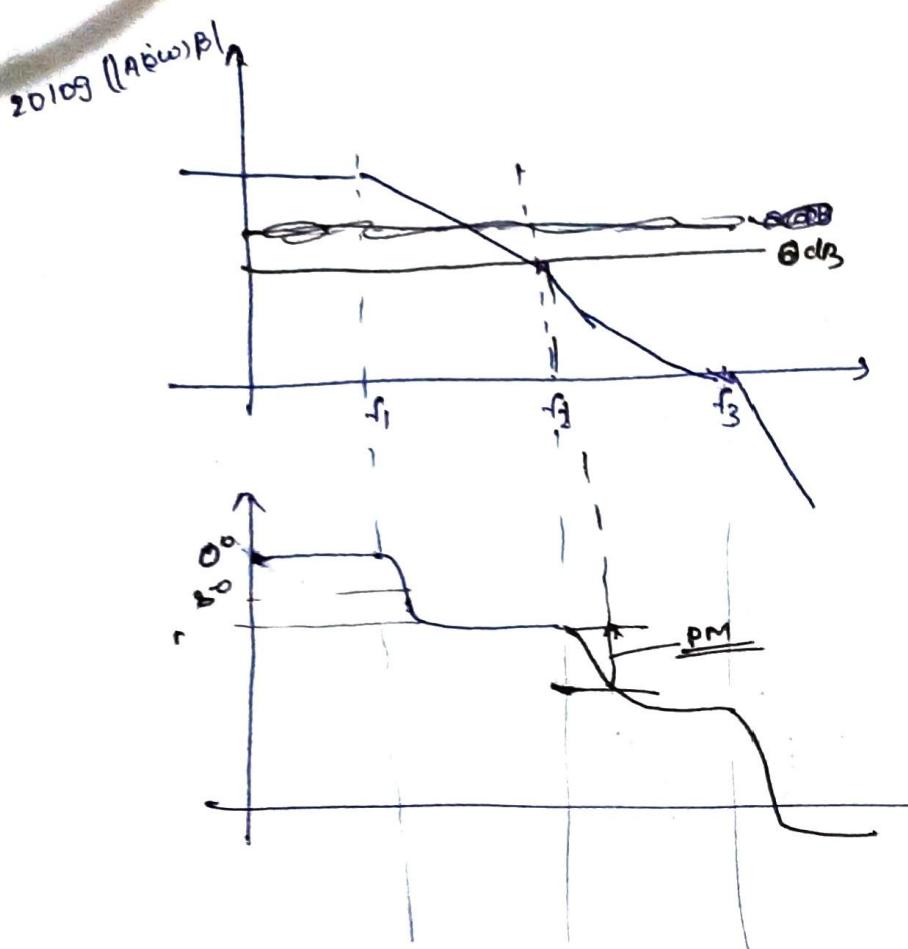

$$\begin{aligned}
 f_1 &= 2 \text{ kHz} \\
 f_2 &= 200 \text{ kHz} \\
 f_3 &= 4 \text{ MHz}
 \end{aligned}$$

$$f_c = 157 \text{ kHz}$$

$$\begin{aligned}
 \angle A(j\omega) \beta &= -\tan^{-1} \frac{f_c}{f_1} - \tan^{-1} \frac{f_c}{f_2} - \tan^{-1} \frac{f_c}{f_3} \\
 &= -89.27^\circ - 38.13^\circ - 2.25^\circ \\
 &\approx -129.65^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{PM} &= 180^\circ - 129.65^\circ \\
 &= 50.35^\circ
 \end{aligned}$$

} General
for circuit
PM should be
 $(50-60)^\circ$

$$\text{Open loop gain} = 40 \text{ dB}$$

$$\text{closed loop gain} = 400 \quad \downarrow$$

~~100~~

$$\frac{A_0}{1 + A_0 \beta} = 100$$

$$100 = \frac{40 \times 10^3}{1 + 40 \times 10^3 \times \beta}$$

$$40 \times 10^3 \times \beta = 100 - 1$$

$$\beta = \frac{399}{40 \times 10^3} \times 10^{-3} \\ = 9.975 \times 10^{-3}$$

$$\beta \approx 0.01$$

$$|A(j\omega) \beta|_{f=f_1} = \frac{A_0 \beta}{\sqrt{\left(1 + \left(\frac{f}{f_1}\right)^2\right)} \sqrt{1 + \left(\frac{f}{f_2}\right)^2} \sqrt{1 + \left(\frac{f}{f_3}\right)^2}}$$

$$At f=f_1 \theta = \frac{40 \times 10^3 \times 10^{-2}}{\sqrt{2} \times \sqrt{1 + (0.01)^2} \sqrt{1 + \left(\frac{2 \times 10^3}{4 \times 10^6}\right)}} \\ \approx -1 \quad \approx 1$$

$$= \frac{400}{\sqrt{2}} = 200\sqrt{2}.$$

$$At f=f_2$$

$$|A(j\omega) \beta| = \frac{A_0 \beta}{\frac{f_2}{f_1} \times \sqrt{2} \times \sqrt{1 + \frac{200 \times 10^3}{4 \times 10^3}}} \\ = \frac{40 \times 10^3 \times 10^{-2}}{\frac{2}{200} \times \sqrt{2} \times \sqrt{1 + \frac{100}{4}} \\ = \frac{2 \sqrt{2}}{2 \sqrt{2}}.$$

At $f = f_3$,

$$\begin{aligned} |A_0(j\omega)\beta| &= \frac{A_0 \beta}{f_3/f_1 \times \frac{f_3}{f_2} \times \sqrt{2}} \\ &= \frac{10 \times 10^3 \times 10^3 \times 10^{-2}}{\frac{10 \times 10^6}{2 \times 10^3} \times \frac{10^3}{200 \times 10^5} \times \sqrt{2}} \\ &\quad \cancel{1000 \times 10^{-2}} \quad \cancel{100} \\ &= \frac{1}{100\sqrt{2}}. \end{aligned}$$

$f_2 < f_c < f_3$ and also $f_c \ll f_3$.

$f_2 \gg f_1, f_c \gg f_1$

at $f = f_c$

$$\begin{aligned} |A_0(j\omega)\beta| &= \frac{A_0 \beta}{\sqrt{1 + \left(\frac{f_c}{f_1}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_2}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_3}\right)^2}} \\ &\approx \frac{A_0 \beta}{\frac{f_c}{f_1} \sqrt{1 + \left(\frac{f_c}{f_2}\right)^2}} > 1. \end{aligned}$$
$$A_0 \beta = \frac{f_c}{f_1} \sqrt{1 + \left(\frac{f_c}{f_2}\right)^2}$$

$$(A_0 \beta)^2 = \left(\frac{f_c}{f_1}\right)^2 + \left(\frac{f_c}{f_2}\right)^2 \left(\frac{f_c}{f_1}\right)^2$$

$$\frac{x^4}{f_1^2 f_2^2} + \frac{x^2}{f_1^2} - A_0^2 \beta^2 = 0$$

$$x^4 + f_2^2 x^2 - f_1^2 f_2^2 (A_0 \beta)^2 = 0$$


$$x^4 + 4 \times 10^{10} x^2 - 4 \times 4 \times 10^6 \frac{16 \times 10^8 * 10^{-4}}{256 \times 10^{20}}$$

$$\left. \begin{array}{l} f_1 = 2K \\ f_2 = 200K \end{array} \right\}$$

$$f_c = 380 \text{ cHz}$$


$$\angle A(j\omega) \beta = -157^\circ \quad PM = 180^\circ - |\angle A(j\omega) \beta|$$

$$PM = 180^\circ - 157^\circ$$

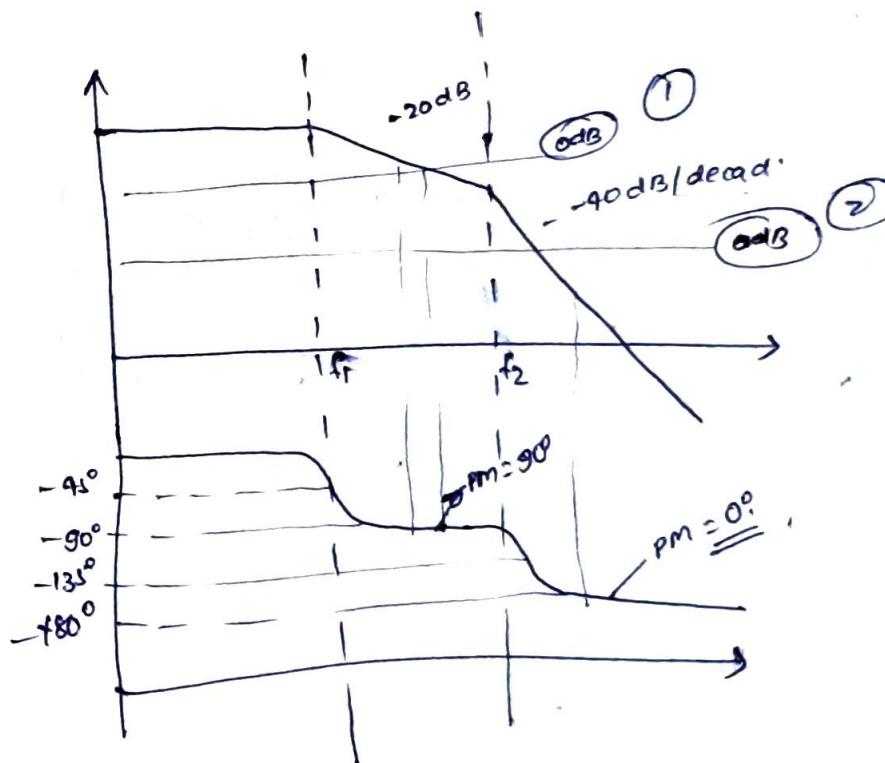


for any two pole system,

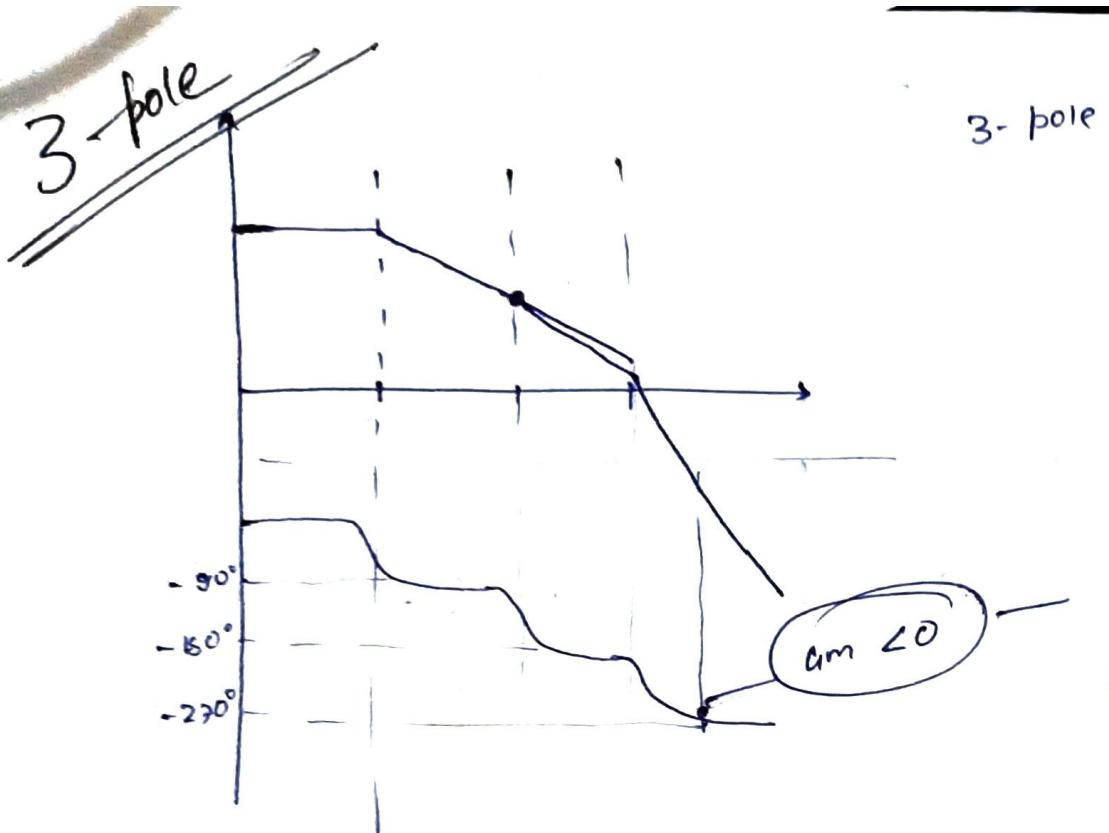it can't be unstable but it may
be very close to instability.



So, for 3-pole system
GM become unstable

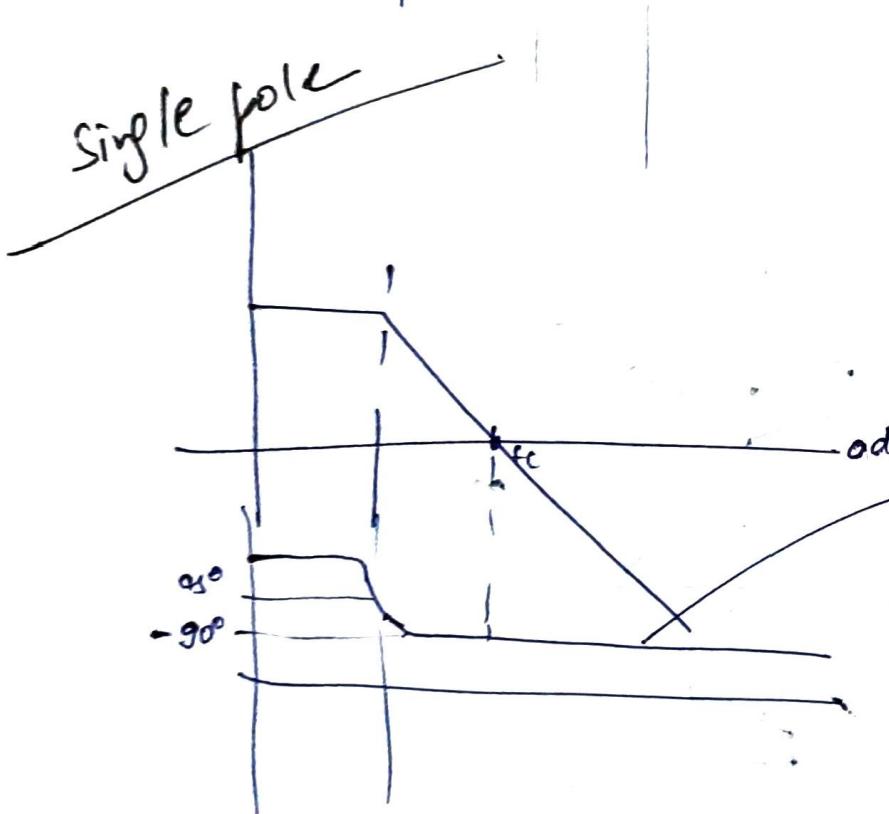

for single pole system
GM always will be 90°
and stable.

$$A_o(j\omega) \beta_B = \frac{A_o B}{\left(1 + j \frac{f}{f_1}\right) \left(1 + j \frac{f}{f_2}\right)}$$

$$A_0(j\omega)\beta = \frac{A_0\beta}{\left(1 + j\frac{f}{f_1}\right)}$$

$f_2 \gg f_1$
domin

$$|A_0(j\omega)\beta| = \frac{A_0\beta}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}}$$


$$|A_0(j\omega_c)\beta| = \frac{A_0\beta}{\sqrt{1 + \left(\frac{f_c}{f_1}\right)^2}}$$

as $f_c \gg f_1$

$$|A_0(j\omega_c)\beta| = \frac{A_0\beta}{f_c/f_1} \approx 1.$$


only
for
single-pole
System
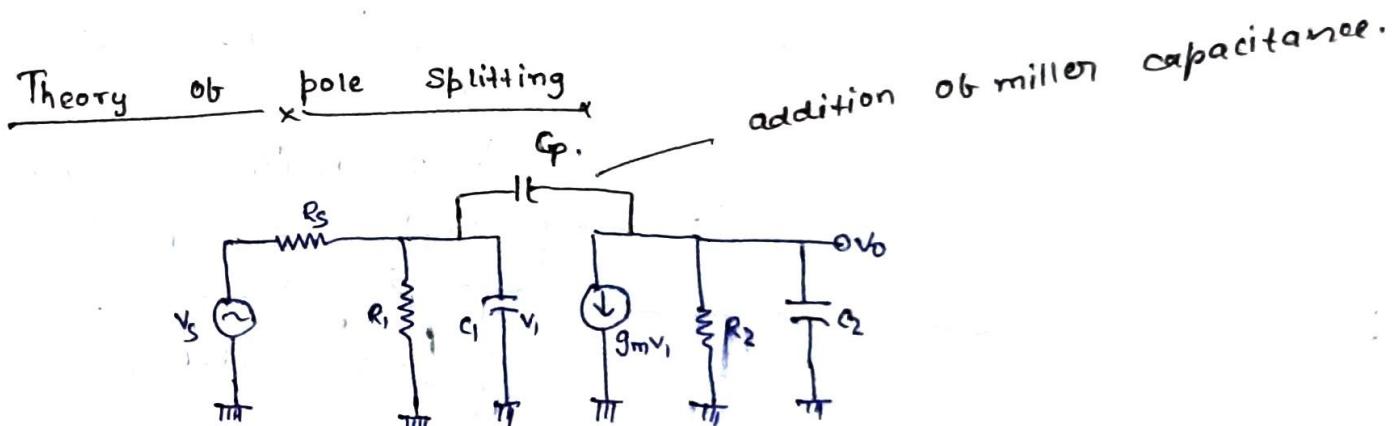
$$\boxed{\frac{A_0\beta}{f_1} = \text{Gain Bandwidth constant}}$$



$$f_d = \frac{1}{2\pi \left\{ C_1 R_1 \| R_s + C_2 R_2 \right\}}$$
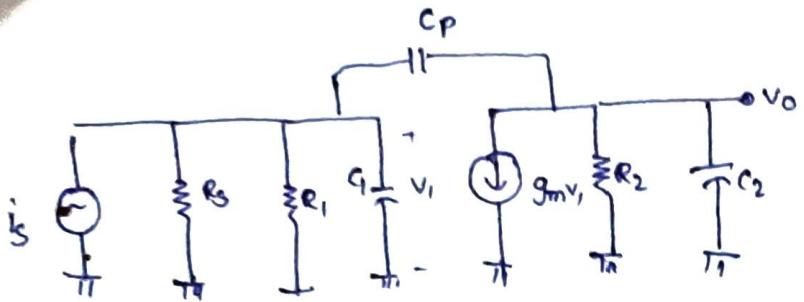
$$f_{nd} = \frac{1}{2\pi} \left\{ \frac{1}{C_1 R_1 R_s} + \frac{1}{C_2 R_2} \right\}.$$



$$R_1' = R_1 \parallel R_S$$

$$\frac{V_o(s)}{i_s(s)} = \frac{C_P (C_P s - g_m) R_2}{s^2 R_2 R_1' (C_1 C_2 + C_P (C_1 + C_2)) + s \{ R_1' (C_P + C_1) + R_2 (C_P + C_2) \\ + g_m R_2 R_1' C_P \} + 1}$$

$$\frac{V_o}{i_s} = \frac{(C_P s - g_m) R_2}{\left(1 + \frac{s}{P_d}\right) \left(1 + \frac{s}{P_{nd}}\right)}$$

$f_d \ll f_{nd}$, after pole splitting.

$$= \frac{(C_P s - g_m) R_2}{\frac{s^2}{P_d P_{nd}} + s \left[\frac{1}{P_d} + \frac{1}{P_{nd}} \right] + 1}$$

$$\frac{1}{P_d} + \frac{1}{P_{nd}} \approx \frac{1}{P_d}$$

$$\approx R_1' (C_P + C_1) + R_2 (C_P + C_2)$$

$$g_m R_2 R_1' C_P \gg R_1' (C_P + C_1) + R_2 (C_P + C_2) + g_m R_2 R_1' C_P$$

$$\frac{1}{P_d} = g_m R_2 R_1' C_P$$

Considering dominant pole analysis,

then

$$R_{C1} = R_S \parallel R_1 = R_1'$$

$$R_{CS} = R_1' + R_2 + g_m R_1' R_2$$

$$R_{C2} = R_2$$

$$f_d = \frac{1}{2\pi \{ C_1 \times R_1' + C_2 R_2 + C_P \{ R_1' + R_2 + g_m R_1' R_2 \} \}}$$

$$f_d \approx \frac{1}{2\pi g_m R_1' R_2 C_p}$$

In this we can't determine non-dominant pole
we have to go through exact solution
method.


$$\frac{1}{P_d P_{nd}} = R_2 R_1' \{ c_1 c_2 + C_p (c_1 + c_2) \}.$$

$$\frac{1}{P_d} = g_m R_2 R_1' C_p$$

$$\Rightarrow \frac{g_m R_2 R_1' C_p}{P_{nd}} = R_2 R_1' \{ c_1 c_2 + C_p (c_1 + c_2) \}.$$

$$P_{nd} = \frac{g_m C_p}{c_1 \cancel{c_2} + C_p (c_1 + c_2)}.$$
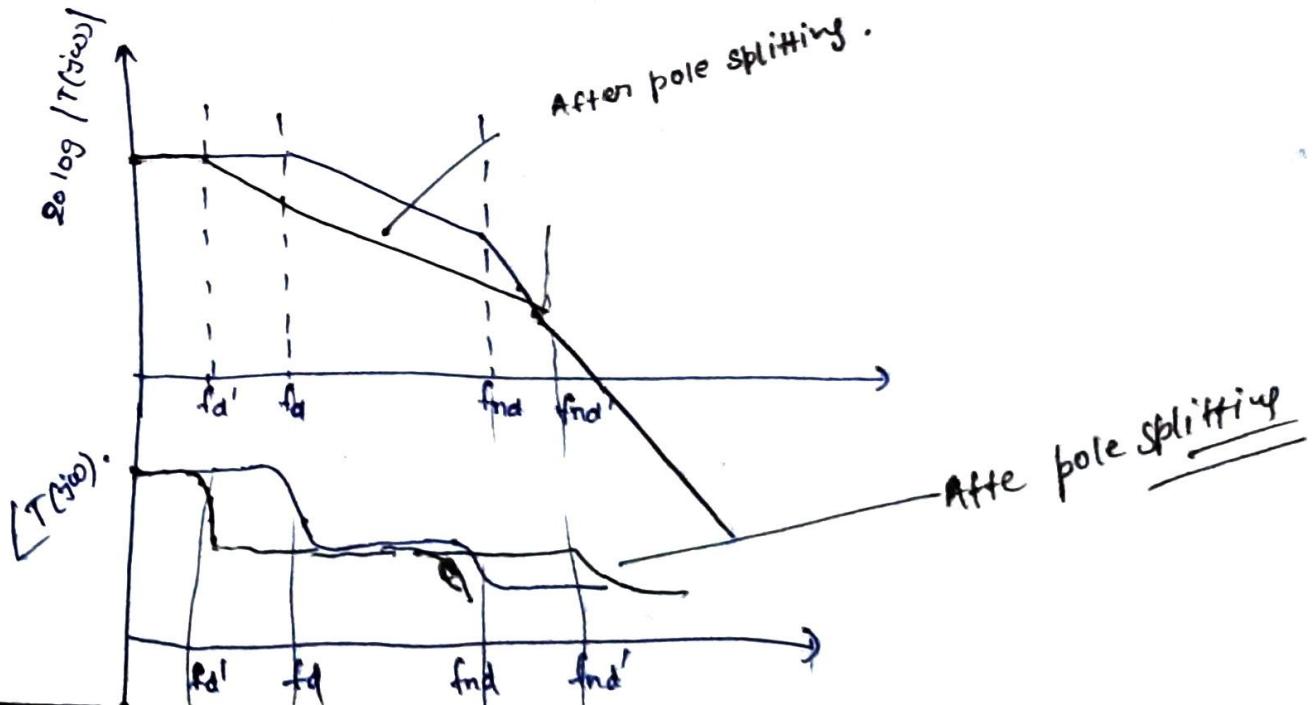
$$f_{nd}' = \frac{g_m C_p}{2\pi \{ c_1 c_2 + C_p (c_1 + c_2) \}},$$




Q1 consider the following transfer fn

$$T(jf) = \frac{5 \times 10^5}{\left(1 + \frac{jf}{1M}\right) \left(1 + \frac{jf}{10M}\right) \left(1 + \frac{jf}{100M}\right)}$$

Insert a dominant pole in the T.F so that
the PM becomes 45° .

Soln:- Step 1 calculate PM for $T(jf)$.

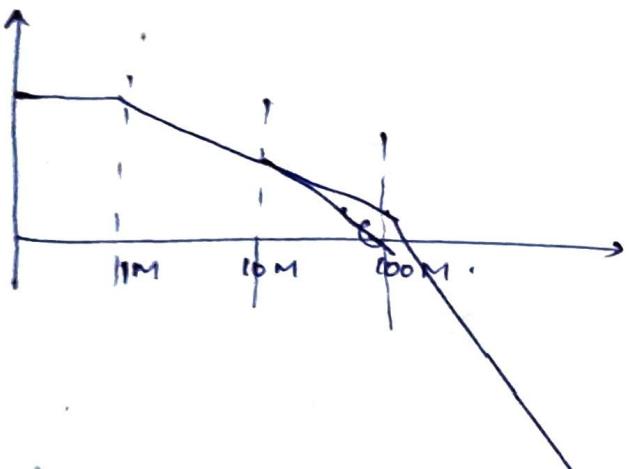

$$|T(jf)| = 1$$

$$\frac{5 \times 10^5}{\sqrt{1 + \left(\frac{fc}{1M}\right)^2} \cdot \sqrt{1 + \left(\frac{fc}{10M}\right)^2} \cdot \sqrt{1 + \left(\frac{fc}{100M}\right)^2}} = 1$$

first determine where fc lies;

$$\text{At } fc = f_1$$

$$|T(jf)| = \frac{5}{\sqrt{2}} \times 10^5$$

$$\text{At } fc = 10M$$

$$|T(jf)| = \frac{5 \times 10^5}{\frac{50}{2} \times \sqrt{2}} = \frac{5}{2\sqrt{2}} \times 10^5$$

$$\text{At } fc = 100M$$

$$|T(jf)| = \frac{5 \times 10^5}{\sqrt{2} \times}$$

$$f_c > 100M$$

from the phase plot we can say,

GM is -ve

\Rightarrow Unstable



Inserting dominant pole.

$$T(j\omega) = \frac{5 \times 10^5}{\left(1 + j\frac{\omega}{f_d}\right) \left(1 + j\frac{\omega}{1M}\right) \left(1 + j\frac{\omega}{10M}\right) \left(1 + j\frac{\omega}{100M}\right)}$$



so to get $\rho M = 90^\circ$, 0dB line cross over

should occur at 135° .




from the phase graph at $f = f_2$ it lies on 135°

Hence,

at $f = f_2$,

$$|T(jf_2)| = 1 \Rightarrow \frac{5 \times 10^5}{\sqrt{1 + \left(\frac{f_2}{f_d}\right)^2} \sqrt{1 + \left(\frac{f_2}{1M}\right)^2} \times 1 \times 1} \approx 1$$

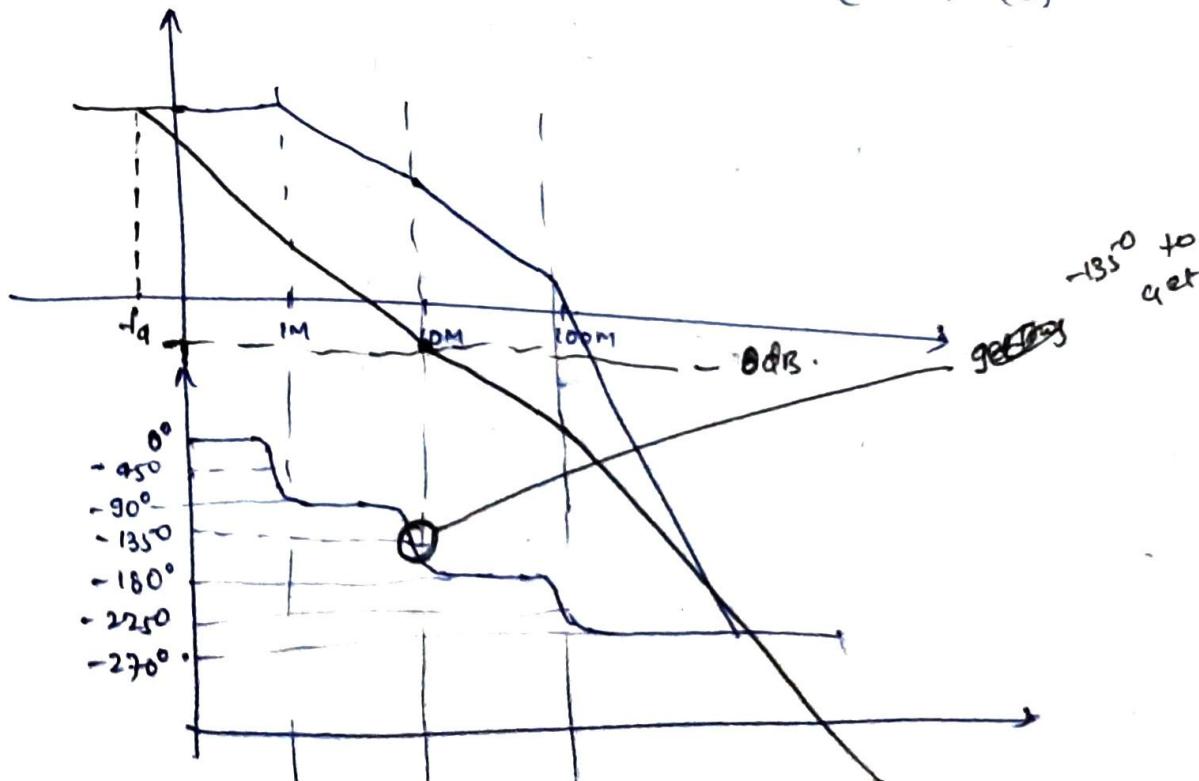

$$(5 \times 10^5)^2 = \left\{ 1 + \left(\frac{f_2}{f_d} \right)^2 \right\} \times 2 \times 1$$

$$\frac{25 \times 10^{10}}{2} = 1 + \left(\frac{f_2}{f_d} \right)^2$$


$$\left(\frac{f_2}{f_d} \right)^2 = \frac{25 \times 10^{10}}{2}$$

$$\frac{\cancel{10^2} \times 10^8}{\cancel{f_d}} = \frac{\cancel{25} \times 10^8}{\sqrt{2}}$$





$$f_d = 20\sqrt{2} = \underline{28.28 \text{ Hz}}$$

21/10/23

Two State CMOS Op-amp.

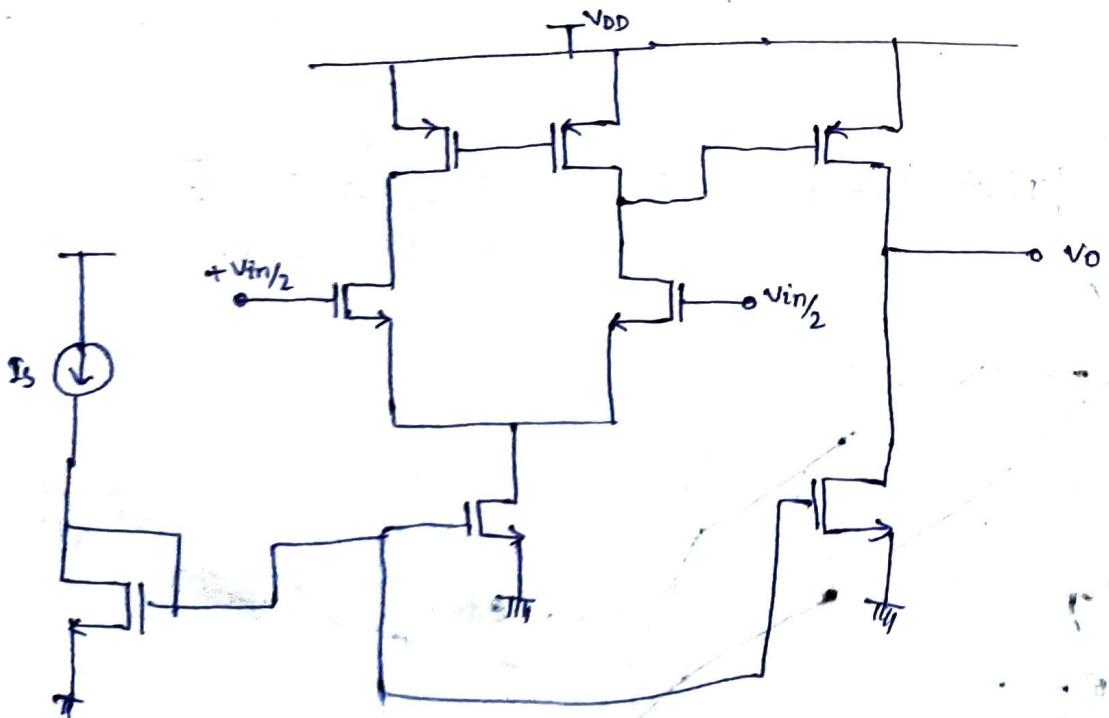

Differential Amplifier

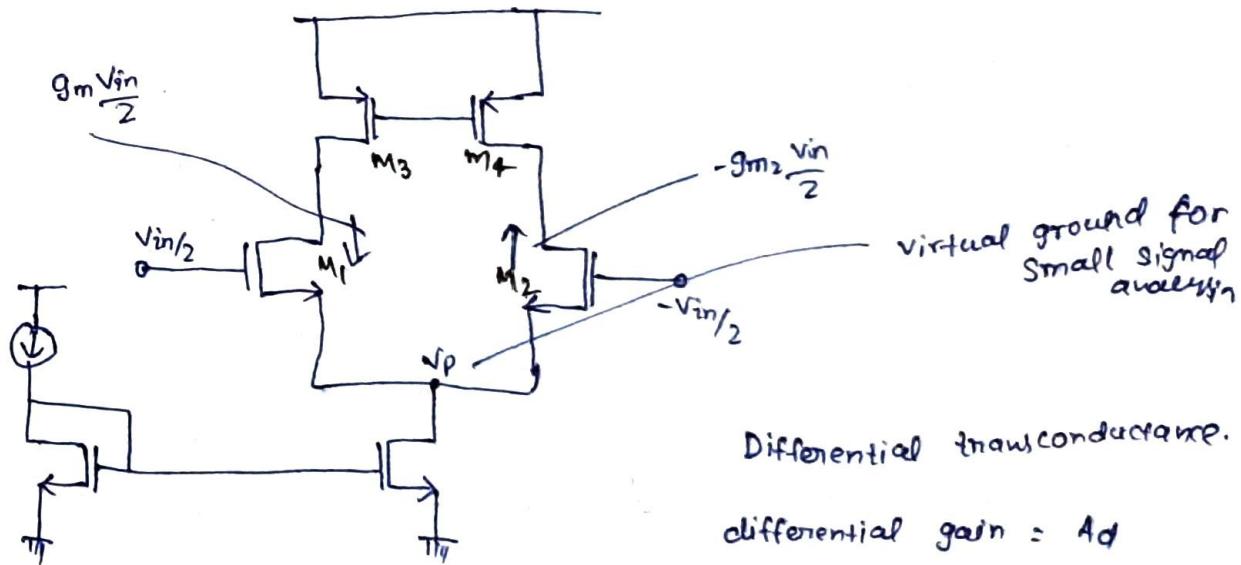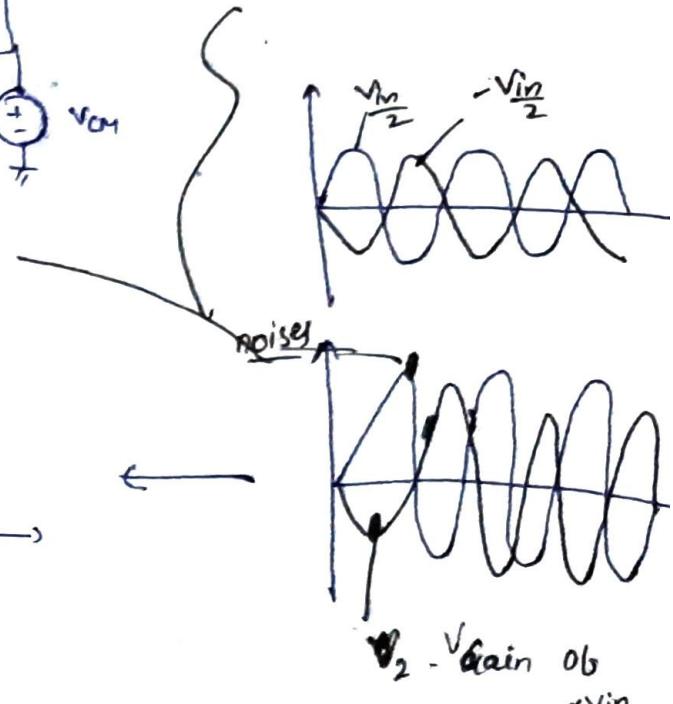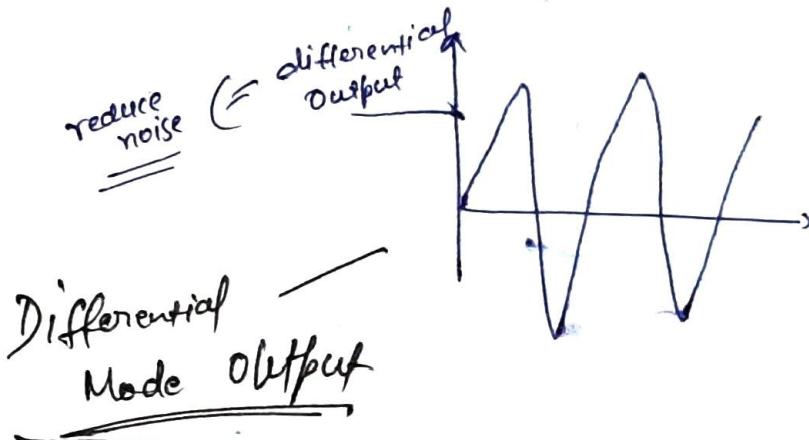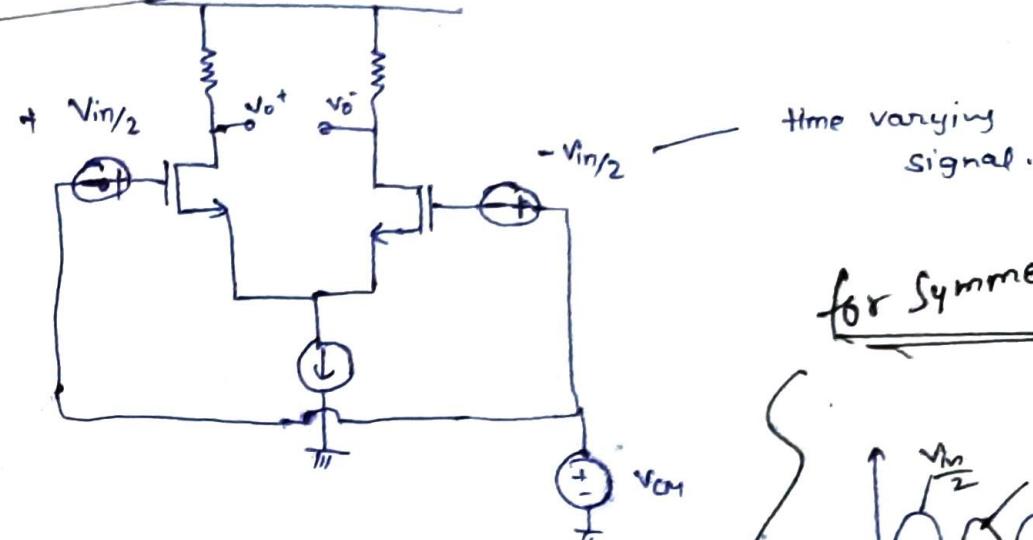

differential gain = A_d


Common mode gain = A_c .

for
 $A_d \rightarrow \infty$
 $A_c \rightarrow 0$

Common mode Rejection Ratio (CMRR)
 $= 20 \log \frac{A_d}{A_c}$


$A_d = G_m \cdot R_{out}$

r_{o1}, r_{o2} very high.

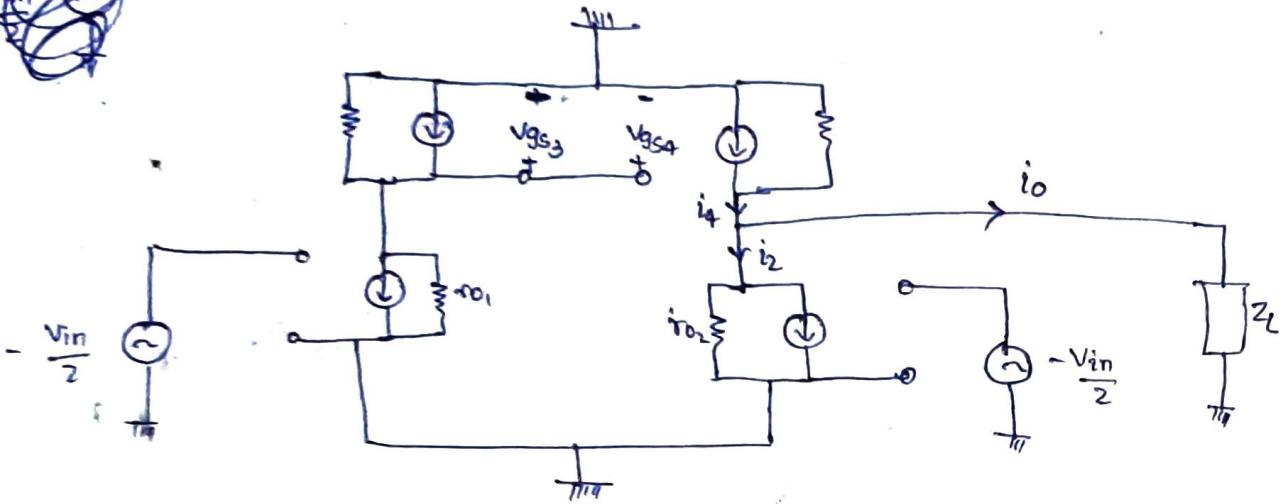


$$V_{in} = \frac{V_{in}}{2} - \left(-\frac{V_{in}}{2} \right)$$

$$G_m = \frac{i_o}{V_{in}}$$

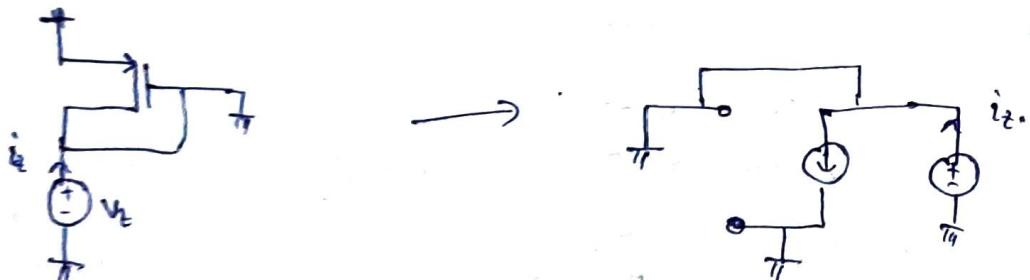

$$\frac{V_t}{R_g} = \frac{1}{g_m} i_d$$

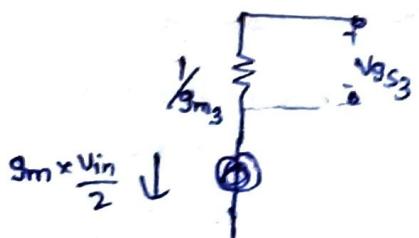In the above M_3 , can be replaced as $\frac{1}{g_m} i_d$ as a resistor



$$V_{gs3} = -g_m \frac{V_{in}}{2} \times \frac{1}{g_m}$$

$$i_4 = -g_{m4} v_{gs4}$$

$$\text{as } v_{gs3} = v_{gs4}$$

$$i_4 = g_{m1} g_{m4} \frac{v_{in}}{2} \frac{1}{g_{m3}}$$

$$\left. \begin{array}{l} g_{m3} = g_{m4} \\ g_{m1} = g_{m2} \end{array} \right\} \text{Symmetric.}$$

$$i_4 = g_{m1} \frac{v_{in}}{2}$$

$$i_2 = -g_{m2} \frac{v_{in}}{2}$$

$$\begin{aligned} i_0 &= i_4 - i_2 \\ &= g_{m1} \frac{v_{in}}{2} - \left(-g_{m2} \frac{v_{in}}{2} \right) \end{aligned}$$

$$= g_{m1} \frac{v_{in}}{2} + g_{m2} \frac{v_{in}}{2}$$




$$i_0 = g_{m1} v_{in} \text{ or } g_{m2} v_{in}$$



$\therefore g_{m1} = g_{m2}$

$$G_M = g_{m1} \text{ or } g_{m2}$$

Equivalent transconductance

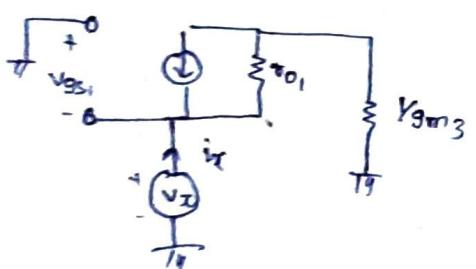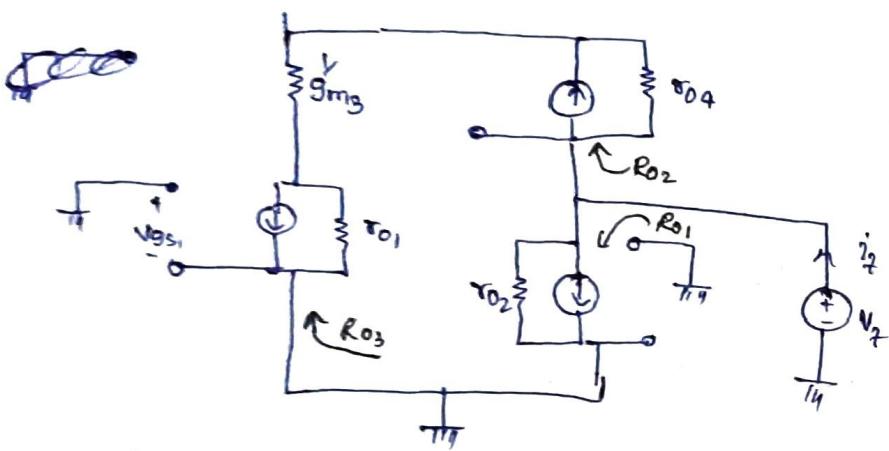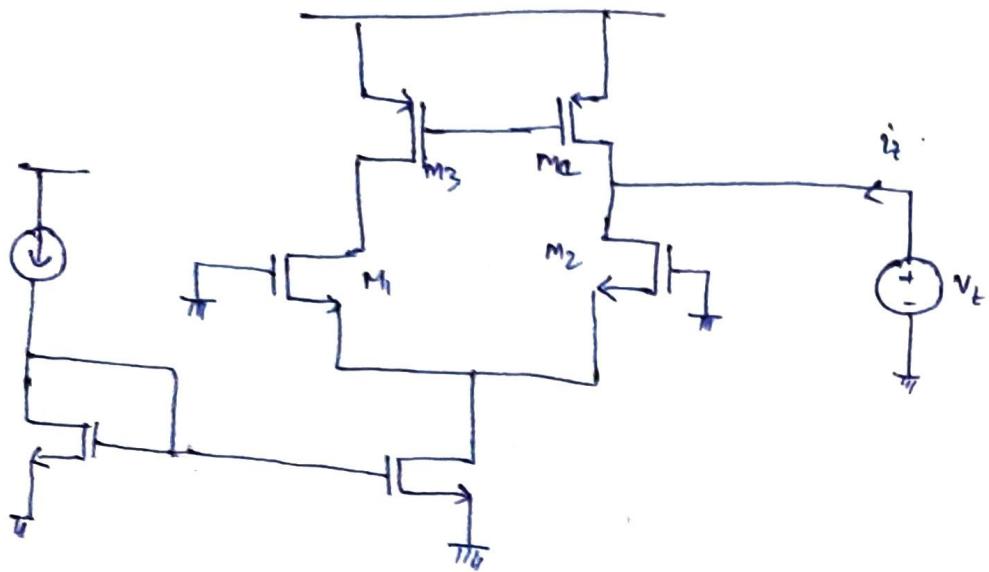

$$-V_{GS1} - V_x = 0$$

$$V_x = -V_{GS1}$$

Q. Consider the following T(s)

$$T(j\omega) = \frac{\beta \times 1000}{(1 + j\frac{\omega}{f_1})(1 + j\frac{\omega}{f_2})(1 + j\frac{\omega}{f_3})}$$

Find the value of β that will yield a PM of 45° .

to $\text{let } \text{tan}(\frac{f}{f_1}) \text{ be } \text{tan}$

At $f = f_2$

$$|T(j\omega)|_{f=f_2} = 1$$

means $0dB$
 $1dB$ off
 $f = f_2$

$$\frac{\beta \times 1000}{\sqrt{1 + (\frac{50}{k})^2}} \sqrt{2} \times \sqrt{1 + \left(\frac{1}{1M}\right)^2} = 1$$

$$\left\{ \beta \times 10^3 \right\}^2 = \sqrt{2} \times \left[1 + (50)^2 \right].$$

$$\beta = \sqrt{2 \times (50)^2} \\ = \sqrt{2} \times 50.$$

$$\beta = \frac{\sqrt{2} \times 50}{10^3}$$

$$= \frac{\sqrt{2} \times 50}{10000} = 0.070.$$

Q. An amplifier has a low freq. forward gain of $20dB$

Transfer fn of the amplifier has poles

$$f_1 = 200\text{kHz}, f_2 = 2\text{MHz}, f_3 = 25\text{MHz}.$$

Calculate the dominant pole magnitude required

to give unity gain compensation of 45° .


$$SOL: -$$

$$A(j\omega) = \frac{A_0}{(1 + j\frac{\omega}{f_1})(1 + j\frac{\omega}{f_2})(1 + j\frac{\omega}{f_3})}$$

$$\beta = 1$$

$$20 \log A_0 = 20$$

$$A_0 = 10.$$

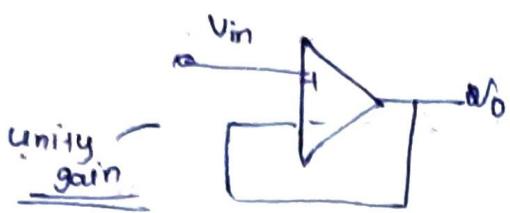

$$A'(j\omega) = \frac{10}{\left(1 + j\frac{\omega}{f_d}\right) \left(1 + j\frac{\omega}{200C}\right) \left(1 + j\frac{\omega}{2M}\right) \left(1 + j\frac{\omega}{25M}\right)}$$

$$|A(f)| = \frac{10}{\sqrt{1 + \left(\frac{\omega}{200C}\right)^2} \sqrt{1 + \left(\frac{\omega}{2M}\right)^2} \sqrt{1 + \left(\frac{\omega}{25M}\right)^2}}$$

f_c

$$\text{At } f = f_c \quad \textcircled{1}$$

$$\text{At } f = f_1$$

f_c

$$|A| = \frac{10}{\sqrt{2} \times \frac{200 \times 10^5}{2 \times 10^5} \times 1 + (0.1)^2} = 5\sqrt{2}. \quad \geq 0$$

}

$$\text{At } f = f_2$$

$$|A| = \frac{10}{\cancel{\frac{200 \times 10^5}{2 \times 10^5} \times \sqrt{2}}} = \frac{1}{\sqrt{2}}. \quad \textcircled{2}$$

f_c

$$\boxed{f_1 < f_c < f_2.}$$

$$\text{At } f = f_3$$

$$\frac{\cancel{\frac{25 \times 10^6}{2 \times 10^5} \times \frac{25 \times 10^6}{2 \times 10^5}} \times \sqrt{2}}{625 \times 5} =$$

$$\frac{10}{\sqrt{1 + \left(\frac{\omega}{200C}\right)^2} \sqrt{1 + \left(\frac{\omega}{2M}\right)^2}} = 1$$

$$100 = \left(1 + \left(\frac{f_c}{200C}\right)^2\right) \left(1 + \left(\frac{f_c}{2M}\right)^2\right)$$

$$100 = 1 + \frac{f_c^4}{f_1^2 f_2^2} + \left(\frac{1}{f_1^2} + \frac{1}{f_2^2} \right) f_c^2 \quad \text{← } 100$$

$$\frac{f_c^4}{f_1^2 f_2^2} + \left(\frac{1}{f_1^2} + \frac{1}{f_2^2} \right) f_c^2 + 99 = 0$$

$$f_1^2 f_2^2 = 4 \times 10^{10} \times 4 \times 10^{12} \quad \text{← } 1 \\ = 16 \times 10^{22}$$


$$\begin{aligned} \frac{1}{f_1^2} &= 2.5 \times 10^{-14} \\ \frac{1}{f_2^2} &= 2.5 \times 10^{-13}. \end{aligned} \quad \left. \begin{array}{c} \\ \end{array} \right\} 2.525 \times 10^{-11}$$

$$f_c = 1.6 \text{ MHz.}$$

$$\begin{aligned} \text{← } 100 &= -\tan^{-1}\left(\frac{f_c}{f_1}\right) - \tan^{-1}\left(\frac{f_c}{f_2}\right) - \tan^{-1}\left(\frac{f_c}{f_3}\right) \\ &= -\tan^{-1}\left(\frac{1.6 \times 10^6}{2 \times 10^8}\right) - \tan^{-1}\left(\frac{1.6 \times 10^6}{2 \times 10^8}\right) - \tan^{-1}\left(\frac{1.6 \times 10^6}{2.5 \times 10^8}\right) \\ &\quad - \tan^{-1}(0.8) - \tan^{-1}(0.8) - \tan^{-1}(0.064). \\ &= -125.196^\circ. \end{aligned}$$

$$\text{PM} = 180 - 125.196 = 54.8^\circ = 55^\circ$$

when forward gain (5000).

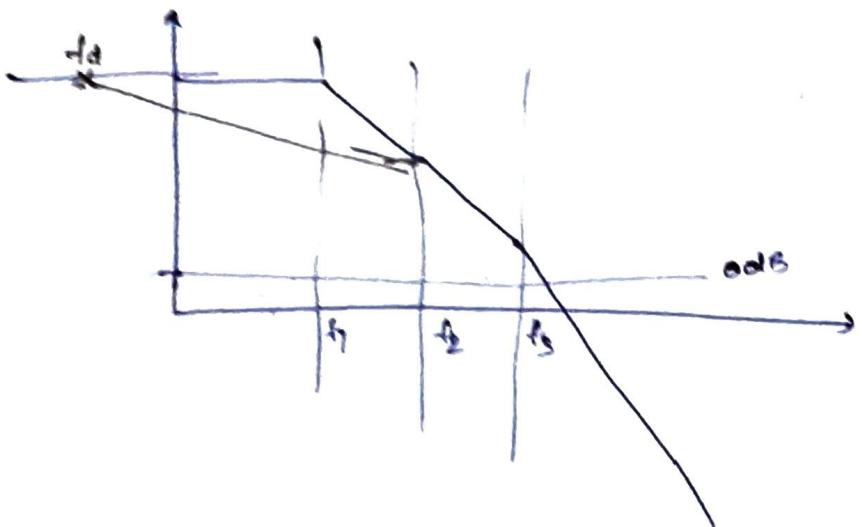

$$A'(j\omega) = \frac{5000}{(1+j\frac{\omega}{f_d})(1+j\frac{\omega}{200\pi})(1+j\frac{\omega}{2M})(1+j\frac{\omega}{25M})},$$

dominant pole insertion

$$At \quad \omega = f_2, \quad (200\pi)$$




$$|A'(j\omega)| = 1 = \frac{5000}{\sqrt{1 + \left(\frac{200\pi}{f_d}\right)^2} \sqrt{1+1} \sqrt{1 + \left(\frac{200\pi}{2M}\right)^2} \sqrt{1 + \left(\frac{200\pi}{25M}\right)^2}}$$

$$(5000)^2 = 1 + \left(\frac{200\pi}{f_d}\right)^2 \times 2 \times \frac{200\pi}{2M} \times 1$$

$$\frac{25 \times 10^6 \times 10}{2} = 25 \times \frac{4 \times 10^{10}}{f_d^2}$$

$$f_d^2 = \frac{8 \times 10^3}{25 \times 10^7}$$

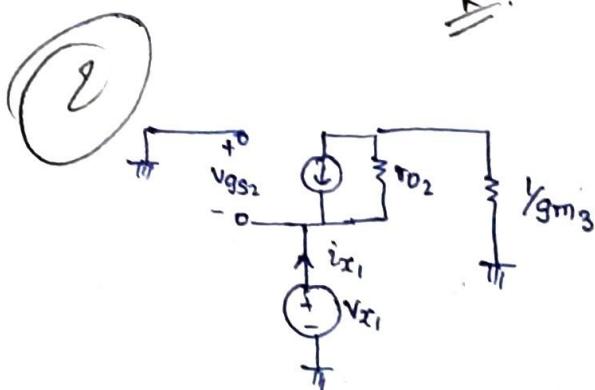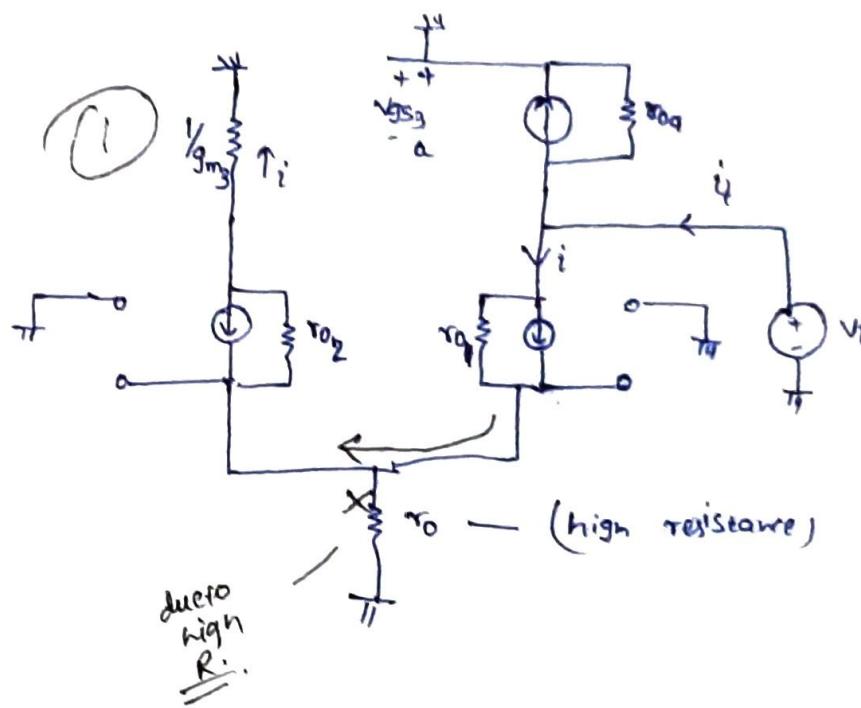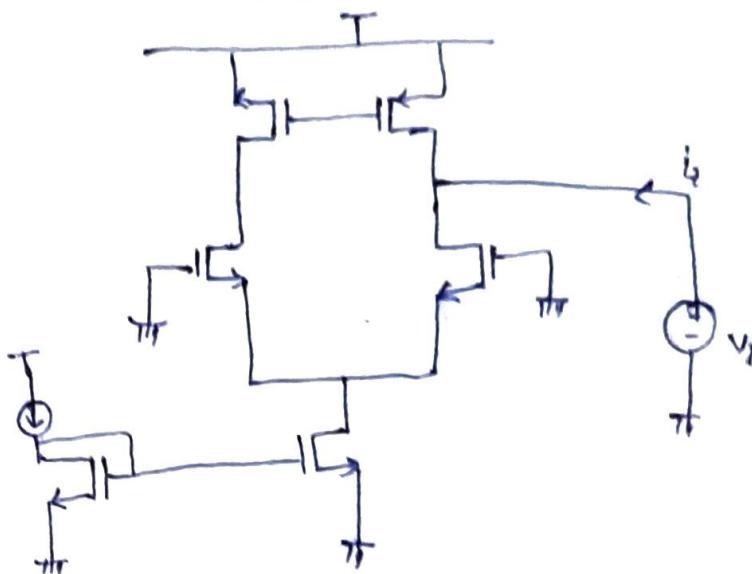Output Resistance of the current mirror loaded Diff. Amplifier



$$Vg_{S_2} + Vx_1 = 0$$

$$i_{x_1} + g_{m_2} v_{GS_2} + \frac{v_{x_1} - i_{x_1} + g_{m_3}}{\tau_{D_2}} = 0$$

$$i_{x_1} - g_{m_2} v_{x_1} + \frac{v_{x_1} - \frac{i_{x_1}}{g_{m_3}}}{r_{0_2}} = 0.$$


$$i_{x_1} \left(1 + \frac{g}{g_{m_3} r_{O_2}} \right) = g_{m_2} \left(-\frac{1}{r_{O_2}} + g_{m_2} \right) v_{x_1}$$

$$\frac{V_{x_1}}{I_{x_1}} = \frac{\frac{g_{m_3} \tau_{o_2} - 1}{g_{m_3} \tau_{o_2}}}{\frac{(g_{m_2} \tau_{o_2} - 1)}{\tau_{o_2}}}$$

$$\begin{aligned}\frac{V_{x_1}}{I_{x_1}} &= \frac{g_{m_3} \tau_{o_2} - 1}{g_{m_3} (g_{m_2} \tau_{o_2} - 1)} \\ &= \frac{g_{m_3} \tau_{o_2} \left(1 - \frac{1}{g_{m_3} \tau_{o_2}}\right)}{g_{m_3} g_{m_2} \tau_{o_2} \left(1 - \frac{1}{g_{m_3} \tau_{o_2}}\right)}\end{aligned}$$

$$g_m \tau_0 \gg 1.$$
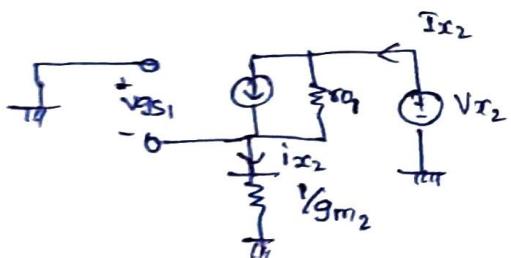
$$\frac{V_{x_1}}{I_{x_1}} \approx \frac{1}{g_{m_2}}$$



$$V_{gs_1} + i_{x_2} \times \frac{1}{g_{m_2}} = 0$$

~~$i_{x_2} = g_{m_1} V_{gs_1}$~~

$$i_{x_2} - g_{m_1} V_{gs_1} - \frac{(V_{x_2} - i_{x_2} \times \frac{1}{g_{m_2}})}{\tau_{o_1}} = 0$$

$$i_{x_2} + g_{m_1} \times i_{x_2} \frac{1}{g_{m_2}} - \frac{V_{x_2}}{\tau_{o_1}} + i_{x_2} \frac{1}{g_{m_2} \tau_{o_1}} = 0$$

$$i_{x_2} \left(1 + \frac{g_{m_1}}{g_{m_2}} + \frac{1}{g_{m_2} \tau_{o_1}} \right) = \frac{V_{x_2}}{\tau_{o_1}}$$

$$\frac{V_{x_2}}{I_{x_2}} = \tau_{01} \left(1 + \frac{g_{m_1}}{g_{m_2}} + \frac{1}{g_{m_2} \tau_{01}} \right)$$

$$g_{m_1} = g_{m_2} \Rightarrow g_{m_2} \tau_{01} \gg 1.$$


$$\frac{V_{x_2}}{I_{x_2}} = 2\tau_{01}$$

considering
M4.

$$i_2 = -g_{m_4} v_{gs_3} - \frac{V_L}{\tau_{04}}$$

$$v_{gs_3} = i \times \frac{1}{g_{m_3}}$$
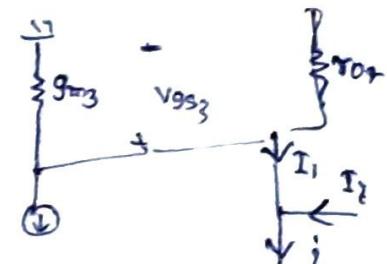
$$i_2 = -g_{m_4} \times i \times \frac{1}{g_{m_3}} - \frac{V_L}{\tau_{04}}$$



$$g_{m_3} = g_{m_4}$$

$$i_L = -i - \frac{V_L}{\tau_{04}}$$


$$i_2 + i_L + i = 0$$

$$\begin{aligned} i_L &= i - i_2 \\ &= \frac{V_L}{2\tau_{04}} + i + \frac{V_L}{\tau_{04}} \\ &= \frac{V_L}{2\tau_{01}} + \frac{V_L}{2\tau_{01}} + \frac{V_L}{\tau_{04}}. \end{aligned}$$

$$V_L = \frac{V_L}{\tau_{01}} + \frac{V_L}{\tau_{04}}$$

$$R_{out} = \tau_{01} \parallel \tau_{04}$$


output resistance

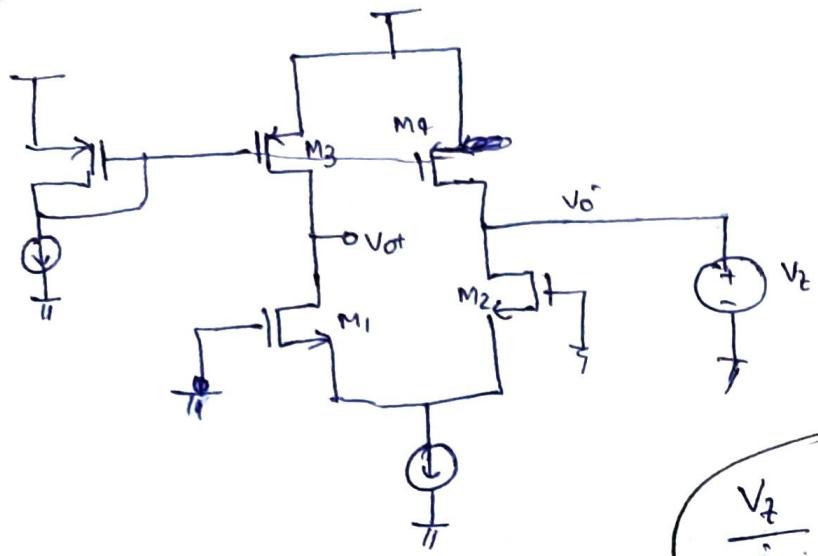


$$\frac{V_2}{i_2} = r_{o2} \parallel r_{o4}$$


differential gain = transconductance \times Output resistance
 $\approx g_{m1} (r_{o1} \parallel r_{o2})$

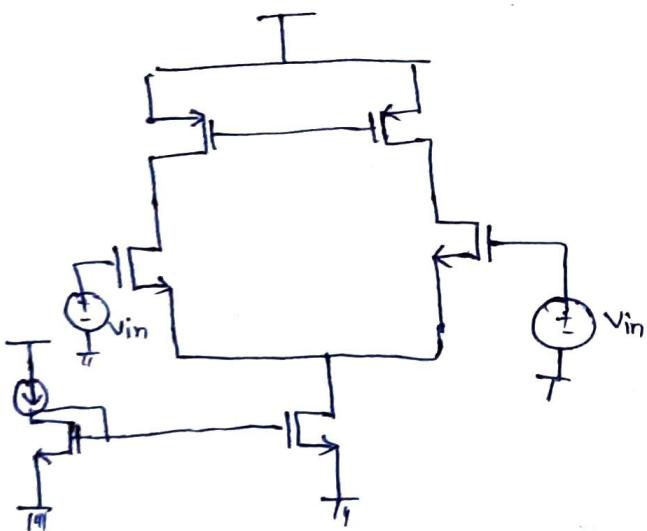Common mode gain of CM loaded diff. Amplifier



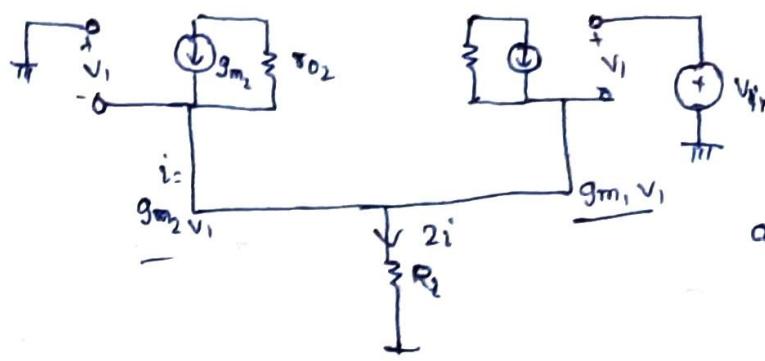


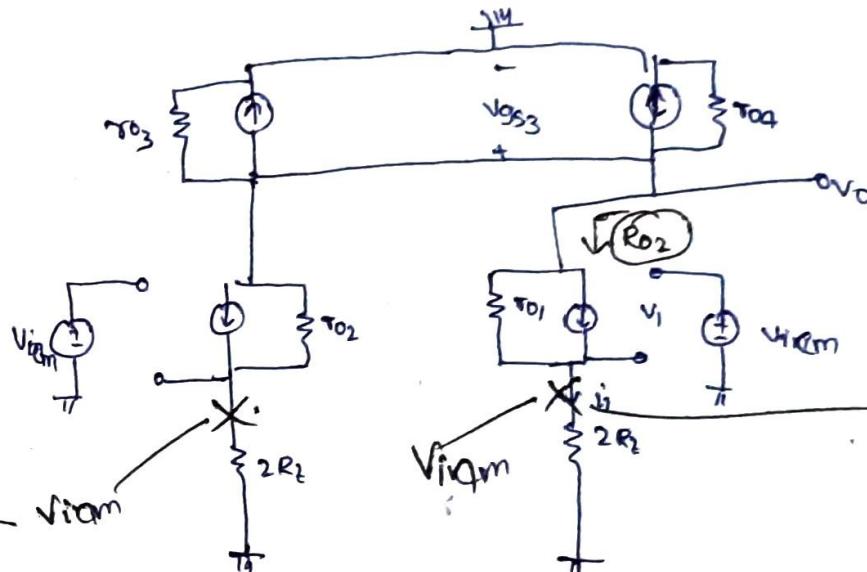$\text{as } g_m_1 = g_m_2$
then $2i$ will
flow through
 R_L .



AS
gain = 1

AS R_L is very high,

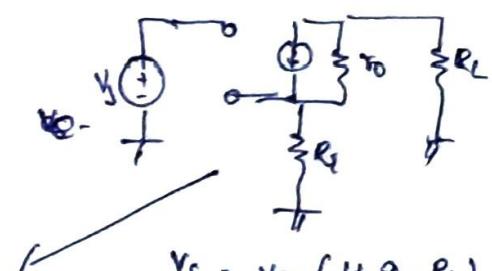

FOR M2.


$$v_o = g_m_2 v_{gs} R_L.$$

$$\therefore \frac{v_o}{v_s} = \frac{g_m R_L}{1 + g_m R_L} \approx 1$$

$$v_s = v_{gs} (1 + g_m R_L).$$

R_L is very high.

$$i_1 = \frac{v_{icm}}{2 R_L}$$

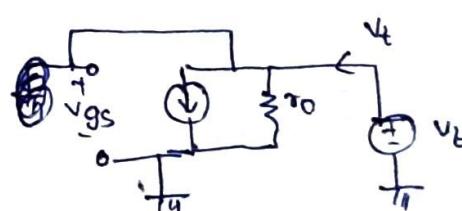

$$\frac{v_{gs}}{r_0} + g_m v_{gs} = i_2$$

$$\frac{v_2}{r_0} + g_m v_{gt} = i_2$$

$$\frac{v_t}{T_f} = \frac{r_0}{1 + g_m r_0}$$

Resistance
of M3


$$\frac{1}{g_m_3} \parallel r_0$$

$$V_{g_3} = -i_1 \times \left(\frac{1}{g_{m_3}} \| r_{o_3} \right)$$

Current flowing $R_{eq.}$

$$V_{g_3} = -i_1 \times \frac{1}{g_{m_3}}$$
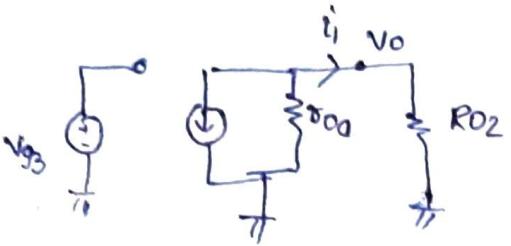
$$V_o = - (g_{m_3} V_{g_3} + i_1) r_{o_4}$$



$$V_o = - \left\{ -g_{m_3} i_1 \times \left(\frac{1}{g_{m_3}} \| r_{o_3} \right) + i_1 \right\} r_{o_4}$$

$g_m V_g$ $\rightarrow i_1$

$$= - \left\{ -g_{m_3} \times \frac{\frac{1}{g_{m_3} r_{o_3}} + 1}{\frac{1}{g_{m_3}} + r_{o_3}} + 1 \right\} i_1 r_{o_4}$$

g_m


$$= \left\{ \frac{r_{o_3}}{\frac{1}{g_{m_3}} + r_{o_3}} - 1 \right\} i_1 r_{o_4}$$

$$= - \frac{r_{o_4}}{g_{m_3} r_{o_3} + 1} \times \frac{V_{icm}}{2R_f}$$


$$= - \frac{r_{o_4}}{g_{m_3} r_{o_3}} \times \frac{V_{icm}}{2R_f}$$

$$\frac{V_o}{V_{icm}} = - \frac{1}{2 g_{m_3} R_f}$$

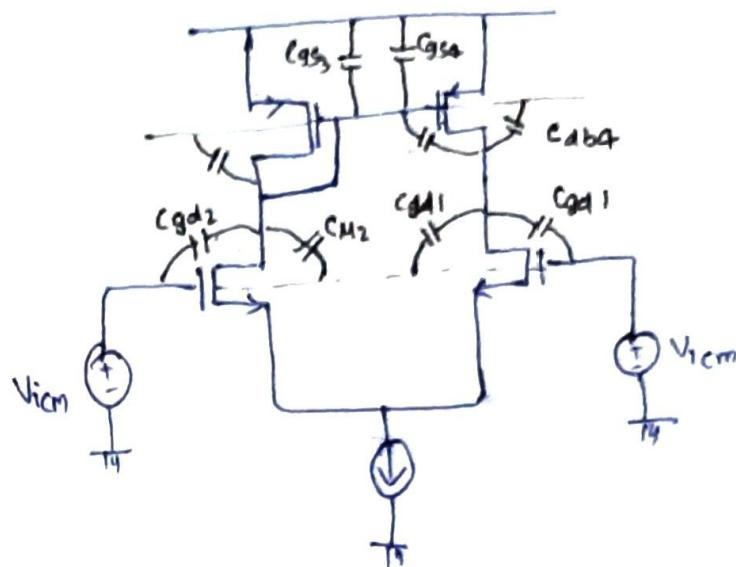A_{CM} = A common mode = $- \frac{1}{2 g_{m_3} R_f}$



For n-type
p-type substrate
is bulk.

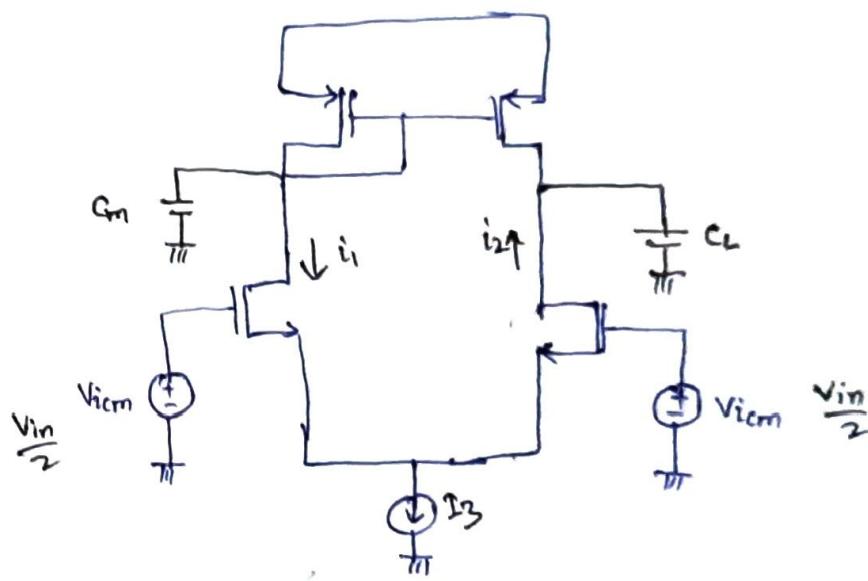


Drain to Bulk capacitance

$$C_m = C_{db3} + C_{gs3} + C_{gs4} + C_{gd2} + C_{db2}$$

$$C_L = C_{db4} + C_{gd1} + C_{db1} + C_{gd4}$$

open circuit time constant

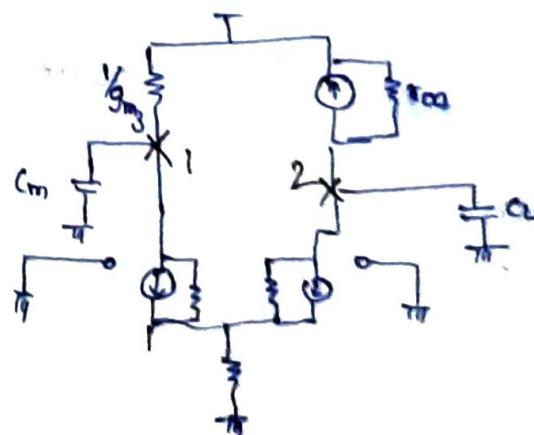

A_{2,1},

$$R_m = \frac{1}{g_{m_3}} \parallel r_{o_1}$$

$$R_L = r_{o_2} \parallel r_{o_4}$$

} open circuit time const.

Short circuit

$$R_m = \frac{1}{g_{m_3}} \parallel r_{o_1}$$

$$R_L = r_{o_2} \parallel r_{o_4}$$

$$f_d = \frac{1}{2\pi \sum RC}$$

$$f_{nd} = \frac{1}{2\pi} \sum \frac{1}{RC}$$

$$f_d = \frac{1}{2\pi \left\{ C_m \left(\frac{1}{g_{m_3}} \parallel r_{o_1} \right) + C_L (r_{o_2} \parallel r_{o_4}) \right\}}$$

$$f_{nd} = \frac{1}{2\pi} \left\{ \frac{1}{C_m \left(\frac{1}{g_{m_3}} \parallel r_{o_1} \right)} + \frac{1}{C_L (r_{o_2} \parallel r_{o_4})} \right\}.$$

non-dominant

Q. $k_n' = 60 \mu A/V^2$ $d_n = d_p \approx 0.02V$
 $k_p' = 30 \mu A/V^2$

$$\left(\frac{w}{L}\right)_n = 10 \quad \left(\frac{w}{L}\right)_p = 20 \quad I_3 \approx 200 \mu A$$

$$C_L = 400 \text{ fF}$$

$$C_m = 100 \text{ fF}$$

Open circuit

$$R_m = \frac{1}{g_{m3}} \parallel r_{o1}$$

$$\left. \begin{aligned} g_{m1} &= \frac{I_c}{V_T} = \frac{100}{25} = 4 \times 10^{-3} \\ g_{m2} &= 4 \times 10^{-3} \end{aligned} \right\} \quad \begin{aligned} r_{o1} &= \frac{1}{d_n} \\ &= \frac{1}{10^{-2}} \\ &= 100 \end{aligned}$$

~~g_{m3} Replaced by~~

$$\begin{aligned} g_{m3} &= \sqrt{2 I_D \mu_p C_OX \times \frac{w}{L}} \\ &= \sqrt{2 \times 100 \times 10^{-6} \times 30 \times 10^{-6} \times \frac{w}{L}} \\ &= \sqrt{6 \times 10^{-9} \times 20} \\ &= \sqrt{12} \times 10^{-4} \\ &= 34.64 \text{ mS} \end{aligned}$$

$$f_d = \frac{1}{2\pi (r_{o2} \parallel r_{o4}) C_L}$$

$$\begin{aligned} f_{nd} &= \frac{1}{2\pi} \sum \frac{1}{R_C} \\ &= \frac{1}{2\pi} \sum \frac{1}{C_m / g_{m3}} \end{aligned}$$

From the same circuit

$$V_o = i_0 \times \frac{1}{C_{LS}} \parallel (r_{o2} \parallel r_{o4})$$

Equivalent resistance at V_o.

$$i_0 = i_4 + i_2$$

$$v_{g3} = -i_1 \times \left(\frac{1}{g_{m3}} \parallel \frac{1}{C_{MS}} \right)$$

$$v_{g3} = -g_{m1} \frac{v_{in}}{2} \left(\frac{1}{g_{m3}} \parallel \frac{1}{C_{MS}} \right)$$

$$i_1 = g_{m1} \frac{v_{in}}{2}$$

$$i_4 = -g_{m4} \times v_{gs}$$

$$= g_{m4} \times g_{m1} \times \frac{v_{in}}{2} \left(\frac{1}{g_{m3}} \parallel \frac{1}{c_{ms}} \right)$$

$$i_0 = i_4 + i_2$$

$$= g_{m4} g_{m1} \frac{v_{in}}{2} \left(\frac{1}{g_{m3}} \parallel \frac{1}{c_{ms}} \right) + g_{m2} \frac{v_{in}}{2}$$

$$i_0 = \frac{v_{in}}{2} \left\{ g_{m1} g_{m4} \left(\frac{1}{g_{m3}} \parallel \frac{1}{c_{ms}} \right) + g_{m2} \right\}$$

$$g_{m1} = g_{m2}$$

$$g_{m3} = g_{m4}$$

$$v_o = \frac{v_{in}}{2} \left\{ g_{m1} g_{m4} \left(\frac{1}{g_{m3}} \parallel \frac{1}{c_{ms}} \right) + g_{m2} \right\}$$

$$\begin{aligned} & g_{m1} \times g_{m4} \times \frac{1}{g_{m3}} \times \frac{1}{c_{ms}} \\ & \quad \frac{1}{g_{m3} + c_{ms}} + g_{m2} \left\{ \frac{\frac{1}{c_{ls}} \parallel (R_o + \cancel{C_{ls} R_o})}{R_o + \frac{1}{c_{ls}}} \right. \\ & \quad \left. \frac{R_o}{c_{ls} R_o + 1} \right\} \end{aligned}$$

$$\frac{g_{m1}}{c_{ms}} \left\{ \frac{g_{m3} c_{ms}}{g_{m3} + c_{ms}} + g_{m2} \right\}$$

zeros

$$v_o = \frac{v_{in}}{2} g_{m1} \left(\frac{c_{ms} + 2g_{m3}}{c_{ms} + g_{m3}} \right) * \frac{R_o}{1 + R_o C_{ls}}$$

poles where $R_o = \tau_{o2} \parallel \tau_{o4}$.

$$f_d = \frac{1}{2\pi (\tau_{D2} || \tau_{O2}) \times C_L}$$

$$= \frac{1}{2\pi \times 500 \times 10^3 \times 400} \times 10^{15}$$

$$= \frac{1}{4\pi} \times 10^7$$

$$= 6.78539 \times 10^7$$

~~285~~

796 MHz.


$$f_{nd} = \frac{1}{2\pi} \left\{ \frac{1}{C_m \times \rho g m_3} \right\}$$

$$= \frac{1}{2\pi} \times \frac{1}{100 \times 10^{-15}} \times 346 \times 10^{-6}$$

$$= \frac{346}{2\pi} \times 10^{15} \times 10^{-6} - 10^7$$

$$= 568 \text{ MHz.}$$

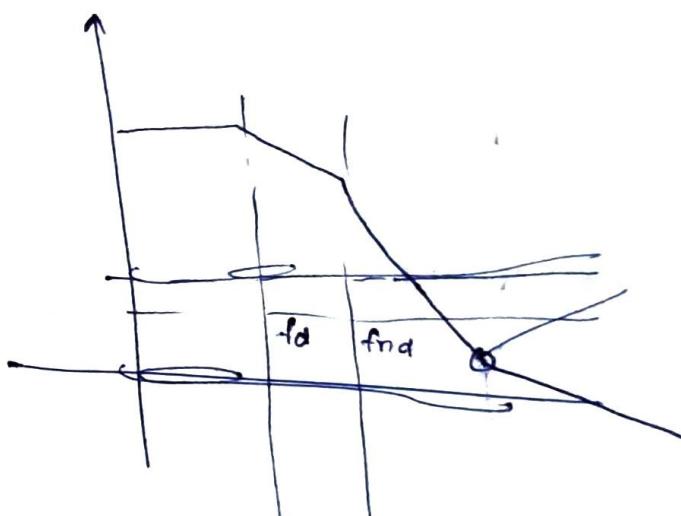Designers choice:-
Increase $\frac{w}{L}$ of pmos
for making more
stable.




closer $\xrightarrow{\text{zero}}$
more \downarrow it $\xrightarrow{\text{zero}}$ to f_nd
~~this~~ to f_nd
will be unstable.

$$f_2 = \frac{2g m_3}{2\pi C_m}$$

$C_m \uparrow$ — zero \downarrow

81/10/23
missing

1/11/23

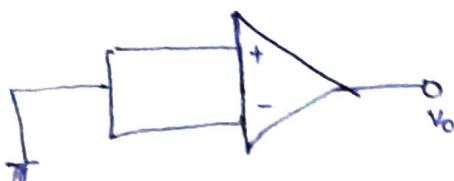


$$V_{OS} = \frac{V_o}{A_d}$$

(g_n input preferred offset)

differential gain

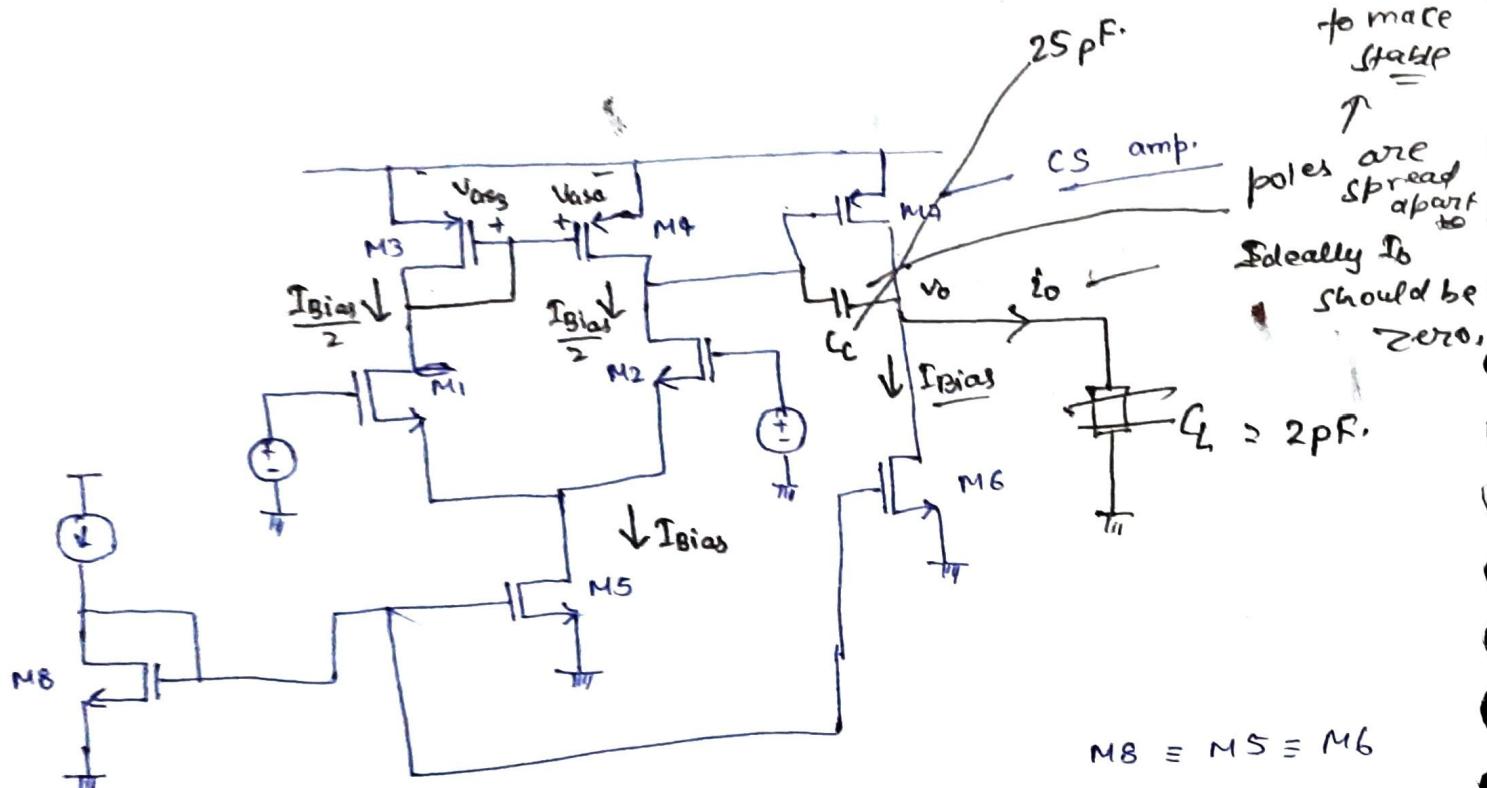If V_{OS} connected to v_p , V_o will become 0.



$$M_8 \equiv M_5 \equiv M_6$$

2 stage CMOS op-amp.

All the transistors in saturation

$$V_{OS3} = V_{DS3} = V_{DS4}$$

due to equal current

Gate and drain is connected.

All the transistors are in saturation

∴

$$\frac{I_{Bias}}{2} = \frac{1}{2} \mu_p Cox \left(\frac{\omega}{L}\right)_P (V_{G4} - |V_{tp}|)^2 (1 + d|V_{SD}|_P).$$

$$V_{G3} = V_{G7}.$$

$$I_7 = \frac{1}{2} \mu_p Cox \left(\frac{\omega}{L}\right)_7 (V_{G7} - |V_{tp}|)^2$$

$$\frac{I_{Bias}}{2} = \frac{1}{2} \mu_p Cox \left(\frac{\omega}{L}\right)_4 (V_{G4} - |V_{tp}|)^2$$

As $V_{G4} = V_{G7}$.

$$\frac{I_7}{\frac{I_{Bias}}{2}} = \frac{\left(\frac{\omega}{L}\right)_7}{\left(\frac{\omega}{L}\right)_4}$$

$$2 \left(\frac{I_7}{I_{Bias}} \right) \left(\frac{\omega}{L}\right)_4 = \left(\frac{\omega}{L}\right)_7.$$

To ensure $I_0 = 0$,
underbrace zero offset

I_7 should be equal to I_{Bias} .

$$\boxed{\left(\frac{\omega}{L}\right)_7 = 2 \times \left(\frac{\omega}{L}\right)_4}$$

$$C_{ox} = \frac{\epsilon_{ox}}{2\alpha_x} \quad \text{same for n-mos & p-mos.}$$

$$I_n = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{l}\right)_n (V_{ds} - V_{tn})^2$$

$$I_p = \frac{1}{2} \mu_p C_{ox} \left(\frac{w}{l}\right)_p (V_{sg} - V_{tp})^2$$

$$\frac{\mu_n}{\mu_p} \approx \underline{\underline{2.5-4}}$$

Given:

$$M_1, M_2 = \frac{10}{1}$$

$$M_7 = \frac{50}{1}$$

$$M_3, M_4 = \frac{25}{1}$$

$$\mu_n C_{ox} = 60 \mu A/V^2$$

$$\mu_p C_{ox} = 30 \mu A/V^2$$

$$I_{bias} = 0.6 \text{ mA}$$

$$A_n = |A_p| = \frac{1}{g} V^{-1}$$

$$C_C = 25 \text{ pF}$$

Q. Find the gain of op-amp.

Gain of first stage = $-g_m (\tau_0, 11 \tau_0)$

differentiql

②

$$g_m = \sqrt{2 \mu_n C_{ox} \left(\frac{w}{l}\right)_n \frac{I_{bias}}{2}}$$

$$= \sqrt{2 \times 60 \times 10^{-6} \times \frac{10}{1} \times \frac{0.6 \times 10^{-3}}{2}}$$

$$= \sqrt{36 \times 10^{-8}}$$


$$= 6 \times 10^{-4}$$

$$= 60 \text{ mV}$$

$$\tau_{02} = \frac{1}{\mu_n \times I_{bias}} = \frac{9 \times 2}{0.6 \text{ mA}} = \frac{\frac{18}{6} \times 10^4}{3} \approx 3 \times 10^3 \text{ K.}$$

$$r_{02} = r_{04} = 30\text{K}$$
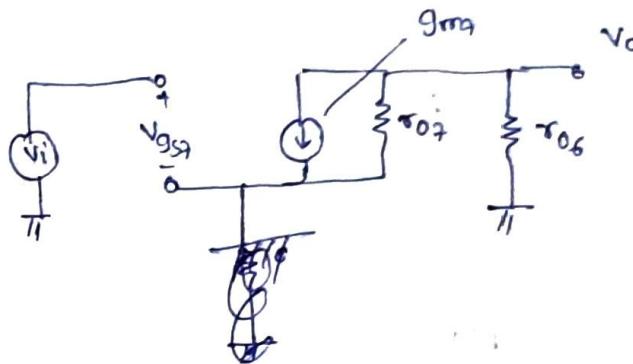
$$\text{gain} = -6 \times 10^4 \times 15 \times 10^3 \\ = -9 \text{ V/V.}$$



$$\frac{V_o}{V_i} = -g_{m7} (r_{07} || r_{06})$$

$$g_{m7} = \sqrt{2 \mu_p C_{OZ} \left(\frac{W}{L}\right)_7 \times I_{Bias}}$$

$$= \sqrt{2 \times 30 \times 10^{-6} \times \frac{50}{1} \times 6 \times 10^{-4}}$$

$$= \sqrt{16000 \times 10^{-10}}$$

$$= 134.16 \times 10^{-5}$$

$$= \frac{134.16 \times 10^{-5}}{1.3416 \times 10^{-2}}$$


$$r_{07} = \frac{1}{r_p I_{Bias}} = \frac{3}{0.162} \times 10^4 \\ = 1.5 \times 10^9 \\ = 15\text{K.}$$

$$\frac{V_o}{V_i} = -1.34 \text{ mV} \times 7.5\text{K} \\ = -10 \text{ V/V}$$

gain of op-amp = 90 V/V

B.W of the op-amp

$$C_m = 0.2 \text{ pF}$$

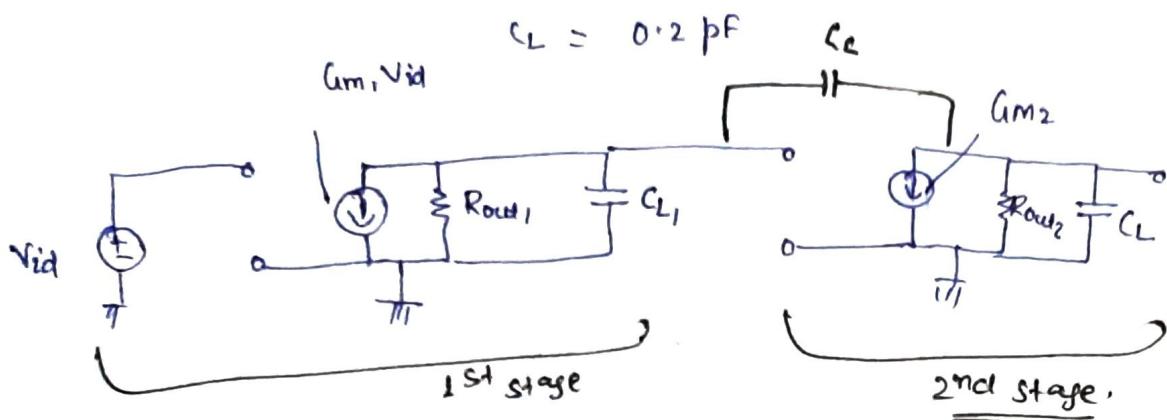

$$G_m = g_m,$$

$$R_{out1} = r_{o2} \| r_{o3}$$

$$G_m = g_m,$$

$$R_{out2} = r_{o6} \| r_{o7}.$$

Already
calculated

$$f_{3dB} = \frac{1}{2\pi \left\{ C_L, R_{out1} + C_L \times R_{out2} + C_C \left(R_{out1} + R_{out2} + G_m R_{out1} \right) \right\}}$$

Given:- $C_C \gg C_L + C_{L1}$

$$f_{3dB} \approx \frac{1}{2\pi C_C \left\{ R_{out1} + R_{out2} + G_m R_{out1} R_{out2} \right\}},$$

$$C_C = 25 \text{ pF}$$

$$R_{out1} = 15K$$

$$R_{out2} = 7.5K$$

$$= \frac{1}{2\pi \times 25 \times 10^{-12} \left\{ 15K + 7.5K + 1.84m \times 15K \times \frac{7.5K}{7.5K} \right\}}.$$


$$2 \quad \frac{1}{2\pi \times 25 \times 10^{-12} \times 123 \times 10^3}.$$

$$= \underline{0.0000519577} \times 10^9$$

$$f_{3dB} = 5.17577 \times 10^4.$$

21/11/23

Oscillators

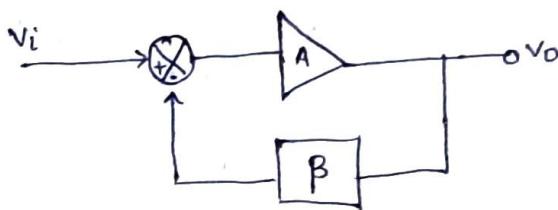

$$\frac{V_o}{V_i} = \frac{A}{1 + AB}$$

Oscillation Condition,

$$|\alpha\beta| = 1$$

$$\angle ABB = 180^\circ$$


for +ve feedback ckt,

$$\frac{V_o}{V_i} = \frac{A}{1 - A\beta}$$

$$|AB|=1$$

$$\angle A\bar{B} = 0^\circ$$

wien Bridge Oscillator

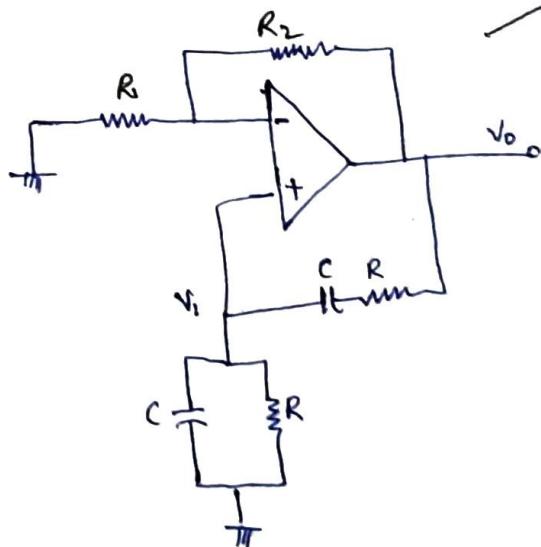

$$|AB|=1$$

$$\angle A\beta = 0^\circ$$

feedback

network K

↓
passive

↓
Simply voltage divisor.

frequency dependent

$$\frac{V_1}{V_0} = \frac{\left(\frac{1}{cs} \parallel R\right)}{\left(\frac{1}{cs} \parallel R\right) + \left(R + \frac{1}{cs}\right)}$$

$$\frac{0 - V_1}{R_1} = \frac{V_1 - V_0}{R_2}$$

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_0}{R_2}$$

$$\frac{1}{cs} \parallel R = \frac{\frac{1}{cs} \times R}{\frac{1}{cs} + R} = \frac{R}{1 + SRC}$$

$$V_1 \left(\frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_0}{R_2}$$

$$\frac{\frac{R}{1 + SRC}}{\frac{R}{1 + SRC} + \frac{(SRC + 1)}{cs}}$$

$$\underbrace{\frac{V_0}{V_{in}}}_{A} = \left(1 + \frac{R_2}{R_1} \right)$$

$$\frac{V_1}{V_0} = \frac{SRC}{SRC + (1 + SRC)^2} \quad \beta$$

$$A \quad \beta$$

$$\text{loop gain} = \underbrace{\frac{V_0}{V_1}}_{\alpha} \times \underbrace{\frac{V_1}{V_0}}_{\beta}$$

$$= \left(1 + \frac{R_2}{R_1} \right) \times \frac{1}{RC_s + \frac{1}{RC_s} + 3}$$

$$AB(j\omega) = \left(1 + \frac{R_2}{R_1} \right) \times \frac{1}{3 + j \left(\frac{1}{RC_s} - \frac{1}{RC_s} \right)}$$

$$\angle AP = -\tan^{-1} \left(\frac{\omega_0 RC - \frac{1}{\omega_0 RC}}{3} \right) = 0^\circ$$

$$\omega_0 RC = \frac{1}{\omega_0 RC}$$

$$\omega_0 = \frac{1}{RC}$$

$$|AP|_{\omega = \frac{1}{RC}} = \frac{\left(1 + \frac{R_2}{R_1}\right)}{3} = 1.$$

$$R_2 = 2R_1$$

Q. For the Wein Bridge oscillator the phase shift by op-amp of resistors is -15° at $\omega = \frac{1}{RC}$. Find the frequency of oscillation.

Soln.

$$\text{Loop phase } (\phi) = -\tan^{-1} \left(\frac{\omega_0 RC - \frac{1}{\omega_0 RC}}{3} \right)$$

$$\frac{d\phi}{d\omega} = \frac{1}{1 + \omega^2} = \frac{1}{1 + \frac{(\omega_0 RC - \frac{1}{\omega_0 RC})^2}{9}}$$

$$\omega^2 = \frac{\omega^2 R^2 C^2 + \frac{1}{\omega^2 R^2 C^2} - 2\alpha + 1}{9}$$

$$\frac{\omega^2 R^2 C^2 + \frac{1}{\omega^2 R^2 C^2} - 2 + 9}{9}$$

$$\frac{9}{\omega^2 R^2 C^2 + \frac{1}{\omega^2 R^2 C^2} + 7} \times \left(RC + \frac{1}{\omega^2} RC \right)$$

$$\frac{\Delta\phi}{4\omega} = -\frac{2}{3} \text{RC}$$

$$\Delta\omega = \frac{\pi}{10 \times \frac{2}{3} \text{RC}}$$

②


$\omega'_{\text{osc}} = \frac{1}{RC} + \Delta\omega$

Phase shift
Oscillator

$$\text{gt } A = -ve$$

$$\text{fhe } \angle AB = 180^\circ.$$

Phase shift
Oscillator

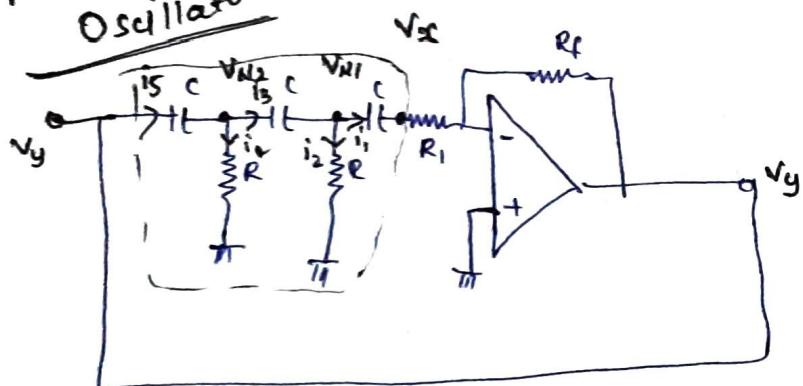

$$A = -\frac{R_f}{R_1}$$

$$\frac{V_y}{V_x} = -\frac{R_f}{R_1}$$

$$i_1 = (V_{N1} - V_x) \cos C$$

$$i_2 = \frac{V_{N1}}{R}$$

$$i_3 = i_1 + i_2 = (V_{N1} - V_x) \sin C + \frac{V_{N1}}{R}$$

$$\therefore i_3 = (V_{N2} - V_{N1}) \sin C$$

$$(V_{N_2} - V_{N_1}) sC = (V_{N_1} - V_x) sC + \frac{V_{N_1}}{R}$$

$$V_{N_2} sC = V_{N_1} (2sC + \frac{1}{R}) - V_x sC$$

$$= V_{N_1} \left(\frac{2sRC + 1}{R} \right) - V_x sC$$

$$i_4 = \frac{V_{N_2}}{R}$$

$$\boxed{(V_{N_1} - V_x) sC = \frac{V_x}{R}}$$

$$i_5 = i_3 + i_4$$

$$= \frac{V_{N_2}}{R} + (V_{N_2} - V_{N_1}) sC$$

$$+ i_5 = (V_y - V_{N_2}) sC$$

$$(V_y - V_{N_2}) sC = \frac{V_{N_2}}{R} + (V_{N_2} - V_{N_1}) sC$$

$$V_y sC = V_{N_2} (2sC + \frac{1}{R}) - V_{N_1} sC$$

$$= V_{N_2} \left(\frac{2sRC + 1}{R} \right) - V_{N_1} sC$$

$$V_y sC = \left\{ V_{N_1} \left(\frac{1+2RCS}{RCS} \right) - V_x \right\} \left(\frac{1+2RCS}{R} \right) - V_{N_1} sC.$$

$$V_y sC = V_{N_1} \left\{ \left(\frac{1+2RCS}{RCS} \right) \left(\frac{1+2RCS}{R} \right) - \frac{1}{CS} \right\} - V_x \left(\frac{1+2RCS}{R} \right)$$

$$= V_{N_1} \left\{ \frac{(1+2RCS)^2 - R^2}{R^2 CS} \right\} - V_x \left(\frac{1+2RCS}{R} \right)$$

$$= \frac{V_x (1+RCS)}{RCS} \left(\frac{(1+2RCS)^2 - R^2}{R^2 CS} \right) - V_x \left(\frac{1+2RCS}{R} \right).$$