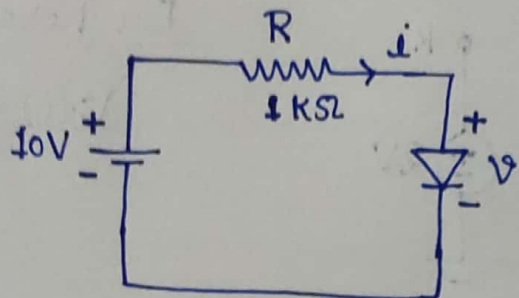


Q.1: For the given circuit, i - v characteristics are

$$i = \begin{cases} 0; & V < 0.7V \\ \frac{V - 0.7}{500} \text{ A}; & V \geq 0.7V. \end{cases}$$



Find Current i ?

Sol: $i = \frac{10 - V}{R}$

$$i = \frac{10 - V}{1000} \quad \text{--- (1)}$$

$$i = \frac{V - 0.7}{500} \quad \text{--- (2)}$$

From (1) & (2),


$$\begin{aligned} i &= \frac{10 - \frac{11.4}{3}}{1000} \\ &= \frac{30 - 11.4}{1000} \\ &= \frac{18.6}{1000 \times 3} \\ &= 6.2 \text{ mA} \end{aligned}$$

From (1) & (2),


$$V = \frac{11.4}{3} \quad \text{--- (3)}$$

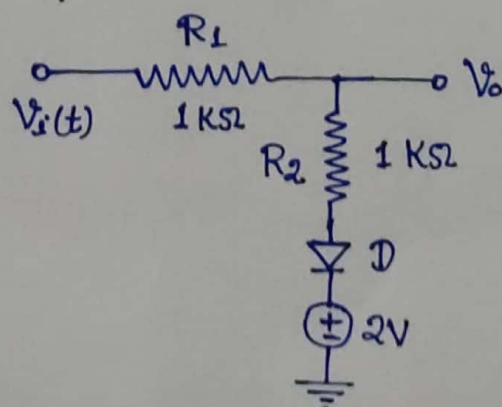Q.2: The diode in the given circuit has cut-in voltage 0.7V. ~~but~~

If $V_i(t) = 5 \sin \omega t$ V, the minimum and the maximum values of V_o (in Volts) are ?



Sol:- Step 1:

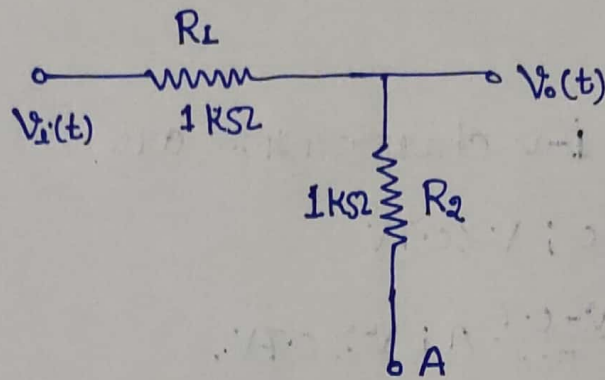

For Forward Bias


$$V_i(t) - 2 > 0.7$$

$$\text{or } V_i(t) > 2.7 \text{ V}$$

For Reverse Bias

$$V_i(t) \leq 2.7 \text{ V}$$

Step 2: When diode is Forward Bias

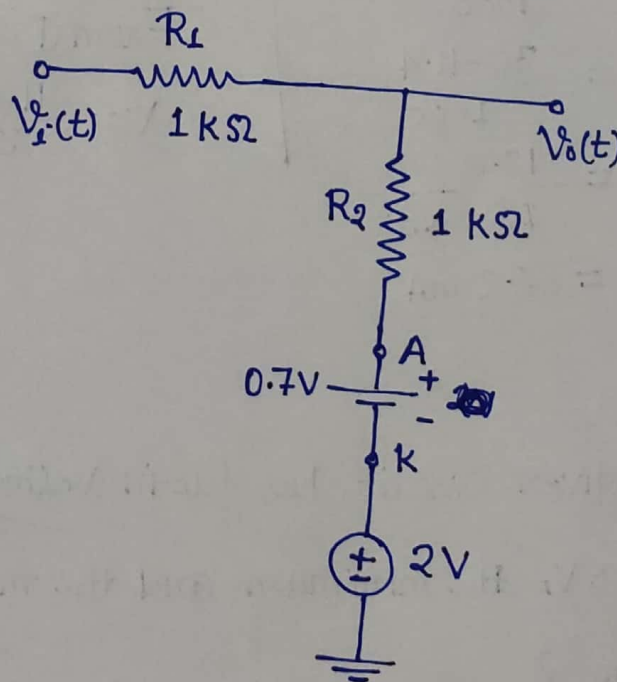


$$\{V_o(t)\}_{\text{max}} = 2.7 + \frac{2.3}{2}$$

$$= 2.7 + 1.15$$

$$= 3.85 \text{ V}$$

$$\{V_o(t)\}_{\text{min}} = 2.7 \text{ V}$$

Step 3: When diode D is in reverse bias

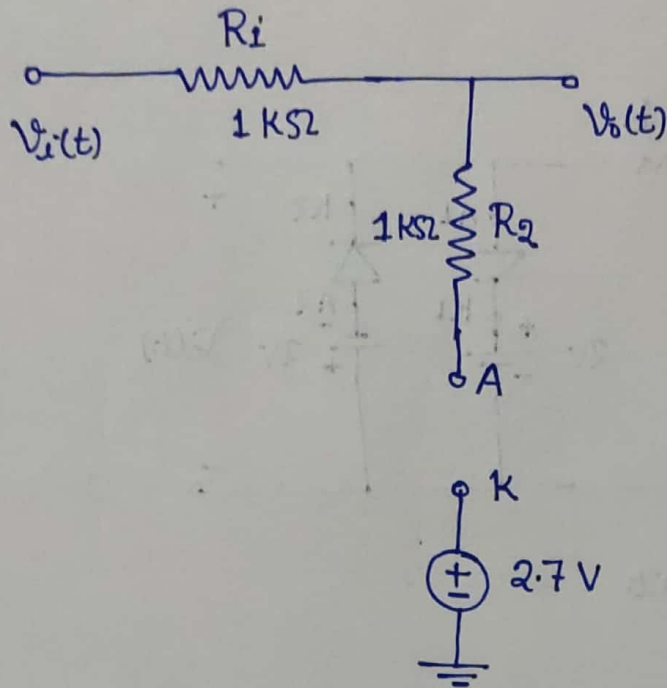


$$\{V_o(t)\}_{\max} = \cancel{3.85\text{ V}} 2.7\text{ V}$$

$$\{V_o(t)\}_{\min} = -5\text{ V}$$

Step 4: $\{V_o(t)\}_{\max} = 3.85\text{ V}$


$$\{V_o(t)\}_{\min} = -5\text{ V}$$

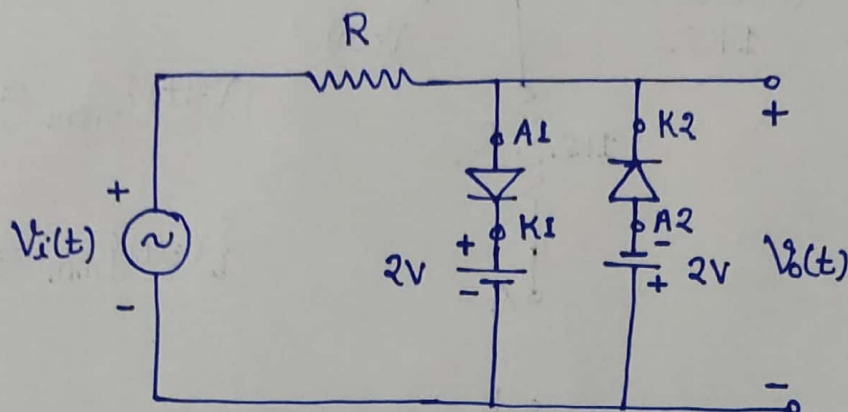Q.3: Determine $V_o(t)$ and transfer characteristic for the given circuit?



$$V_i(t) = 5 \sin \omega t$$

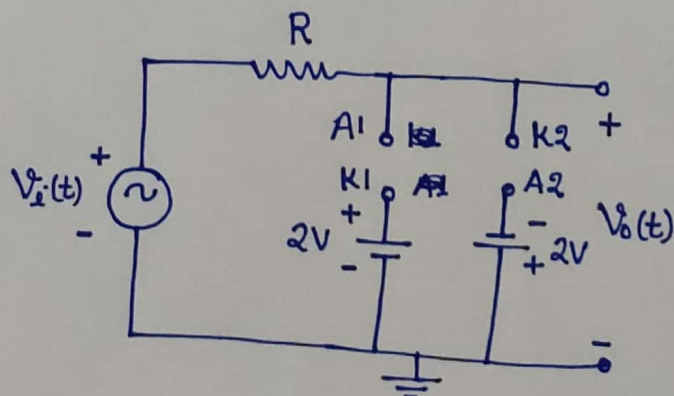Sol: Determine condition for F.B. and R.B. for diodes
Step 1: \uparrow



For D1

$$V_i(t) > 2V \Rightarrow \text{F.B.}$$

$$V_i(t) \leq 2V \Rightarrow \text{R.B.}$$


For D2

$$-2 - V_i(t) > 0$$

$$\text{or } V_i(t) < -2V \Rightarrow \text{F.B.}$$


$$V_i(t) \geq -2V \Rightarrow \text{R.B.}$$

Step 2: when $V_i(t) > 2V$

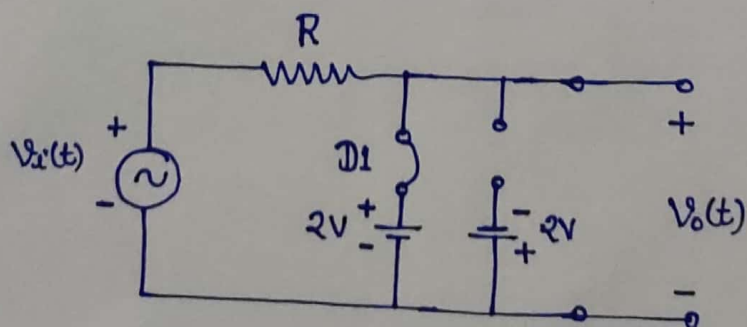


$$V_o(t) = 2V$$


Step 3: When $V_i < -2V$

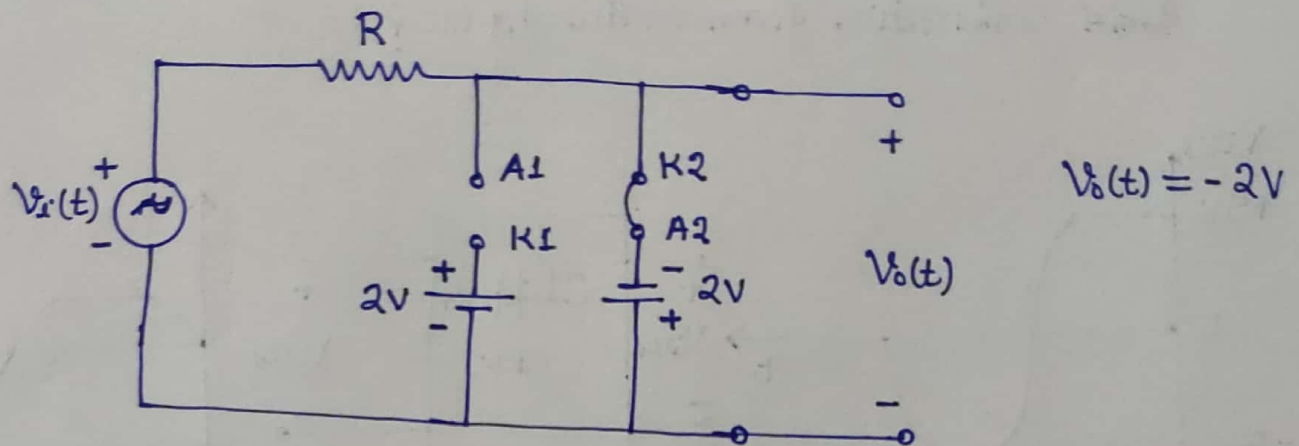


Step 4: When $-2V < V_i < +2V$

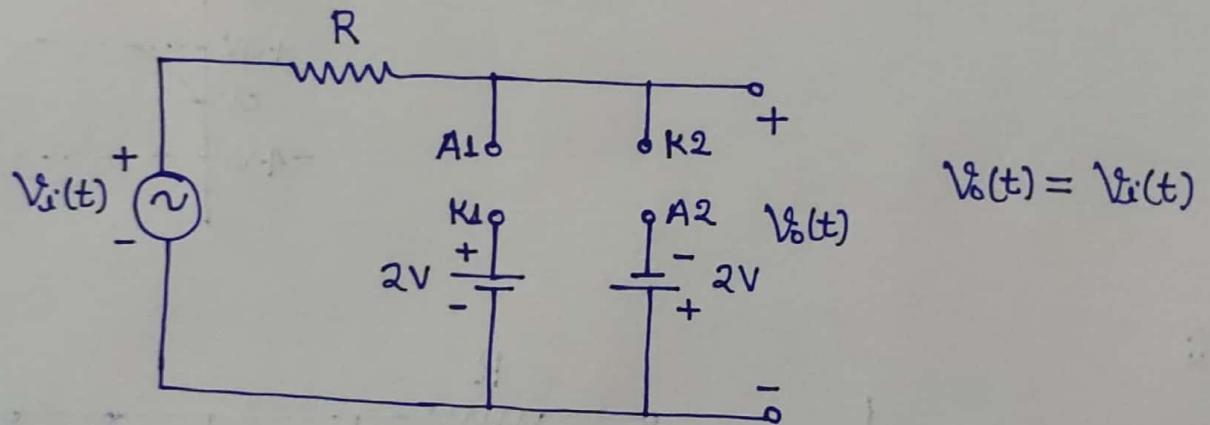


Step 5: Plot $V_o(t)$

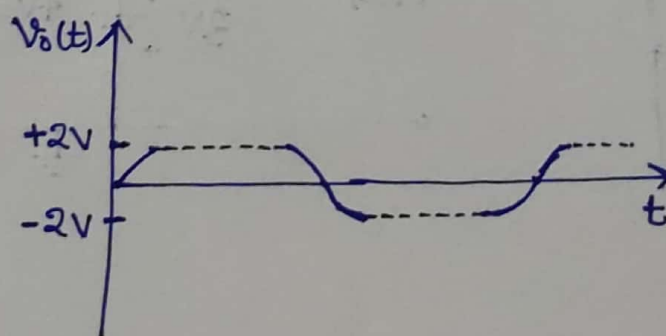


Step 6: Transfer Characteristics

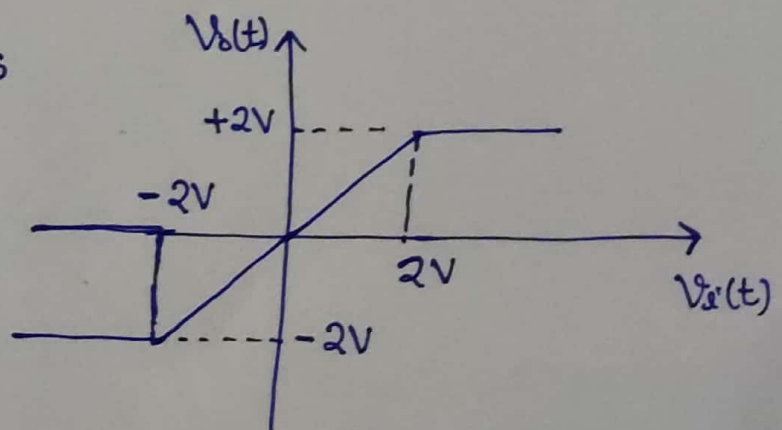

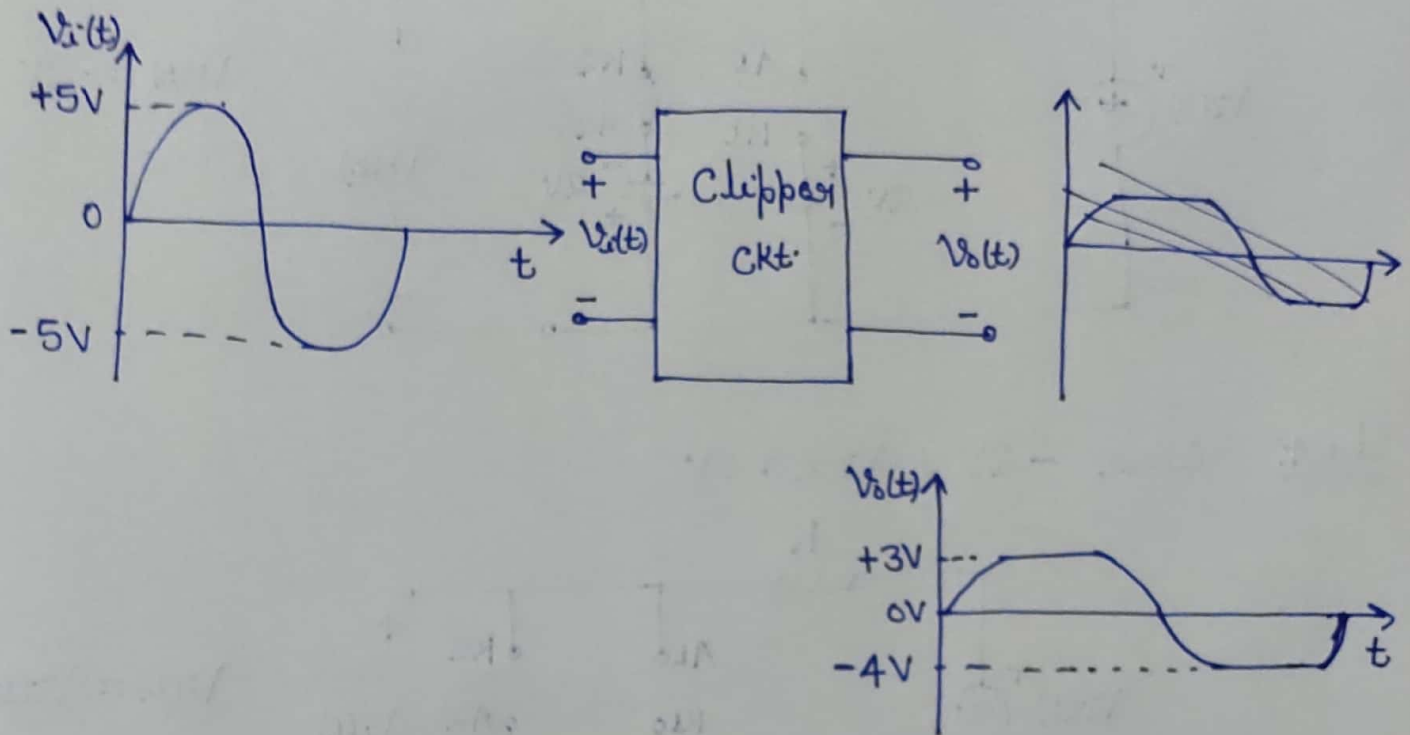
Q. 4:- Determine the clipper circuit corresponding to the input-Output combination given in the figure?



Sol:

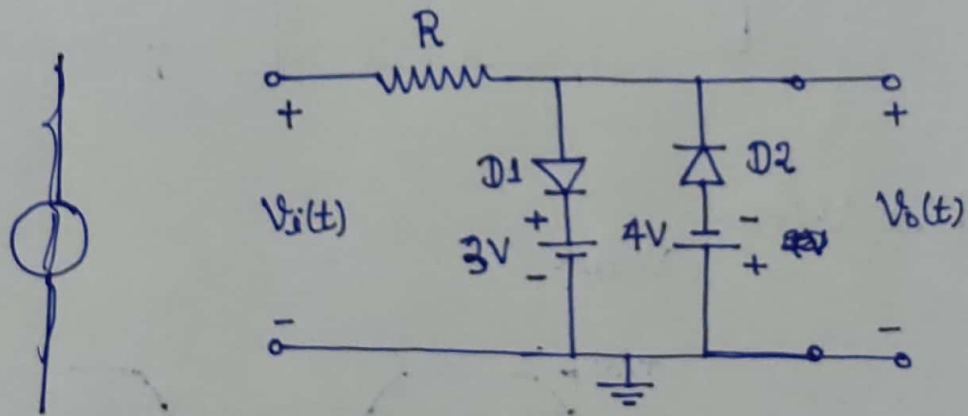

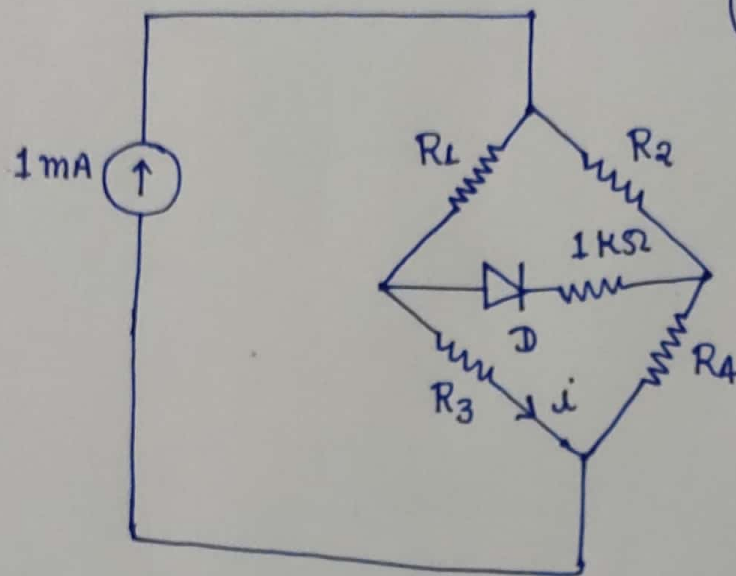Q. 5: In the given circuit, $V_f = 0.7V$. Find the current through 4Ω resistor?



Given that

$$R_1 = 2\text{ k}\Omega$$


$$R_2 = 3\text{ k}\Omega$$

$$R_3 = 4\text{ k}\Omega$$

$$R_4 = 6\text{ k}\Omega$$

Sol:
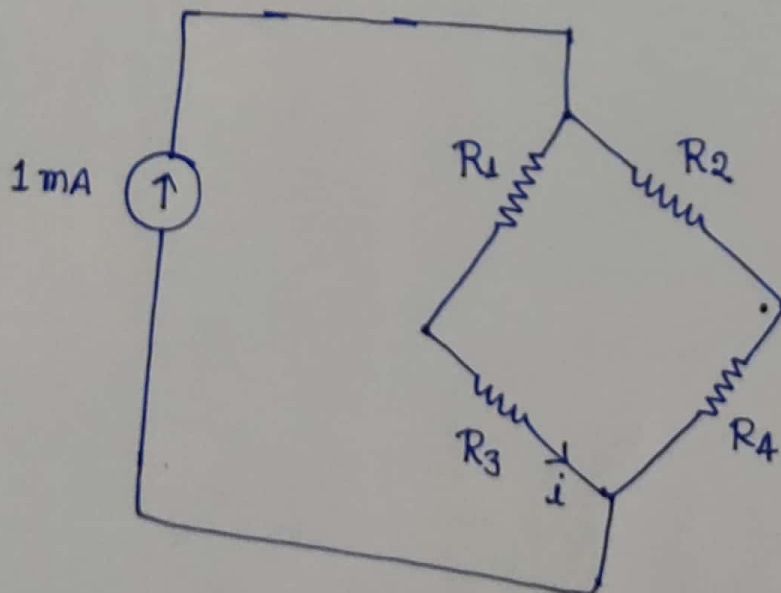
$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow \text{Balance bridge}$$



$$i = \frac{9}{15} \times 1\text{ mA}$$

$$= \frac{3}{5}\text{ mA}$$

$$= 0.6\text{ mA}$$