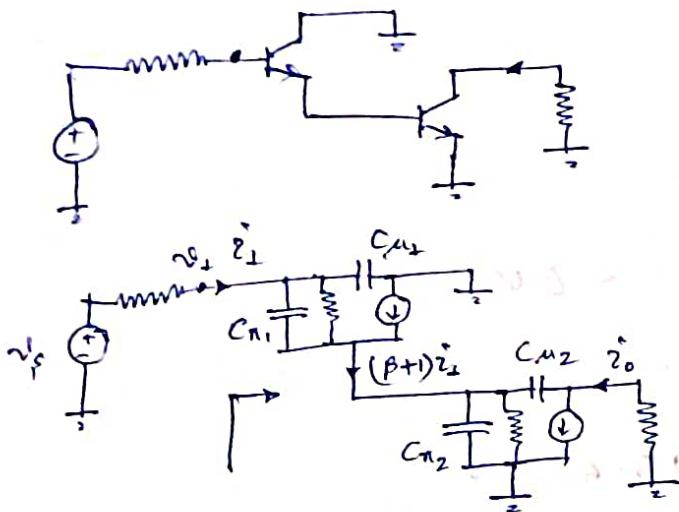


P. Common collector - Common Emitter stage:



Absence of shunt  
Miller Capacitance.

$$R_i \rightarrow \text{as before}, \quad i_o = \beta(B+1)i_s$$

$$= (\beta^2 + \beta) \times \frac{V_s}{R_i}$$

$$G_m = \frac{100(10)}{523K} = 19.3 \text{ mS}$$

$$\Rightarrow \frac{i_o}{V_s} = -G_m R_L \times \frac{R_i}{R_i + R_s}$$


$$\approx -49 \text{ V/V}$$

$$R_{\pi_1} \rightarrow \text{as before} = 43K$$


$$R_{\pi_2} \rightarrow \text{as before} = 1.5K$$

$$R_{\mu_2} \rightarrow \text{as before} = 177.3K$$

$$R_{\mu_2} \rightarrow ? = 84K\Omega$$

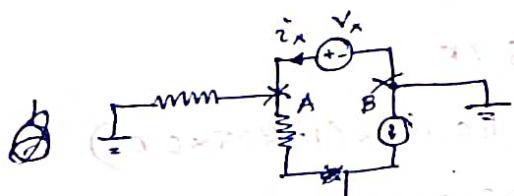

$$R_{AB} = R_i$$

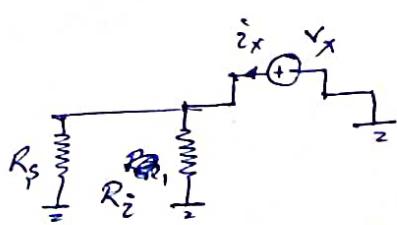

$$\Rightarrow R_{AB} = R_i \parallel R_s \\ = 84K\Omega$$

$$\Rightarrow T = \sum R_i C_i = 43K \times 2.1p + 84K \times 0.4p + 1.5K \times 11.84pF \\ + 177.3K \times 0.4pF \\ = 2.12 \text{ nS}$$

$$\Rightarrow f_{-3dB} = \frac{1}{2\pi \times 2.12 \text{ nS}} = 748 \text{ kHz}$$

## Cascade Amplifier:




Another case of avoiding shunt Miller effect

P.

$$C_{gs} = 90 \text{ fF}$$


$$C_{gd} = 14 \text{ fF}$$
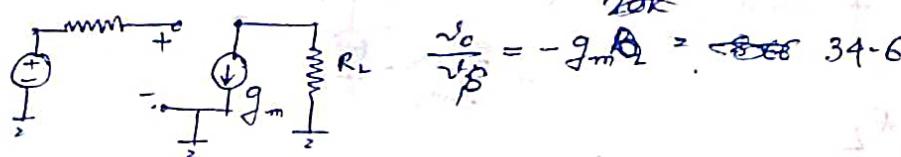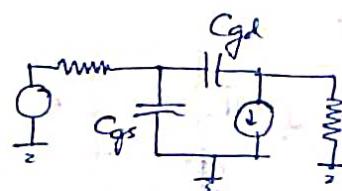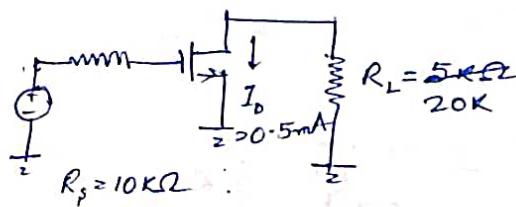
$$k_m' = 60 \mu A/V^2, \frac{W}{L} = \frac{100}{2}$$




$$g_m = \sqrt{2k_m' \left(\frac{W}{L}\right) I_d} = \sqrt{2.60 \mu \times 50 \times 0.5} = 7.73 \text{ mA/V}$$

Q.  $f_{-3\text{dB}} = ?$

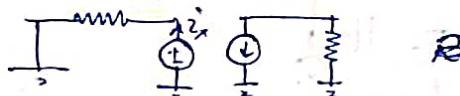
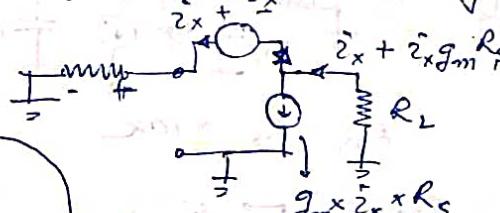
$$\Rightarrow R_{gs} = R_s, \therefore R_{gs} \cdot C_{gs} = 10k \times 90 \text{ fF} = 900 \text{ pS}$$



$$i_x R_s - v_x - (i_x + i_x g_m R_s) R_L = 0$$

$$\frac{v_x}{i_x} = R_s + R_L + g_m R_s R_L = R_{gd}$$

$$= 10k + 20k + 1.73 \times 25k \times 10k$$

$$= 101.5k \approx 376k$$

$$\Rightarrow R_{gd} > 101.5k$$

$$\Rightarrow R_{gd} \cdot C_{gd} = 421 \text{ pS} = 5.24 \text{ n}$$

$$\Rightarrow f_{-3\text{dB}} = \frac{1}{2\pi(1.42 \text{ n} + 0.9 \text{ n})} = 68 \text{ MHz}$$

$$\frac{C_{\pi} \cdot r_{\pi} + C_{gd} \cdot R'}{1}$$

$$\frac{10 \text{ pF} \times 2.5 \text{ k}}{1} + \frac{1 \text{ pF} \times 1.0125 \text{ M}}{1}$$

$$r_{\pi} + r_o + g_m r_{\pi} r_o$$

$$= 2.5 \text{ k} + 10 \text{ k} + 40 \text{ m} \times 2.5 \text{ k} \times 10 \text{ k}$$

$$= 12.5 \text{ k} + 100 \times 10 \text{ k} = 1.0125 \text{ M}$$

$$= \frac{1}{6.52 \times 10^{-6}}$$

$$= 153 \text{ kHz}$$

$$\frac{1}{2\pi(5.4 \text{ n} + 0.9 \text{ n})} = 25 \text{ MHz}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

$$g_m = \frac{I_c}{V_T} = \frac{1 \text{ mA}}{25 \text{ mV}}$$



$$\frac{1}{25} = 40 \text{ mS}$$

$$= \frac{100}{40 \text{ mS}} = 2.5 \text{ k} \Omega$$



$$r_o = \frac{10}{1 \text{ mA}} = 10 \text{ k}$$

$$-\frac{g_m}{2} \frac{g_m}{2} (r_o || R_{L2}) (r_o' || R_L') \\ = -\frac{g_m}{2} \frac{g_m}{2} \times \frac{R_L'}{g_m} = -g_m R_L'$$

Cascade Amp:

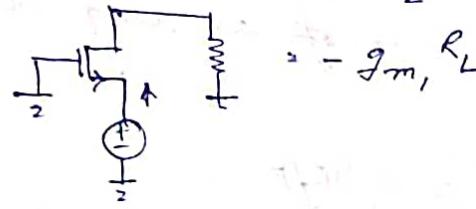
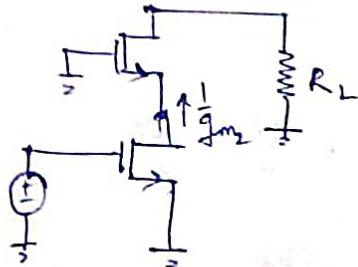


$$z_x = g_m v_{gs}$$

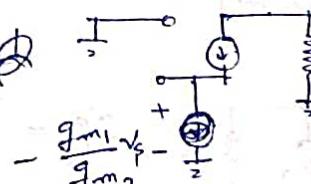
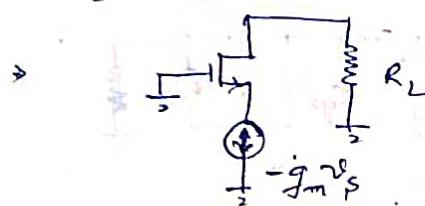


$$\frac{V_o}{V_i} = -g_m R_L$$

$$f_{-3dB} = ?$$

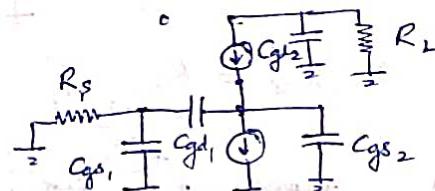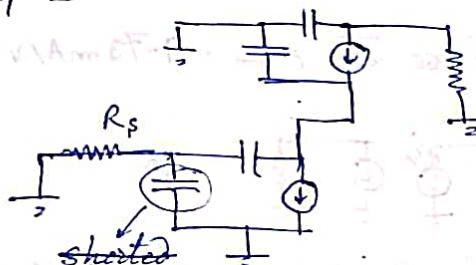


$$R_{gs1} = R_s \approx 10k$$

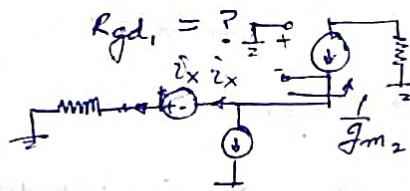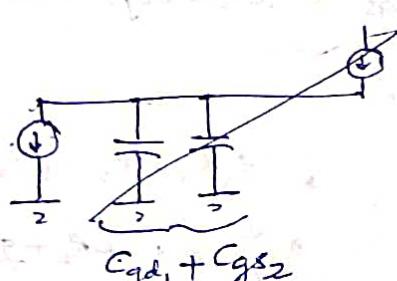

$$R_{gd2} = R_L = 20k$$

$$R_{gs2} = \frac{1}{g_m} = 0.56k$$

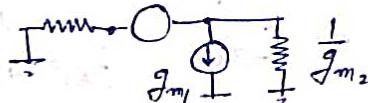

$$\Rightarrow R_{gd1} = R_s + \frac{1}{g_m} + g_m \times \frac{1}{g_m} \times R_s$$

$$= 10k + 0.56k + 10k$$

$$= 20.56k$$

$$\Rightarrow \tau = 10k \times 90f$$

$$+ 0.56k \times 90f$$

$$+ 20.56k \times 14f$$

$$+ 20k \times 14f = 1.51ms$$

$$\Rightarrow f_{-3dB} = \frac{1}{2\pi \cdot 1.51ms} = 104MHz$$

## stability of feedback amplifier

consider a single pole amplifier.

$$a(s) = \frac{a_0}{1 + \frac{s}{P_1}} \quad \text{= open loop gain.}$$


$$\text{closed loop gain: } A(s) = \frac{a(s)}{1 + f a(s)},$$

assuming  
 $f \rightarrow$  only formed  
 only by passive  
 component.

$$A(s) = \frac{\frac{a_0}{1 + \frac{s}{P_1}}}{1 + f \frac{a_0}{1 + \frac{s}{P_1}}} = \frac{a_0}{1 + f a_0 + \frac{s}{P_1}}$$

$$A(s) = \frac{(1 + f a_0) a_0}{1 + \frac{s}{P_1} + f a_0} = \frac{a_0}{1 + f a_0 + \frac{s}{P_1}} = \frac{a_0}{1 + \frac{s}{P_1(1 + f a_0)}}$$

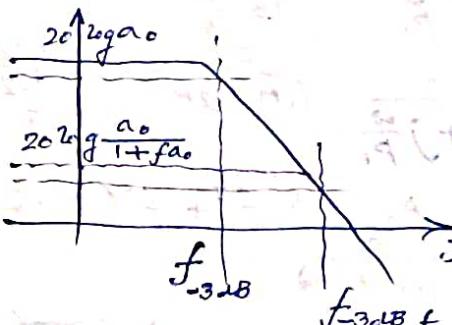clearly, gain falls by  $1 + f a_0$ , BW increases by the same factor.




$$f_{-3dB} = \frac{P_1}{2\pi f}$$

$$(1 - \frac{s}{P_1})$$


$$\Rightarrow \sqrt{1 + \frac{\omega^2}{P_1^2}}$$

$$f_{-3dB_f} = \frac{P_1 (1 + f a_0)}{2\pi}$$
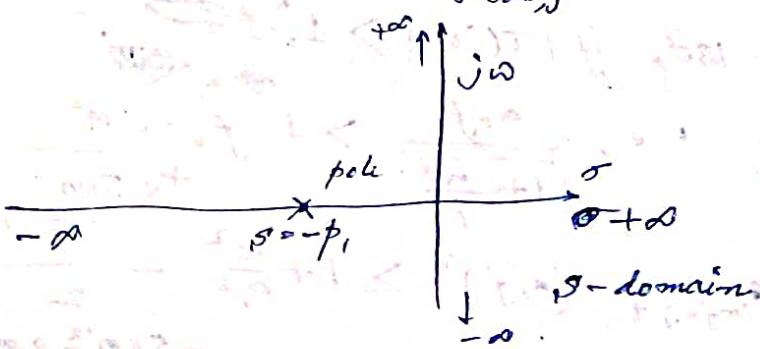
$$\omega = f, \\ \Rightarrow 2\pi f = P_1$$


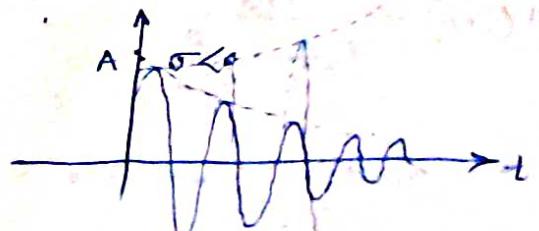
$$\text{let } f(t) = A \cdot e^{\sigma t} \\ = A \cdot e^{\sigma t} \cdot e^{j\omega t}$$





$$T(s) = \frac{1}{s+a} = \frac{v_i(s)}{v_o(s)}$$

$$\Rightarrow v_o(s) = \frac{v_i(s)}{s+a}$$

$$\begin{aligned}\Rightarrow v_o(t) &= L^{-1}\left\{\frac{1}{s+a}\right\} \\ &= \frac{1}{a} e^{-at} \left\{ \frac{1}{s} - \frac{1}{s+a} \right\} \\ &= \frac{1}{a} (1 - e^{-at})\end{aligned}$$

$$\text{if } a(s)f = T(s)$$

$$\text{if } T(s) = \text{loop gain: } a(s)f$$

$$\text{if } |a(s)f| \text{ at } \angle T = 180^\circ > 1,$$

$$\text{i.e., let, } a(s)f = R + jI$$

$$= \text{Re } L(j\omega) + j \text{Im}(j\omega)$$

$$(1 + \frac{s}{P_1})$$

$$\frac{10}{(1 + j \frac{4 \cdot 17M}{2M})(1 + j \frac{4 \cdot 17M}{1M})}$$

$$\begin{aligned}&= \frac{10}{e^{j64.37} \cdot e^{j76.51}} \\&= 1 \cdot e^{-j140.88^\circ}\end{aligned}$$

$$\text{let, } a(s)f = \frac{R \cdot a_0 f}{(1 + \frac{s}{P_1})(1 + \frac{s}{P_2})} = \frac{K}{(1 + j \frac{\omega}{P_1})(1 + j)}$$

$$\frac{a_0 f}{\sqrt{(1 + (\frac{f}{2M})^2)(1 + (\frac{f}{1M})^2)}}$$

$$= \frac{a_0 f}{(1 + \frac{s}{P_1})} = \frac{a_0 f}{1 + \frac{\sigma + j\omega}{P_1}} \quad \cancel{\frac{f^4}{(2M)^2}}$$

$$= \frac{a_0 f}{1 + \frac{\sigma}{P_1} + j \frac{\omega}{P_1}} \quad \cancel{\frac{f^4}{(1M)^2 (2M)^2}} + \cancel{\frac{f^2 (\frac{1}{2M^2} + \frac{1}{1M^2})}{(1M)^2 (2M)^2}} + 1 = 0$$

$$A(s) = \frac{\frac{a_0}{1 + f a_0}}{1 + \frac{s}{P_1(1 + f a_0)}} = \frac{A_0}{1 + \frac{s}{A_0(1 + f a_0)}} \Rightarrow f^4 + f^2 (1M^2 + (2M)^2) - 99 \times 1M^2 \times (2M)^2 = 0$$

at  $\angle T(j\omega) = 180^\circ$ , if  $|T(j\omega)| > 1$ ,  $f^2 = \cancel{\frac{f^2}{(2M)^2}}$ .

$$\text{i.e., } \frac{a_0 f}{\sqrt{1 + \frac{\omega^2}{P_1^2}}} > 1 \cdot f^2 = 5M^2$$

$$A(j\omega) = \frac{A_0}{1 + \frac{s}{P_1(1 + f a_0)}}$$

$$\Rightarrow v_o(t) = v_{in}(t) \times A_0 \cdot e^{-P_1(f a_0) t} \cdot (a_0 f)^2 > 1 + \frac{\omega^2}{P_1^2} \quad \cancel{\frac{-5 \times 10^{12} + 3.99 \times 10^8}{2}}$$

$$f = 4.17 \text{ MHz}$$

$$A(j\omega) = \frac{(1+j\frac{\omega}{\omega_1})(1+j\frac{\omega}{\omega_2}) + fa_o}{s + p_1 + fa_o} \rightarrow 1 - \frac{\omega^2}{\omega_1 \omega_2} + j\left(\frac{\omega}{\omega_1} + \frac{\omega}{\omega_2}\right) + fa_o = 0$$

$$T(j\omega) = \frac{10}{(1+j\frac{\omega}{\omega_1})(1+j\frac{\omega}{\omega_2})(1+j\frac{\omega}{\omega_3})}$$

$$\Rightarrow v_o(t) = v_{in}(t) \cdot a_o p_1 e^{-p_1 t} e^{-(p_1 + fa_o) \cdot t}$$

$$a(j\omega)f = \frac{a_o f}{1 + \frac{s}{p_1}} = \frac{a_o f p_1}{s + p_1}$$

$$a(s) = \frac{R a_o}{(s + p_1)(s + p_2)}$$

$$s + p_1 < a_o f p_1$$

$$A(s) = \frac{a(s)}{1 + f a(s)} = \frac{\frac{a(s)}{f}}{1 + \frac{f a_o}{(s + p_1)(s + p_2)}} = \frac{a_o}{1 + \frac{f a_o}{(s + p_1)(s + p_2)}}$$

$$\text{let, } (a_o f)^2 = K \cdot (1 + \frac{\omega_0}{p_1})^2$$

where  $K > 1$

$$A(j\omega) =$$

$$\Rightarrow p_1 = K \cdot \frac{\omega_0}{a_o f}$$

$$\frac{A_o}{1 + \frac{j\omega_0}{p_1(1+fa_o)}}$$

$$\Rightarrow A(s) = \frac{a_o}{(s + p_1)(s + p_2) + fa_o}$$

$$\Rightarrow \text{at, } \omega^2 - j\left(\frac{1}{\omega_1} + \frac{1}{\omega_2}\right)\omega - (1+fa_o) = 0$$

$$\frac{1}{(s-2p_1)} \cdot a(s) \cdot f = \frac{1}{(s-2+j3)} \Rightarrow \omega^2 - j(\omega_1 + \omega_2)\omega - (1+fa_o) = 0$$

$$A(s) = \frac{1}{(s-2+j3)}$$

$$\Rightarrow v_{in}(t) =$$

$$\angle \frac{-3}{2+j(\omega+3)}$$

$$= -\tan^{-1} \frac{\omega+3}{2}$$

$$\text{at, } f = \frac{1}{s+2+j3} = \frac{a_o}{s+2+j3}$$

$$\text{at, } \angle a_o(s) \cdot f = \tan^{-1} \left( -\frac{\omega}{\omega+3} \right)$$

$$-\tan^{-1} \frac{\omega+3}{2} = 180^\circ$$


$$\Rightarrow \omega = -3$$

$$\Rightarrow \frac{a_o(s)}{1 + a_o(s)f} = \frac{1}{s+2+j3} \cdot \frac{1}{1 + \frac{1}{s+2+j3}} = \frac{1}{s+3+j3}$$



$$a_o(s) \cdot f = \frac{3}{s+2+j3} \cdot \frac{1}{s+2+j3} = \frac{1}{s+3+j3}$$

$$\Rightarrow \frac{\frac{1}{s+2+j3}}{1 - \frac{3}{s+2+j3}} = \frac{1}{s+2+j3-3} = \frac{1}{s-1+j3}$$

1st stage equivalent ckt:


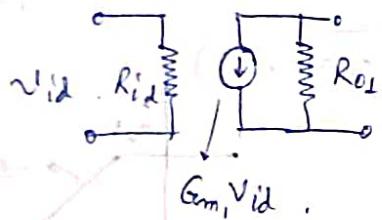


ac schematic:

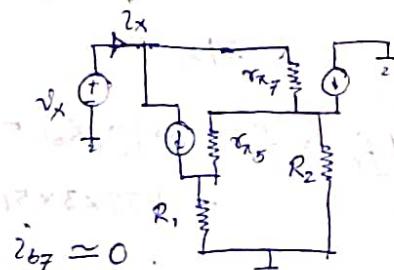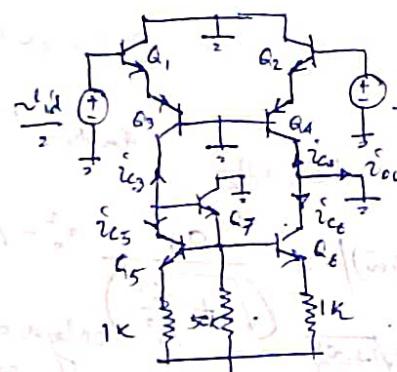

$$\begin{aligned} i_{c7} &\approx 0 \\ i_{c7} &= -(i_{c4} + i_{c6}) \\ &= -(i_{c4} - i_{c3}) \end{aligned}$$
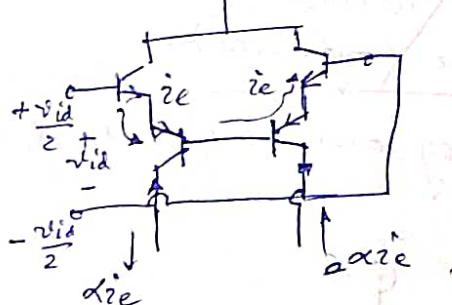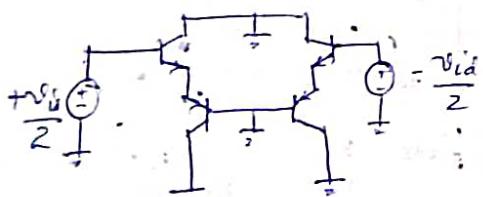
$$\begin{aligned} \beta_{n-pm} &= 200 \\ \beta_{p-np} &= 50 \end{aligned}$$




$$v_{id} = i_e \times 4 \cdot r_e$$

$$2 i_e \times 4 \cdot \frac{r_e}{\beta+1} \rightarrow v_{id} = \frac{\beta \cdot 2 i_e (\beta+1)}{\beta+1} \cdot i_e \times 4 \cdot \frac{r_e}{\beta+1}$$

$$\rightarrow \frac{v_{id}}{i_e} = 4 r_e = 4 \cdot \frac{\beta}{g_m}$$

## CS amplifier

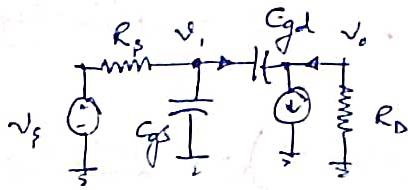

$$(v_i - v_o) s C_{gd} + \frac{v_o}{R_D} - g_m v_i = 0$$

$$v_i (s C_{gd} - g_m) = v_o (s C_{gs} + \frac{1}{R_D})$$

$$v_i = \frac{s C_{gs} \frac{1}{s C_{gd}} \times v_s}{R_s + \frac{1}{s C_{gs}}} = \frac{v_s \cdot 1}{(1 + s C_{gs} R_s)}$$

$$v_o = \frac{(s C_{gd} - g_m) \times v_s}{(s C_{gd} + \frac{1}{R_D})(1 + s C_{gs} R_s)}$$

$$= \frac{R_D (s C_{gd} - g_m) v_s}{(1 + s C_{gd} R_D)(1 + s C_{gs} R_s)} \Rightarrow v_o = \frac{(s C_{gd} - g_m)}{(s C_{gd} + \frac{1}{R_D})} v_i$$

~~$$v_o = \frac{(s C_{gd} + \frac{1}{R_D})}{(s C_{gd} - g_m)}$$~~

$$\frac{(v_f - v_o)}{R_s} = v_i \cdot s C_{gs} + (v_i - v_o) s C_{gd}$$

$$\frac{v_f}{R_s} = v_i \left( \frac{1}{R_s} + s C_{gs} + s C_{gd} \right) - v_o s C_{gd}$$

$$v_i \left( \frac{1}{R_s} + s (C_{gs} + C_{gd}) \right) = \frac{v_f}{R_s} + v_o s C_{gd}$$

$$\Rightarrow v_o = \frac{(s C_{gd} - g_m)}{(s C_{gd} + \frac{1}{R_D})} \times \frac{\left( \frac{v_f}{R_s} + v_o s C_{gd} \right)}{\left( \frac{1}{R_s} + s (C_{gs} + C_{gd}) \right)}$$

$$\Rightarrow v_o \left\{ 1 - \frac{(s C_{gd} - g_m) s C_{gd}}{(s C_{gd} + \frac{1}{R_D}) \left( \frac{1}{R_s} + s (C_{gs} + C_{gd}) \right)} \right\} = \frac{(s C_{gd} - g_m) \frac{v_f}{R_s}}{(s C_{gd} + \frac{1}{R_D}) \left( \frac{1}{R_s} + s (C_{gs} + C_{gd}) \right)}$$

$$\Rightarrow v_o \left\{ s^2 C_{gd}^2 + s^2 C_{gs} C_{gd} + \frac{s C_{gd}}{R_s} + s \frac{(C_{gs} + C_{gd})}{R_D} + \frac{1}{R_s R_D} - s^2 C_{gd}^2 + s g_m C_{gd} \right\}$$

$$- (s C_{gd} - g_m) \frac{v_f}{R_s}$$

$$\rightarrow \left( s^2 C_{gs} C_{gd} + \frac{s C_{gd}}{R_f} + \frac{s(C_{gs} + C_{gd})}{R_D} + s g_m C_{gd} + \frac{1}{R_f R_D} \right) V_o = - \frac{v_f (g_m - s C_{gd})}{R_f}$$

$$\rightarrow \left( s^2 C_{gs} C_{gd} R_f R_D + s C_{gd} R_D + s(C_{gs} + C_{gd}) R_f + s g_m C_{gd} R_f R_D + 1 \right) V_o = - \frac{v_f (g_m - s C_{gd})}{R_f} R_D$$

$$\rightarrow \left( 1 + \frac{s}{P_1} \right) \left( 1 + \frac{s}{P_2} \right) V_o = - \frac{v_f (g_m - s C_{gd})}{R_f} R_D$$

$$\rightarrow \left\{ \frac{s^2}{P_1 P_2} + s \left( \frac{1}{P_1} + \frac{1}{P_2} \right) + 1 \right\} V_o = - \frac{v_f (g_m - s C_{gd})}{R_f} R_D$$

$$\frac{1}{P_1} + \frac{1}{P_2} = C_{gd} R_D + (C_{gs} + C_{gd}) R_f + g_m C_{gd} R_f R_D$$

$$\frac{1}{P_1} \cdot \frac{1}{P_2} = C_{gs} C_{gd} R_f R_D \quad \frac{1}{P_1} + \frac{1}{P_2} \approx \frac{1}{P_1},$$

$$\frac{1}{P_1} = C_{gs} C_{gd} R_f R_D \quad \text{then} \quad \frac{1}{P_1} = C_{gd} R_D + (C_{gs} + C_{gd}) R_f + g_m C_{gd} R_f R_D$$

$$\rightarrow \frac{1}{P_1} \cdot \frac{1}{P_2} = C_{gs} C_{gd} R_f R_D \quad \rightarrow \frac{1}{P_1} \approx g_m C_{gd} R_f R_D$$

$$\rightarrow \frac{1}{P_2} = C_{gs} C_{gd} R_f R_D \cdot \frac{1}{g_m C_{gd} R_f R_D} \quad \rightarrow P_1 = \frac{1}{g_m C_{gd} R_f R_D}$$

$$\rightarrow P_2 \approx \frac{g_m}{C_{gs}}$$

Poles :



$$s^2 4.05 \times 10^{-19} + s 1.054 \times 10^{-8} + s \cdot 7.785 \times 10^{-9} + 1 = 0$$

$$\rightarrow s = \frac{-1.054}{s^2 4.05 \times 10^{-19} + s 1.837 \times 10^{-8} + 1} = 0$$

$$\rightarrow s = \frac{-1.837 \times 10^{-8} \pm \sqrt{(1.837 \times 10^{-8})^2 - 4 \cdot 4.05 \times 10^{-19}}}{2 \cdot 4.05 \times 10^{-19}}$$

$$\rightarrow \frac{-1.837 \times 10^{-8} \pm 1.825 \times 10^{-8}}{8 \cdot 1 \times 10^{-19}}$$

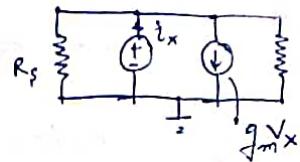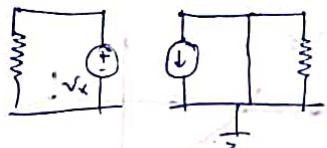
$\Rightarrow s_1 \text{ & } s_2 = 13.75 \text{ MHz}$   
 $7.2 \text{ GHz}$




$$P_1 = -\frac{1}{R_s \{ G_S + (1 + g_m R_D) G_D \}}$$

$$P_2 = -\frac{1}{R_D \cdot G_D}$$


$$\frac{1}{3k \times 15f} =$$

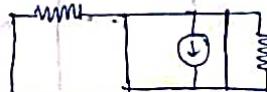


$$R_2 C_2$$

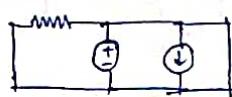

### Theory of pole splitting:

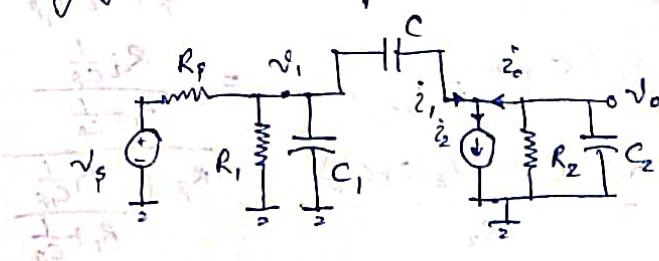

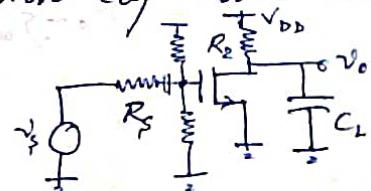a typical MOS amplifier  
with capacitive load:



$$\begin{aligned} i_1 &= (v_i - v_o) s C \\ i_2 &= g_m v_i \\ i_o &= -\frac{v_o}{R_2 \parallel \frac{1}{s C_F}} = -\frac{v_o (1 + R_2 C_2 F)}{R_2} \end{aligned}$$

$$R_1 \parallel \frac{1}{s C_F} \cdot v_s = \frac{R_1}{R_s + R_1 \parallel \frac{1}{s C_F}} = \frac{R_1}{R_s + \frac{R_1}{1 + R_1 C_1 F}}$$

$$= \frac{R_1}{R_s + R_1 R_s C_1 F + R_1}$$


$$= \frac{R_1}{R_s + R_s + s R_1 C_1 R}$$

$$(v_i - v_o) s C - \frac{v_o (1 + R_2 C_2 F)}{R_2} - g_m v_i = 0$$

$$v_i (s C - g_m) = v_o s C + \frac{v_o (1 + R_2 C_2 F)}{R_2}$$




$$2 v_o \frac{s C R_2 + 1 + R_2 C_2 F}{R_2}$$
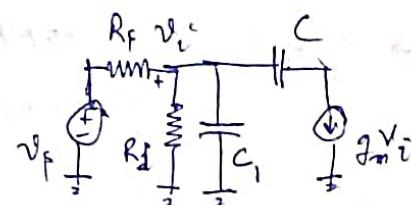
$$\Rightarrow v_1(sC - g_m) = v_o \frac{(1 + sCR_2 + sC_2R_2)}{R_2}$$



$$v_o \frac{v_o}{v_i} = \frac{R_2(sC - g_m)}{1 + sR_2(C + C_2)} \cdot v_1$$
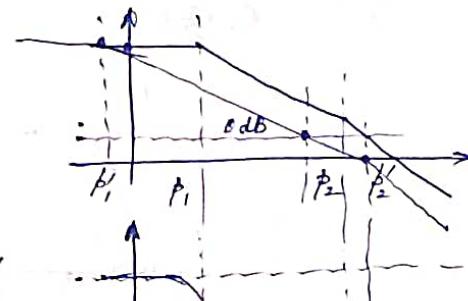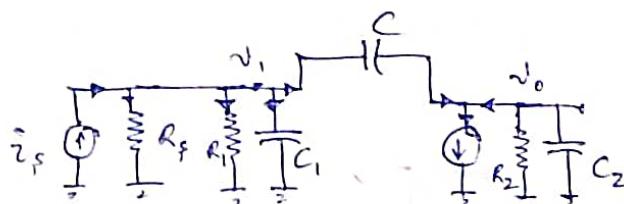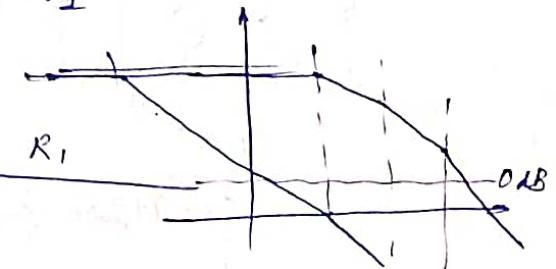
$$= \frac{R_2(sC - g_m)}{1 + sR_2(C + C_2)} \times R_1$$



$$v_s = i_s \cdot R_s$$

$$\text{let, } R_f \parallel R_1 = R_1'$$

$$i_s = \frac{v_1}{R_1' \parallel \frac{1}{C_1 s}} + (v_1 - v_o) C_F$$

$\rightarrow$  PM  $\rightarrow$  very small


$$(v_1 - v_o) C_F - \frac{v_o}{R_2 \parallel \frac{1}{C_2 s}} = g_m v_1, \quad v_1 = \frac{R_2 \parallel \frac{1}{C_1 s}}{R_f + R_2 \parallel \frac{1}{C_1 s}} v_o$$

$$\Rightarrow v_1 C_F - g_m v_1 = v_o \left( C_F + \frac{1}{R_2 \parallel \frac{1}{C_2 s}} \right) = \frac{R_2 \parallel \frac{1}{C_F}}{R_f + R_2 \parallel \frac{1}{C_F}} v_o$$

$$\Rightarrow v_o = \frac{v_1 (C_F - g_m) R_2}{\{1 + sR_2(C + C_2)\}} = \frac{R_1 / R_F + 1}{R_f + \frac{R_1}{1 + R_F}} v_i$$

$$\Rightarrow \frac{v_1 (1 + sR_1(C + C_1))}{R_1} = i_s + v_o C_F = \frac{R_1}{R_f + R_1 + R_1 G_F} v_i$$
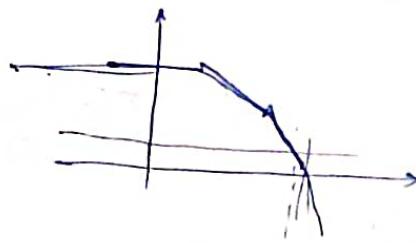
$$\Rightarrow v_1 = \frac{(i_s + v_o s) R_1}{1 + sR_1(C + C_1)}$$



741 op-amp

$$\omega_{\text{crossover}} = \frac{\omega_0}{(1 + \frac{s}{P_1})(1 + \frac{s}{P_2})} \quad (1 + \frac{s}{P_3})$$

$$\Rightarrow \omega_0 = \frac{(C_F - g_m) R_2}{\{1 + s R_2 (C + C_2)\}} \times \frac{(i_s + \omega_0 C_F) R'_1}{\{1 + s R'_1 (C + C_1)\}} = A \quad B$$

$$P_1 = 30 \text{ Hz}$$

$$P_2 = 500 \text{ Hz}$$

$$P_3 = 10 \text{ MHz}$$

$$= \frac{(C_F - g_m) R_2 \cdot i_s}{\{A\}\{B\}} + \frac{\omega_0 C R'_1 s (C_F - g_m) R_2}{\{A\}\{B\}}$$

$$\Rightarrow \omega_0 \left\{ 1 - \frac{C R'_1 s (C_F - g_m) R_2}{\{A\}\{B\}} \right\} = \frac{(C_F - g_m) R_2 \cdot i_s}{\{A\}\{B\}}$$

$$\Rightarrow \omega_0 \left\{ s^2 R_2 R'_1 (C + C_1) (C + C_2) + s \{R_2 (C + C_2) + R'_1 (C + C_1)\} - \cancel{s^2 C^2 R'_1 R_2 + g_m R_2 R'_1 C_F} + 1 \right\}$$

$$= (C_F - g_m) R_2 \cdot i_s$$

$$\Rightarrow \omega_0 \left\{ s^2 R_2 R'_1 (C_1 C_2 + C(C_1 + C_2)) + s \{R'_1 (C + C_1) + R_2 (C + C_2) + g_m R'_1 R'_2 C\} + 1 \right\}$$

$$= (C_F - g_m) R_2 \cdot i_s$$

$$\Rightarrow \omega_0 = \frac{(C_F - g_m) R_2 \cdot i_s}{\{s^2 R_2 R'_1 (C_1 C_2 + C(C_1 + C_2)) + s \{R'_1 (C + C_1) + R_2 (C + C_2) + g_m R'_1 R'_2 C\} + 1\}}$$

$$\frac{\omega_0}{i_s} = \frac{(C_F - g_m) R_2 \cdot i_s}{(1 + \frac{s}{P_1})(1 + \frac{s}{P_2})} \quad \text{if } P_1 \ll P_2, \quad \frac{1}{P_1} + \frac{1}{P_2} \approx \frac{1}{P_1}$$

$$\Rightarrow \frac{1}{P_1} \approx R'_1 (C + C_1) + R_2 (C + C_2) + g_m R'_1 R'_2 C$$

$$= \frac{(C_F - g_m) R_2 \cdot i_s}{\frac{s^2}{P_1 P_2} + s \left( \frac{1}{P_1} + \frac{1}{P_2} \right) + 1} \approx g_m R_2 R'_1 C$$

$$\therefore \frac{1}{P_1 P_2} = R_2 R'_1 \{C_1 C_2 + C(C_1 + C_2)\} \Rightarrow P_2 = \frac{g_m}{C}$$

$$\Rightarrow P_1 = \frac{1}{g_m R_2 R_1 C}$$

$\beta! \quad T(jf) = \frac{\alpha_0 \beta}{(1+j\frac{f}{f_1})(1+j\frac{f}{f_2})} \quad \beta = 1, \alpha_0 = 100dB$

$f_1 = 100Hz$

$f_2 = 120kHz$

$$P_2 = \frac{g_m C}{C_1 C_2 + C(C_1 + C_2)}$$

$\beta! \quad T(jf) = \frac{\alpha_0 \beta (1+j\frac{f}{f_2})}{(1+j\frac{f}{f_1})(1+j\frac{f}{f_2})} \quad f_2 = 100kHz$

for  $\beta = 1$  &  $\beta = 10^{-3}$

as  $C$  increases,  $P_1$  &  $P_2$  split further.

Q. an amplifier has a phase margin of  $20^\circ$ , what is the closed loop gain peak

An amplifier with low freq. fed. gain:  $40K$ . compared to the low freq. value  
-ve real poles at  $-2kHz, 200kHz, 4MHz$ , at  $f$ .

If it is connected in feedback with  $f = \text{constant}$ . i.e.  $|T(jf)| = 1$

Q.  $\infty$  closed loop gain:  $400$ . or closed loop gain is  $9.2dB$

i) determine the phase margin.

ii)

$$A_{CL} = \frac{A_o}{1+f \cdot A_o} \quad A_o = 40K$$

$$\Rightarrow \frac{40K}{1+f \cdot 40K} = 400$$

$$\Rightarrow 1+f \cdot 40K = \frac{40K}{400} = 100$$

$$\Rightarrow f \cdot 40K = 100 \Rightarrow f = 2.5 \times 10^{-3}$$

$$\text{loop gain} = A_o(j\omega) \cdot f = \frac{A_o f}{(1+j\frac{\omega}{\omega_1})(1+j\frac{\omega}{\omega_2})(1+j\frac{\omega}{\omega_3})}$$

the PM when

$$|A_o(j\omega) \cdot f| = 1,$$

$$100 \cdot \frac{A_o f}{\sqrt{1+(\frac{\omega}{\omega_1})^2} \sqrt{1+(\frac{\omega}{\omega_2})^2} \sqrt{1+(\frac{\omega}{\omega_3})^2}} = 1$$

$$\Rightarrow 100 = \sqrt{1+(\frac{\omega}{\omega_1})^2} \sqrt{1+(\frac{\omega}{\omega_2})^2} \sqrt{1+(\frac{\omega}{\omega_3})^2}$$

$$\therefore 20 \log 100 = 20 \log \left\{ 1 + \left( \frac{\omega}{\omega_1} \right)^2 \right\} + 20 \log \left\{ 1 + \left( \frac{\omega}{\omega_2} \right)^2 \right\} + 20 \log \left\{ 1 + \left( \frac{\omega}{\omega_3} \right)^2 \right\}$$

at  $\omega = \omega_1$ ,  $\omega_1 \ll \omega_2, \omega \ll \omega_3$

$$\text{Loop gain} = \frac{100}{\sqrt{1 + 1 \cdot 1}} = \frac{100}{\sqrt{2}} = 70 \cdot 7.$$

at  $\omega = \omega_2$ ,  $\omega_2 \gg \omega_1, \omega_2 \ll \omega_3$ .

$$\text{then, loop gain} = \frac{A_{of} \cdot}{\sqrt{1 + \sqrt{\left(\frac{\omega_2}{\omega_1}\right)^2 + 1}}}$$

$$= \frac{A_{of} \cdot}{\frac{\omega_2 \times \sqrt{2}}{\omega_1}} = \frac{A_{of} \omega_1}{\omega_2 \cdot \sqrt{2}} = \frac{100 \times 2K}{200K \cdot \sqrt{2}} = \frac{1}{\sqrt{2}} = 0.707$$

clearly, loop gain will be unity at  $\omega_c$ , where  $\omega_1 < \omega_c < \omega_2$

$\therefore \omega_c \ll \omega_3$

$\therefore$  at  $\omega = \omega_c$ ,

$$\text{loop gain} = \frac{A_{of} \cdot}{\sqrt{1 + \left(\frac{\omega_c}{\omega_1}\right)^2} \cdot \sqrt{1 + \left(\frac{\omega_c}{\omega_2}\right)^2}} = 1$$

$$\Rightarrow 100 = \sqrt{\left\{ 1 + \left( \frac{\omega_c}{\omega_1} \right)^2 \right\} \left\{ 1 + \left( \frac{\omega_c}{\omega_2} \right)^2 \right\}}$$

$$\Rightarrow 1 + \frac{\omega_c^4}{\omega_1^2 \omega_2^2} + \omega_c^2 \left( \frac{1}{\omega_1^2} + \frac{1}{\omega_2^2} \right) = 100^2$$

$$\Rightarrow \omega_c^2 \left\{ \frac{\omega_c^4}{\omega_1^2 \omega_2^2} + \omega_c^2 \left( \frac{\omega_1^2 + \omega_2^2}{\omega_1^2 \omega_2^2} \right) \right\} \approx 100^2$$

$$\Rightarrow \omega_c^4 + \omega_c^2 (\omega_1^2 + \omega_2^2) - 100^2 \cdot \omega_1^2 \omega_2^2 = 0$$

Consider the following  
 $T(f)$   
 $\alpha = \beta \cdot (1000)$

$$\frac{1}{(1 + j \frac{f}{1K})(1 + j \frac{f}{50K})} < (1 + j \frac{f}{1M})$$

find the value of  $\beta$   
 that yields a PM of  $45^\circ$

$$\beta = 0.0707$$

$$T(f) = \frac{5 \times 10^5}{(1 + j \frac{f}{1M})(1 + j \frac{f}{100M})} \cdot (1 + j \frac{f}{100M})$$

Insert a dominant pole  
 such that PM =  $45^\circ$

$$f_{PD} = 2.83 \text{ Hz}$$

$$\omega_c^2 = \frac{-(\omega_1^2 + \omega_2^2) + \sqrt{(\omega_1^2 + \omega_2^2)^2 + 4 \cdot 100 \cdot \omega_1^2 \omega_2^2}}{2}$$

$$\approx \frac{-\omega_2^2 + \sqrt{\omega_2^4 + \frac{400}{4 \times 100} \omega_1^2 \omega_2^2}}{2}$$


$$\approx \frac{-\omega_2^2 + \omega_2 \sqrt{\omega_2^2 + \frac{400}{4 \times 100} \omega_1^2}}{2}$$

$\Rightarrow f_c^2 = \frac{\omega_2^2 + \omega_2}{2} \approx \frac{-f_2^2 + f_2 \cdot \sqrt{f_2^2 + 400 f_1^2}}{2}$

$f_{FO-3-dB} = 396.07 \times 10^6$

$\Rightarrow f_c \approx 20 \text{ kHz} \approx 157.25 \text{ kHz}$

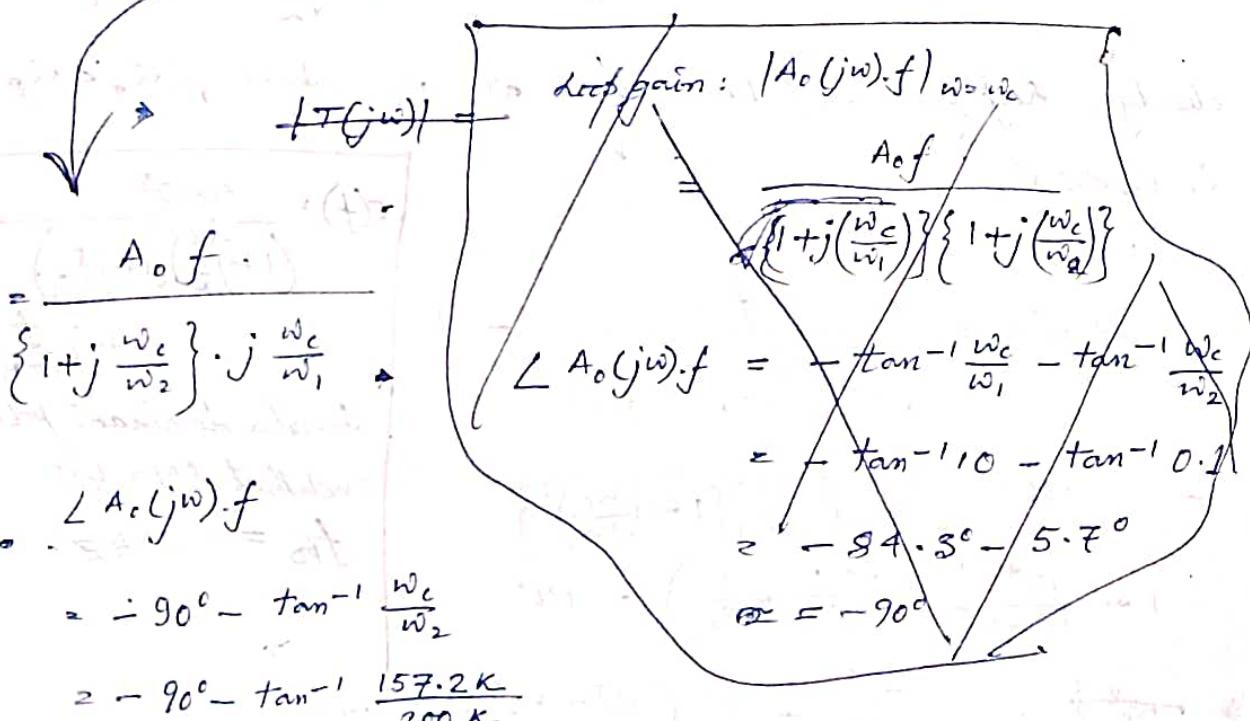at  $f = 20 \text{ kHz}$ ,  $\omega_c \gg \omega_1$ ,  $\omega_c < \omega_2$ ,  $\omega_c \ll \omega_3$



$$\angle A_o(jw).f$$

$$= -90^\circ - \tan^{-1} \frac{\omega_c}{\omega_2}$$

$$= -90^\circ - \tan^{-1} \frac{157.2 \text{ K}}{200 \text{ K}}$$

$$= -90^\circ - 38.16^\circ$$

$$= -128.16^\circ$$

$$PM = 180^\circ - 128.16^\circ$$

$$= 51.84^\circ$$

if  $A_{OL} = 100$ ,

$$f = 0.01,$$

$$\therefore \text{loop gain} = \frac{100 \times 0.01 \times 400 \times \omega_1}{\omega_2 \times \sqrt{2}}$$

$$100 = \frac{40K}{1 + f40K}$$

$\omega_c$  in this case,

$$\omega_c \gg \omega_1, \quad \omega_c > \omega_2, \quad \omega_c < \omega_3$$

at  $\omega = \omega_3$ .

$$\text{loop gain} / \omega = \omega_3$$

$$\frac{40K}{1 + 0.01 \times 40K}$$

$$\text{loop gain} =$$

$$\omega_c^2 = -\frac{\omega_3^2 + \omega_3 \cdot \sqrt{\omega_3^2 + 1600 \cdot \omega_2^2}}{2}$$

$$= \frac{400}{\frac{\omega_3}{\omega_1} \times \frac{\omega_3}{\omega_2} \times \sqrt{2}}$$

$$= \frac{400}{\sqrt{2} \times \frac{(4M)^2}{2K \times 200K}}$$

$$= \frac{400}{\sqrt{2} \times 40K}$$

$$100 = \frac{40K}{1 + f40K}$$

$$\approx -\frac{(4M)^2 + 4M \cdot \sqrt{(4M)^2 + 1600 \cdot (200K)^2}}{2}$$

$$\Rightarrow f_c = 3.14 \text{ MHz} \Rightarrow f_c =$$

$$\Rightarrow \omega_c \gg \omega_2, \quad \omega_c \gg \omega_1.$$

$$\text{loop gain}$$

$$\therefore \text{loop gain at } \omega = \omega_c$$

$$A_{of} = \frac{A_{of}}{\left( \frac{\omega_c}{\omega_1} \right) \times \sqrt{1 + \left( \frac{\omega_c}{\omega_2} \right)^2} \times \sqrt{1 + \left( \frac{\omega_c}{\omega_3} \right)^2}}$$

$$= 1$$

$$\frac{A_{of}}{\left( 1 + j \frac{\omega_c}{\omega} \right)} = 1$$

$$\Rightarrow \omega_c^4 + \omega_c^2 \omega_3^2 = \omega_2^2 \omega_3^2 \times 100^2 \times \left( \frac{\omega_1}{\omega_c} \right)^2$$

$$= \omega_2^2 \omega_3^2 \times$$

$$\text{act, } \omega_c \ll \omega_3, \text{ then, loop gain} = \frac{A_{of}}{\frac{\omega_c}{\omega_1} \sqrt{1 + \left( \frac{\omega_c}{\omega_2} \right)^2}}$$

$$\Rightarrow \left( \frac{\omega_c}{\omega_1} \right)^2 \cdot \left( 1 + \frac{\omega_c^2}{\omega_2^2} \right) = A_{of}$$

$$\Rightarrow \frac{\omega_c^4}{\omega_1^2 \omega_2^2} + \frac{\omega_c^2}{\omega_1^2} = A_{of}$$


$$\Rightarrow \omega_c^4 + \omega_c^2 \omega_2^2 = A_{of} \cdot \omega_1^2 \omega_2^2$$

$$\begin{aligned} \angle A' &= -120^\circ \\ \frac{\omega}{P_2} - \tan^{-1} \frac{\omega}{P_3} &= -120^\circ \end{aligned}$$

$$A_{of} = 400,$$

so that,  $PM = 60^\circ$  & new  $P_2, P_3 \approx P_3$
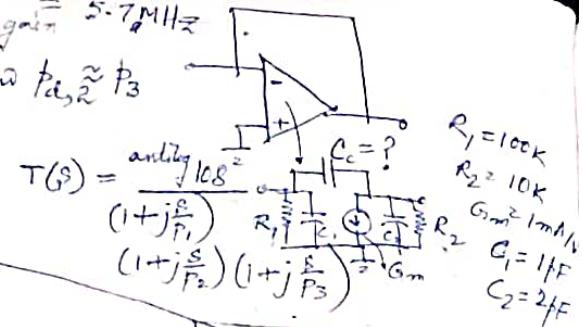
$$A' = \frac{108 \text{ dB}}{(1 + j \frac{\omega}{P_1})(1 + j \frac{\omega}{P_3})}$$



$$f_c^2 = \frac{-f_2^2 + f_2 \sqrt{f_2^2 + 4 \cdot 400^2 \cdot f_1^2}}{2}$$

$$\Rightarrow f_c = 375 \text{ kHz}$$

$$\therefore \text{Loop gain } \left| f_2 f_c \right| = \left| \frac{A_{of}}{\left( j \frac{\omega_c}{\omega_1} \right) \left( 1 + j \frac{\omega_c}{\omega_2} \right)} \right|$$

$$\begin{aligned} \angle \text{Loop gain} &= -90^\circ - \tan^{-1} \frac{375K}{200K} \\ &= -90^\circ - 62^\circ \\ &\approx -152^\circ \end{aligned}$$

$$\Rightarrow PM \approx -28^\circ$$

$\Rightarrow$  variation of  $f$  changes the PM.  
 → gives the idea of phase-ed/freq. dependent feedback ckt.

### 2 stage CMOS opamp:

differential amplifier with active load

→ common source amp with active load

$$A \times p_L = p_1$$

$$\Rightarrow p_L = \frac{p_1}{A_1} \cdot 600$$

BW:

$$(1+A) \times p_L$$

$$\approx A \cdot p_L \approx 300k$$



$$T(j\omega) = \frac{K}{(1 + j \frac{\omega}{P_1})}$$

$$\omega = \omega_c, |T(j\omega_c)| = 1$$

Q. tot find  $p'_1 = ?$




if  $P_2 = 2 \text{ MHz}$  consider  $P_3 = 25 \text{ MHz}$  unity gain feedback  
 i.e.,  $P_2, P_3$  do not move

$$|T(j\omega)| = \sqrt{1 + \frac{\omega^2}{P_1^2}}$$

$$1 = \frac{K}{\sqrt{1 + \frac{\omega_c^2}{P_1^2}}}$$

$$\omega_c \gg p_1 \Rightarrow 1 = \frac{K}{\frac{\omega_c}{P_1}}$$
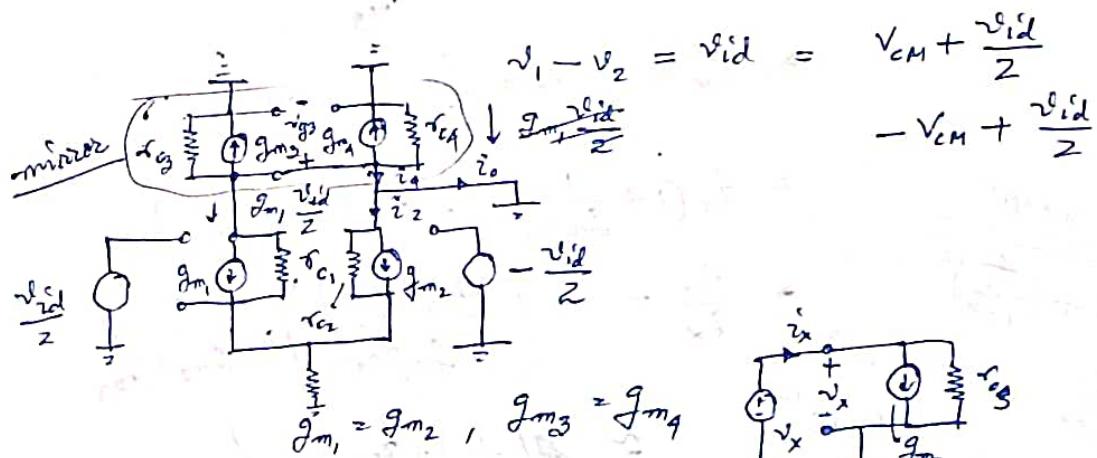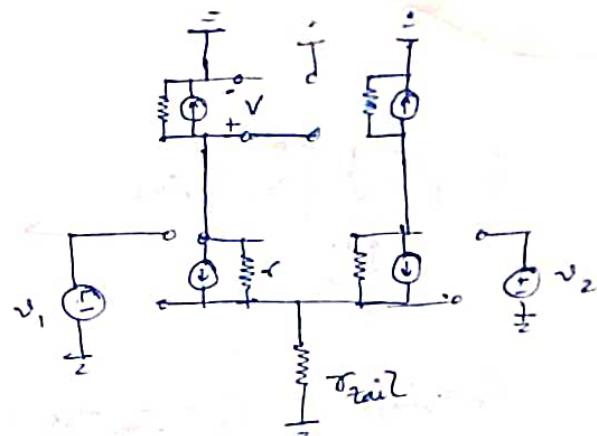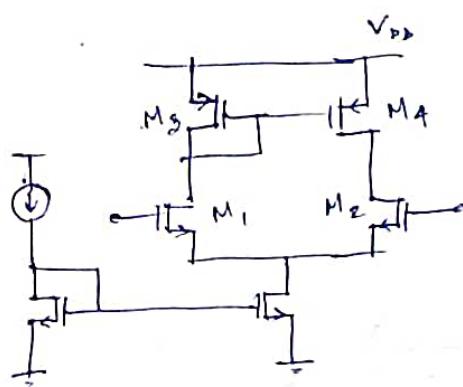
$$\Rightarrow \text{ADD } \frac{\omega_c}{P_1} = K \Rightarrow \omega_c = P_1 K$$



$$\text{as, } \frac{1}{g_m3} \ll r_{o3},$$

$$\therefore g_{m3} = -g_m, \frac{v_{id}}{Z} \cdot \frac{1}{g_{m3}}$$


$$\therefore i_1 = -g_{m4} v_{g2} = +g_{m4} \cdot \frac{g_{m1}}{g_{m3}} \cdot \frac{v_{id}}{Z}$$


$$\therefore i_2 = g_{m2} \left( -\frac{v_{id}}{Z} \right) = -g_{m2} \cdot \frac{v_{id}}{Z}$$

$$\begin{aligned} i_o &= i_1 - i_2 = g_{m4} \cdot \frac{g_{m1}}{g_{m3}} \cdot \frac{v_{id}}{Z} + g_{m2} \cdot \frac{v_{id}}{Z} \\ &= g_m \cdot \frac{v_{id}}{Z} + g_m \cdot \frac{v_{id}}{Z} = g_m \cdot v_{id} \end{aligned}$$

$$\Rightarrow G_m = g_m,$$

$$\& R_{out} = ?$$

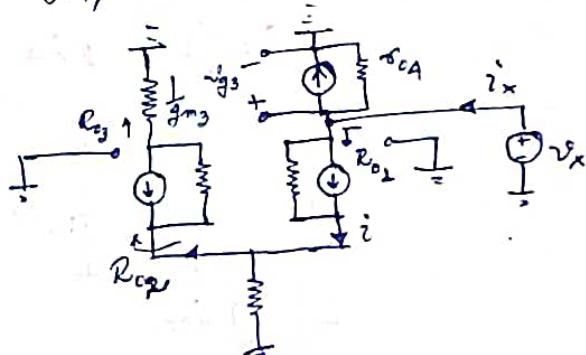

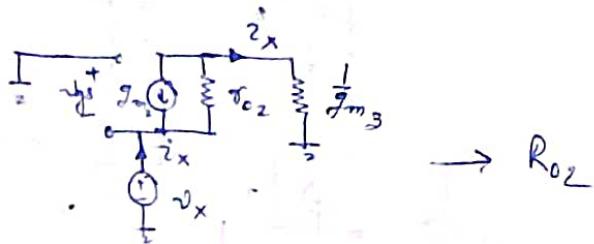

$$\dot{i}_x = \frac{v_x}{g_{m2}} \quad \dot{i}_x + g_{m2} v_{gs} + \left( \frac{\dot{i}_x \frac{1}{g_{m3}} - v_x}{\tau_{c3}} \right) = 0$$

$$\Rightarrow \dot{i}_x - g_{m2} v_x + \frac{\dot{i}_x}{g_{m3} \tau_{c3}} - \frac{\dot{i}_x}{\tau_{c3}} = 0.$$

$$\Rightarrow \dot{i}_x \left( 1 + \frac{1}{g_{m3} \tau_{c3}} \right) = v_x \left( g_{m2} + \frac{1}{\tau_{c3}} \right)$$


$$\Rightarrow \frac{\dot{i}_x}{\dot{i}_x} = \left( \frac{g_{m3} \tau_{c3} + 1}{g_{m3} \tau_{c3}} \right) \times \frac{1}{g_{m2} + \frac{1}{\tau_{c3}}}$$

$$\sqrt{1 + \left( \frac{f_c}{10^8} \right)^2} = 5 \times 10^5$$

$$\Rightarrow 1 + \frac{f_c^2}{10^{16}} = 25 \times 10^{10}$$

$$\Rightarrow f_c^2 \approx \frac{25 \times 10^{10} \times 10^{16}}{f_a} = \left( \frac{1}{g_{m2}} \right) \tau_{c3} \approx \frac{1}{g_{m2}}$$

∴ equivalent ckt:

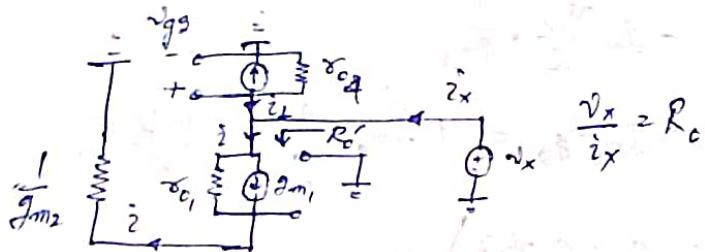


$$v_{gs} = \dot{i}_x \frac{1}{g_{m3}} \quad \text{&} \quad \dot{i}_1 = -g_{m4} \times \dot{i}_x \left( \frac{1}{g_{m3}} \right) - \frac{v_x}{\tau_{c4}}$$

$$= -\dot{i}_x - \frac{\dot{i}_x}{\tau_{c4}}$$

$$\therefore \dot{i}_x = \dot{i} - \dot{i}_1$$

$$= \dot{i} + \dot{i} + \frac{v_x}{\tau_{c4}} = 2\dot{i} + \frac{v_x}{\tau_{c4}}$$

$$R'_o = \frac{v_x}{\dot{i}}$$

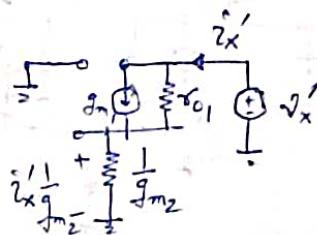

$$\Rightarrow i'_x = g_{m_1} \left( -i'_x \frac{1}{g_{m_2}} \right) + \frac{v_x - i'_x \frac{1}{g_{m_2}}}{r_{o_1}}$$

$$\Rightarrow i'_x \left( 1 + \frac{g_{m_1}}{g_{m_2}} + \frac{1}{g_{m_2} r_{o_1}} \right) = \frac{v_x}{r_{o_1}}$$


$$\Rightarrow i'_x \left( 2 + \frac{1}{g_{m_2} r_{o_1}} \right) = \frac{v_x'}{r_{o_1}} \Rightarrow \frac{v_x'}{i'_x} = \frac{r_{o_1}}{2} \approx 2r_{o_1}$$

$$\Rightarrow i_x = 2 \cdot \frac{v_x}{R_o'} + \frac{v_x}{r_{o_1} r_{o_2}} \\ = 2 \cdot \frac{v_x}{2r_{o_1}} + \frac{v_x}{r_{o_1} r_{o_2}} \Rightarrow \frac{v_x}{i_x} = r_{o_1} \parallel r_{o_2}$$


$$\text{gain} = G_m \cdot R_o$$

$$= g_{m_1} (r_{o_1} \parallel r_{o_2}) \\ = g_{m_2} (r_{o_2} \parallel r_{o_3}) \quad \left. \begin{array}{l} \text{differential gain} \\ \text{common mode gain} \end{array} \right\}$$

Common-mode gain:

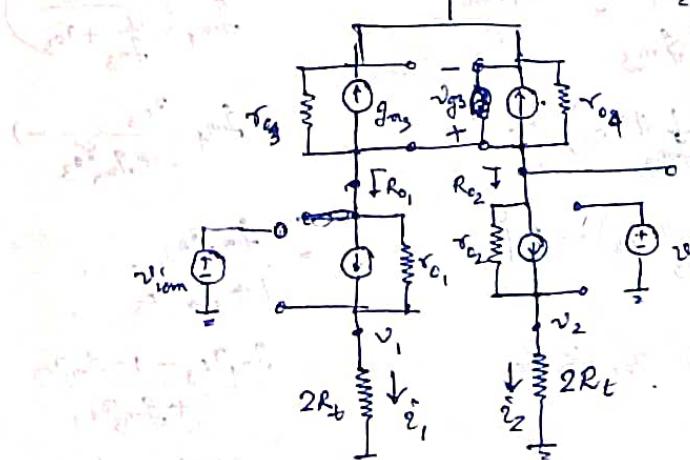
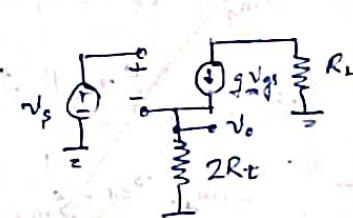
$$v_1 = v_2 \approx v_{icm} \Rightarrow i_1 = i_2 = \frac{v_{icm}}{2R_L}$$



$$v_s - v_{gs} - g_m v_{gs} \cdot 2R_L = 0 \\ v_s - v_{gs} - v_o = 0 \\ \Rightarrow v_{gs} = v_s - v_o \\ g_m v_{gs} = g_m (v_s - v_o) \\ \frac{v_o}{v_s} = \frac{g_m 2R_L}{1 + g_m^2 R_L} \\ \frac{v_x'}{i'_x} = r_{o_1} \left\{ 1 + g_m 2R_L + \frac{2R_L}{r_{o_1}} \right\} \\ = \frac{r_{o_1}}{r_{o_1}} \left\{ r_{o_1} + g_m 2R_L r_{o_1} + 2R_L \right\} \\ \approx g_m r_{o_1} \cdot 2R_L \\ = R_{o2}$$


$$v_{g3} = -i_1 \times \left( \frac{1}{g_{m3}} \right) \quad \text{or} \quad v_{g3} = -i_1 \left( \frac{1}{g_{m3}} \| r_{o3} \right)$$

$$= -i_1 \cdot \frac{r_{o3}}{1 + g_{m3} r_{o3}}$$

$$\frac{\frac{1}{g_{m3}} r_{o3}}{1 + \frac{1}{g_{m3}} r_{o3}} \\ = \frac{r_{o3}}{1 + g_{m3} r_{o3}}$$

8.

$$v_{g3}$$

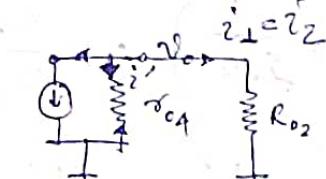

$$v_o = -g_{m1} v_{g3} \cdot r_{o1}$$

$$= -g_{m1}^2 v_{g3}^2$$

$v_o$

$$v_{g3} = -i \cdot \frac{1}{g_{m3}} - g_m v_{g3}^2 i' - i =$$

$$v_o = + \frac{g_{m1}}{g_{m3}} \cdot \frac{r_{o1}}{r_{o1} + r_{o2}} i' r_{o1}$$

$$v_o = g_{m1} v_{g3} i \quad \therefore v_o = i' r_{o1}$$

$$i' = i' + g_{m1} v_{g3} + i = 0$$

$$\downarrow \text{follow this} \Rightarrow i' = -g_{m1} \left( -i \frac{1}{g_{m3}} \right) - i$$

$$= \frac{v_{icm}}{2R_t} \cdot r_{o1}$$

$$v_o = + \frac{g_{m1}}{g_{m3}} \cdot i - i$$

$$r_{o1} \ll R_{o2}$$

$$v_o = -(g_{m1} v_{g3} + i) r_{o1}$$

$$\approx 0$$

$$= -\left( g_{m1} \frac{i + r_{o2}}{1 + g_{m3} r_{o3}} + i \right) r_{o1} = -g_{m1} (r_{o1} \| R_{o2}) \cdot v_{g3}$$

$$v_o = 0 \cdot v_{icm}$$

$$\frac{1}{g_{m3}} \ll r_{o3}$$

$$= \left\{ \frac{g_{m1} r_{o3}}{1 + g_{m3} r_{o3}} \cdot i - i \right\} r_{o1}$$

$$= -g_{m1} (r_{o1} \| g_{m1} r_{o1} 2R_t) v_{g3}$$

$$1 \ll g_{m3} r_{o3}$$

$$\approx g_{m3} \cdot g_{m4}$$

$$= g_{m1} r_{o1} \cdot \frac{1}{g_{m3}} \times \frac{v_{icm}}{2R_t}$$

$$= \left\{ \frac{g_{m1} r_{o3} - 1 - g_{m3} r_{o3}}{1 + g_{m3} r_{o3}} \right\} i$$

$$= -g_{m1} \left\{ -i \left( \frac{1}{g_{m3}} \| r_{o3} \right) \right\} - i$$

$$g_{m1} \left( \frac{r_{o3}}{\frac{1}{g_{m3}} + r_{o3}} \right)$$

$$= -\frac{r_{o4}}{1 + g_{m3} r_{o3}} \cdot \frac{v_{icm}}{2R_t}$$

$$= i \left\{ g_{m1} \cdot \left( \frac{1}{g_{m3}} \| r_{o3} \right) - 1 \right\}$$

$$= \frac{g_{m1} r_{o3}}{1 + g_{m3} r_{o3}} - 1$$

$$= -\frac{v_{icm}}{2R_t \cdot g_{m3}}$$

$$v_o = i' \times r_{o1}, \quad \text{as } r_{o1} \ll R_{o2}$$

$$= \frac{g_{m1} r_{o3} - 1 - g_{m3} r_{o3}}{1 + g_{m3} r_{o3}}$$

$$= -g_{m1} \times v_{g3} - i' - i_1 = 0$$




$$\Rightarrow -g_{m1} \left( -i_1 \frac{r_{o3}}{1 + g_{m3} r_{o3}} \right) - \frac{v_o}{r_{o1}} - i_1 = 0$$

$$\Rightarrow \frac{v_o}{r_{o1}} = i_1 \left\{ \frac{g_{m1} r_{o3}}{1 + g_{m3} r_{o3}} - 1 \right\} = i_1 \left\{ \frac{1}{1 + g_{m3} r_{o3}} \right\}$$

$$v_o = r_{o1} \cdot \frac{v_{icm}}{2R_t} \cdot \frac{1}{1 + g_{m3} r_{o3}}$$

$$= \frac{g_{m1} v_{icm}}{2R_t \cdot g_{m3}} = \frac{v_{icm}}{2g_{m3} R_t}$$

frequency analysis:

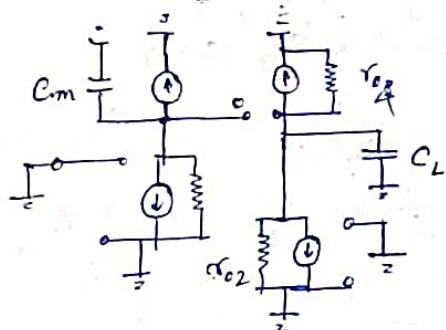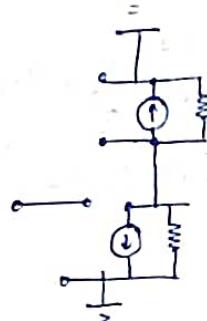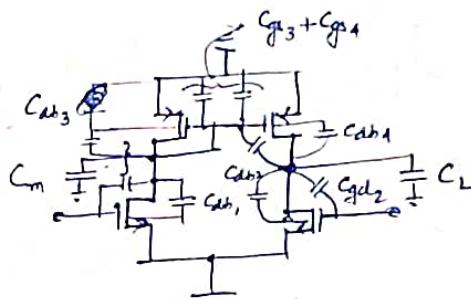

$$C_m = C_{gd_1} + C_{ds_1} + C_{gs_3} + C_{gs_4} + C_{ds_3}$$

$$C_L = C_{gd_4} + C_{ds_2} + C_{ds_3} + C_{ds_4}$$

for  $C_{gd_1}$ , gate variation is much less than drain.  
 $C_{gd_4}$

hence, gate terminals are approximated as ground terminals

$$R_{cm} = \frac{1}{g_{m_3}} \parallel \tau_{o_1}$$

$$R_L = \tau_{o_2} \parallel \tau_{o_3}$$

$$\therefore 2\pi f_{p_1} = \frac{1}{(\frac{1}{g_{m_3}} \parallel \tau_{o_1}) \cdot C_m + (\tau_{o_2} \parallel \tau_{o_3}) C_L}$$

$$\Rightarrow \text{as } \tau_{o_2} \parallel \tau_{o_3} \gg (\frac{1}{g_{m_3}} \parallel \tau_{o_1})$$


$$\Rightarrow f_{p_1} = \frac{1}{2\pi(\tau_{o_2} \parallel \tau_{o_3}) C_L}$$

non-dominant pole:

$$\tau = \sum \frac{1}{R_i C_i} = \frac{1}{R_{L_2} \cdot C_L} + \frac{1}{R_{cm} \cdot C_m}$$

$$\approx \frac{1}{R_{cm} \cdot C_m} = \frac{1}{(\frac{1}{g_{m_3}} \parallel \tau_{o_1}) \cdot C_m} \approx \frac{g_{m_3}}{C_m}$$

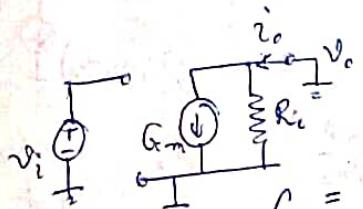
$$f_{p_2} = \frac{\frac{g_{m_3}}{2\pi C_m}}{R_{L_2}}$$



$$G_m = \left. \frac{i_o}{v_i} \right|_{v_o=0}$$

↓ short circuit trans. conductance

## Determination of zero.

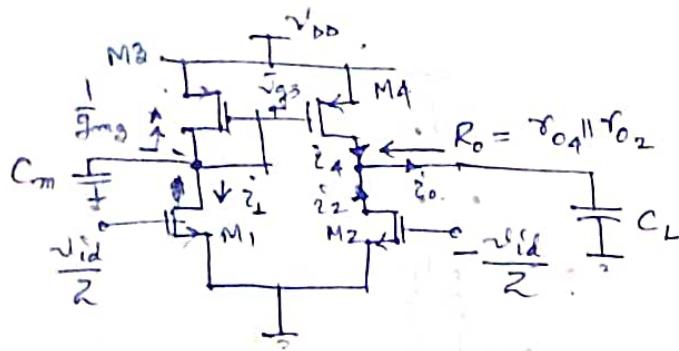

$$G_m V_{id} + \frac{V_{id}}{R_1} + s C_1 V_{i2} + s C_c (V_c - V_{i2}) = 0$$

$$G_m V_{i2} + \frac{V_c}{R_2} + s C_2 V_o + s C_c (V_o - V_{i2}) = 0$$

$V_2 = -AV_1$

$$\dot{i} = g_m \frac{v_{id}}{2}, \quad v_{g3} = -g_m \frac{v_{id}}{2} \times \left( \frac{1}{g_{m3}} \parallel \frac{1}{C_m s} \right)$$

$$= -g_m \frac{v_{id}}{2} \times \frac{\frac{1}{g_{m3} C_m s}}{\frac{1}{g_{m3}} + \frac{1}{C_m s}}$$

$$= -g_m \frac{v_{id}}{2} \times \frac{1}{g_{m3} + C_m s}$$

$$C_c \left( 1 + \frac{1}{g_m R_o} \right)$$

$$\dot{i}_4 = -g_m v_{g3} = + g_m g_{m1} \frac{v_{id}}{2} \times \frac{1}{g_{m3} + C_m s}$$


$$\dot{i}_2 = g_m \frac{v_{id}}{2}, \quad \therefore \dot{i}_o = \dot{i}_4 + \dot{i}_2$$

$$= \frac{g_m g_{m1} v_{id}}{2(g_{m3} + C_m s)} + \frac{g_m v_{id}}{2}$$

$$\Rightarrow \frac{V_2}{I_c} = \frac{Z_o}{(1 + \frac{1}{A})}$$

$$= \frac{g_m v_{id}}{2} \cdot \left\{ \frac{g_{m1}}{g_{m3} + C_m s} + 1 \right\}$$
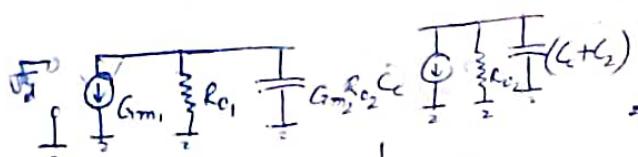
$$= \frac{g_m v_{id}}{2} \cdot \left\{ \frac{2g_{m1} + C_m s}{g_{m3} + C_m s} \right\}$$





$$\frac{1}{L} = \frac{1}{g_{m1} R_o C_c} + \frac{1}{R_o (C_c + C_2)}$$

~~$$= \frac{1}{g_{m1} R_o C_c}$$~~

$$\Rightarrow v_o = \dot{i}_o \times (R_o \parallel \frac{1}{C_m s})$$

$$\frac{1}{G_m}$$
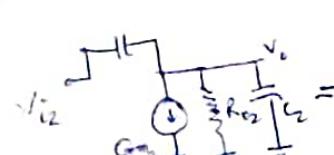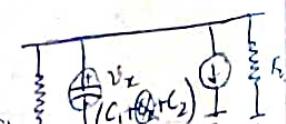
$$\dot{i}_o \cdot \frac{\frac{R_o}{C_m s}}{R_o + \frac{1}{C_m s}} = \dot{i}_o \frac{R_o}{1 + R_o C_m s}$$




$$(V_{id} - V_o) C_m s = G_m V_{id} + \frac{V_c}{R_o \parallel \frac{1}{C_m s}}$$

$$(r_s - G_m) = V_o (C_m s + \frac{1}{R_o \parallel \frac{1}{C_m s}}) \Rightarrow \frac{G_m}{r_s - G_m}$$

$$\Rightarrow R_{req} = R_o \parallel \frac{1}{C_m s}$$

$$\Rightarrow \tau \approx \frac{1}{G_m (C_c + C_2)}$$


for 2 stage CMOS opamp.

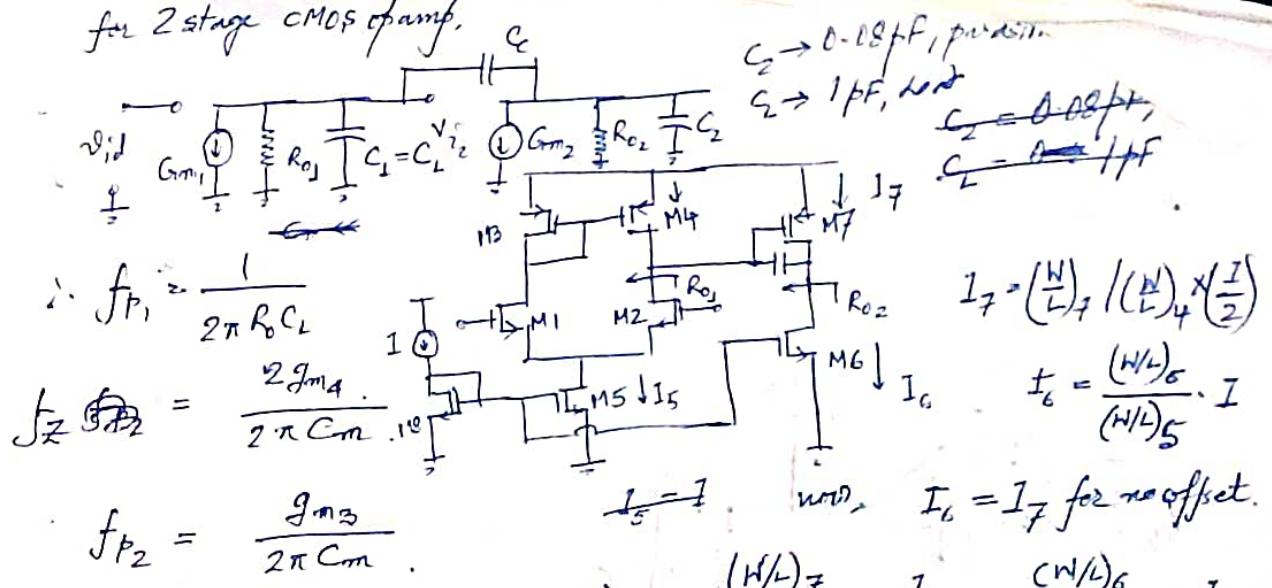

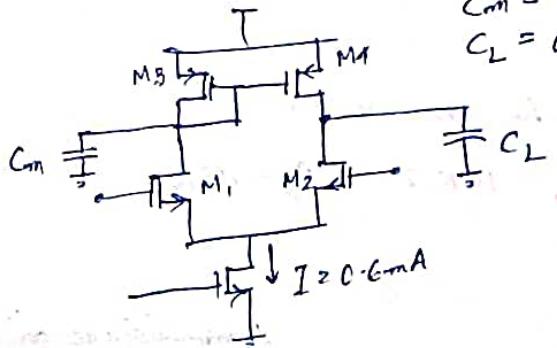b) A current mirror is added if  $M_5 \equiv M_6$ ,  $(W/L)_7 = 2 \times (W/L)_4$

$C_m = 0.1 \text{ pF} \rightarrow \text{Cap at the input of the mirror}$

$C_L = 0.2 \text{ pF} \rightarrow \text{Cap at the output}$



$$V_{OV1,2} = 0.3V \quad V_{A_n} = |V_{AP}| = 9V$$

$$V_{OV3,4} = 0.5V \quad r_{c1,2,3,4} = \frac{V_A}{(I/2)}$$

$$= \frac{9}{(0.3m)} = 30 \text{ k}\Omega$$

$$V_{ov} = V_{GS} - V_{TH}$$

$$\frac{I}{2} = \frac{1}{2} K_n' \left(\frac{W}{L}\right) \cdot (V_{GS} - V_{TH})^2$$

$$\text{find the poles \& zeros, } \text{find the differential gain} \quad = 0.3m = \frac{1}{2} K_n' \left(\frac{W}{L}\right) 0.3^2 \Rightarrow K_n' \left(\frac{W}{L}\right) < \frac{0.6m}{(0.3)^2} = 6.67 \text{ mA/V}^2$$

$$\rightarrow g_{m1} = \sqrt{2K_n \left(\frac{W}{L}\right) \left(\frac{I}{2}\right)}$$

$$= \sqrt{2 \times 6.67 \text{ mA/V}^2 \times 0.3 \text{ m}} = \frac{4 \text{ mA/V}}{2 \text{ mA/V}} \cdot g_{m2}$$


$$K_p' \left(\frac{W}{L}\right) = \frac{0.6m}{(0.5)^2} = 2.4 \text{ mA/V}^2$$

$$r_o = r_{o2}$$

$$g_{m3,4} = \sqrt{2.5p' \left(\frac{W}{L}\right) \left(\frac{I}{2}\right)}$$

$$K_n' = 90 \mu \text{A/V}^2$$

$$K_p' = 30 \mu \text{A/V}^2$$

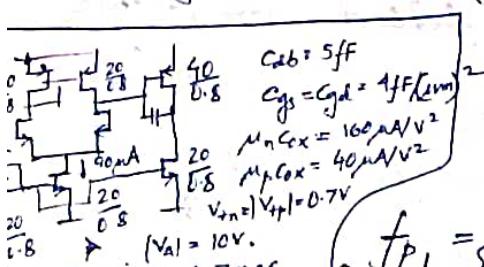

$$f_1 = \frac{1}{2\pi (R_C g_{m1} R_2)}$$

$$f_2 = \frac{g_{m2} C_C}{2\pi (C_1 C_2 + C_C (C_1 + C_2))}$$

$$Z = \frac{g_{m2}}{2\pi C_C}$$

$$f_{P1} = \frac{1}{\{C_2 \times (r_{o2}/(r_{o1}))\} \times 2\pi}$$

$$= \frac{1}{2\pi \times 0.2 \text{ pF} \times 15 \text{ k}}$$

$$= 53 \text{ MHz}$$

$$f_{P2} = \frac{g_{m2}}{2\pi C_m} = 74$$

$$= \frac{1.2 \text{ m}}{2\pi \times 0.1 \text{ pF}} \quad \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_4$$

$$= 80$$



$$= 1.9 \text{ GHz}$$

$$f_Z = 3.8 \text{ GHz}$$

$$\text{Gain} = g_{m1} \cdot (r_{o2}/r_{o1})$$

$$= 60 \text{ V/V}$$


ii) series shunt ckt.

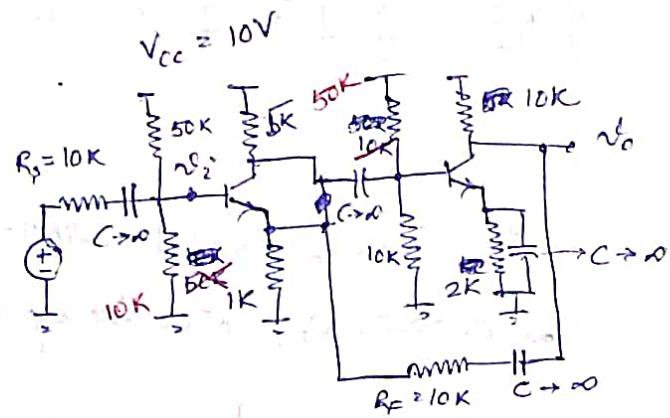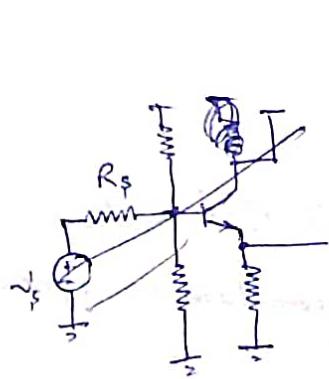

$$\beta = 120, \text{ assume } V_{A1,2} = 0, I_{B1}, I_{B2} = 0, V_{BE1}, V_{BE2} = 0.7V$$

find  $g_{m1}, g_{m2}, r_{\pi1}, r_{\pi2}$  (2x4)

find the feedback factor  $f$ . (2)

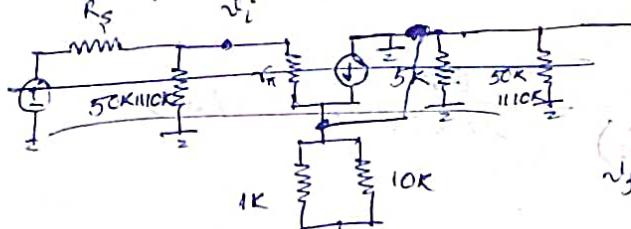


$$I_C \approx \frac{5-0.7}{1k}$$

$$= 4.3mA$$

$$\Rightarrow g_{m1} = \frac{I_C}{V_T} = 1653m$$

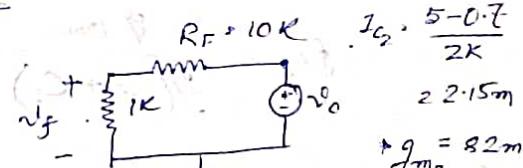find the small signal voltage closed loop voltage gain  $\frac{v_o}{v_i}$ ,  $\frac{v_o}{v_f}$




$$\Rightarrow g_{m2} = 82m$$

$$\therefore r_{\pi1} = \frac{\rho}{g_{m1}}$$

$$= 726\Omega$$
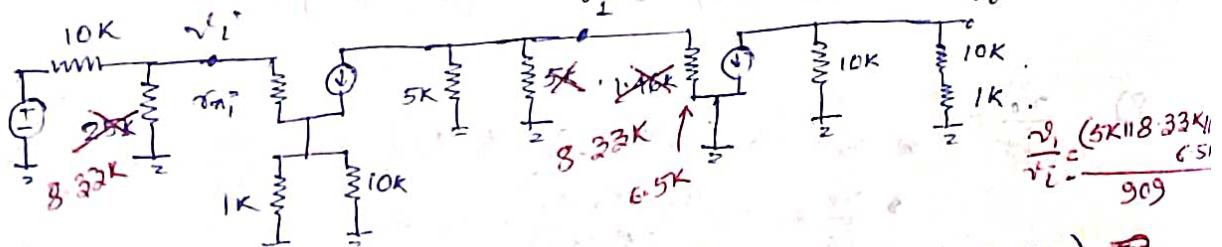
$$r_{\pi2} = \frac{\rho}{g_{m2}} = 1.46k\Omega$$



$$\begin{aligned} r_{\pi1} &= 3.26k \\ r_{\pi2} &= 6.5k \end{aligned}$$

$$\frac{v_o}{v_i} = -\frac{(5k \parallel 5k \parallel 1.46k)}{(1k \parallel 10k)}$$

$$\frac{v_o}{v_i} = -g_{m2} \times (10k \parallel 1.1k) = -\frac{3.12k \times 5.23k}{909} = -2.108$$

$$\begin{aligned} &= -92m \times 5.23k \\ &= -428. \\ &= -2.32 \end{aligned}$$

$$\begin{aligned} \frac{v_o}{v_i} &= -g_{m2} \times (10k \parallel 1.1k) = -\frac{92.2}{909} = -1.01 \\ &= -18.44m \times 5.23k \\ &= -96.44 \end{aligned}$$

$$\left(\frac{v_o}{v_i}\right)_{OL} = +433 V/V$$


$$\left(\frac{v_o}{v_i}\right)_{OL} = +223.7 V/V$$

$$\left(\frac{v_o}{v_i}\right)_{CL} = \frac{433}{1 + 433 \times 0.09} = 10.2 V/V$$

$$\begin{aligned} &= \frac{223.7}{1 + 223.7 \times 0.09} \\ &= 10.48 V/V \end{aligned}$$

$$(1 + AB) = (1 + 223.7 \times 0.09) = 21.133$$

## Wien Bridge Oscillator

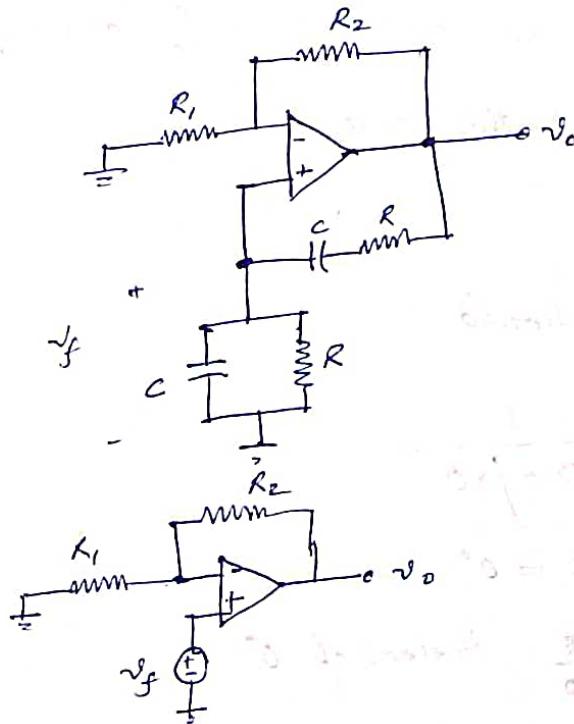

$$\frac{R}{\frac{C_S}{R} + \frac{1}{C_F}} = \frac{R}{1 + RCF}$$

$$v_f = \frac{\frac{1}{C_S} \parallel R}{R \parallel \frac{1}{C_S} + R + \frac{1}{C_F}} \times v_o$$

$$= \frac{\frac{R}{1 + RCF}}{\frac{R}{1 + RCF} + R + \frac{1}{C_F}} \times v_o$$

$$= \frac{RCF}{RCF + R(1 + RCF)C_F + (1 + RCF)} v_o$$

$$= \frac{RCF}{RCF + R_C + R^2 C_F^2 + 1 + RCF} v_o$$

$$\Rightarrow \frac{v_o - v_f}{R_1} = \frac{v_f - v_o}{R_2}$$

$$\Rightarrow -\frac{v_f}{R_1} - \frac{v_f}{R_2} = -\frac{v_o}{R_2}$$

$$\Rightarrow v_f \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_o}{R_2}$$

$$\Rightarrow v_f \cdot \frac{R_1 + R_2}{R_1} = v_o$$

$$\Rightarrow v_o = v_f \cdot \left( 1 + \frac{R_2}{R_1} \right)$$


$$\therefore \text{Zero gain} = \frac{\left( 1 + \frac{R_2}{R_1} \right)}{3 + \left( RCF + \frac{1}{RC_S} \right)}$$

$$\text{at } s = j\omega_0 = \frac{\left( 1 + \frac{R_2}{R_1} \right)}{3 + \left( RCF + \frac{1}{RC_S} \right)}$$

$$\frac{v_i}{v_s} \approx \frac{R_1}{R_1 + R_S}$$

$\approx R_{if} \gg R_1$

$$\Rightarrow 0.45$$

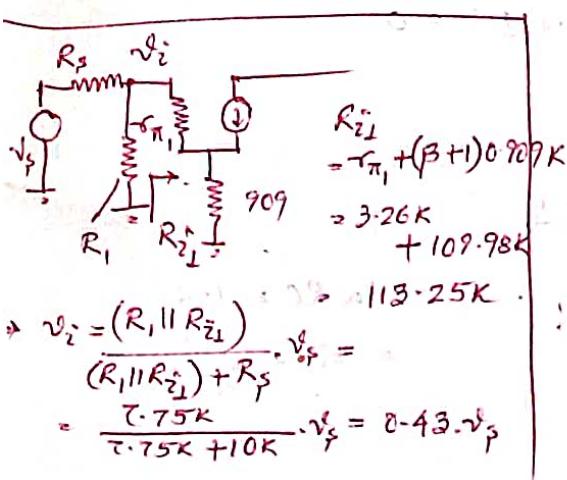

$$\Rightarrow v_i = \frac{(R_1 \parallel R_{2i})}{(R_1 \parallel R_{2i}) + R_S} \cdot v_o = \frac{113.25K}{113.25K + 10K} \cdot v_o = 0.43 \cdot v_o$$

$$= \frac{1.75K}{1.75K + 10K} \cdot v_o = 0.43 \cdot v_o$$

$$= \frac{\left( 1 + \frac{R_2}{R_1} \right)}{3 + j \left( \omega_0 RC - \frac{1}{\omega_0 RC} \right)}$$

$$\therefore R_{2f} = R_{2i} (1 + A\beta) = 113.25K \times 21.13 = 2.4M$$

$$\therefore \frac{v_o}{v_s} = \frac{v_o}{v_i} \cdot \frac{v_i}{v_s}$$

$$\therefore \left( \frac{v_o}{v_s} \right)_{CL} \approx \left( \frac{v_o}{v_i} \right)_{CL} \times \frac{v_i}{v_s} = 10.48 \times 0.45 = 4.76$$

for the Wien Bridge oscillator,

the phase shift by op-amp and resistors :  $-\frac{\pi}{10}$  at  $\omega = \frac{1}{RC}$ .

find the freq. of oscillation in this case.

In this case, RC circuit should

$$\text{at } \omega = \frac{1}{RC}, \quad \frac{v_f}{v_o} = \frac{1}{3 + j \times 0}$$

$$\text{hence, } \angle \frac{v_f}{v_o} = 0^\circ$$

Loop phase :  $-\frac{\pi}{10}$  instead of  $0^\circ$ .

$\therefore \angle \frac{v_f}{v_o} = +\frac{\pi}{10}$ , for oscillation.

$$\text{or i.e., } \angle \frac{1}{3 + j(RC\omega - \frac{1}{RC\omega})} = \frac{\pi}{10}$$

$$\Rightarrow -\tan^{-1} \left( \frac{RC\omega - \frac{1}{RC\omega}}{3} \right) = \frac{\pi}{10}$$

$$\Rightarrow -\frac{RC\omega - \frac{1}{RC\omega}}{3} = \tan \frac{\pi}{10}$$

$$= 0.9249 \quad 0.1$$

$$\Rightarrow -RC\omega f \frac{1}{RC\omega} = +0.97 \quad 0.3$$

$$\Rightarrow -RC\omega^2 + 1 = -0.97RC\omega$$

$$+RC\omega^2 - 0.97RC\omega + 1 = 0$$

$$\Rightarrow \omega = -0.97$$

$$\omega_{RC} = \frac{0.97 + \sqrt{0.97^2 + 4.1}}{2}$$

$$= \frac{0.97 + 2.22}{2} = 1.6$$

$$\Rightarrow \omega_{RC} = \frac{1.6}{RC}$$

$$4.57 \times 10^{-3} = \frac{1.6}{2014 \times 285.7}$$

Loop gain :

$$\text{Loop phase : } \phi = -\tan^{-1} \left( \frac{\omega RC - \frac{1}{\omega RC}}{\frac{1}{3}} \right)$$

$$\frac{d \tan^{-1} x}{dx}$$

$$\Rightarrow \cot \theta$$

$$\frac{d}{dx} \tan^{-1} x$$

$\therefore$  change of loop phase w.r.t. freq. :


$$\frac{d \phi}{d \omega}$$

$$= \frac{1}{1 + x^2} \cdot \frac{dx}{dx}$$

$$\frac{d\phi}{d\omega} = -\frac{1}{\omega} \tan^{-1} \left( \frac{\omega RC - \frac{1}{\omega RC}}{\frac{1}{3}} \right)$$

$$= -\frac{1}{1 + \left( \frac{\omega RC - \frac{1}{\omega RC}}{\frac{1}{3}} \right)^2} \times \frac{1}{3} \cdot \frac{d}{d\omega} \left( \omega RC - \frac{1}{\omega RC} \right)$$
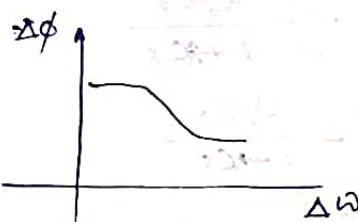
$$= -\frac{1}{1 + \left( \frac{\omega RC - \frac{1}{\omega RC}}{\frac{1}{3}} \right)^2} \times \frac{1}{3} \cdot \left( RC + \frac{1}{\omega^2 RC} \right)$$



$$\therefore \left. \frac{d\phi}{d\omega} \right|_{\omega = \frac{1}{RC}} = -\frac{1}{1 + \left( \frac{1}{RC} \right)^2} \times \frac{1}{3} \times \left( RC + \frac{1}{RC} \right) = -\frac{2}{3} RC$$


$\therefore$  at  $\omega = \frac{1}{RC}$ , change of phase :  $-\frac{\pi}{10}$ .

$$\frac{\Delta\phi}{\Delta\omega} = -\frac{2}{3} RC \Rightarrow -\frac{\pi}{10} \times \frac{1}{\frac{2}{3} RC} = \Delta\omega$$


$$1^\circ \rightarrow 180^\circ$$

$$1^\circ \rightarrow \frac{180}{\pi}$$
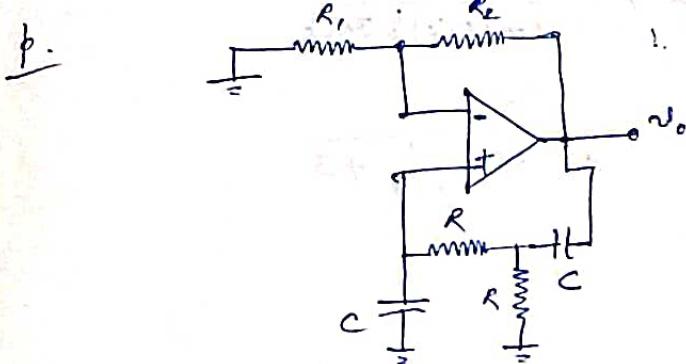
$$0.1 \rightarrow \frac{180}{\pi} \times 0.1$$



$$f_{osc} =$$

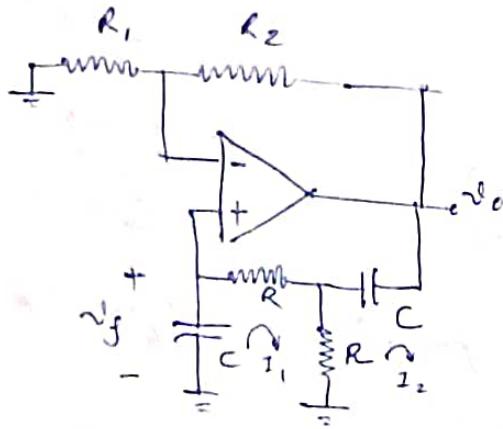

$$I_1 \frac{1}{C_S} + I_1 R + (I_1 - I_2) R = 0$$

$$(I_2 - I_1) R + I_2 \frac{1}{C_S} + v_o = 0$$

$$\Rightarrow I_2 \left( R + \frac{1}{C_S} \right) = -v_o + I_1 R$$

$$I_2 \left( \frac{RC_S + 1}{C_S} \right) = -I_1 R - v_o$$

$$\Rightarrow I_2 = \frac{(I_1 R - v_o) C_S}{1 + RC_S}$$

$$\Rightarrow I_1 \left( \frac{1}{C_S} + 2R \right) = \cancel{I_1 R} = \frac{(I_1 R - v_o) C_S}{1 + RC_S} \times R$$

$$I_1 \left( \frac{2RC_S + 1}{C_S} \right) = \frac{I_1 R^2 C_S}{1 + RC_S} - \frac{v_o R C_S}{1 + RC_S}$$

$$I_1 \left\{ \frac{1 + 3RC_S + 2(RC_S)^2 - RC_S^2}{C_S (1 + RC_S)} \right\} = - \frac{v_o R C_S}{1 + RC_S}$$


$$I_1 \left\{ \frac{1 + 3RC_S + (RC_S)^2}{C_S} \right\} = -v_o R C_S$$

$$\Rightarrow I_1 = - \frac{v_o R C_S \cdot C_S}{1 + (RC_S)^2 + 3RC_S}$$

$$\Rightarrow v_f = - I_1 \times \frac{1}{C_S} = + \frac{v_o R C_S}{1 + (RC_S)^2 + 3RC_S}$$

$$\frac{v_o}{RC_S + \frac{1}{RC_S} + 3}$$

Ans

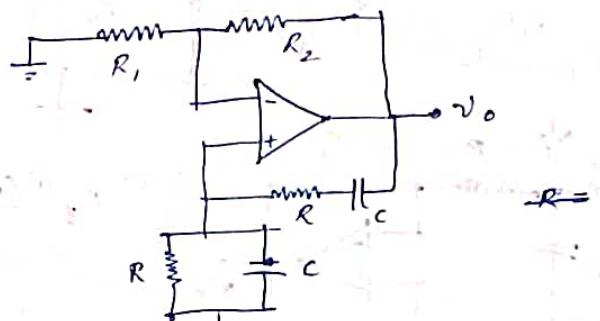


If the op-amp B  
 $R_1, R_2$  produces a  
phase lag of  $-\frac{\pi}{10}$   
at  $\omega = \frac{1}{RC}$

$$\text{loop gain} = \frac{(1 + \frac{R_2}{R_1})}{3 + j(\omega RC - \frac{1}{\omega RC})}$$

$$\angle \text{loop gain} = -\tan^{-1}\left(\frac{\omega RC - \frac{1}{\omega RC}}{3}\right)$$

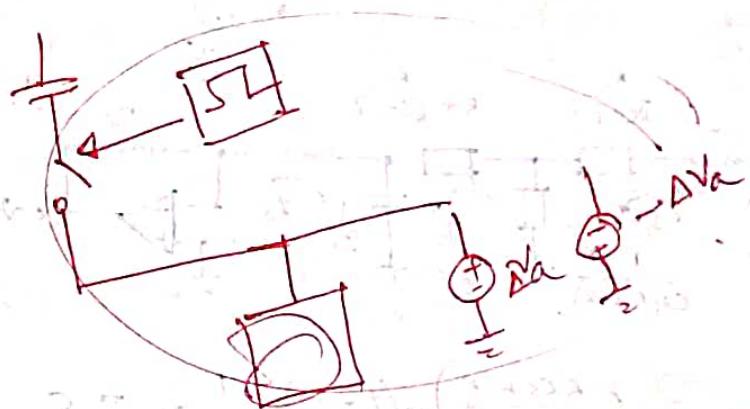- find the new value of  $R_2$ , for which oscillation at  $\omega = \frac{1}{RC}$  is recovered.
- what is the new value of  $\frac{R_2}{R_1}$  at the recovered oscillation frequency?



$$0 = 1/(1 + (R_2/R_1)) + (1/(1 + (R_2/R_1))) \cdot (-1/(1 + (R_2/R_1)))$$

$$0 = 1/(1 + (R_2/R_1)) + (1/(1 + (R_2/R_1))) \cdot (-1/(1 + (R_2/R_1)))$$

phase shift oscillator :  $V_f = \frac{R_1}{R_1+R_2+R_3+R_4} \times \frac{V_o R_3}{R_3+R_4}$

$$= \frac{R_1 R_3}{R_1 R_3 + R_2 R_4 + R_3 R_4} \times V_o$$

$V_f = \frac{V_o \times R_3}{R_3+R_4} \times \frac{R_3 R_4}{R_3+R_4}$

$R_3 || (R_1+R_2)$

$\frac{R_3(R_1+R_2)}{R_1+R_2+R_3}$

$V_i = \frac{R_3(R_1+R_2)}{R_1+R_2+R_3} \times V_o$

$R = \frac{R_3(R_1+R_2)V_o}{R_3(R_1+R_2) + R_4(R_1+R_2+R_3)}$

$V_f = \frac{R_1}{R_1+R_2} \times V_i$

$= \frac{R_1 \times R_3(R_1+R_2) V_o}{R_1+R_2 + R_3(R_1+R_2) + R_4(R_1+R_2+R_3)}$

$R = \frac{R_3(R_1+R_2)V_o}{R_1 R_3 + R_2 R_3 + R_1 R_4 + R_2 R_4 + R_3 R_4}$

$\frac{R^2 C_F + 3R}{R C_F + 2}$

$\frac{R}{R C_F + 2}$

$R + \frac{R}{R C_F + 2}$

$R$

$R_f$

$\frac{R^2 C_F + 3R}{R C_F + 2}$

$\frac{0 - V_o}{R_f} = I_3$

$\Rightarrow V_o = -I_3 R_f$

$\omega_x - I_1 \left( \frac{R^2 C_F + 3R}{R C_F + 2} \right) - \left( I_1 - I_2 \right) \frac{1}{C_F (R C_F + 2)} = 0$

$- (I_2 - I_1) \frac{1}{C_F (R C_F + 2)} - I_2 \left( \frac{R^2 C_F + 3R}{R C_F + 2} \right) - (I_2 - I_3) \frac{1}{C_F} = 0$

$- (I_3 - I_2) \frac{1}{C_F} - I_3 (R + R_f) = 0$

$V_o = -I_3 R_f$

$$v_2 - I_1 \left( \frac{R^2 C_F + 3R}{RC_F + 2} + \frac{1}{C_F(RC_F + 2)} \right) = -I_2 \frac{1}{C_F(RC_F + 2)}$$

$$\Rightarrow v_x = I_1 \left( \frac{R^2 C_F^2 + 3RC_F + 1}{(RC_F + 2)C_F} \right) - I_2 \frac{1}{C_F(RC_F + 2)} + I_3 \cdot 0$$

$$I_1 \cdot \frac{1}{C_F(RC_F + 2)} - I_2 \left( \frac{1}{C_F(RC_F + 2)} + \frac{R^2 C_F + 3R}{RC_F + 2} \right) + I_3 \cdot \frac{1}{C_F} = 0$$

$$\Rightarrow I_1 \cdot \frac{1}{C_F(RC_F + 2)} - I_2 \left( \frac{1 + R^2 C_F^2 + 3RC_F + RC_F + 2}{C_F(RC_F + 2)} \right) + I_3 \cdot \frac{1}{C_F} = 0$$

$$\Rightarrow I_1 \cdot \frac{1}{C_F(RC_F + 2)} - I_2 \cdot \left( \frac{R^2 C_F^2 + 4RC_F + 3}{C_F(RC_F + 2)} \right) + I_3 \cdot \frac{1}{C_F} = 0$$

$$-I_3 \cdot \left( \frac{1}{C_F} + R + R_F \right) + I_2 \cdot \frac{1}{C_F} = 0$$

$$\begin{bmatrix} \frac{R^2 C_F^2 + 3RC_F + 1}{(RC_F + 2)C_F} & -\frac{1}{C_F(RC_F + 2)} & 0 \\ \frac{1}{C_F(RC_F + 2)} & -\frac{R^2 C_F^2 + 4RC_F + 3}{C_F(RC_F + 2)} & \frac{1}{C_F} \\ 0 & \frac{1}{C_F} & -\frac{(R + R_F)C_F + 1}{C_F} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} v_x \\ 0 \\ 0 \end{bmatrix}$$

$$\rightarrow I_2 = \Delta = \frac{R^2 C_F^2 + 3RC_F + 1}{(RC_F + 2)C_F} \times \frac{R^2 C_F^2 + 4RC_F + 3}{C_F(RC_F + 2)}$$

$$= \begin{bmatrix} a & -b & 0 \\ b & -a & c \\ 0 & c & -d \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} v_x \\ 0 \\ 0 \end{bmatrix}$$

$$\therefore \Delta = \begin{vmatrix} a & b & v_x \\ b & -a-c & 0 \\ 0 & 0 & 1 \end{vmatrix}$$

$$= a \cdot \{(a+c)d - c^2\} - b \cdot (-bd)$$

$$= a \{(a+c).d - c^2\} + b^2.d$$


$$I_3 = \frac{\begin{bmatrix} a & -b & v_x \\ b & -(a+c) & 0 \\ 0 & c & 0 \end{bmatrix}}{\Delta}$$

$$= \frac{v_x \cdot bc}{a \{(a+c)d - c^2\} + b^2.d}$$

$$= \frac{v_x \cdot \frac{1}{C_F(RC_F+2)} \cdot \frac{1}{C_F}}{\frac{R^2C_F^2 + 3RC_F + 1}{C_F(RC_F+2)} \times \left\{ \frac{R^2C_F^2 + 4RC_F + 3}{C_F(RC_F+2)} \times \frac{(R+R_f)(C_F+1)}{C_F} - \frac{1}{(C_F)^2} \right\} + \frac{1}{(C_F)^2(RC_F+2)^2} \times \frac{(R+R_f)C_F + 1}{C_F}}$$

$$v_x \cdot \frac{1}{(C_F)^2(RC_F+2)}$$
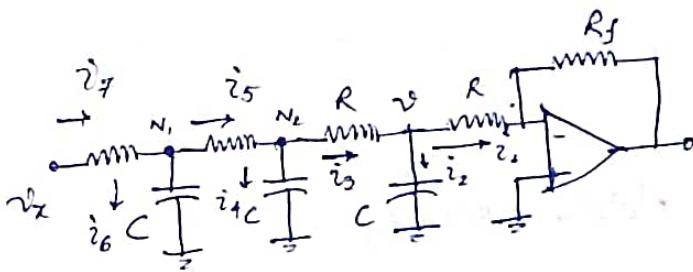
$$= \frac{R^2C_F^2 + 3RC_F + 1}{C_F(RC_F+2)} \times \left\{ \frac{-1}{(C_F)^2(RC_F+2)} \right\}$$



$$\dot{i}_1 = \frac{v}{R}, \quad \dot{i}_2 = v s C$$

$$\dot{i}_3 = \frac{v}{R} + v_f C$$

$$= v \left( \frac{1}{R} + s C \right) = \frac{v(RC_f + 1)}{R}$$

$$\begin{aligned} \therefore \cancel{\dot{v}_{N_2}} &= v_{N_2} - \dot{i}_3 R = v \\ \Rightarrow v_{N_2} &= v + \dot{i}_3 R = v + \frac{(RC_f + 1)v}{R} \times R \\ &= v + v(RC_f + 1) \\ &= v(RC_f + 2) \end{aligned}$$

$$\Rightarrow \dot{i}_4 = v(RC_f + 2) \times s C \quad \text{& } \dot{i}_5 = \dot{i}_4 + \dot{i}_3$$

$$= v \left( \frac{RC_f + 1}{R} + v(RC_f + 2) \cdot s C \right)$$

$$= v \left\{ \frac{RC_f + 1}{R} + R(C_f)^2 + 2C_f \right\}$$

$$= v \cdot \left\{ \frac{RC_f + 1 + R^2 C_f^2 + 2RC_f}{R} \right\}$$

$$= v \cdot \left\{ \frac{R^2 C_f^2 + 3RC_f + 1}{R} \right\}$$

$$+ v(RC_f + 2)$$

$$= v \cdot \left\{ R^2 C_f^2 + 4RC_f + 3 \right\}$$

$$\therefore \dot{i}_6 = v_{N_1} C_f \quad \therefore \dot{i}_7 = \dot{i}_6 + \dot{i}_5.$$

$$= v \left\{ R^2 C_f^2 + 4RC_f + 3 \right\} C_f + v \left\{ \frac{R^2 C_f^2 + 3RC_f + 1}{R} \right\}$$

$$= v \left\{ R^2 C_f^3 + 4RC_f^2 + 3C_f + \frac{R^2 C_f^2 + 3RC_f + 1}{R} \right\}$$

$$= v \left\{ \frac{R^3 C_f^3 + 4R^2 C_f^2 + 3RC_f + R^2 C_f^2 + 3RC_f + 1}{R} \right\}$$

$$= v \left( \frac{R^5 C_f^3 + 5R^2 C_f^2 + 6RC_f + 1}{R} \right)$$

$$\text{& } v_x - \dot{i}_7 \cdot R = v_{N_1}$$

$$\begin{aligned}
 \Rightarrow v_x &= i_f R + v_n \\
 &\approx i_f R + v \left\{ R^2 C_f^2 s^2 + 4 R C_f + 3 \right\} \\
 &= v \left( R^3 C_f^3 s^3 + 5 R^2 C_f^2 s^2 + 6 R C_f + 1 + R^2 C_f^2 s^2 + 4 R C_f + 3 \right) \\
 &= v \left( R^3 C_f^3 s^3 + 6 R^2 C_f^2 s^2 + 10 R C_f + 4 \right)
 \end{aligned}$$

$\therefore \frac{v_o - v}{R} = \frac{v_o - v_0}{R_f}$

$$\Rightarrow \frac{v}{R} = -\frac{v_0}{R_f} \Rightarrow v = \cancel{-v_0} - v_0 \times \frac{R}{R_f}$$

$$\Rightarrow v_x = -v_0 \cdot \frac{R}{R_f} \propto \left( R^3 C_f^3 s^3 + 6 R^2 C_f^2 s^2 + 10 R C_f + 4 \right)$$

$$\frac{v_o}{v_x} = \frac{\left( -\frac{R_f}{R} \right)}{R^3 C_f^3 s^3 + 6 R^2 C_f^2 s^2 + 10 R C_f + 4}$$

$$\begin{aligned}
 \text{at } s = j\omega &= \frac{\left( -\frac{R_f}{R} \right)}{-j R^3 C_f^3 \omega^3 - 6 R^2 C_f^2 \omega^2 + j 10 R C_f \omega + 4} \\
 &= \frac{\left( -\frac{R_f}{R} \right)}{(4 - 6 R^2 C_f^2 \omega^2) + j (10 R C_f \omega - R^3 C_f^3 \omega^3)}
 \end{aligned}$$

$$\text{if } 10 R C_f \omega = R^3 C_f^3 \omega^3,$$

$$\Rightarrow \omega^2 = \frac{1}{10 R^2 C_f^2} \Rightarrow \omega = \frac{1}{\sqrt{10}} \cdot \frac{1}{RC}$$


$$\begin{aligned}
 &- \tan^{-1} \frac{10 R C_f \omega - R^3 C_f^3 \omega^3}{4 - 6 R^2 C_f^2 \omega^2} \\
 &= \pi
 \end{aligned}$$

at  $\omega = \frac{1}{\sqrt{10} \cdot RC}$ , attenuation by a phase shift ckt :

$$|A_f| = 1$$

$$\begin{aligned}
 \therefore \frac{R_f}{R} &= \frac{17}{5} \\
 \Rightarrow 5 R_f &\geq 17 R
 \end{aligned}$$

## RC phase shift oscillator:

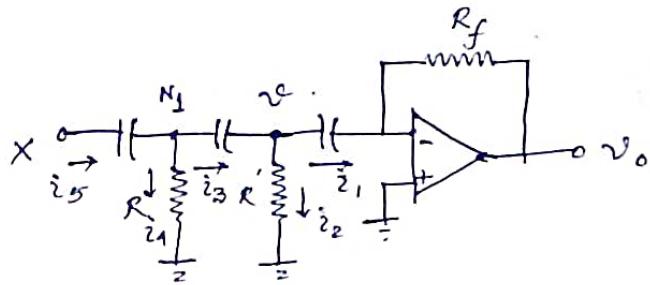

$$\dot{i}_1 = v \cdot sC \quad \dot{i}_2 = \frac{v}{R} \quad \Rightarrow \dot{i}_3 = \dot{i}_1 + \dot{i}_2 = v \left( sC + \frac{1}{R} \right) \\ = v \left( \frac{RC_f + 1}{R} \right)$$

~~( $v_{N_1} - v$ )~~  $v_{N_1} - \dot{i}_3 \times \frac{1}{C_f} = v$

$$\Rightarrow v_{N_1} = \dot{i}_3 \cdot \frac{1}{C_f} + v$$

$$= v \left( \frac{RC_f + 1}{RC_f} \right) + v$$

$$= v \left( \frac{2RC_f + 1}{RC_f} \right)$$

$$\therefore \dot{i}_4 = \frac{v_{N_1}}{R} = \frac{v \left( 2RC_f + 1 \right)}{R^2 C_f}$$

$$\Rightarrow \dot{i}_5 = \dot{i}_4 + \dot{i}_3 = \frac{v \left( 2RC_f + 1 \right)}{R^2 C_f} + v \left( \frac{RC_f + 1}{R} \right)$$

$$= \frac{v \left( RC_f + 1 \right)}{R} \left( \frac{1}{RC_f} + 1 \right)$$

$$= \frac{v \left( RC_f + 1 \right)^2}{R^2 C_f} = \frac{v \left( RC_f + 1 \right)^2}{R^2 C_f} = \frac{v \cdot \left( RC_f + 1 \right)^2}{R^2 C_f}$$

$$\Rightarrow v_x - \dot{i}_5 \frac{1}{C_f} = v_{N_1}$$

$$\Rightarrow v_x = \frac{v \left( RC_f + 1 \right)^2}{R^2 C_f} \cdot \frac{1}{C_f} + v \cdot \frac{\left( 2RC_f + 1 \right)}{RC_f}$$

$$= v \cdot \left\{ \frac{\left( RC_f + 1 \right)^2}{R^2 C_f^2} + \frac{2RC_f + 1}{RC_f} \right\} = \frac{R^2 C_f^2 + 2RC_f + 1 + 2RC_f^2 + 2RC_f}{R^2 C_f^2} \times v$$

$$= v \times \frac{3R^2 C_f^2 + 3RC_f + 1}{R^2 C_f^2}$$

$$v_{sc} = \frac{0 - v_o}{R_f}$$

$$v = - \frac{v_o}{R_f C_s}$$

$$v_x = \frac{v_o}{C_s} + v_N,$$

$$= v \cdot \frac{R^2 C_s^2 + 3RC_s + 1}{R^2 C_s^2} + v \cdot \frac{2RC_s + 1}{RC_s}$$

$$= v \cdot \left\{ \frac{R^2 C_s^2 + 3RC_s + 1 + 2R^2 C_s^2 + RC_s}{R^2 C_s^2} \right\}$$

$$= v \cdot \left\{ \frac{3R^2 C_s^2 + 4RC_s + 1}{R^2 C_s^2} \right\}$$

$$= - \frac{\frac{v_o}{R_f C_s}}{\frac{3R^2 C_s^2 + 4RC_s + 1}{R^2 C_s^2}}$$

$$\Rightarrow \frac{v_o}{v_x} = \frac{- R^2 C_s^2 \cdot R_f C_s}{3R^2 C_s^2 + 4RC_s + 1}$$

$$= - \frac{R^2 C_s^2 \cdot R_f C_s}{R^2 C_s^2 + 4RC_s + 1}$$

at  $s = j\omega$

$$= - \frac{R C_s \cdot R_f C_s}{3RC_s + 4 + \frac{1}{\omega RC}}$$

$$= - \frac{R R_f C^2 \omega^2}{4 + j(3\omega RC - \frac{1}{\omega RC})}$$

$$\text{at } 3\omega RC = \frac{1}{\omega RC}$$


$$\omega = \frac{1}{\sqrt{3} \cdot RC}$$

$$2\pi f = \frac{1}{\sqrt{3} \cdot RC}$$

$$\text{at } \omega = \frac{1}{\sqrt{3} RC}$$

$$|AP| = 1, = \frac{RR_f \cdot \frac{1}{3R^2 C^2}}{1} = \frac{R_f}{12R} = 1 \Rightarrow \frac{R_f}{R} = 12$$

Actual phase-shift ckt:

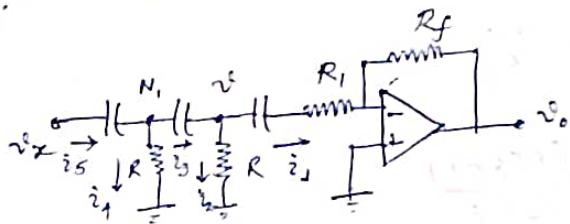

$$i_1 = \frac{v}{R + \frac{1}{C_F}} = \frac{v C_F}{R C_F + 1} \quad i_2 = \frac{v}{R}$$

$$i_3 = v \left( \frac{1}{R} + \frac{C_F}{R C_F + 1} \right) = v \left( \frac{R + 1 + R C_F}{R (R C_F + 1)} \right)$$

$$= v \left\{ \frac{2 R C_F + 1}{R (R C_F + 1)} \right\}$$

$$v_{N_1} - \frac{i_3}{C_F} = v \Rightarrow v_{N_1} = v + \frac{v \{ 2 R C_F + 1 \}}{R C_F (R C_F + 1)}$$

$$= v \left\{ \frac{R^2 C_F^2 + R C_F + 2 R C_F + 1}{R C_F (R C_F + 1)} \right\}$$

$$= v \left\{ \frac{R^2 C_F^2 + 3 R C_F + 1}{R C_F (R C_F + 1)} \right\}$$

$$\therefore i_4 = \frac{v_{N_1}}{R} = v \left\{ \frac{R^2 C_F^2 + 3 R C_F + 1}{R^2 C_F (R C_F + 1)} \right\}$$

$$\rightarrow v_x - i_4 \Rightarrow i_5 = i_4 + i_3 = v \left\{ \frac{R^2 C_F^2 + 3 R C_F + 1}{R^2 C_F (R C_F + 1)} + \frac{2 R C_F + 1}{R (R C_F + 1)} \right\}$$

$$\Rightarrow v_x - \frac{i_5}{C_F} = v_{N_1}, \Rightarrow v \left\{ \frac{R^2 C_F^2 + 3 R C_F + 1 + 2 R^2 C_F^2 + R C_F}{R^2 C_F (R C_F + 1)} \right\}$$

$$\Rightarrow v_x = \left\{ \frac{3 R^2 C_F^2 + 4 R C_F + 1}{R^2 C_F^2 (R C_F + 1)} + \frac{R^2 C_F^2 + 3 R C_F + 1}{R^2 C_F (R C_F + 1)} \right\} \times v$$

$$= v \left\{ \frac{5 R^2 C_F^2 + 4 R C_F + 1}{R^2 C_F (R C_F + 1)} \right\}$$

$$= \left\{ \frac{5 R^2 C_F^2 + 4 R C_F + 1 + R^5 C_F^3 + 3 R^2 C_F^2 + R C_F}{R^2 C_F^2 (R C_F + 1)} \right\} v$$

$$= \left\{ \frac{R^3 C_F^3 + 6 R^2 C_F^2 + 5 R C_F + 1}{R^2 C_F^2 (R C_F + 1)} \right\} v$$

\* now,

$$\frac{v^e C_f}{RC_f + 1} = - \frac{v_o}{R_f}$$

$$v = - v_o \frac{(RC_f + 1)}{R_f C_f}$$

$$v_x = \frac{R^3 C_f^3 s^3 + 6R^2 C_f^2 s^2 + 5RC_f s + 1}{R^2 C_f^2 (RC_f + 1)} \times - v_o \frac{(RC_f + 1)}{R_f C_f}$$

$$\Rightarrow \frac{v_o}{v_x} = - \frac{R^2 C_f^2 \cdot R_f \cdot C_s}{R^3 C_f^3 s^3 + 6R^2 C_f^2 s^2 + 5RC_f s + 1}$$

$$= \frac{R C_s \cdot R_f C_f}{R^2 C_f^2 + 6R C_f + 5 + \frac{1}{R C_f}}$$

$$\text{at } s = j\omega, \Rightarrow \frac{v_o}{v_x} = \frac{+ \omega^2 R R_f C^2}{(5 - \omega^2 R^2 C^2) + j(\omega R C G - \frac{1}{\omega R C})}$$

$$\text{if } \omega = \frac{1}{\sqrt{G} \cdot R C}$$

$$\text{at } \omega = \frac{1}{\sqrt{G}} \cdot \frac{1}{R C}, \quad \text{phase shift attenuation}$$

$$\text{as } |A_\beta| = 1, \quad \left(5 - \frac{1}{6}\right) = \frac{29}{6}$$




we must have,

$$\frac{\frac{1}{6} R^2 C^2 \cdot R_f}{\left(5 - \frac{1}{6}\right)} = 1$$

$$\frac{\frac{1}{6} \cdot \frac{R_f}{R}}{\frac{29}{6}} = 1$$

$$\therefore R_f = 29R$$

### Colpitt's Oscillator

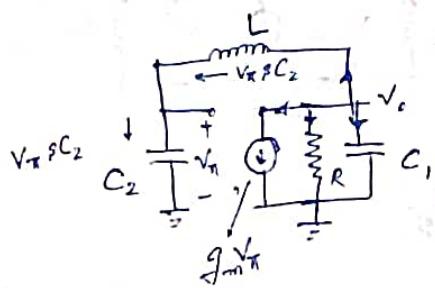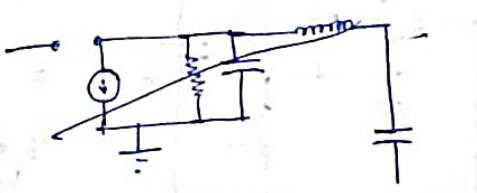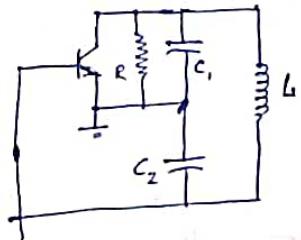

$$\frac{(V_o - V_n)}{Ls} = V_\pi s C_2$$

$$\Rightarrow V_o - V_n = V_\pi L C_2 s^2$$

$$\Rightarrow V_o = V_\pi (1 + L C_2 s^2)$$

also,  $g_m V_\pi + \frac{V_o}{R} + V_o s C_1 + V_\pi s C_2 = 0$ .

$$\Rightarrow g_m V_\pi + V_\pi s C_2 + V_\pi (1 + L C_2 s^2) \left( \frac{1}{R} + s C_1 \right) = 0$$

$\therefore V_\pi \neq 0$ ,

$$g_m + s C_2 + (1 + L C_2 s^2) \left( \frac{1}{R} + s C_1 \right) = 0$$

$$\Rightarrow g_m + s C_2 + \frac{1}{R} + s C_1 + \frac{L C_2}{R} s^2 + L C_1 C_2 s^3 = 0$$

$$\Rightarrow s^3 L C_1 C_2 R + L C_2 s^2 + s R (C_1 + C_2) + g_m R = 0$$

at  $s = j\omega$ ,

$$-j\omega^3 L C_1 C_2 R - L C_2 \omega^2 + j\omega R (C_1 + C_2) + g_m R = 0$$

$$\Rightarrow 1 + g_m R - L C_2 \omega^2 + j \{ \omega R (C_1 + C_2) - \omega^3 L C_1 C_2 R \} = 0$$



$$\Rightarrow 1 + g_m R = L C_2 \cdot \omega^2$$

$$= L C_2 \times \frac{(C_1 + C_2)}{9\zeta_L} \times \frac{1}{\zeta_L}$$

$$\therefore \omega_0^2 = \left( \frac{C_1 + C_2}{9\zeta_L} \right)_n$$

$$\therefore 1 + g_m R = 1 + \frac{C_2}{C_1} \Rightarrow g_m R = \frac{C_2}{C_1}$$

## Hartley Oscillator:

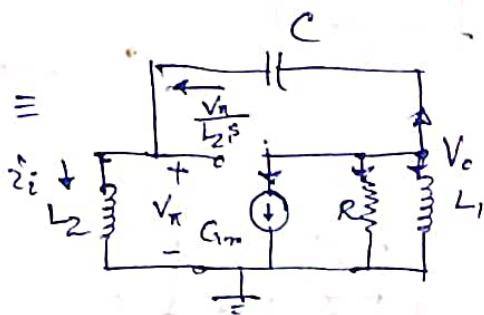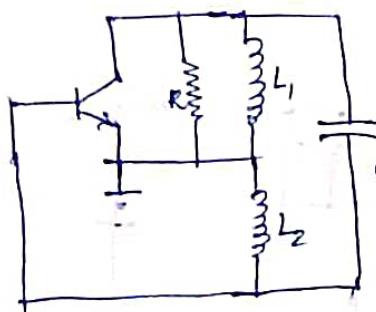

$$\dot{V}_i = \frac{V_\pi}{L_2 s}$$

$$(V_o - V_\pi) C_S = \frac{V_\pi}{L_2 s} \Rightarrow V_o C_S = V_\pi \left( C_S + \frac{1}{L_2 s} \right)$$

$$\Rightarrow V_o = \frac{V_\pi (L_2 C_S^2 + 1)}{L_2 C_S^2}$$

also,

$$G_m V_\pi + \frac{V_o}{R} + \frac{V_o}{L_1 s} + \frac{V_\pi}{L_2 s} = 0$$

$$\Rightarrow \left( G_m + \frac{1}{L_2 s} \right) V_\pi + V_o \left( \frac{1}{R} + \frac{1}{L_1 s} \right) = 0$$

$$\Rightarrow \left( G_m + \frac{1}{L_2 s} \right) V_\pi + \frac{V_\pi (L_2 C_S^2 + 1)}{L_2 C_S^2} \left( \frac{L_1 s + R}{4 R s} \right) = 0$$

$$\Rightarrow \text{as } V_\pi \neq 0,$$

$$\frac{G_m L_2 s + 1}{L_2 s} + \frac{(L_2 C_S^2 + 1)(L_1 s + R)}{L_2 L_1 R C_S^2 s^3} = 0$$

$$\Rightarrow \frac{(G_m L_2 s + 1)(L_1 R C_S^2 s^2 + L_2 L_1 C_S^3 + L_2 R C_S^2 + 4 s + R)}{L_2 L_1 R C_S^2 s^3} = 0$$

$$\Rightarrow G_m L_2 L_1 R C_S^2 s^2 + L_2 L_1 C_S^3 + L_2 R C_S^2 + L_2 R C_S^2 + 4 s + R = 0$$

$$-j(G_m R + 1) L_2 L_1 C \omega^3 - \omega^2 (L_1 R C + L_2 R C) + R + j \omega L_1 = 0$$

$$R = \omega^2 (L_1 R C + L_2 R C) + j \{ \omega L_1 - (G_m R + 1) L_2 L_1 C \omega^3 \} = 0$$

$$R = \omega^2 (L_1 R C + L_2 R C) \quad \text{&} \quad \omega L_1 = (G_m R + 1) L_2 L_1 C \omega^3.$$

at  $\omega = \omega_0$


$$\Rightarrow I = \omega^2 (L_1 C + L_2 C) \quad \text{&} \quad L_1 = (G_m R + 1) L_2 L_1 C \times \omega_0^2$$

$$\Rightarrow \omega_0 = \sqrt{\frac{1}{C(L_1 + L_2)}} \quad L_1 = \frac{(G_m R + 1) L_2 L_1 C}{C(L_1 + L_2)} \times \frac{1}{\omega_0^2}$$

$$\Rightarrow G_m R + 1 = \frac{L_1 + L_2}{L_2}$$

$$\Rightarrow G_m R = \frac{L_1}{L_2}$$

p. a BJT is biased at  $I_c > 1mA$

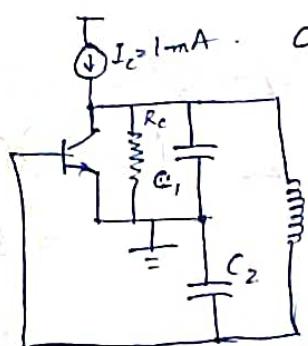

$$R_C = 2k\Omega, \quad \omega_0 = 10^6 \text{ rad/s},$$

$$\tau_o = 100 \mu\text{s}$$

coil : Q : 100. find  $C_2$  &  $L$ .

$$Q = \omega_0 R C$$


$$100 \cdot 10^6 \times R \cdot C_1, \quad C_1 = 0.01 \mu\text{F}$$

$$\therefore R_{eq} = R_C \parallel \tau_o \parallel R \Rightarrow R = \frac{100}{10^6 \times 0.01 \times 10^{-6}} = 10k\Omega$$

$$= 2k \parallel 100k \parallel 10k$$

$$\approx 2k \parallel 10k = 1.67k\Omega$$

G factor:  $2\pi f$

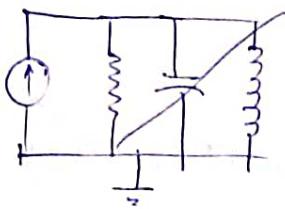

$$\omega_0^2 = \frac{C_1 + C_2}{C_1 C_2} \times \frac{1}{L}$$

$$g_m R = \frac{C_2}{C_1}$$

$$10^{12} = \frac{0.01 + 0.64}{0.01 \times 0.64} \times \frac{1}{L} \times 10^{-6} \frac{1}{10^{-6}}$$


$$\Rightarrow \frac{I_C}{V_T} \cdot (1.67 \text{ k}\Omega) = \frac{C_2}{0.01 \mu}$$

$$\Rightarrow \omega_0^2 = \frac{1}{L} = 101.56 \times 10^6 \times 10^{-12}$$


$$\approx 101.56 \text{ mH}$$

$$\Rightarrow C_2 = \frac{1 \text{ m}}{26 \text{ m}} \times 0.01 \mu \times 1.67 \text{ k}$$

$$= 0.64 \mu\text{F}$$

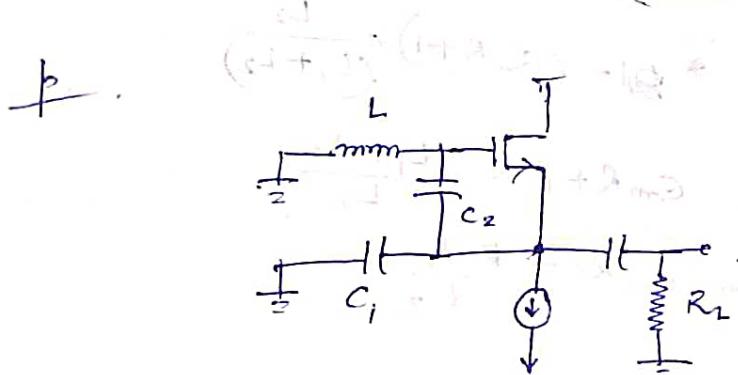

find frequency of oscillation:

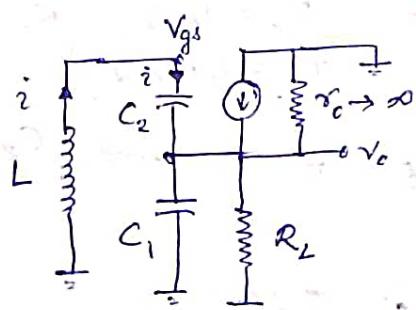

$$i = V_{gs} \cdot C_2 s$$

$$(V_{gs} - V_o) C_2 s = i$$

$$= \frac{C - V_{gs}}{L s}$$

$$\Rightarrow (V_{gs} - V_o) C_2 s = -\frac{V_{gs}}{L s}$$

$$\Rightarrow V_{gs} (C_2 s + \frac{1}{L s}) = V_o C_2 s$$

$$\Rightarrow V_o = \left( \frac{L C_2 s^2 + 1}{L C_2 s^2} \right) V_{gs}$$

$$g_m V_{gs} = V_o \left( C_1 s + \frac{1}{R} \right)$$

$$\Rightarrow g_m V_{gs} - \frac{V_{gs}}{L_s} = V_o \left( C_1 s + \frac{1}{R} \right)$$

$$\Rightarrow \left( \frac{g_m L_s - 1}{L_s} \right) V_{gs} - V_o \left( C_1 s + \frac{1}{R} \right) = 0$$

$$\Rightarrow \left( \frac{g_m L_s - 1}{L_s} \right) V_{gs} - \left( \frac{L_2 C_s^2 + 1}{L_2 C_s^2} \right) \left( \frac{R C_1 s + 1}{R} \right) V_{gs} = 0$$

$$(V_{gs} - V_o) C_2 s = \frac{0 - (V_{gs} + V_o)}{L_s}$$

$$V_{gs} C_2 s = \frac{0 - (V_{gs} + V_o)}{L_s}$$

$$\Rightarrow V_{gs} \left( C_2 s + \frac{1}{L_s} \right) = -\frac{V_o}{L_s} + V_o C_2 s \Rightarrow V_{gs} \left( C_2 s + \frac{1}{L_s} \right) = -\frac{V_o}{L_s}$$

$$\Rightarrow V_{gs} \left( \frac{L C_2 s^2 + 1}{L_s} \right) = V_o \left( \frac{L C_2 s^2 - 1}{L_s} \right) \Rightarrow V_{gs} (L C_2 s^2 + 1) = -V_o$$

$$\Rightarrow V_{gs} = V_o \left( \frac{L C_2 s^2 - 1}{L C_2 s^2 + 1} \right) \Rightarrow V_o = -V_{gs} (L C_2 s^2 + 1)$$

~~$$g_m V_{gs} = g_m V_{gs} + (V_{gs} - V_o) C_2 s = V_o \left( C_1 s + \frac{1}{R_L} \right)$$~~

~~$$\Rightarrow (g_m + C_2 s) V_{gs} = V_o \left( C_2 s + C_1 s + \frac{1}{R_L} \right)$$~~

~~$$(g_m + C_2 s) V_{gs} = \frac{(L C_2 s^2 + 1)(R_L(C_1 + C_2)s + 1)}{R_L} V_{gs}$$~~

~~$$\Rightarrow (g_m + C_2 s) R_L \times (L C_2 s^2 + 1) V_{gs} - (L C_2 s^2 + 1)(R_L(C_1 + C_2)s + 1) V_{gs} = 0$$~~

$V_{gs} \neq 0$ ,

~~$$\Rightarrow g_m R_L L C_2 s^2 + g_m R_L + R_L L C_2 s^3 + R_L C_2 s - \{ L C_2 R_L (C_1 + C_2) s^3 + L C_2 s^2 + R_L (C_1 + C_2) s + 1 \} = 0$$~~

~~$$\Rightarrow g_m R_L L C_2 s^2 - L C_2 s^2 + g_m R_L + 1 + R_L L C_2 s^3 - L C_2 R_L C_1 s^3 - L C_2^2 R_L s^3 + R_L C_2 s$$~~

$$g_m v_{gs} + v_{gs} \cdot C_2 s = V_o \left( C_1 s + \frac{1}{R_L} \right)$$

$$= - \frac{v_{gs} (LC_2 s^2 + 1) (R_L C_1 s + 1)}{R_L}$$

$\Rightarrow$  if  $v_{gs} \neq 0$ ,

$$(g_m + C_2 s) R_L + (LC_2 s^2 + 1)(R_L C_1 s + 1) = 0$$

$$\Rightarrow g_m R_L + R_L C_2 s + LC_1 C_2 R_L s^3 + LC_2 s^2 + R_L C_1 s + 1 = 0$$

$$\Rightarrow (g_m R_L + 1) + j\omega^3 LC_1 C_2 R_L + j\omega R_L (C_1 + C_2) - \omega^2 LC_2 = 0$$


$$\Rightarrow g_m R_L + 1 - \omega^2 LC_2 + j\{\omega R_L (C_1 + C_2) - \omega^3 LC_1 C_2 R_L\} = 0$$

$$\Rightarrow \omega (C_1 + C_2) = \omega^3 LC_1 C_2$$

$$\Rightarrow \omega^2 = \frac{C_1 + C_2}{LC_1 C_2}$$

$$\therefore g_m R_L + 1 - \frac{C_1 + C_2}{LC_1 C_2} \cdot LC_2 = 0$$

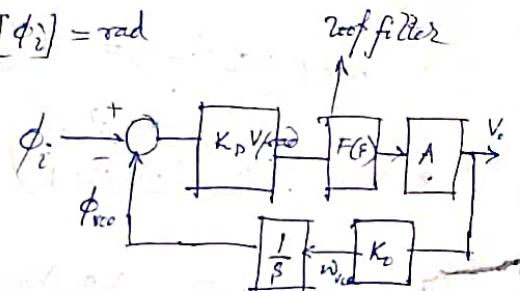
$$\Rightarrow g_m R_L + 1 = 1 + \frac{C_2}{C_1} \Rightarrow g_m R_L = \frac{C_2}{C_1}$$



$$\phi_{vco} = \int_0^t \omega_{vco} dt$$

$$\omega_{vco} = K_o V_o + \omega_o$$

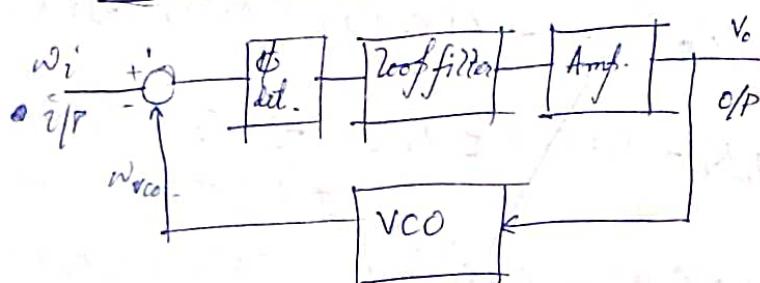$\omega_o$  = free running freq., when  $V_o = 0$



$$\omega_i = \omega_{vco} \pm \Delta\omega$$

capture range



locked signal  
 $\omega_i = \omega_{vco}$

$$\omega_{vco} = f(V_o) = k \cdot V_o$$

when  $V_o = 0$


$\omega_{vco} = \omega_o$  = free running PLL freq. condition

Analog Multiplex:

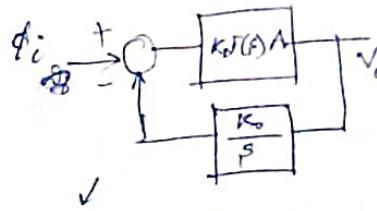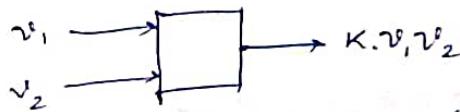

$$\frac{V_o}{\phi_i} = \frac{K_d F(s) A}{1 + \frac{K_d K_o F(s) A}{s}} = \frac{s K_d F(s) A}{s + K_d K_o F(s) A}$$

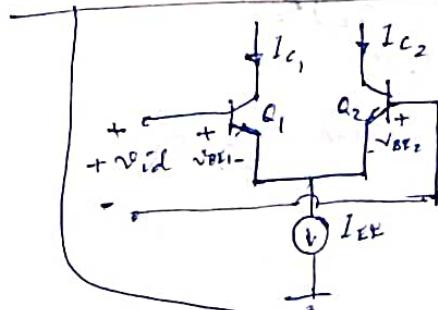for expressing  $V_o$  vs V.P. freq.,  $\omega_i$   $\omega_i = \frac{d\phi_i}{dt}$



$$v_{id} - v_{be1} + v_{be2} = 0$$

$$v_{be1} = V_T \ln \frac{I_{c1}}{I_{s1}}$$


$$v_{be2} = V_T \ln \frac{I_{c2}}{I_{s2}}$$

$$\begin{aligned} \frac{V_o(s)}{s \phi_i(s)} &= \frac{K_d F(s) A}{s + K_d K_o F(s) A} = \frac{V_o(s)}{\omega_i(s)} \\ &= \frac{K_d K_o F(s) A}{s + K_d K_o F(s) A} \cdot \frac{1}{K_o} \\ &= \left( \frac{K_v}{s + K_v} \right) \frac{1}{K_o} \end{aligned}$$

$$\text{e.g. } \frac{I_{c1}}{I_{c2}} = e^{\frac{v_{id}}{V_T}}$$

$$\omega_i = 2\pi 500 (1 + 0.1 \sin 2\pi 100t)$$
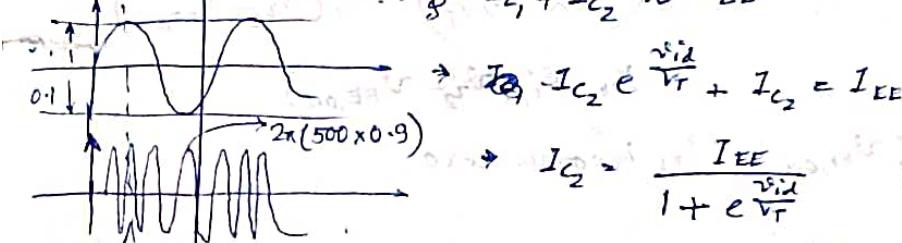
$$\therefore I_{c1} + I_{c2} \approx I_{EE}$$



$$\Delta I_c = I_{c1} - I_{c2} =$$

$$\omega_{osc} K_o \times V_o(t)$$

$$= 0.031 \times (2\pi \times 1000) \times \sin(2\pi 100t - 51^\circ)$$

$$= 0.031 \times 2\pi \times 1000 \cdot \sin(2\pi 100t - 51^\circ)$$

$$\tanh \frac{v_{id}}{2V_T} = \frac{e^{\frac{v_{id}}{V_T}} - 1}{e^{\frac{v_{id}}{V_T}} + 1}$$

if  $v_{id} \gg V_T$ ,  $e^{\frac{v_{id}}{V_T}} \gg 1$ ,

$$\tanh \frac{v_{id}}{2V_T} \rightarrow 1$$

$$\Rightarrow v_{id} - V_T \ln \frac{I_{c1}}{I_{s1}} + V_T \ln \frac{I_{c2}}{I_{s2}} = 0$$

$$\therefore Q_1 \equiv Q_2, I_{s1} = I_{s2}$$

$$\Rightarrow v_{id} = V_T \ln \frac{I_{c2}}{I_{s2}} - V_T \ln \frac{I_{c1}}{I_{s1}}$$

$$= V_T \ln \frac{I_{c2}}{I_{c1}}$$

$$I_{c2} = \frac{I_{EE}}{1 + e^{\frac{v_{id}}{V_T}}} \quad \text{if } I_{c1} = \frac{I_{EE}}{1 + e^{-\frac{v_{id}}{V_T}}}$$


$$I_{EE} \left( \frac{1 + e^{\frac{v_{id}}{V_T}} - 1 - e^{-\frac{v_{id}}{V_T}}}{1 + 1 + e^{\frac{v_{id}}{V_T}} + e^{-\frac{v_{id}}{V_T}}} \right)$$

$$= I_{EE} \left\{ \frac{\left( e^{\frac{v_{id}}{2V_T}} + e^{-\frac{v_{id}}{2V_T}} \right) \left( e^{\frac{v_{id}}{2V_T}} - e^{-\frac{v_{id}}{2V_T}} \right)}{\left( e^{\frac{v_{id}}{2V_T}} + e^{-\frac{v_{id}}{2V_T}} \right)^2} \right\}$$

$$= I_{EE} \cdot \frac{e^{\frac{v_{id}}{2V_T}} - e^{-\frac{v_{id}}{2V_T}}}{e^{-\frac{v_{id}}{2V_T}} + e^{\frac{v_{id}}{2V_T}}} = I_{EE} \cdot \tanh \frac{v_{id}}{2V_T}$$

∴ if  $v_{id} \ll V_T$ ,  $\tanh \frac{v_{id}}{2V_T} \rightarrow -1$

complete off

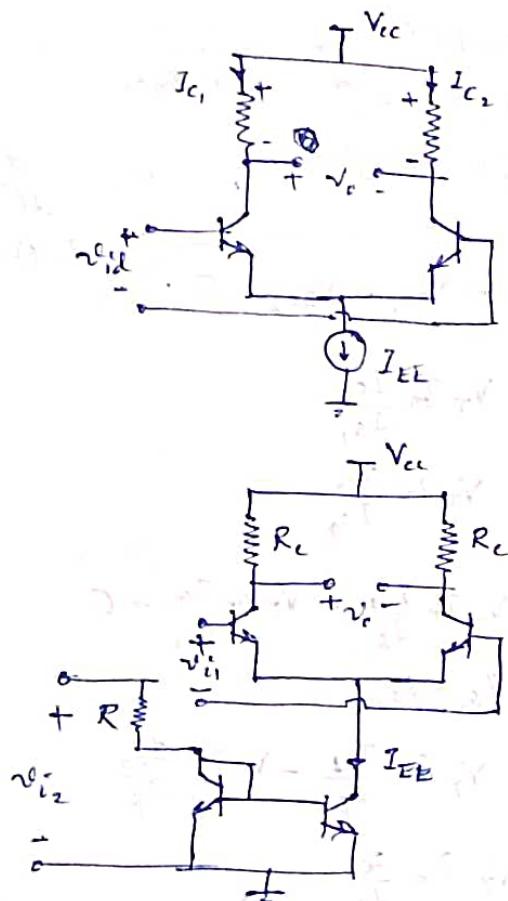

$$v_o + I_{C1}R_C - I_{C2}R_C = 0$$

$$\Rightarrow v_o = -(I_{C1} - I_{C2})R_C$$

$$= -\Delta I_C R_C$$

$$= -I_{EE} \cdot \tanh \frac{v_{id}}{2V_T} \cdot R_C$$

$$I_{EE} = \frac{v_{i2} - V_{BE,ON}}{R}$$

$$\Rightarrow v_o = -\frac{R_C}{R} \cdot (v_{i2} - V_{BE,ON}) \tanh \frac{v_{id}}{2V_T}$$


$$\approx -\frac{R_C}{R} \cdot (v_{i2} - V_{BE,ON}) \frac{v_{id}}{2V_T}$$

$$= \left( -\frac{R_C}{R} \times \frac{1}{2V_T} \right) \cdot v_{i2} \cdot (v_{i2} - V_{BE,ON})$$


$$= K_v \cdot v_{i2} \cdot (v_{i2} - V_{BE,ON})$$

if  $v_{i2} < V_{BE,ON}$ ,  $I_{EE}$  becomes zero.

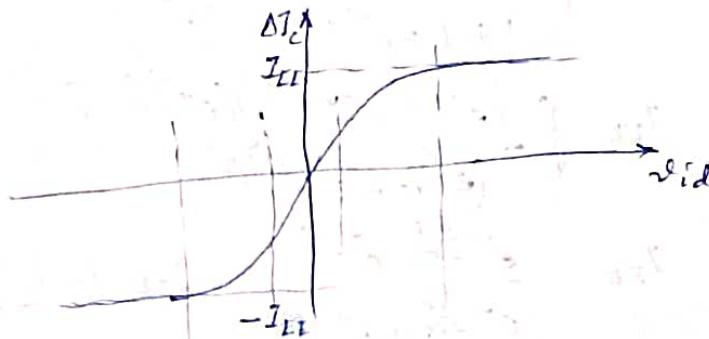slope of  ~~$\Delta I_C$~~   $\Delta I_C$  vs  $v_{id}$



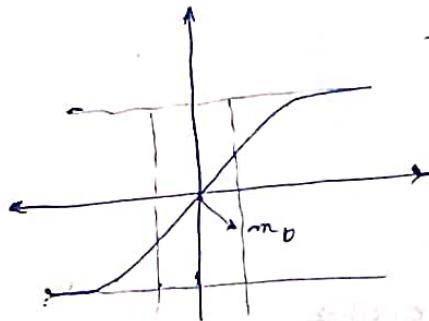for the 2 quadrant multiplier,  
 find the magnitude of the dc differential voltage  
 required to cause the slope of the transfer curve  
 $(\Delta I_c \text{ vs } v_{id})$  to change by 1% from that of the origin.



$$\Delta I_c = I_{EE} \cdot \frac{e^{\frac{v_{id}}{V_T}} - 1}{e^{\frac{v_{id}}{V_T}} + 1}$$

$$\therefore \frac{d\Delta I_c}{dv_{id}} = I_{EE} \left\{ \frac{e^{\frac{v_{id}}{V_T}}}{V_T (e^{\frac{v_{id}}{V_T}} + 1)} \right. \\ \left. - \frac{(e^{\frac{v_{id}}{V_T}} - 1) \times e^{\frac{v_{id}}{V_T}}}{(e^{\frac{v_{id}}{V_T}} + 1)^2} \right\}$$

$$= \frac{I_{EE}}{V_T} \left\{ \frac{e^{\frac{v_{id}}{V_T}}}{e^{\frac{v_{id}}{V_T}} + 1} - \frac{e^{\frac{v_{id}}{V_T}} (e^{\frac{v_{id}}{V_T}} - 1)}{(e^{\frac{v_{id}}{V_T}} + 1)^2} \right\}$$

$$= \frac{I_{EE}}{V_T} \left\{ \frac{e^{\frac{v_{id}}{V_T}} (1 + e^{\frac{v_{id}}{V_T}}) - e^{\frac{v_{id}}{V_T}} (e^{\frac{v_{id}}{V_T}} - 1)}{(e^{\frac{v_{id}}{V_T}} + 1)^2} \right\}$$

$$= \frac{I_{EE} \cdot e^{\frac{v_{id}}{V_T}}}{V_T} \left\{ \frac{e^{\frac{v_{id}}{V_T}} + e^{\frac{2v_{id}}{V_T}} - e^{\frac{v_{id}}{V_T}} + e^{\frac{v_{id}}{V_T}}}{(1 + e^{\frac{v_{id}}{V_T}})^2} \right\}$$

$$= \frac{I_{EE} 2e^{\frac{v_{id}}{V_T}}}{V_T (1 + e^{\frac{v_{id}}{V_T}})^2}$$

$$\therefore m_0 = \left. \frac{d\Delta I_c}{dv_{id}} \right|_{v_{id}=0} = \frac{2I_{EE}}{2V_T}$$

$$\text{now, } m_1 - m_0 = -0.01m_0 \Rightarrow m_1 = 0.99m_0$$

$$\frac{I_{EE} \cdot 2e^{\frac{v_{id}}{V_T}}}{V_T (1 + e^{\frac{v_{id}}{V_T}})^2} = 0.99 \times \frac{I_{EE}}{2V_T} \quad \text{let, } e^{\frac{v_{id}}{V_T}} = x$$

$$\therefore \frac{2x}{(1+x)^2} = \frac{1.01 \cdot 0.99}{2} \Rightarrow 2x(1+x) = 1.01 \{x^2 + 2x + 1\}$$

$$\Rightarrow 1.01x^2 + 2.02x + 1.01 - 4x = 0$$

$$\Rightarrow 1.01x^2 - 1.98x + 1.01 = 0$$

$$\Rightarrow x^2 - 1.96x + 1 = 0$$

$$\rightarrow z = -196 \pm \sqrt{196^2 - 4}$$

$$\rightarrow z = \frac{-204 \pm \sqrt{196-4}}{2}$$

$$= 1.22 \text{ or } 0.80$$

$$e^{\frac{v_{id}}{V_T}} = 1.22$$

$$\rightarrow \frac{v_{id}}{V_T} = \pm 0.2V_T$$

b) differential  
a sinusoidal voltage is applied to a emitter coupled pair.

for the maximum allowable  $v_{id}$ ,  
such that 3rd harmonic at the output is  $\leq 1\%$  of  
the fundamental

$$\tan h x \approx x - \frac{x^3}{3}$$


$$\Delta I_C = I_{CE} \cdot \tan \left( \frac{v_{id}}{2V_T} \right)$$

$$= I_{CE} \cdot 6 \left\{ \frac{v_{id}}{2V_T} - \frac{1}{3} \left( \frac{v_{id}}{2V_T} \right)^3 \right\}$$

$$\text{but, } v_{id} = V_m \sin \omega t$$

$$\Delta I_C = \frac{I_{CE}}{2V_T} \left[ V_m \sin \omega t - \frac{V_m^3}{48V_T^2} (3 \sin \omega t - \sin^3 \omega t) \right]$$

Remedy of 2 qdrnt multiplier:

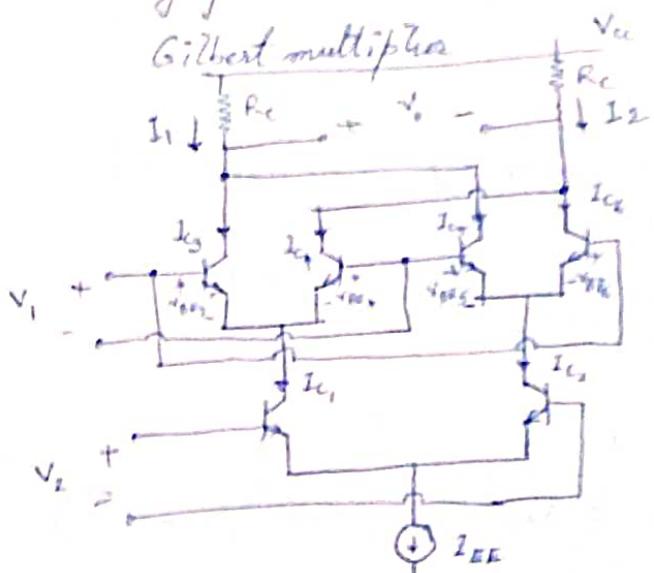

$$V_1 - V_{BE3} + V_{BE4} = 0$$

$$\Rightarrow V_1 = V_T \ln \frac{I_{C3}}{I_S} - V_T \ln \frac{I_{C4}}{I_S}$$

$$= V_T \ln \frac{I_{C3}}{I_{K_0}}$$

$$\therefore \frac{I_{C3}}{I_{C4}} = e^{\frac{V_1}{V_T}}$$

$$\therefore I_{C3} + I_{C4} = I_C$$

$$\Rightarrow I_{C3} + I_{C3} e^{-\frac{V_1}{V_T}} = I_C$$

$$\Rightarrow I_{C3} = \frac{I_C}{1 + e^{-\frac{V_1}{V_T}}}$$

$$I_{C4} = \frac{I_C}{1 + e^{\frac{V_1}{V_T}}}$$

$$\text{Also, } -V_1 - V_{BE5} + V_{BE6} = 0$$

$$\Rightarrow V_1 = V_{BE6} - V_{BE5}$$

$$= V_T \ln \frac{I_{C6}}{I_{E5}} + I_{C6} + I_{C5} e^{\frac{V_1}{V_T}}$$

$$\text{But } I_{C6} + I_{C5} = I_{C2} \Rightarrow I_5 = \frac{I_{C2}}{1 + e^{\frac{V_1}{V_T}}}$$

$$I_{C6} = \frac{I_5}{1 + e^{-\frac{V_1}{V_T}}}$$

$$I_{C1} = \frac{I_{E5}}{1 + e^{-\frac{V_1}{V_T}}} \quad I_{C2} = \frac{I_{EE}}{1 + e^{-\frac{V_1}{V_T}}}$$

$$I_{C5} = \frac{I_{EE}}{(1 + e^{-\frac{V_1}{V_T}})(1 + e^{-\frac{V_1}{V_T}})}, \quad I_{C6} = \frac{I_{EE}}{(1 + e^{-\frac{V_1}{V_T}})(1 + e^{\frac{V_1}{V_T}})}$$

$$I_{C2} = \frac{I_{EE}}{(1 + e^{-\frac{V_1}{V_T}})(1 + e^{\frac{V_1}{V_T}})} \quad I_{C4} = \frac{I_{EE}}{(1 + e^{\frac{V_1}{V_T}})(1 + e^{-\frac{V_1}{V_T}})}$$

$$I_1 = I_{C3} + I_{C5} = \frac{I_{EE}}{(1 + e^{-\frac{V_1}{V_T}})(1 + e^{-\frac{V_1}{V_T}})} + \frac{I_{EE}}{(1 + e^{\frac{V_1}{V_T}})(1 + e^{\frac{V_1}{V_T}})}$$

$$\Rightarrow I_1 = I_{EE} \times \left\{ \frac{1}{(1+e^{-\frac{V_2}{V_T}})(1+e^{-\frac{V_1}{V_T}})} + \frac{1}{(1+e^{\frac{V_2}{V_T}})(1+e^{\frac{V_1}{V_T}})} \right.$$

$$= I_{EE} \times \frac{1}{(1+e^{\frac{V_2}{V_T}})(1+e^{\frac{V_1}{V_T}})} \times \left( e^{\frac{V_2}{V_T}} e^{\frac{V_1}{V_T}} + 1 \right)$$

*Similarly,*  $I_2 = I_{EE} \times \left\{ \frac{1}{(1+e^{-\frac{V_2}{V_T}})(1+e^{\frac{V_1}{V_T}})} + \frac{1}{(1+e^{\frac{V_2}{V_T}})(1+e^{-\frac{V_1}{V_T}})} \right\}$

$$= I_{EE} \times \frac{1}{(1+e^{\frac{V_2}{V_T}})(1+e^{-\frac{V_1}{V_T}})} \times \left( e^{\frac{V_2}{V_T}} e^{-\frac{V_1}{V_T}} + 1 \right)$$

$$\Rightarrow \Delta I = I_1 - I_2 =$$

$$I_{EE} \times \left\{ \frac{\left( e^{\frac{V_2}{V_T}} e^{\frac{V_1}{V_T}} + 1 \right)}{(1+e^{\frac{V_2}{V_T}})(1+e^{\frac{V_1}{V_T}})} - \frac{\left( e^{\frac{V_2}{V_T}} e^{-\frac{V_1}{V_T}} + 1 \right)}{(1+e^{\frac{V_2}{V_T}})(1+e^{-\frac{V_1}{V_T}})} \right\}$$

$$= I_{EE} \times \frac{1}{(1+e^{\frac{V_2}{V_T}})} \left\{ \frac{\left( e^{\frac{V_2}{V_T}} e^{\frac{V_1}{V_T}} + 1 \right)(1+e^{-\frac{V_1}{V_T}}) - \left( e^{\frac{V_2}{V_T}} e^{-\frac{V_1}{V_T}} + 1 \right)(1+e^{\frac{V_1}{V_T}})}{(1+e^{\frac{V_1}{V_T}})(1+e^{-\frac{V_1}{V_T}})} \right\}$$

$$= I_{EE} \times \frac{1}{(1+e^{\frac{V_2}{V_T}})} \left\{ \frac{e^{\frac{V_2}{V_T}} + e^{-\frac{V_1}{V_T}} + e^{\frac{V_1}{V_T}} e^{\frac{V_2}{V_T}} - \left( e^{\frac{V_2}{V_T}} + e^{-\frac{V_1}{V_T}} + e^{\frac{V_1}{V_T}} e^{-\frac{V_2}{V_T}} \right)}{(e^{\frac{V_1}{V_T}} + e^{-\frac{V_1}{V_T}})^2} \right\}$$

$$= I_{EE} \times \frac{1}{(1+e^{\frac{V_2}{V_T}})} \times \frac{e^{\frac{V_2}{V_T}} e^{\frac{V_1}{V_T}} + \left( e^{-\frac{V_1}{V_T}} - e^{\frac{V_1}{V_T}} \right) - e^{\frac{V_2}{V_T}} e^{-\frac{V_1}{V_T}}}{(e^{\frac{V_1}{V_T}} + e^{-\frac{V_1}{V_T}})^2}$$


$$= I_{EE} \times \frac{1}{(1+e^{\frac{V_2}{V_T}})} \times \frac{\left( e^{-\frac{V_1}{V_T}} - e^{\frac{V_1}{V_T}} \right) \left( e^{\frac{V_2}{V_T}} + 1 \right) \left( 1 - e^{\frac{V_2}{V_T}} \right)}{(e^{\frac{V_1}{V_T}} + e^{-\frac{V_1}{V_T}})^2}$$

$$= I_{EE} \cdot \frac{\left(1 - e^{\frac{V_2}{V_T}}\right)}{\left(1 + e^{\frac{V_2}{V_T}}\right)} \times \frac{\left(e^{-\frac{V_1}{V_T}} - e^{\frac{V_1}{V_T}}\right)}{\left(e^{\frac{V_1}{2V_T}} + e^{-\frac{V_1}{2V_T}}\right)^2}$$

$$= I_{EE} \cdot e^{\frac{V_2}{2V_T}} \frac{\left(e^{-\frac{V_2}{2V_T}} - e^{\frac{V_2}{2V_T}}\right)}{e^{\frac{V_2}{2V_T}} \left(e^{-\frac{V_2}{2V_T}} + e^{\frac{V_2}{2V_T}}\right)} \times \frac{e^{-\frac{V_1}{2V_T}} - e^{\frac{V_1}{2V_T}}}{\left(e^{\frac{V_1}{2V_T}} + e^{-\frac{V_1}{2V_T}}\right)}$$



$$= I_{EE} \cdot \tanh\left(\frac{V_1}{2V_T}\right) \tanh\left(\frac{V_2}{2V_T}\right)$$

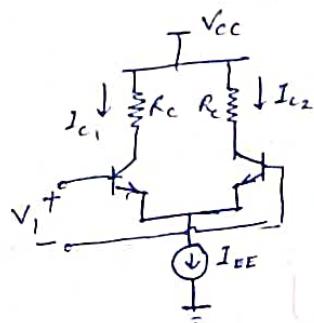Consider a differential amplifier: how to increase the linear range



$$I_{c1} = \frac{I_{EE}}{1 + e^{-\frac{V_1}{V_T}}}$$
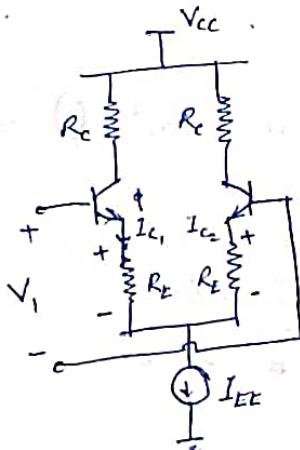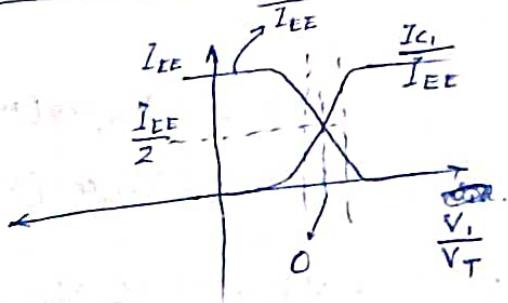
$$I_{c2} = \frac{I_{EE}}{1 + e^{\frac{V_1}{V_T}}}$$



$$V_1 - V_{BE1} - I_{c1}R_E + I_{c2}R_E + V_{BE2} = 0$$

$$\Rightarrow V_1 = V_{BE1} - V_{BE2} + (I_{c1} - I_{c2})R_E$$

$$= V_T \ln \frac{I_{c1}}{I_{c2}} + \Delta I_c \cdot R_E$$

$$I_{c1} + I_{c2} = I_{EE}$$

$$V_T \ln \frac{I_{c1}}{I_{c2}} = V_1 - \Delta I_c \cdot R_E$$

$$\Rightarrow I_{c1} + I_{c1} e^{-\frac{V_1 - \Delta I_c R_E}{V_T}} = I_{EE}$$

$$\frac{I_{c1}}{I_{c2}} = e^{\frac{V_1 - \Delta I_c R_E}{V_T}}$$


$$I_{c1} = \frac{I_{EE}}{1 + e^{-\frac{V_1 - \Delta I_c R_E}{V_T}}}$$

$$I_{c2} = \frac{I_{EE}}{1 + e^{\frac{V_1 - \Delta I_c R_E}{V_T}}}$$

$$\Delta I_c = I_{EE} \times$$

$$\text{if } I_{c1} \approx I_{EE}, \quad V_1 = V_T \ln \dots$$
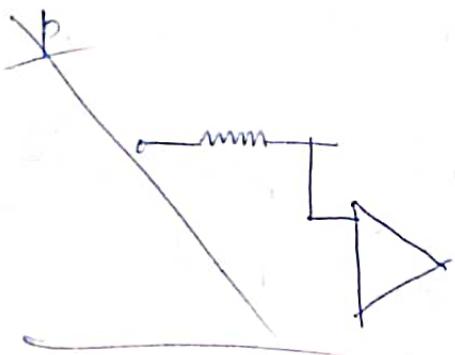
$$I_{c1} = \frac{I_{EE}}{1 + e^{-\frac{(V_1 - I_{EE} R_E)}{V_T}}}$$



$$\tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}}$$

$$\tanh \approx \frac{e^{2x} - 1}{e^{2x} + 1} \approx e^2$$

multiplier as phase detector:

$$v_1 = V_{m_1} \cos(\omega_c t)$$

$$v_2 = V_{m_2} \cos(\omega_c t + \theta)$$




$$\Rightarrow v_1 v_2 = \frac{V_{m_1} V_{m_2}}{2} \cdot \left\{ \cos(\omega_c t + \omega_c t + \theta) + \cos \theta \right\}$$

phase difference:  $\theta$ .

$$\Rightarrow v_1 v_2 = \underbrace{\frac{V_{m_1} V_{m_2}}{2} \cdot \cos \theta}_{\text{dc component}} + \underbrace{\frac{V_{m_1} V_{m_2}}{2} \cdot \cos(2\omega_c t + \theta)}_{\text{ac component}}$$

if, the signals are large square wave signals,  
then, the output dc component will be a direct  
linearly related to the phase difference.

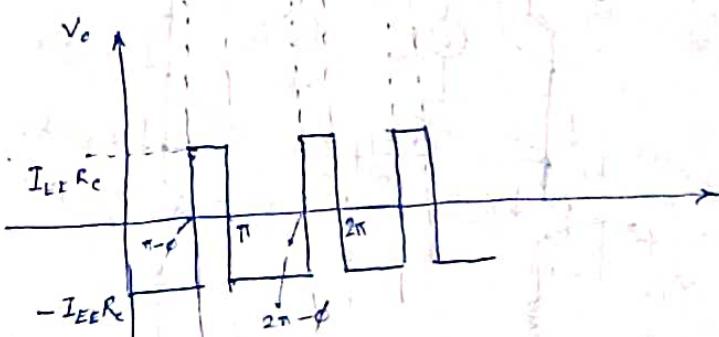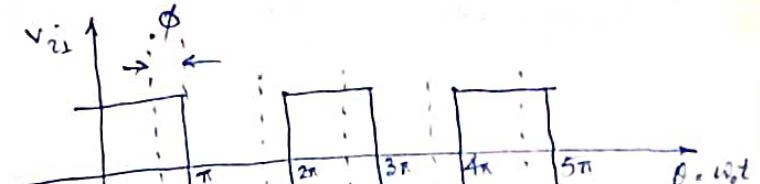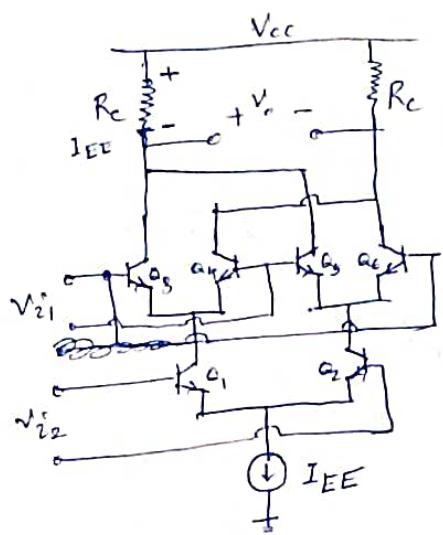as in this case, transistors work as switches.



when  $V_{i1}, V_{i2}$  high,

$Q_1, Q_3, Q_4$  will be on.

as  $I_{EE}$  will not go through  $Q_2$ ,

$Q_1, Q_3 \rightarrow ON, V_o = +I_{EE} \cdot R_c$ .

during  $\phi$ ,  $V_{i1} \rightarrow$  high,  $V_{i2} \rightarrow 2\pi$

$Q_2 \rightarrow ON, Q_4 \rightarrow ON$ ,

$$\Rightarrow V_o = +I_{EE} \cdot R_c$$

when both  $V_{i1}, V_{i2} \rightarrow 2\pi$ ,

$Q_2 \rightarrow ON, Q_5 \rightarrow ON$ ,

$$\Rightarrow V_o = -I_{EE} \cdot R_c$$

when  $V_{i2} \rightarrow$  high,

$V_{i1} \rightarrow 2\pi$ ,

$Q_1 \rightarrow ON, Q_4 \rightarrow ON$ ,

$$V_o = +I_{EE} \cdot R_c$$

$$V_{avg} = V_{dc} = \frac{1}{2\pi} \cdot \int_0^{2\pi} V_o(\theta) \cdot d\theta$$

$$= \frac{1}{2\pi} \cdot \int_0^{\pi} (-I_{EE} \cdot R_c) \cdot d\theta$$

$$+ \int_{\pi}^{2\pi} I_{EE} \cdot R_c \cdot d\theta + \int_{2\pi}^{2\pi-\phi} (-I_{EE} \cdot R_c) \cdot d\theta$$

$$+ \int_{2\pi-\phi}^{2\pi} I_{EE} \cdot R_c \cdot d\theta$$

$$= \frac{1}{2\pi} \cdot (-I_{EE} \cdot R_c) \{ (\phi - \pi)\}$$

$$+ \phi + (\phi - \pi) + \phi \}$$

$$\Rightarrow \frac{1}{2\pi} \cdot I_{EE} \cdot R_c \left\{ 4\phi - 2\pi \right\} = I_{EE} \cdot R_c \left\{ \frac{2\phi}{\pi} - 1 \right\}$$